

Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 5-II
FALL 2016



(1)

Agenda

Structural way in VHDL


Mixed Example

Modeling the Structural way

- *Structural* architecture
 - implements the module as a composition of subsystems
 - contains
 - *signal declarations*, for internal interconnections
 - the entity ports are also treated as signals
 - *component instances*
 - instances of previously declared entity/architecture pairs
 - *port maps* in component instances
 - connect signals to component ports

Structural way Example

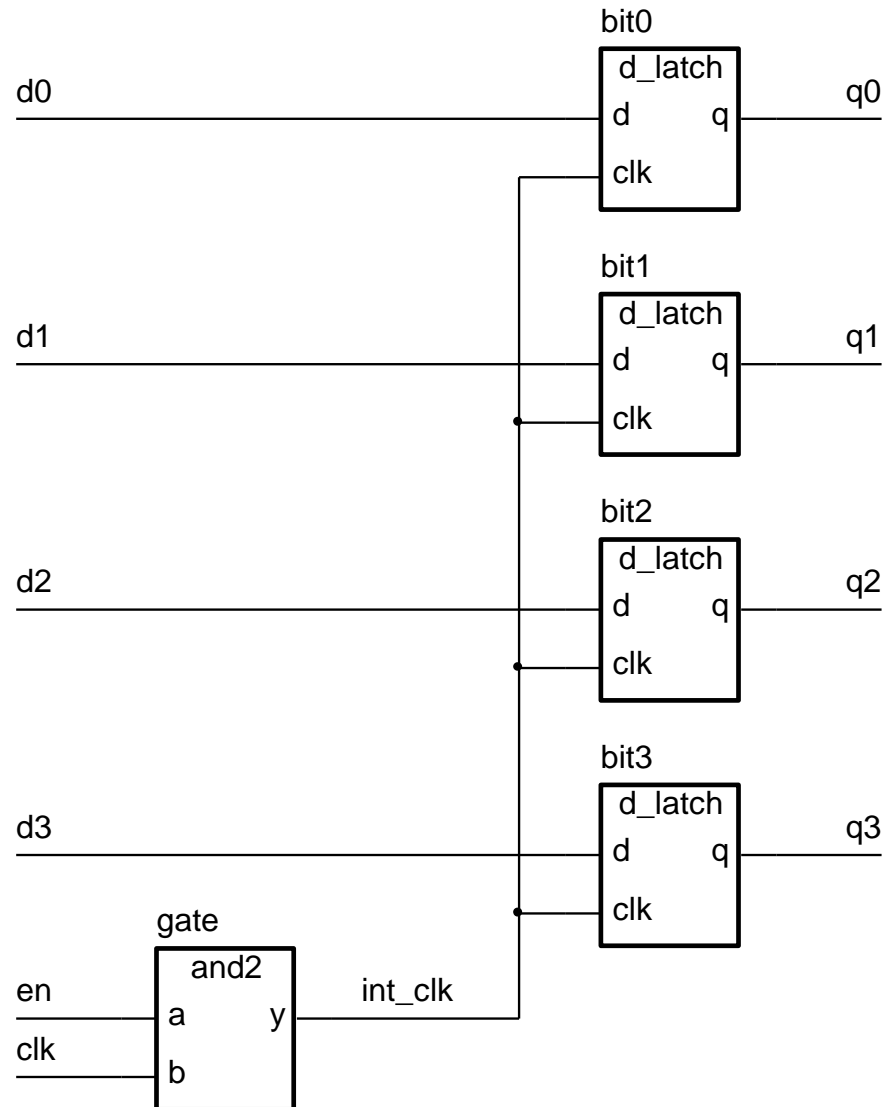Not complete example, just for concept justification ..



Structural way..

- First **declare D-latch** and **and-gate** entities and architectures

```
entity d_latch is  
    port ( d, clk : in bit; q : out bit );  
end entity d_latch;  
  
architecture basic of d_latch is  
begin  
    process (clk, d)  
    begin  
        if clk = '1' then  
            q <= d;  
        end if;  
    end process;  
end basic;
```

```
entity and2 is  
    port ( a, b : in bit; y : out bit );  
end entity and2;  
  
architecture basic of and2 is  
begin  
    process (a, b)  
    begin  
        y <= a and b;  
    end process ;  
end basic;
```


Structural way...

- **Declare** corresponding **components** in register architecture body

```
architecture struct of reg4 is  
  component d_latch  
    port ( d, clk : in bit; q : out bit );  
  end component;  
  component and2  
    port ( a, b : in bit; y : out bit );  
  end component;  
  signal int_clk : bit;  
  
  ...
```

Structural way....

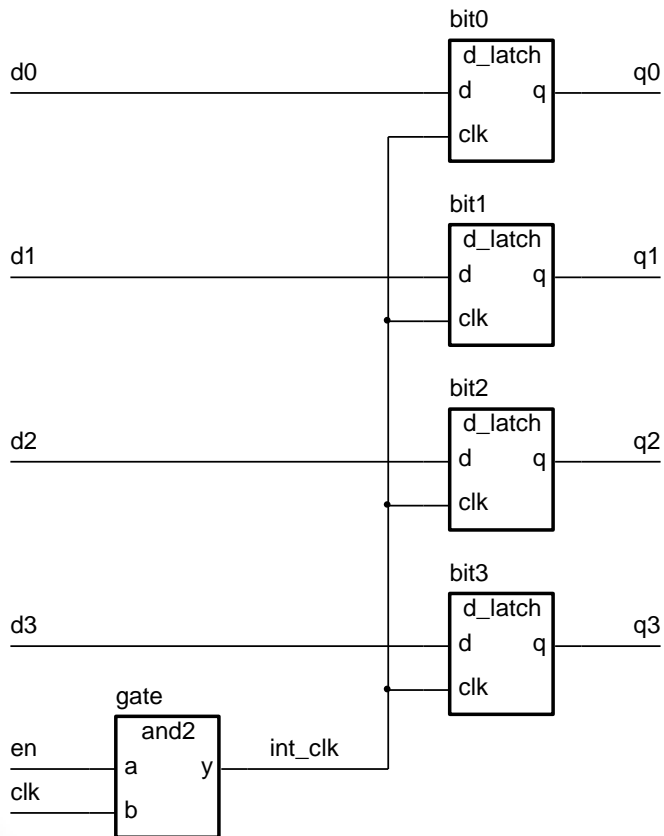- Now **use them** to implement the register



```
...
begin
    bit0 : d_latch
        port map ( d0, int_clk, q0 );
    bit1 : d_latch
        port map ( d1, int_clk, q1 );
    bit2 : d_latch
        port map ( d2, int_clk, q2 );
    bit3 : d_latch
        port map ( d3, int_clk, q3 );
    gate : and2
        port map ( en, clk, int_clk );
end struct;
```

Trace the code & Draw the model structure

```
-----  
-- Combinational Logic Design  
-- (ESD book figure 2.4)  
-- by Weijun Zhang, 04/2001  
--  
-- A simple example of VHDL Structure Modeling  
-- we might define two components in two separate files,  
-- in main file, we use port map statement to instantiate  
-- the mapping relationship between each components  
-- and the entire circuit.  
-----
```

```
library ieee;                                -- component #1  
use ieee.std_logic_1164.all;  
  
entity OR_GATE is  
port(   X:    in std_logic;  
        Y:    in std_logic;  
        F2:   out std_logic  
);  
end OR_GATE;  
  
architecture behv of OR_GATE is  
begin  
process(X,Y)  
begin  
    F2 <= X or Y;                            -- behavior des.  
end process;  
end behv;
```


```
-----  
library ieee;                                -- component #2  
use ieee.std_logic_1164.all;  
  
entity AND_GATE is  
port(   A:    in std_logic;  
        B:    in std_logic;  
        F1:   out std_logic  
);  
end AND_GATE;  
  
architecture behv of AND_GATE is  
begin  
process(A,B)  
begin  
    F1 <= A and B;                            -- behavior des.  
end process;  
end behv;
```


Trace the code &
Draw the model
structure..


```
-----  
library ieee;                                -- top level circuit  
use ieee.std_logic_1164.all;  
use work.all;  
  
entity comb_ckt is  
port(   input1: in std_logic;  
        input2: in std_logic;  
        input3: in std_logic;  
        output: out std_logic  
);  
end comb_ckt;  
  
architecture struct of comb_ckt is  
  
    component AND_GATE is                    -- as entity of AND_GATE  
    port(   A: in std_logic;  
           B: in std_logic;  
           F1: out std_logic  
    );  
    end component;  
  
    component OR_GATE is                     -- as entity of OR_GATE  
    port(   X: in std_logic;  
           Y: in std_logic;  
           F2: out std_logic  
    );  
    end component;  
  
    signal wire: std_logic;                  -- signal just like wire  
  
begin  
  
    -- use sign "=>" to clarify the pin mapping  
  
    Gate1: AND_GATE port map (A=>input1, B=>input2, F1=>wire);  
    Gate2: OR_GATE port map (X=>wire, Y=>input3, F2=>output);  
  
end struct;  
-----
```

Trace the code & Draw the model structure..

- the model

 

- Simulation waveform

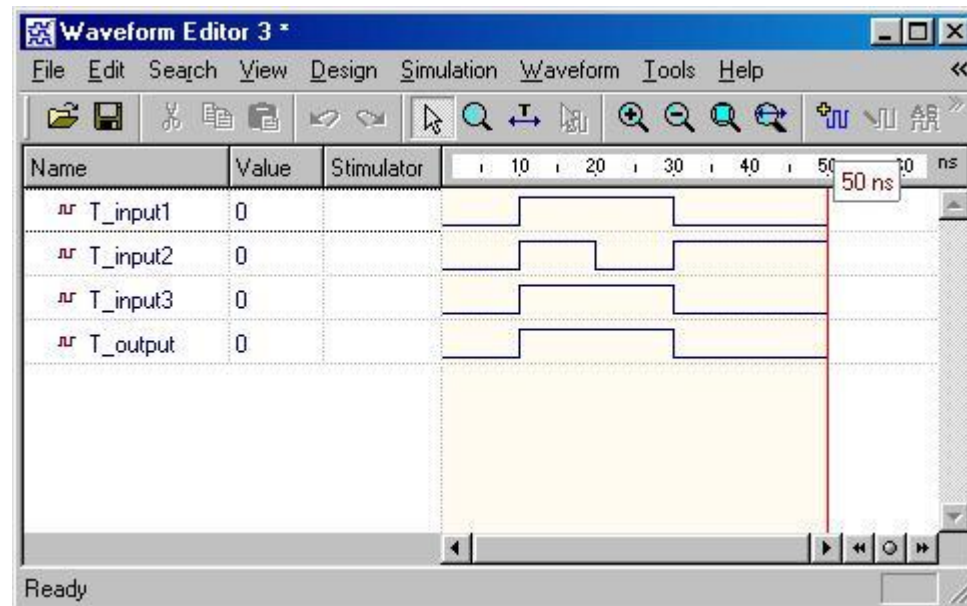


Mixed Behavior and Structure

- An architecture can contain both behavioral and structural parts
 - process statements and component instances
 - collectively called *concurrent statements*
 - processes can read and assign to signals
- Example: register-transfer-level (RTL) Model
 - data path described structurally
 - control section described behaviorally

Mixed Example

 Not complete example, just for concept justification ..



Mixed Example

```
entity multiplier is
  port ( clk, reset : in bit;
         multiplicand, multiplier : in integer;
         product : out integer );
end multiplier;

architecture mixed of multiplier is
  signal partial_product, full_product : integer;
  signal arith_control, result_en, mult_bit, mult_load : bit;
begin
  arith_unit : entity work.shift_adder(behavior)
    port map ( addend => multiplicand, augend => full_product,
              sum => partial_product,
              add_control => arith_control );
  result : entity work.reg(behavior)
    port map ( d => partial_product, q => full_product,
              en => result_en, reset => reset );
  ...
```

...

Mixed Example..

```
...
multiplier_sr : entity work.shift_reg(behavior)
  port map ( d => multiplier, q => mult_bit,
            load => mult_load, clk => clk );
product <= full_product;

process (clk, reset)
  -- variable declarations for control_section
  -- ...
begin
  -- sequential statements to assign values to control signals
  -- ...
end process;
end mixed;
```

- For more details, refer to:
 - VHDL Tutorial: Learn by Example by Weijun Zhang
 - <http://esd.cs.ucr.edu/labs/tutorial/>
 - **VHDL GUIDELINES FOR SYNTHESIS**
 - ➔ • <http://www.utdallas.edu/~zxb107020/EE6306/Tutorial/VHDL.pdf>
 - “Introduction to VHDL” presentation by Dr. Adnan Shaout, *The University of Michigan-Dearborn*
 - **The VHDL Cookbook**, Peter J. Ashenden, 1st edition, 1990.
- The lecture is available online at:
 - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12135>
- For inquires, send to:
 - ahmad.elbanna@feng.bu.edu.eg

Designing with VHDL and FPGA

Instructor:

Dr. Ahmad El-Banna

LAB# 6
FALL 2016



Agenda

Testbench

- Testbench Definition
- Testbench Environment
- Steps of constructing a testbench
- Assert statement
- Examples


Programming the Spartan-3E FPGA Board

- Why Spartan-3E ?
- Step by Step Example

Test Bench your Model

- Testing a design by simulation
- Use a *test bench* model
 - a Model that uses your Model
 - apply test sequences to your inputs
 - monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation
 - or logic analyzer
- VHDL designers use testbench to ensure timing, correctness, and to speed up testing.
- Previously, you had to force signals and setup the clock. A testbench sets this up for you.

Testbench environment

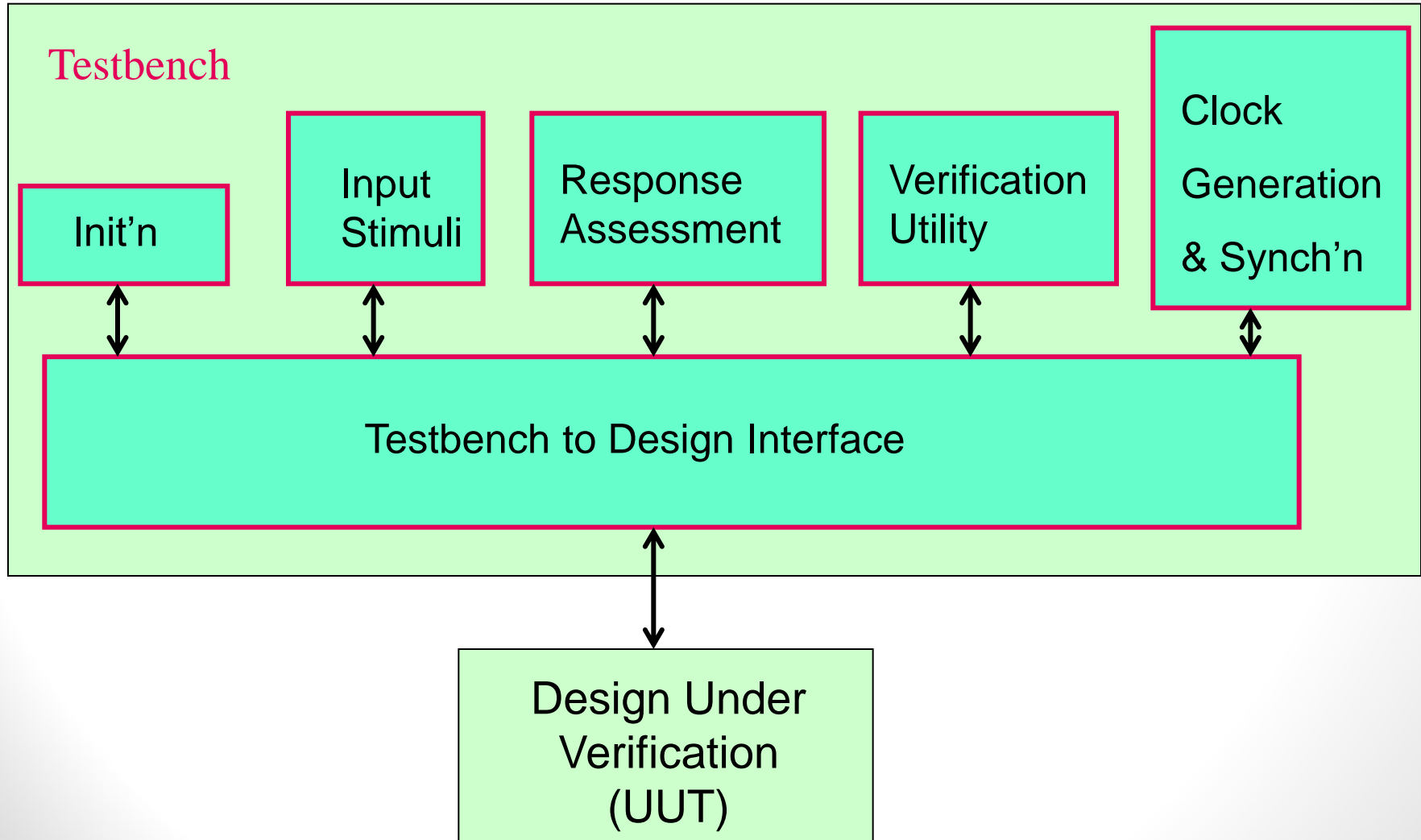

Steps of a test bench:

1. entity declaration for your test bench.
2. Component Declaration for the Unit Under Test (UUT)
3. declare inputs and initialize them
4. declare outputs and initialize them
5. Clock period definitions
6. Stimulus process

Assert statement

- A common statement in testbench module and is ignored by logic synthesis tools.

- Its function:

check that a specified condition is true and reports an error if it is not

- syntax:


`assert (condition)`

`report "message"`

`severity level (note, failure, error or warning)`

- Examples:

 1. `assert (T_O="001") report "Error Case 3" severity error;`
2. `assert (false)`
`report "Testbench of Mux completed successfully!"`
`severity note;`



Test Bench of the multiplexer example

-- Test Bench for Multiplexer (ESD figure 2.5)-- by Weijun Zhang, 04/2001
-- four operations are tested in this example.

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;
```

```
entity Mux_TB is          -- empty entity  
end Mux_TB;
```

architecture TB of Mux_TB is

```
-- initialize the declared signals  
signal T_I3: std_logic_vector(2 downto 0):="000";  
signal T_I2: std_logic_vector(2 downto 0):="000";  
signal T_I1: std_logic_vector(2 downto 0):="000";  
signal T_I0: std_logic_vector(2 downto 0):="000";  
signal T_O: std_logic_vector(2 downto 0);  
signal T_S: std_logic_vector(1 downto 0);
```

```
component Mux  
port(  
    I3:          in std_logic_vector(2 downto 0);  
    I2:          in std_logic_vector(2 downto 0);  
    I1:          in std_logic_vector(2 downto 0);  
    I0:          in std_logic_vector(2 downto 0);  
    S:           in std_logic_vector(1 downto 0);  
    O:           out std_logic_vector(2 downto 0)  
);  
end component;
```

```
entity Mux is  
port(  
    I3:          in std_logic_vector(2 downto 0);  
    I2:          in std_logic_vector(2 downto 0);  
    I1:          in std_logic_vector(2 downto 0);  
    I0:          in std_logic_vector(2 downto 0);  
    S:           in std_logic_vector(1 downto 0);  
    O:           out std_logic_vector(2 downto 0)  
);  
end Mux;
```

Test Bench of the multiplexer example..

```
begin
  U_Mux: Mux port map (T_I3, T_I2, T_I1, T_I0, T_S, T_O);
  process

variable err_cnt: integer :=0;
  begin

    T_I3 <= "001";           -- I0-I3 are different signals
    T_I2 <= "010";
    T_I1 <= "101";
    T_I0 <= "111";

    -- case select equal "00"
    wait for 10 ns;
    T_S <= "00";
    wait for 1 ns;
    assert (T_O="111") report "Error Case 0" severity error;
    if (T_O/="111") then
      err_cnt := err_cnt+1;
    end if;
    -- case select equal "01"
    wait for 10 ns;
    T_S <= "01";
    wait for 1 ns;
    assert (T_O="101") report "Error Case 1" severity error;
    if (T_O/="101") then
      err_cnt := err_cnt+1;
    end if;
```

Test Bench of the multiplexer example...

```
-- case select equal "10"
    wait for 10 ns;
    T_S <= "10";
    wait for 1 ns;
    assert (T_O="010") report "Error Case 2" severity error;
    if (T_O/="010") then
        err_cnt := err_cnt+1;
    end if;
-- case select equal "11"
    wait for 10 ns;
    T_S <= "11";
    wait for 1 ns;
    assert (T_O="001") report "Error Case 3" severity error;

    if (T_O/="001") then
        err_cnt := err_cnt+1;
    end if;
-- case equal "11"
    wait for 10 ns;
    T_S <= "UU";

-- summary of all the tests
    if (err_cnt=0) then
        assert (false)
        report "Testbench of Mux completed sucessfully!"
        severity note;
    else
        assert (true)
        report "Something wrong, try again!"
        severity error;
    end if;

    wait;

end process;
end TB;

-----
configuration CFG_TB of Mux_TB is
    for TB
        end for;
end CFG_TB;
-----
```


Testbench example2

- A basic 4 bit counter with reset input.
- Find it at:
 - <http://vhdlguru.blogspot.com.eg/2010/03/how-to-write-testbench.html>


PROGRAMING SPARTAN 3E KIT

Why Spartan-3E ?

- Simply, it is available in our lab 😊
- Technically,
 - It's one of 5 platforms each delivering a unique cost-optimized balance of programmable logic, connectivity, and dedicated hard IP for your low-cost applications.
 - It is used for Logic Optimized applications.
 - For applications where logic densities matter more than I/O count Ideal for logic integration, DSP co-processing and embedded control, requiring significant processing and narrow or few interfaces

Lecture Reference

 - We will follow the presentation talks about:
“How to program the FPGA SPARTAN-3E Board”
 - By anonymous.
 - Found at:
 - <http://web.ewu.edu/groups/technology/Claudio/ee360/Protected/PresentationFPGA.pdf>



Intel®
Flash
Memory



PB200-087

REV B1

LD7 (F10)
 LD6 (F10)
 LD5 (F11)
 LD4 (F11)
 LD3 (F11)
 LD2 (F11)
 LD1 (F12)
 LD0 (F12)



IO0(C0) IO1(C0)
 IO10(C0) IO2(A4)
 IO11(C0) IO3(D8)
 IO12(C0) IO4(C8)
 GND GND
 UCC UCC

J4

J1

J2

IO0(C0)
 IO1(C0)
 GND
 UCC

J3

PL10MS (L1A1H5) 5WZMS (L1A1H5)

- For more details, refer to:
 - VHDL Tutorial: Learn by Example by Weijun Zhang
 - <http://esd.cs.ucr.edu/labs/tutorial/>
 - <http://vhdlguru.blogspot.com.eg/2010/03/how-to-write-testbench.html>
 - <http://users.wpi.edu/~rjduck/VHDL%20module8%20a.pdf>
 - <http://web.ewu.edu/groups/technology/Claudio/ee360/Protected/PresentationFPGA.pdf>
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg