



- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- The exam consists of two pages.

- No. of questions: 3
- Total marks: 30
- Examiner: Dr. Abdallah Hammad

Question 1

- (a) Compare between LM7812, LM7912, LM317, LM337
- (b) Determine the minimum and maximum output voltages for the voltage regulator in figure 1. Assume $I_{ADJ} = 50 \text{ mA}$.

Question 2

- (a) What is RGB LED? Explain how you can drive it
- (b) If the voltages in figure 2 are applied to **OR gate** and **AND gate**. Sketch the output voltage for each case

Question 3

- (a) Determine v_o for each the network of figure (3)
- (b) The Zener diode in the voltage-regulator circuit of figure (4) has a constant reverse breakdown voltage $V_Z = 8.2 \text{ V}$, for $75 \text{ mA} \leq i_Z \leq 1 \text{ A}$. If $R_L = 9 \Omega$, find a range for R_S to maintain regulation while V_b varies by 10% from its value of 12 V.

<p style="text-align: center;">Figure (1)</p>	<p style="text-align: center;">(b) Figure (2)</p>
<p style="text-align: center;">(a) Figure (3)</p>	<p style="text-align: center;">Figure (4)</p>