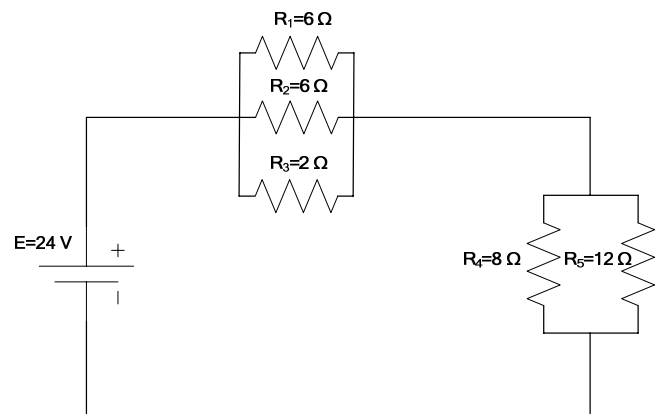


## Sheet (1)


1. What is the diameter of a copper wire with a resistance of  $0.5 \Omega$  and a length of 45 m. knowing that the resistivity of copper is  $1.72 \times 10^{-8} \Omega \cdot \text{m}$ .

2. For the circuit shown in Fig. (1) find:
  - a) The current in each branch
  - b) The power consumed in each resistance.



3. Find the capacitance of a parallel plate capacitor if the area of each plate is  $0.075 \text{ m}^2$  and the distance between the plates is  $1.77 \text{ mm}$ . The dielectric is air with relative permittivity of  $1.0006$ .

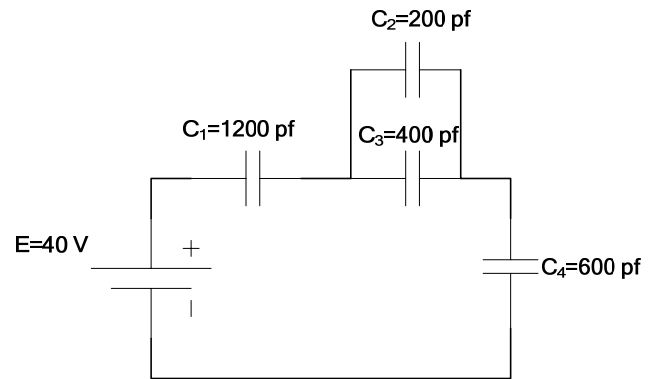4. Find the voltage across and charge on each capacitor for the circuit shown in Fig. (2).



5. Find the inductance of the coil of Fig. (3).

$$L = \frac{N^2 \mu A}{l}$$

$$\mu = \mu_r \mu_0$$

Where,

$L$  = Inductance of coil in Henrys

$N$  = Number of turns in wire coil (straight wire = 1)



$\mu$  = Permeability of core material (absolute, not relative)

$\mu_r$  = Relative permeability, dimensionless ( $\mu_0=1$  for air)

$\mu_0 = 1.26 \times 10^{-6} \text{ T-m/At}$  permeability of free space


$A$  = Area of coil in square meters =  $\pi r^2$

$l$  = Average length of coil in meters

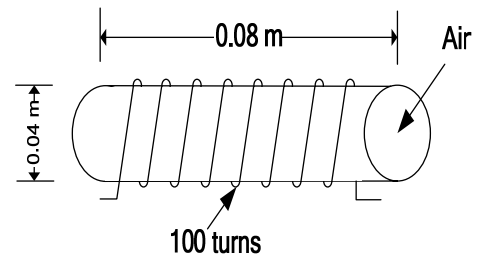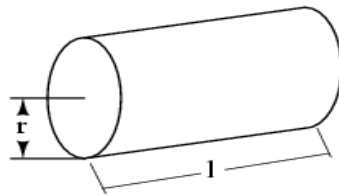


6. For the Circuit of Fig. (4):








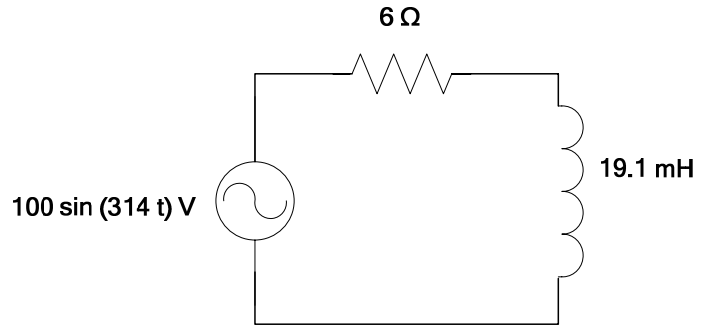
- a) Find the total impedance.
- b) Draw the impedance diagram.
- c) Find the supply current and the voltages across the resistor and inductor.
- d) Draw the phasor diagram of the voltages and current.
- e) Find the apparent, active and reactive powers.
- f) Find the power factor of the circuit and indicate whether it is leading or lagging.



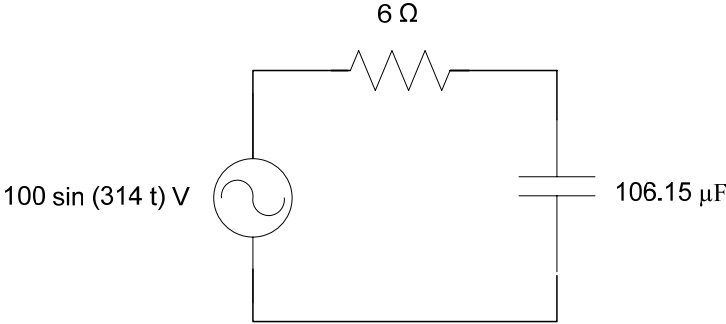7. Repeat problem (6) for the circuit of Fig. (5) Replacing inductor by capacitor in part (c).



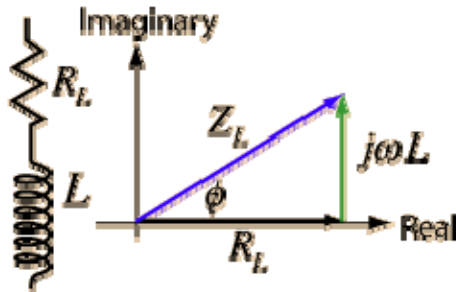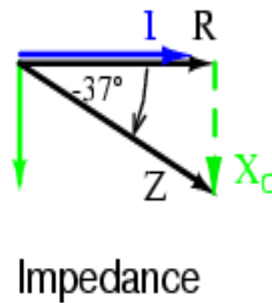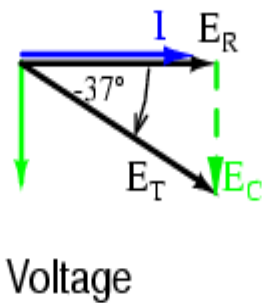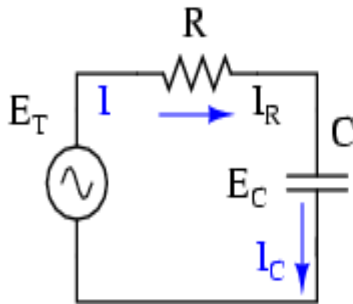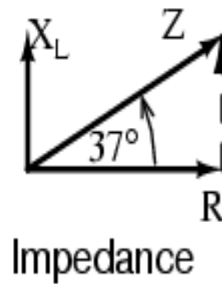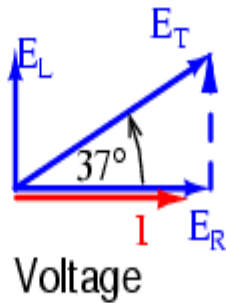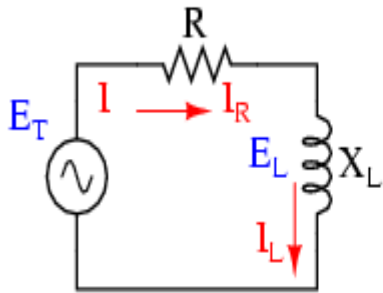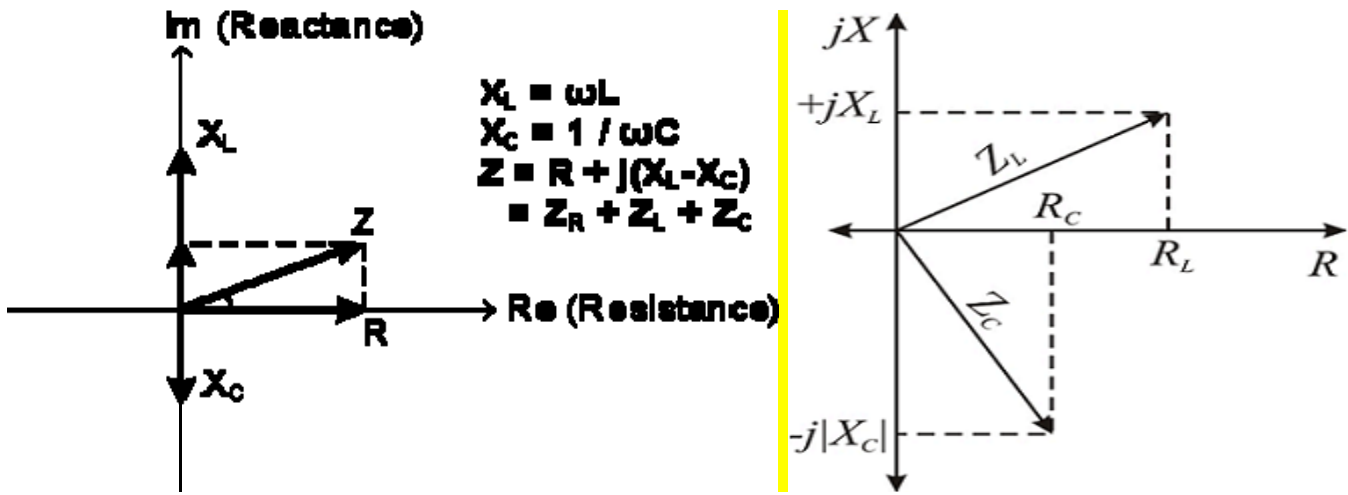8. A single-phase transformer has a ratio of 1:10 and a secondary winding of 1000 turns. The primary winding is connected to a 25 V sinusoidal supply. If the maximum core flux is 2.25 mWb, determine:
- The secondary voltage.
  - The number of primary turns.
  - The frequency of the supply.




Cartesian form:  $Z_L = R_L + j\omega L$

Polar form:  $Z_L = |Z_L| e^{j\phi}$

where  $|Z_L| = \sqrt{R_L^2 + \omega^2 L^2}$

$\phi = \tan^{-1} \frac{\omega L}{R_L}$

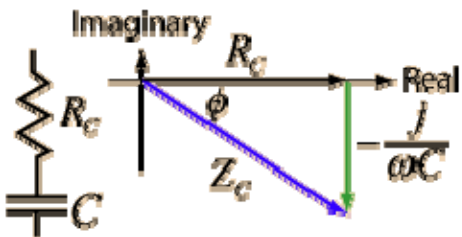



Cartesian form:  $Z_C = R_C - \frac{j}{\omega C}$

Polar form:  $Z_C = |Z_C| e^{-j\phi}$

where  $|Z_C| = \sqrt{R_C^2 + \frac{-1}{\omega C R_C}}$

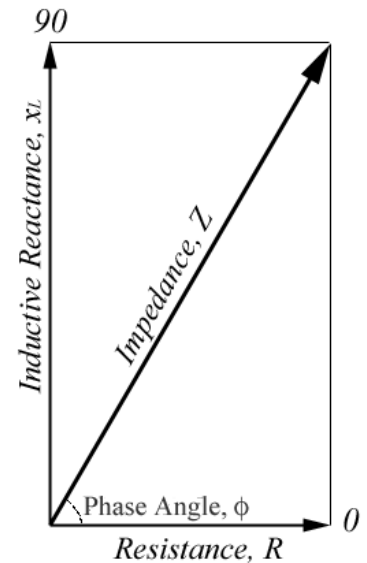$\phi = \tan^{-1} \frac{-1}{\omega C R_C}$



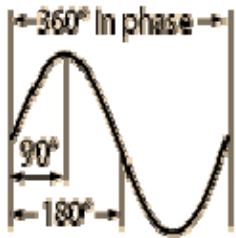

Phase relates a full cycle or period to  $360^\circ$  as a reference.


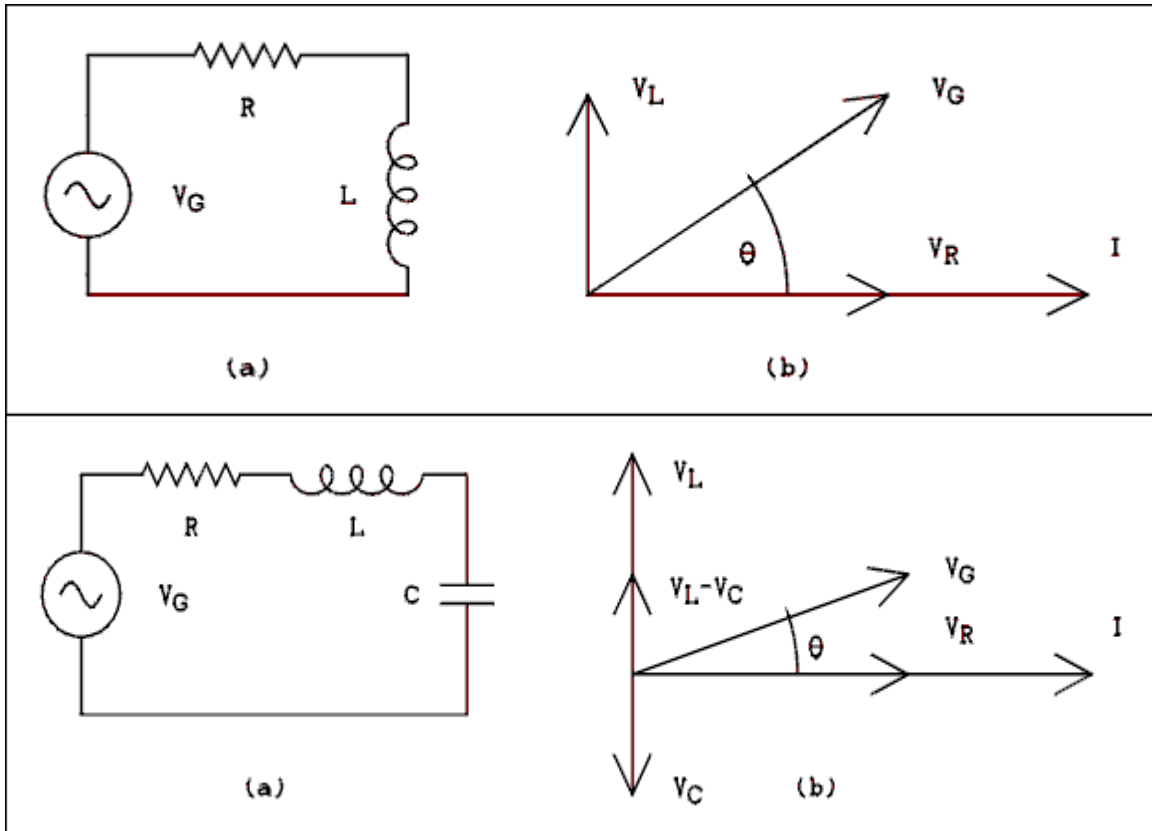
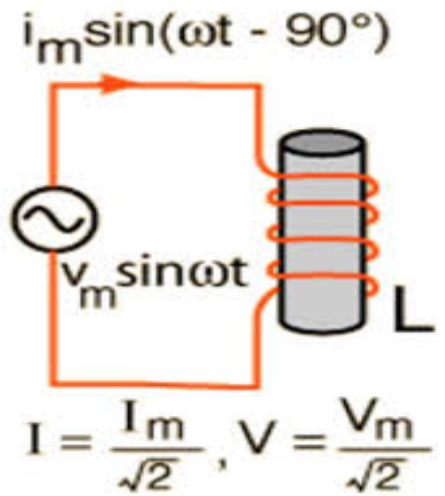
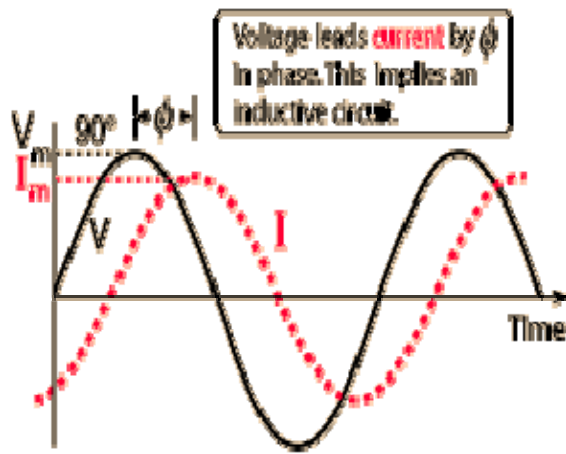


Fig. 10.1.2

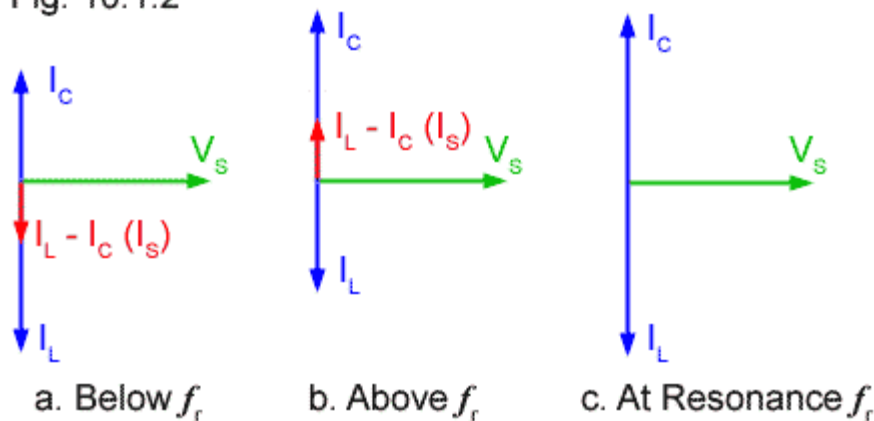

There are three options in a circuit for current. It can be **leading**, **lagging**, or in phase with voltage. These can all be seen when one maps current and voltage of alternating (AC) circuits against time. The only time that the voltage and current are in phase together is when the load is resistive.

### ***Lagging Current***

Lagging current can be formally defined as “an alternating current that reaches its maximum value up to  $90^\circ$  behind the voltage that produces it”.<sup>[6]</sup> This can also be stated as the voltage and current being out of phase. In an inductive circuit, current will be at its maximum phase shift and lagging the voltage.

### ***Leading Current***

Leading current can be formally defined as “an alternating current that reaches its maximum value up to  $90^\circ$  ahead of the voltage that produces it”.<sup>[7]</sup> They are both out of phase from each other. In a purely capacitive circuit, current will be at its maximum phase shift and leading the voltage.

**Inductor current lags voltage**

**Capacitor voltage lags current**



**Example 3** : A single phase transformer has 350 primary and 1050 secondary turns. The primary is connected to 400 V, 50 Hz a.c. supply. If the net cross-sectional area of the core is 50 cm<sup>2</sup>, calculate i) The maximum value of the flux density in the core  
ii) The induced e.m.f. in the secondary winding.

**Solution**

The given value are,

$$N_1 = 350 \text{ turns}, \quad N_2 = 1050 \text{ turns}$$

$$V_1 = 400 \text{ V}, \quad A = 50 \text{ cm}^2 = 50 \times 10^{-4} \text{ m}^2$$

The e.m.f. of the transformer is,

$$E_1 = 4.44 f \Phi_m N_1$$

$$E_1 = 4.44 B_m A f N_1 \quad \text{as } \Phi_m = B_m A$$

Flux density  $B_m = E_1 / (4.44 A f N_1)$

$$= 400 / (4.44 \times 50 \times 10^{-4} \times 50 \times 350) \quad \text{assume } E_1 = V_1$$

$$= 1.0296 \text{ Wb/m}^2$$

$$K = N_2 / N_1 = 1050 / 350 = 3$$

And  $K = E_2 / E_1 = 3$

$\therefore E_2 = 3 \times E_1 = 3 \times 400 = 1200 \text{ V}$

Consider a transformer shown in Fig.1 indicating various voltages and currents.

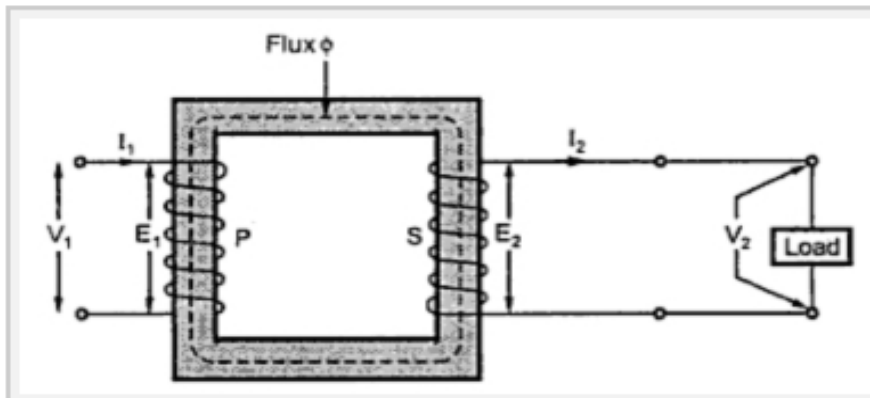


Fig. 1 Ratios of transformer

### 1. Voltage Ratio

We know from the e.m.f. equations of a transformer that

$$E_1 = 4.44 f \Phi_m N_1 \quad \text{and} \quad E_2 = 4.44 f \Phi_m N_2$$









Taking ratio of the two equations we get,

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

This ratio of secondary induced e.m.f. to primary induced e.m.f. is known as voltage transformation ratio denoted as K,

Thus,
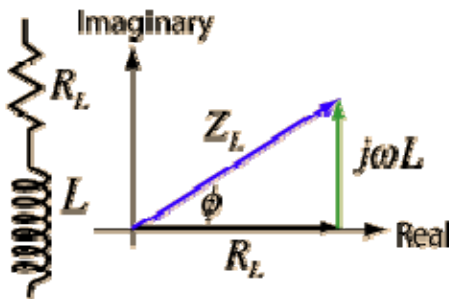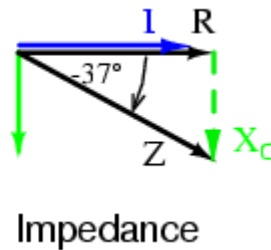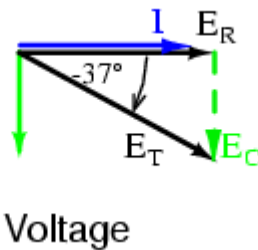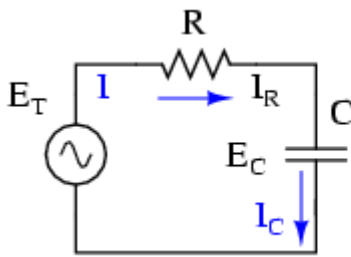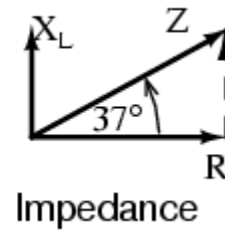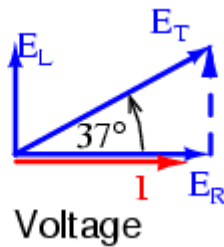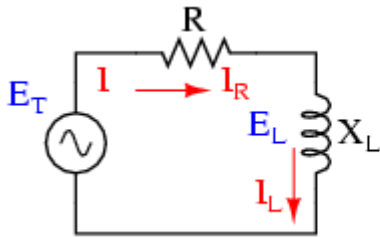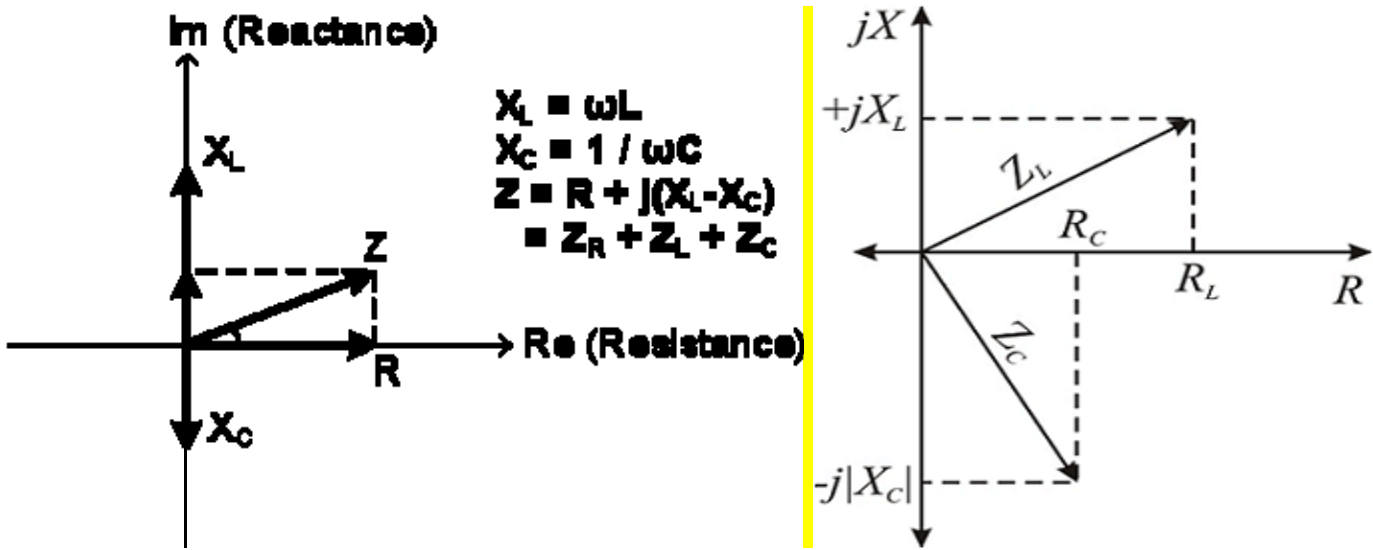
$$E_2 = K E_1 \quad \text{where} \quad K = \frac{N_2}{N_1}$$




Cartesian form:  $Z_L = R_L + j\omega L$

Polar form:  $Z_L = |Z_L| e^{j\phi}$

where  $|Z_L| = \sqrt{R_L^2 + \omega^2 L^2}$

$\phi = \tan^{-1} \frac{\omega L}{R_L}$

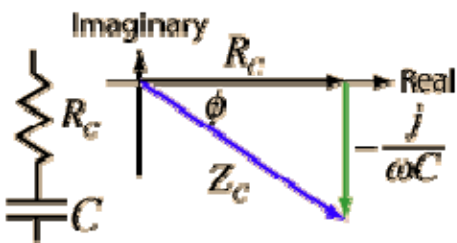



Cartesian form:  $Z_C = R_C - \frac{j}{\omega C}$

Polar form:  $Z_C = |Z_C| e^{-j\phi}$

where  $|Z_C| = \sqrt{R_C^2 + \frac{1}{\omega^2 C^2}}$

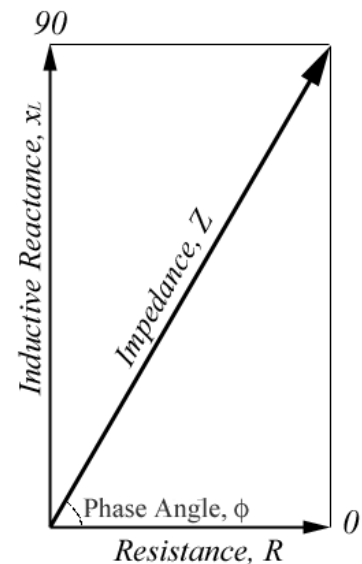$\phi = \tan^{-1} \frac{-1}{\omega C R_C}$



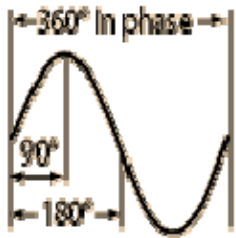

Phase relates a full cycle or period to  $360^\circ$  as a reference.


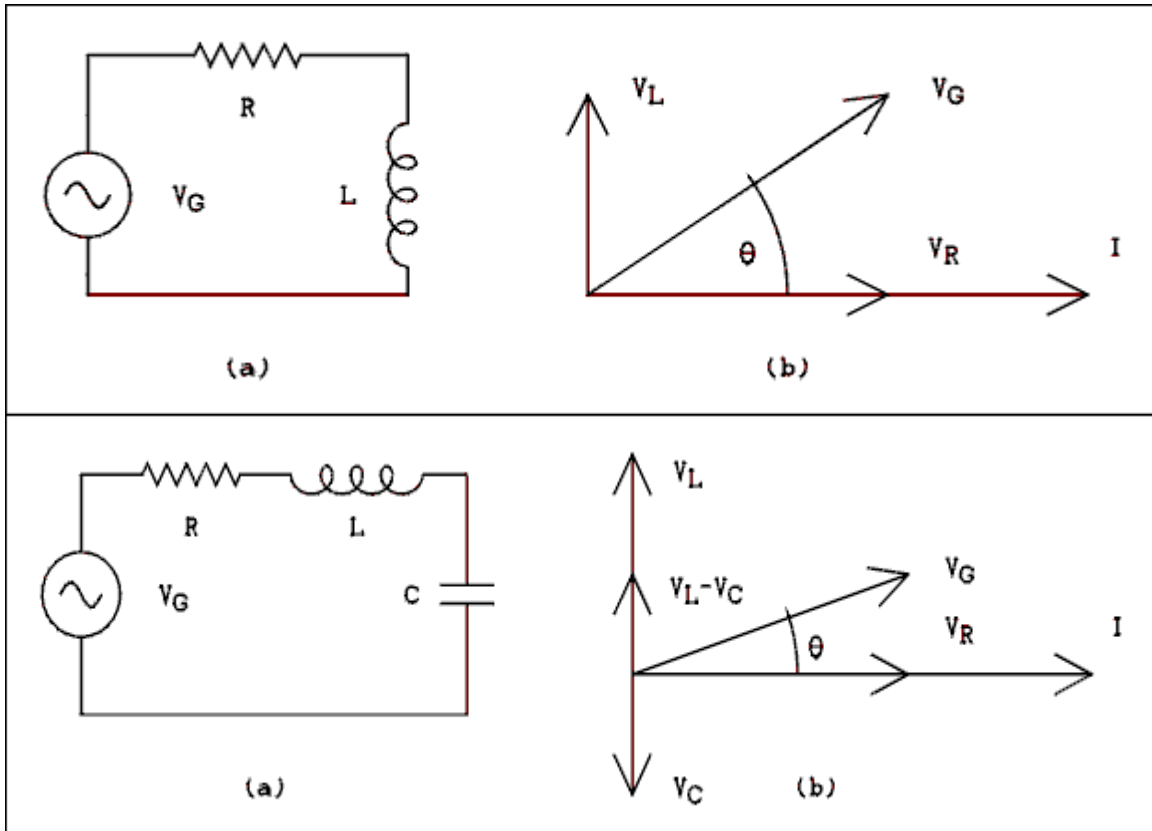
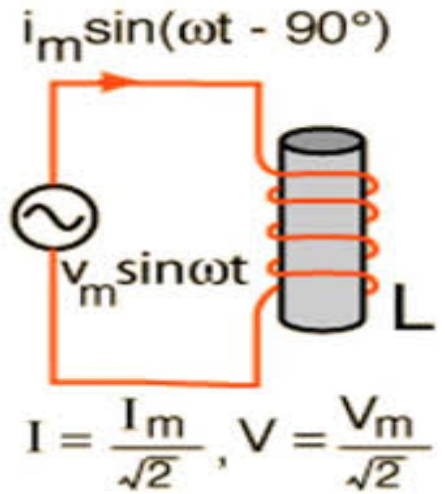
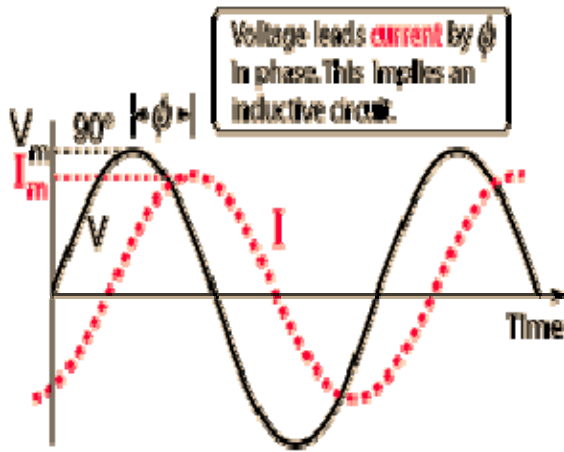


Fig. 10.1.2

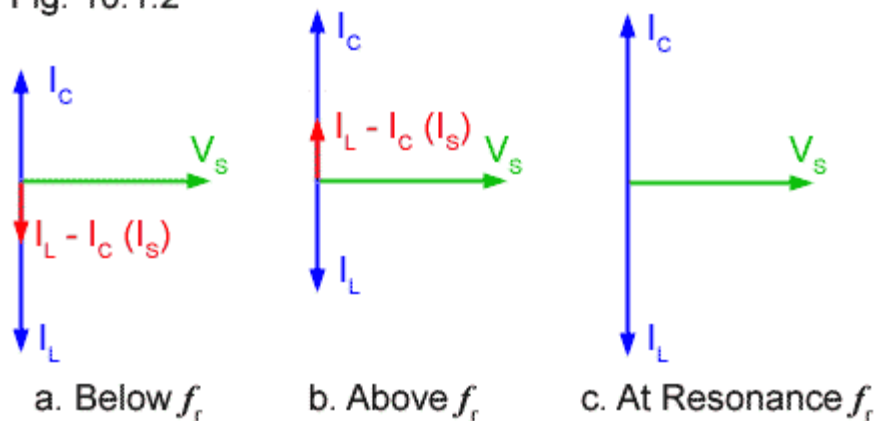

There are three options in a circuit for current. It can be **leading**, **lagging**, or in phase with voltage. These can all be seen when one maps current and voltage of alternating (AC) circuits against time. The only time that the voltage and current are in phase together is when the load is resistive.

### ***Lagging Current***

Lagging current can be formally defined as “an alternating current that reaches its maximum value up to  $90^\circ$  behind the voltage that produces it”.<sup>[6]</sup> This can also be stated as the voltage and current being out of phase. In an inductive circuit, current will be at its maximum phase shift and lagging the voltage.

### ***Leading Current***

Leading current can be formally defined as “an alternating current that reaches its maximum value up to  $90^\circ$  ahead of the voltage that produces it”.<sup>[7]</sup> They are both out of phase from each other. In a purely capacitive circuit, current will be at its maximum phase shift and leading the voltage.

**Inductor current lags voltage**

**Capacitor voltage lags current**