

1. At a large generation station, two generators are connected to the station bus, having the following parameters:

Generator 1	Generator 2
$X_d'' = 0.08 pu$	$X_d'' = 0.09 pu$
$X_d' = 0.12 pu$	$X_d' = 0.13 pu$
$X_d = 1.10 pu$	$X_d = 1.20 pu$
$\tau_d'' = 0.020 s$	$\tau_d'' = 0.020 s$
$\tau_d' = 0.500 s$	$\tau_d' = 0.500 s$

Generator 1 supplies 0.6 pu power at unity power factor and Generator 2 supplies 0.8 pu power at unity power factor to the transmission network. The station bus is maintained at 1.0 pu voltage by adjusting the excitation at each generator.

- Calculate the excitation voltage behind each generator's synchronous reactance under normal operating conditions. (15 pts)
- Using the excitation voltages of part a), determine the steady state, transient, and subtransient short circuit currents for a fault on the station bus. (15 pts)
- The station's circuit breakers take 9.0 cycles (0.150 s) to open during a fault. Specify the maximum fault-interrupting current rating for the circuit break connecting the generator to the station bus. (10 pts)

$$a) \quad E_1 = 1.0 \angle 0^\circ + j0.10 \left(\frac{0.6 - j0.0}{1.0} \right) = 1.2 \angle 33.42^\circ$$

$$E_2 = 1.0 \angle 0^\circ + j1.20 \left(\frac{0.8 - j0.0}{1.0} \right) = 1.39 \angle 43.83^\circ$$

$$b) \quad I_{d1}' = \frac{1.2}{j0.12} = 10 \qquad I_{d2}' = \frac{1.39}{j0.13} = 10.7$$

$$I_{d1}'' = \frac{1.2}{j0.08} = 15 \qquad I_{d2}'' = \frac{1.39}{j0.09} = 15.4$$

$$I_{d1} = \frac{1.2}{j1.10} = 1.09 \qquad I_{d2} = \frac{1.39}{j1.2} = 1.158$$

$$c) \quad I_{\max \text{ GEN CB}} = 10.7$$

2. Consider the following bus-impedance matrix that has been partially completed up to three nodal buses. Compute the new matrix for each new line (branch segment) listed below.

$$Z_{bus} = \begin{bmatrix} j0.08 & j0.03 & j0.07 \\ j0.03 & j0.05 & j0.04 \\ j0.07 & j0.04 & j0.11 \end{bmatrix}$$

- a) Start from the given matrix above, add a branch between bus 2 and 3 having an impedance of $j 0.05$ pu (5 pts)

$$j \begin{bmatrix} 0.08 & 0.03 & 0.07 & -0.04 \\ & 0.05 & 0.04 & 0.01 \\ & & 0.11 & -0.07 \\ & & & 0.13 \end{bmatrix} \xrightarrow[\text{REDUK.}]{\text{KRON}} j \begin{bmatrix} 0.0677 & 0.0331 & 0.0485 \\ & 0.0492 & 0.0454 \\ & & 0.0723 \end{bmatrix}$$

- b) Start from the given matrix above, add a branch starting from bus 2 to a new bus 4 having an impedance of $j 0.03$ pu (5 pts)

$$j \begin{bmatrix} 0.08 & 0.03 & 0.07 & 0.03 \\ & 0.05 & 0.04 & 0.05 \\ & & 0.11 & 0.04 \\ & & & 0.08 \end{bmatrix}$$

- c) Start from the given matrix above, add a branch between bus 1 and the reference node having an impedance of $-j 0.02$ pu (5 pts)

$$j \begin{bmatrix} 0.08 & 0.03 & 0.07 & 0.08 \\ & 0.05 & 0.04 & 0.03 \\ & & 0.11 & 0.09 \\ & & & 0.06 \end{bmatrix} \xrightarrow[\text{REDUK.}]{\text{KRON}} j \begin{bmatrix} -0.0267 & -0.01 & -0.233 \\ & 0.035 & 0.085 \\ & & 0.0283 \end{bmatrix}$$

- d) Start from the given matrix above, add a branch starting from the reference node to a new bus 4 having an impedance of $j 0.05$ pu (5 pts)

$$j \begin{bmatrix} 0.08 & 0.03 & 0.07 & 0 \\ & 0.05 & 0.04 & 0 \\ & & 0.11 & 0 \\ & & & 0.05 \end{bmatrix}$$

3. A large network has the following bus-impedance matrices. Calculate the fault current, I_f and the resulting phase voltages (for each phase, V_a , V_b , & V_c) of all four buses for the following faults. Assume a 1.0 per unit prefault voltage profile throughout the network.

$$Z_{bus}^+ = Z_{bus}^- = j \begin{bmatrix} 0.05 & 0.01 & 0.03 & 0.02 \\ 0.01 & 0.06 & 0.04 & 0.03 \\ 0.03 & 0.04 & 0.05 & 0.02 \\ 0.02 & 0.03 & 0.02 & 0.05 \end{bmatrix} \quad Z_{bus}^0 = j \begin{bmatrix} 0.10 & 0.06 & 0.04 & 0.06 \\ 0.06 & 0.07 & 0.01 & 0.01 \\ 0.04 & 0.01 & 0.03 & 0.01 \\ 0.06 & 0.01 & 0.01 & 0.10 \end{bmatrix}$$

- a) A single-line-to-ground fault at Bus 4 (10 pts)
 b) A double-line-to-ground fault at Bus 3 (10 pts)
 c) A line-to-line fault at Bus 2 (10 pts)
 d) A three-phase fault at Bus 1 (10 pts)

$$a) \quad I_0 = I_1 = I_2 = \frac{V_4}{Z_{44}^0 + Z_{44}^+ + Z_{44}^-} = \frac{1.0}{j0.1 + 2 \times j0.05} = -j5 = I_4^+ = I_4^- = I_4$$

$$I_f = 3I_0 = -j15$$

$$V_N^{[0+-]} = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} - \begin{bmatrix} Z_{N4}^0 \cdot I_4^0 \\ Z_{N4}^+ \cdot I_4^+ \\ Z_{N4}^- \cdot I_4^- \end{bmatrix} \quad Z_{N4}^0 \cdot I_4^0 = j \begin{bmatrix} 0.06 \\ 0.01 \\ -0.01 \\ -0.10 \end{bmatrix} (-j5) = \begin{bmatrix} 0.3 \\ 0.05 \\ 0.05 \\ 0.5 \end{bmatrix}$$

$$Z_{N4}^+ \cdot I_4^+ = Z_{N4}^- \cdot I_4^- = j \begin{bmatrix} 0.02 \\ 0.03 \\ 0.02 \\ 0.05 \end{bmatrix} (-j5) = \begin{bmatrix} 0.1 \\ 0.15 \\ 0.1 \\ 0.25 \end{bmatrix}$$

$$V_N^{ABC} = [A] \cdot \begin{bmatrix} -0.3 & -0.05 & -0.05 & -0.5 \\ 0.9 & 0.85 & 0.9 & 0.75 \\ -0.1 & -0.15 & -0.1 & -0.25 \end{bmatrix} = \begin{matrix} A \\ B \\ C \end{matrix} \begin{matrix} 0.5 \angle 0 & 0.65 \angle 0 & 0.75 \angle 0 & 0 \angle 0 \\ 1.11 \angle -128 & 0.95 \angle -114 & 0.98 \angle -117 & 115 \angle - \\ 1.11 \angle 128 & 0.95 \angle 114 & 0.98 \angle 117 & 115 \angle 1 \end{matrix}$$

N=1 N=2 N=3 N=4

$$b) \quad I_0 = \frac{V_3}{Z_{33}^+ + \frac{Z_{33}^0 Z_{33}^-}{Z_{33}^- + Z_{33}^0}} = \frac{1.0}{j0.05 + \frac{(j0.05)(j0.03)}{(j0.05) + (j0.03)}} = -j14.55 = I_3^+$$

$$I_2 = - \frac{V_3 - Z_{33}^+ I_3^+}{Z_{33}^-} = - \frac{1 - (j0.05)(-j14.55)}{j0.03} = j5.45 = I_3^-$$

$$I_0 = - \frac{V_3 - Z_{33}^0 I_3^+}{Z_{33}^0} = - \frac{1 - (j0.05)(-j14.55)}{j0.03} = j9.10 = I_3^0$$

$$I_f = 3I_3^0 = j27.3$$

Continuation of problem 3

$$b) \text{ CONT} \quad Z_{N3}^+ \cdot I_3^+ = \begin{bmatrix} 0.4365 \\ 0.5820 \\ 0.7275 \\ 0.2910 \end{bmatrix} \quad Z_{N3}^- \cdot I_3^- = \begin{bmatrix} -0.1635 \\ -0.2180 \\ -0.2725 \\ -0.1090 \end{bmatrix} \quad Z_{N3}^0 \cdot I_3^0 = \begin{bmatrix} -0.364 \\ -0.091 \\ -0.273 \\ -0.091 \end{bmatrix}$$

$$V_N^{ABC} = [A] \cdot \begin{bmatrix} 0.364 & 0.091 & 0.273 & 0.091 \\ 0.5635 & 0.418 & 0.2725 & 0.709 \\ 0.1635 & 0.218 & 0.2725 & 0.109 \end{bmatrix} = \begin{bmatrix} 1.091 \angle 0 & 0.727 \angle 0 & 0.818 \angle 0 & 0.909 \angle 0 \\ 0.35 \angle -89 & 0.29 \angle -143 & 0 \angle 0 & 0.61 \angle -121 \\ 0.35 \angle 89 & 0.29 \angle 143 & 0 \angle 0 & 0.61 \angle 121 \end{bmatrix}$$

$$c) \quad I_0 = 0 \\ I_1 = -I_2 = \frac{V_2}{Z_{22}^+ + Z_{22}^-} = \frac{1.0}{2(j0.06)} = -j8.3 = I_2^+ = -I_2^-$$

$$I_f = -j\sqrt{3} I_1 = -14.38 \quad Z_{N2}^+ \cdot I_2^+ = -Z_{N2}^- \cdot I_2^- = \begin{bmatrix} 0.083 \\ 0.498 \\ 0.332 \\ 0.249 \end{bmatrix}$$

$$V_N^{ABC} = [A] \cdot \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0.917 & 0.502 & 0.668 & 0.751 \\ 0.083 & 0.498 & 0.332 & 0.249 \end{bmatrix} = \begin{bmatrix} 1.0 \angle 0 & 1.0 \angle 0 & 1.0 \angle 0 & 1.0 \angle 0 \\ 0.98 \angle -124 & 0.5 \angle -180 & 0.58 \angle 150 & 0.66 \angle 139 \\ 0.98 \angle 124 & 0.5 \angle 180 & 0.58 \angle 150 & 0.66 \angle 139 \end{bmatrix}$$

$$d) \quad I_f = \frac{V_1}{Z_{11}^+} = \frac{1.0}{j0.05} = -j20 = I_1^+ \quad I_1^- = I_1^0 = 0$$

$$V_{N0}^+ = 1 - Z_{N1}^+ I_1^+ = \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix} - j \begin{bmatrix} 0.05 \\ 0.01 \\ 0.03 \\ 0.02 \end{bmatrix} (-j20) = \begin{bmatrix} 0 \\ 0.8 \\ 0.4 \\ 0.6 \end{bmatrix}$$

$$V_N^{ABC} = [A] \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0.8 & 0.4 & 0.6 \\ 0 & 0 & 0 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0.8 \angle 0 & 0.4 \angle 0 & 0.6 \angle 0 \\ 0 & 0.8 \angle -120 & 0.4 \angle -120 & 0.6 \angle -120 \\ 0 & 0.8 \angle 120 & 0.4 \angle 120 & 0.6 \angle 120 \end{bmatrix}$$