

# Power system Line Analysis

کامپوٹیشنل پاور سسٹم

## Load flow studies

### Data for Load-flow studies:-

- self and mutual admittances.
- the one-line diagram and all its values.
- Transformer rating and impedance, shunt Capacitor rating
- all real power are known at all buses except one
- The swing bus is determined (it is the bus at which the real power is not specified, and it is connected to Gen)
- 

### Gauss-Seidel Method:-


$$V_2 I_2^* = P_2 + jQ_2$$

$$\therefore I_2 = \frac{P_2 - jQ_2}{V_2^*}$$

$$= Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4$$

$$\frac{P_2 - jQ_2}{V_2^*} = Y_{21}V_1 + Y_{22}V_2 + Y_{23}V_3 + Y_{24}V_4$$

$$\therefore V_2 = \frac{1}{Y_{22}} \left[ \frac{P_2 - jQ_2}{V_2^*} - (Y_{21}V_1 + Y_{23}V_3 + Y_{24}V_4) \right]$$

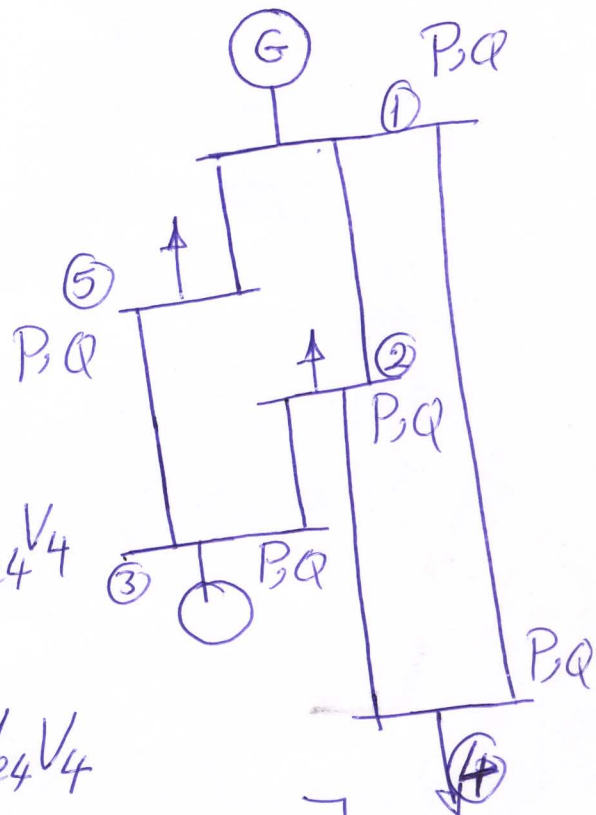


Example 1:-

Given then table 1

bus to bus	R	X
1-2	0.1	0.4
1-4	0.15	0.6
1-5	0.05	0.2
2-3	0.05	0.2
2-4	0.1	0.4
3-5	0.05	0.2

per unit values

Bus	P	Q	V	Remark
1	—	—	1.02∠0°	swing bus
2	-0.6	-0.3	1.0∠0°	Load
3	1	—	1.04	V≠const
4	-0.4	-0.1	1.0∠0°	load
5	-0.6	-0.2	1.0∠0°	load

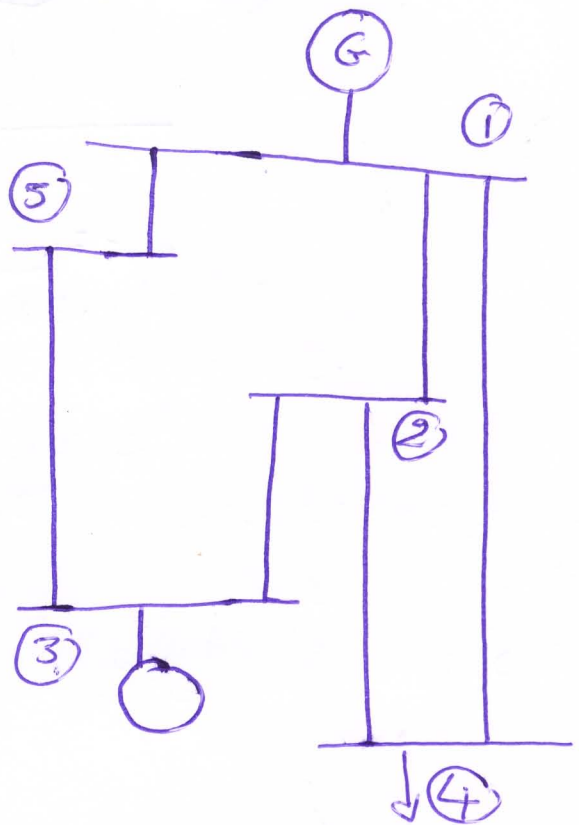

test

$$Z_{12} = 0.1 + j0.4$$

$$Y_{12} = \frac{1}{0.1 + j0.4}$$

$$= \frac{0.1}{(0.1)^2 + (0.4)^2} - j \frac{0.4}{(0.1)^2 + (0.4)^2}$$

$$Y_{12} = 0.5882 - j2.3529$$

After converting  $Z = Y$ , then

Line	G	B
1-2	0.588	-2.359
1-4	0.3921	-1.5686
1-5	1.17647	-4.70588
2-3	0.17647	-4.70588
2-4	-0.588235	-2.352941
3-5	1.176471	-4.705882

We have to find the  $V_2$  for the first iteration

① 1st iteration

$$V_2 = \frac{1}{Y_{22}} \left[ \frac{P_2 - jQ_2}{V_2^*} - (Y_{21}V_1 + Y_{23}V_3 + Y_{24}V_4 + Y_{25}V_5) \right]$$

$$\therefore V_2 = \frac{1}{Y_{22}} \left\{ \frac{-0.6 + j0.3}{1.0 + j0} - [1.02(-0.5882 + j2.3529) + 1.04(-1.17647 + j4.70588) + (-0.588235 + j2.3529)] \right\}$$

②

$$\therefore V_2 = \frac{1}{Y_{22}} (-0.6 + j0.3 + 2.411764 - j9.647058)$$

$$= 0.98 - j0.0525 \text{ P.u}$$

by the correction factor  $\equiv$  acceleration factor

$V_2$  is calculated again by using  $V_2^*$

$$\therefore V_2 = \frac{1}{Y_{22}} \left( \frac{-0.6 + j0.3}{0.98 + j0.0525} + 2.411764 - j9.647 \right)$$

$$= 0.976351 - j0.050965$$

$$P_k - jQ_k = (Y_{kk} V_k + \sum_{n=1}^n Y_{kn} V_n) V_k^*$$

if  $n \neq k$

$$\therefore P_k - jQ_k = V_k^* \sum_{n=1}^N Y_{kn} V_n$$

$$\therefore Q_k = -\text{Im} \left\{ V_k^* \sum_{n=1}^N Y_{kn} V_n \right\}$$

Example 2 - find the first iteration of  $V_3$  at the previous example using the last value of  $V_2$

$$Q_3 = -\text{Im} \left\{ [V_3^* (Y_{13} V_1 + Y_{23} V_2 + Y_{34} V_4 + Y_{35} V_5) + Y_{33} V_3] \right\}$$

$$= -\text{Im} \left\{ [1.04 (2.352941 - j9.4117) + (0.976351 - j0.0509) (-1.1764 + j4.7058) + (-1.17647 + j4.70588) ] 1.04 \right\}$$

$$= \underline{\underline{0.444913}}$$

$$\therefore V_3 = \frac{1}{y_{33}} \left\{ \frac{1.0 - j0.444913}{1.04} - \left[ (-1.176 + j4.70588)(0.9763 - j0.0509) + (-1.176471 + j4.705882) \right] \right\}$$

$$= 1.054984 + j0.059979 \Rightarrow |V_3| = 1.056688$$

This  $V_3$  is recalculated as follows

$$V_3 = \frac{1.04}{1.056688} (1.054984 + j0.059979)$$

$$= 1.038322 + j0.059032 \text{ p.u.}$$