

- 1- Three loads are connected in parallel across a 12.47 kV three-phase supply.
Load 1: Inductive load, 60 kW and 660 kvar. Load 2: Resistive load of 60 kW.
Load 3: Capacitive load, 240 kW at 0.8 power factor. Write Matlab Script File to:
- (a) Find the total complex power, power factor, and the supply current.
 - (b) A Y-connected capacitor bank is connected in parallel with the loads. Find the total kvar and the capacitance per phase in μF to improve the overall power factor to 0.8 lagging?
 - (c) What is the new line current in part (b)?
- 2- A 34.64-kV, 60-MVA, three-phase salient-pole synchronous generator has a direct axis reactance of 13.5Ω and a quadrature-axis reactance of 9.333Ω . The armature resistance is negligible. Write Matlab Script File to Compute the load angle δ and the per phase excitation voltage E when the generator delivers rated MVA, 0.8 power factor lagging to an infinite bus bar of 34.64-kV line-to-line voltage.
-

- 1- Three loads are connected in parallel across a 12.47 kV three-phase supply.
Load 1: Inductive load, 60 kW and 660 kvar. Load 2: Resistive load of 60 kW.
Load 3: Capacitive load, 240 kW at 0.8 power factor. Write Matlab Script File to:
- (a) Find the total complex power, power factor, and the supply current.
 - (b) A Y-connected capacitor bank is connected in parallel with the loads. Find the total kvar and the capacitance per phase in μF to improve the overall power factor to 0.8 lagging?
 - (c) What is the new line current in part (b)?
- 2- A 34.64-kV, 60-MVA, three-phase salient-pole synchronous generator has a direct axis reactance of 13.5Ω and a quadrature-axis reactance of 9.333Ω . The armature resistance is negligible. Write Matlab Script File to Compute the load angle δ and the per phase excitation voltage E when the generator delivers rated MVA, 0.8 power factor lagging to an infinite bus bar of 34.64-kV line-to-line voltage.
-

- 1- Three loads are connected in parallel across a 12.47 kV three-phase supply.
Load 1: Inductive load, 60 kW and 660 kvar. Load 2: Resistive load of 60 kW.
Load 3: Capacitive load, 240 kW at 0.8 power factor. Write Matlab Script File to:
- (a) Find the total complex power, power factor, and the supply current.
 - (b) A Y-connected capacitor bank is connected in parallel with the loads. Find the total kvar and the capacitance per phase in μF to improve the overall power factor to 0.8 lagging?
 - (c) What is the new line current in part (b)?
- 2- A 34.64-kV, 60-MVA, three-phase salient-pole synchronous generator has a direct axis reactance of 13.5Ω and a quadrature-axis reactance of 9.333Ω . The armature resistance is negligible. Write Matlab Script File to Compute the load angle δ and the per phase excitation voltage E when the generator delivers rated MVA, 0.8 power factor lagging to an infinite bus bar of 34.64-kV line-to-line voltage.

PROB. (1).....

j

$$\begin{aligned} S_1 &= 60 \text{ kW} + j660 \text{ kvar} \\ S_2 &= 60 \text{ kW} + 0 \text{ kvar} \\ S_3 &= 240 \text{ kW} - 180 \text{ kvar} \end{aligned}$$

(a) The total complex power is

$$S = 360 \text{ kW} + j480 \text{ kvar} = 600 \angle 53.13^\circ \text{ kVA}$$

The phase voltage is

$$V = \frac{12.47}{\sqrt{3}} = 7.2 \angle 0^\circ \text{ kV}$$

The supply current is

$$I = \frac{600 \angle -53.13^\circ}{(3)(7.2)} = 27.77 \angle -53.13^\circ \text{ A}$$

The power factor is $\cos 53.13^\circ = 0.6$ lagging.

(b) The net reactive power for 0.8 power factor lagging is

$$Q' = 360 \tan 36.87^\circ = 270 \text{ kvar}$$

Therefore, the capacitor kvar is $Q_c = 480 - 270 = 210 \text{ kvar}$, or $S_c = -j210 \text{ kVA}$.

$$X_c = \frac{|V_L|^2}{S_c^*} = \frac{(12.47 \times 1000)^2}{j210000} = -j740.48 \Omega$$

$$C = \frac{10^6}{(2\pi)(60)(740.48)} = 3.58 \mu\text{F}$$

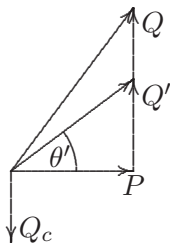


FIGURE 14

The power diagram for Problem 2.15.

$$I = \frac{S^*}{V^*} = \frac{360 - j270}{7.2} = 20.835 \angle -36.87^\circ \text{ A}$$

Solution OF MID TERM EXAM

Prob. (1) Matlab Program

Solution OF MID TERM EXAM

PROB. (2).....

$$V_{\phi} = \frac{34.64}{\sqrt{3}} = 20 \text{ kV}$$

For 60 MVA, 0.8 power factor lagging, $S = 60 \angle 36.87^{\circ}$ MVA

$$I_a = \frac{S^*}{3V_{\phi}^*} = \frac{60000 \angle -36.87^{\circ}}{(3)(20)} = 1000 \angle -36.87^{\circ} \text{ A}$$

$$\delta = \tan^{-1} \frac{(9.333)(1000)(0.8)}{20000 + (9.333)(1000)(0.6)} = 16.26^{\circ}$$

The magnitude of the no-load generated emf per phase is given by

$$\begin{aligned} |E| &= |V| \cos \delta + X_d |I_a| \sin(\theta + \delta) \\ &= 20 \cos 16.26^{\circ} + (13.5)(1000)(10^{-3}) \sin 53.13^{\circ} = 30 \text{ kV} \end{aligned}$$

Prob. (2) Matlab Program