



ECE 344

Microwave Fundamentals


Assistant Professor
Dr. Gehan Sami

- Review :
 - Smith chart example
 - SWR meaning

- Quiz

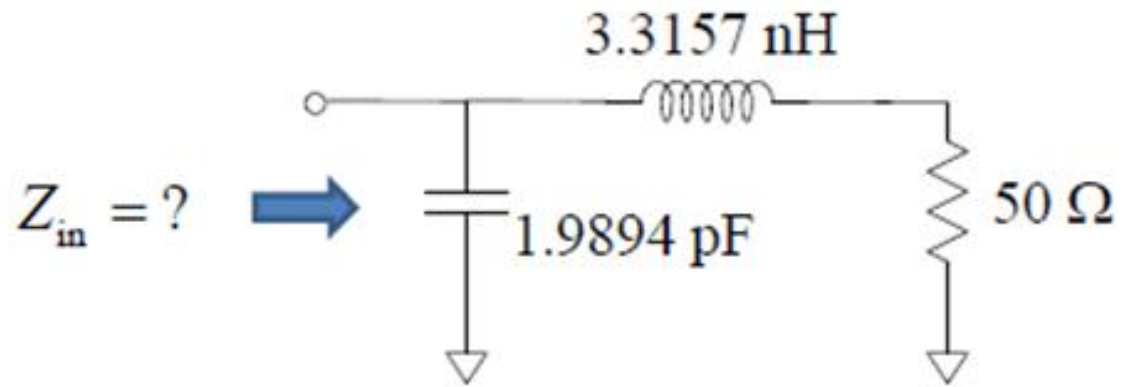Example 1

$$\begin{aligned} Z_{in} &= \frac{1}{j\omega C} \parallel (R + j\omega L) \\ &= \frac{\frac{1}{j\omega C}(R + j\omega L)}{\frac{1}{j\omega C} + (R + j\omega L)} \\ &= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC} \end{aligned}$$





$$\begin{aligned} f &= 2.4 \text{ GHz} \\ Z_0 &= 50 \Omega \end{aligned}$$

$$\begin{aligned} &= \frac{50 + j(1.5080 \times 10^{10})(3.3157 \times 10^{-9})}{1 - (1.5080 \times 10^{10})^2 (3.3157 \times 10^{-9})(1.9894 \times 10^{-12}) + j(1.5080 \times 10^{10})(50)(1.9894 \times 10^{-12})} \\ &= 20 - j40 \Omega \end{aligned}$$

$$\Gamma = \frac{(20 - j40) - 50}{(20 - j40) + 50} = 0.62 \angle -98^\circ$$

$$\text{VSWR} = 4.2654$$

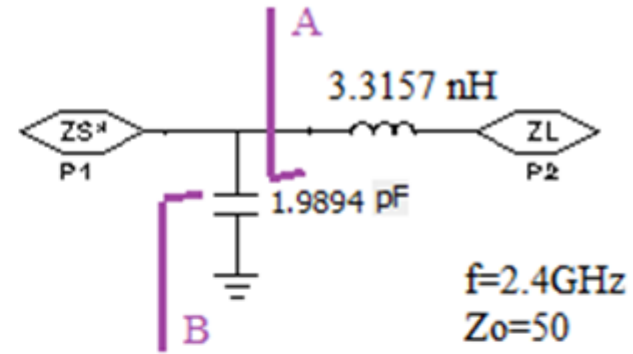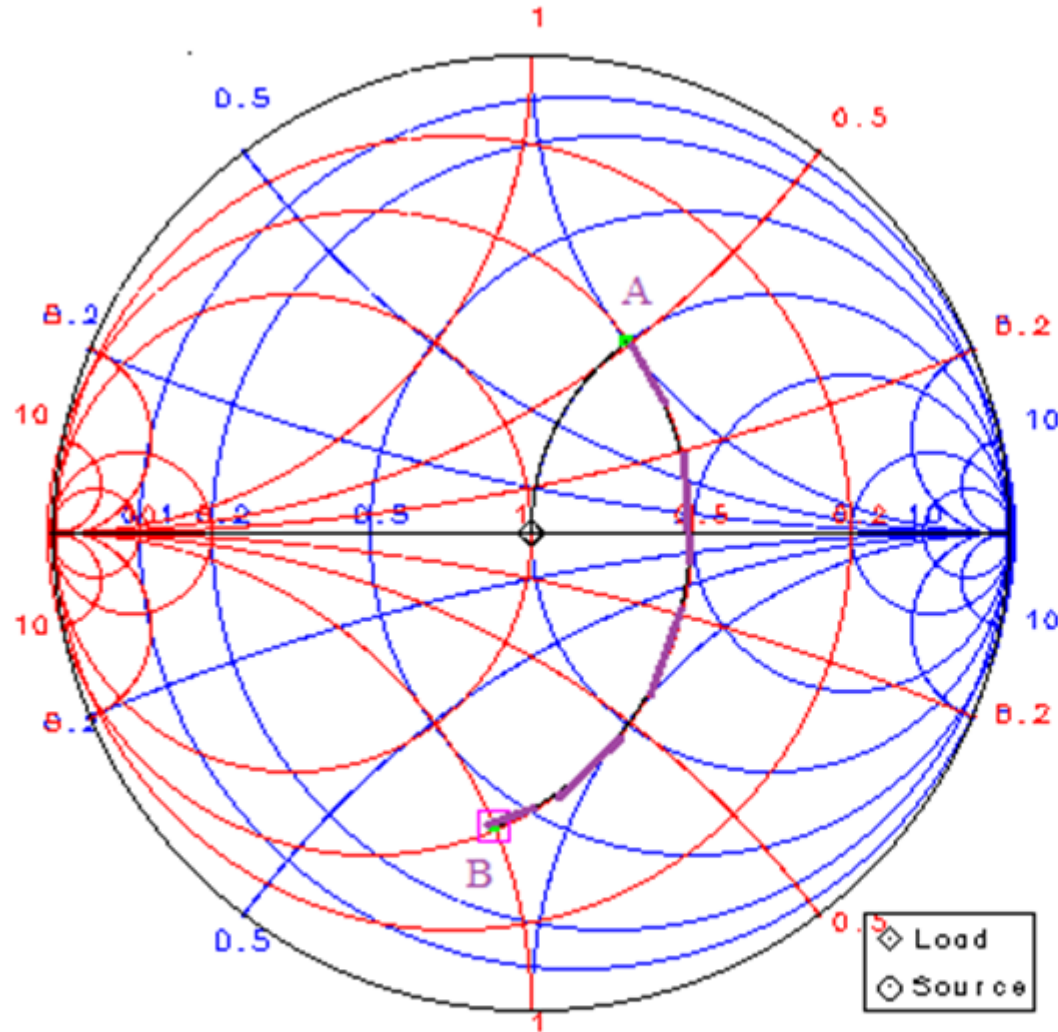Normalized value is used in impedance admittance smith chart (also using ADS smithchart)



$$Z_L = 50$$

$$Z_A = 50 + j2\pi \cdot 2.4 \cdot 3.3157$$

$$Z_A / Z_0 = 1 + j1$$


$$B_{cn} = 2\pi \cdot 2.4 \cdot 10^9 \cdot 1.9894 \cdot 10^{-12} \cdot 50 = 1.5$$

(B) Z, Y, and Gamma

Gamma:	0.62016	<	-97.1237	Z:	0.40002	+j	-0.80001	← ZB/Zo
VSWR:	4.26541			Y:	0.50000	+j	0.99997	ZB=20-j40

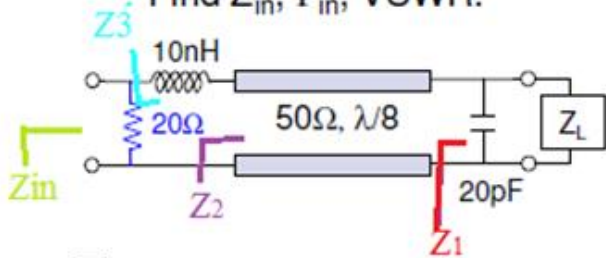Example 2 with shunt C, G, series L and TL

e.g. $Z_L = 20 - j25 \Omega$
 $f = 159 \text{ MHz}$ ($\omega = 10^9$)
 Find Z_{in} , Γ_{in} , VSWR.



$$\bar{Z}_L = 0.4 - j0.5$$



$$\bar{B} = \omega C / Y_0 = 0.02 Z_0 = 1$$

$$\bar{X} = \omega L / Z_0 = 10 / Z_0 = 0.2$$

$$\bar{G} = G / Y_0 = Z_0 / R = 50 / 20 = 2.5$$

$$Z_{in} = 50(0.28 + j0.13) = 14 + j7 \Omega$$

$$\Gamma_{in} = 0.57 (164^\circ)$$

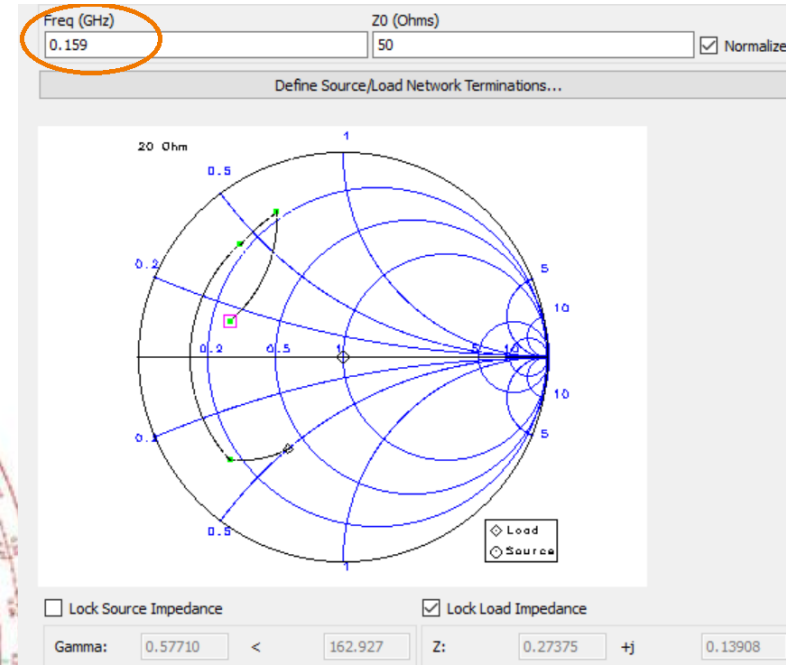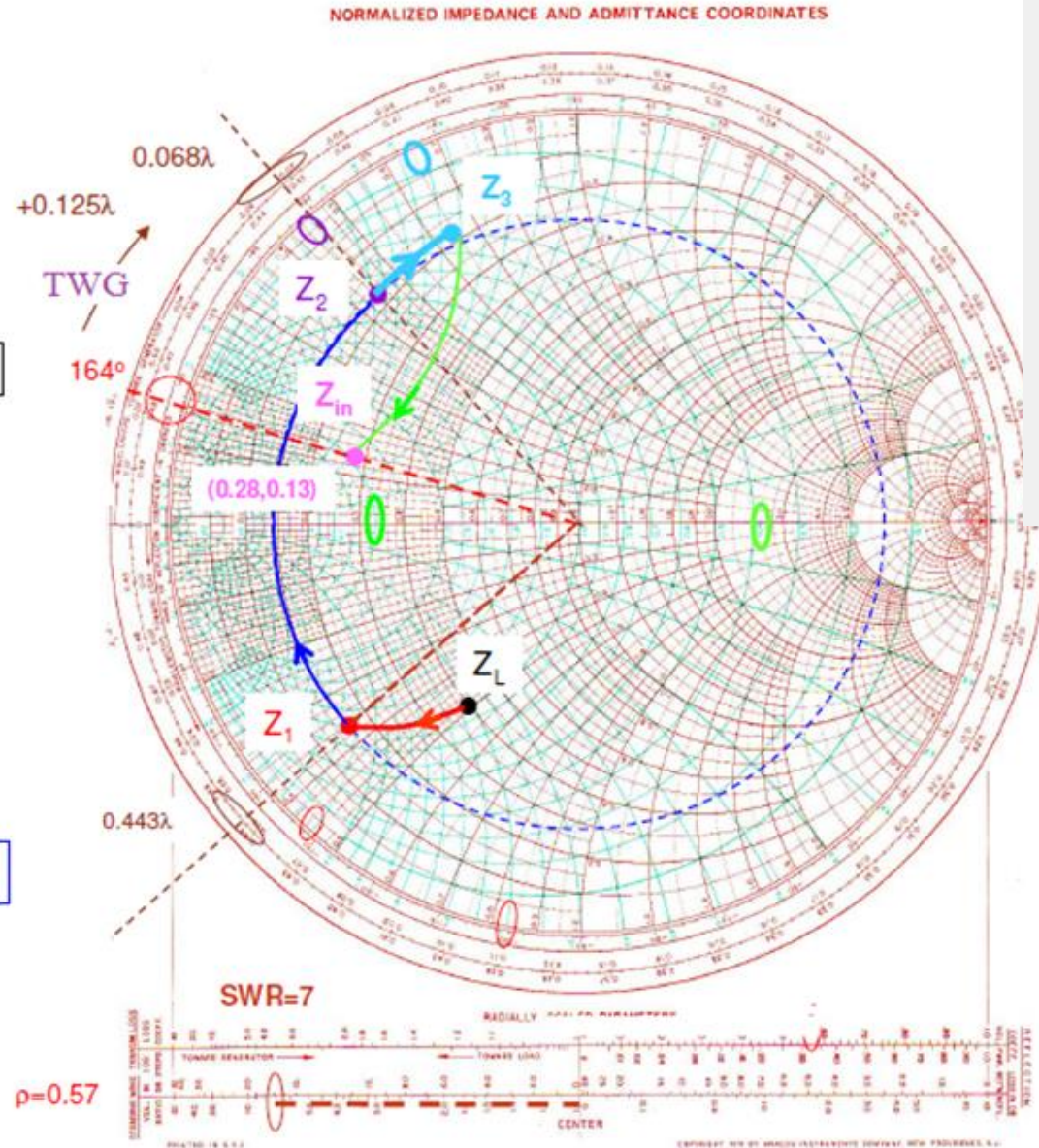

Voltage Standing Wave Ratio


$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$= V_0^+ e^{j\beta\ell} (1 + |\Gamma_L| e^{j\phi_L} e^{-2j\beta\ell})$$

$$|V(-\ell)| = |V_0^+| |1 + |\Gamma_L| e^{j\phi_L} e^{-j2\beta\ell}|$$

$$V_{\max} = |V_0^+| (1 + |\Gamma_L|)$$

$$V_{\min} = |V_0^+| (1 - |\Gamma_L|)$$

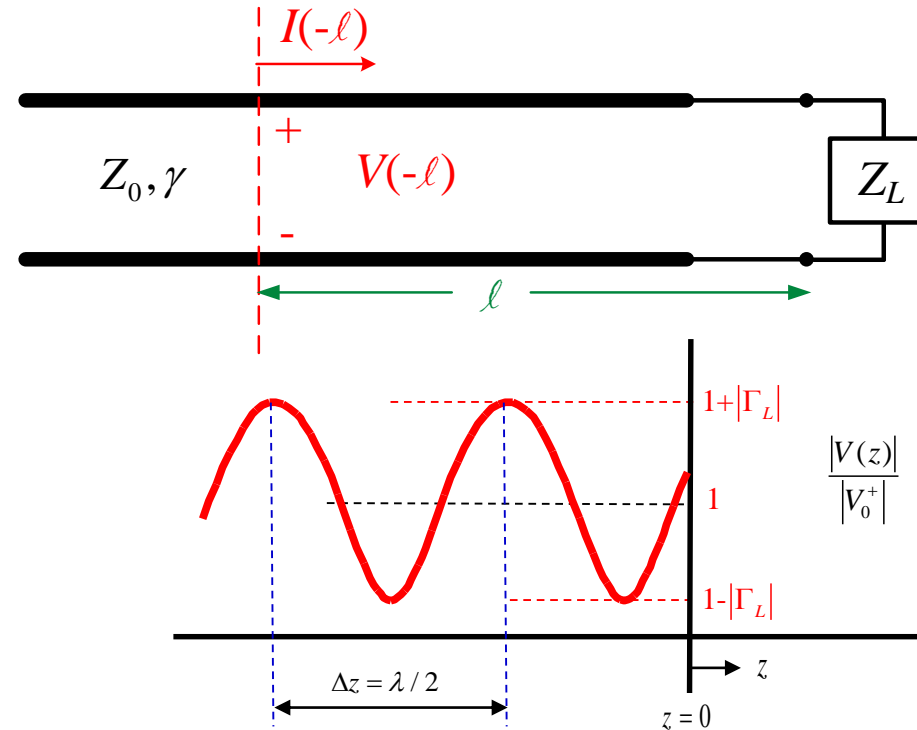

$$\text{Voltage Standing Wave Ratio (VSWR)} = \frac{V_{\max}}{V_{\min}}$$

$$\text{VSWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Standing Waves -Matched

Matched Line ($Z_L = Z_o$), we had

$$Z_{in} = Z_o, \quad \Gamma_L = 0, \quad s = 1$$

■ So substituting in $V(z)$


$$V(z) = V^+ [e^{j\beta l} + (0)e^{-j\beta l}]$$

$$V(z) = V^+ e^{j\beta l}$$


$$|V(z)| = |V^+| |e^{j\beta l}|$$

$$|V(z)| = |V^+|$$

$|V(z)|$ does not depend on z

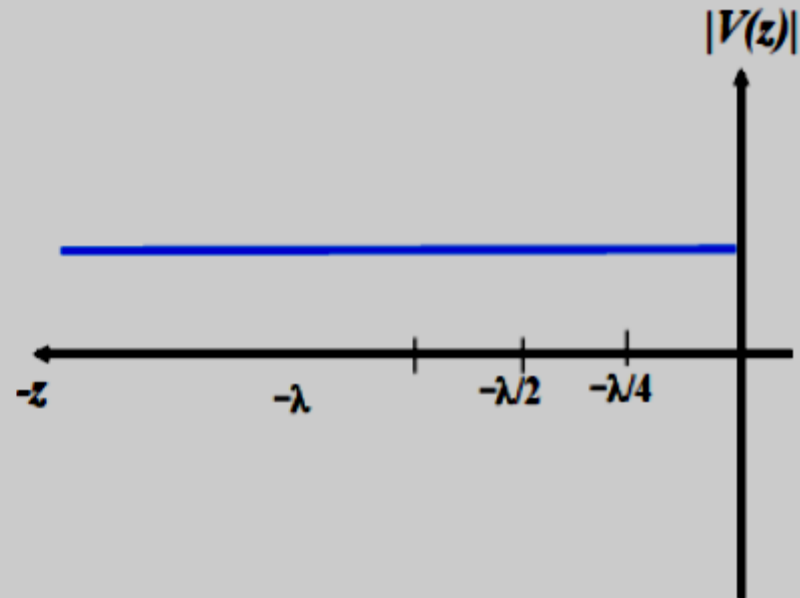

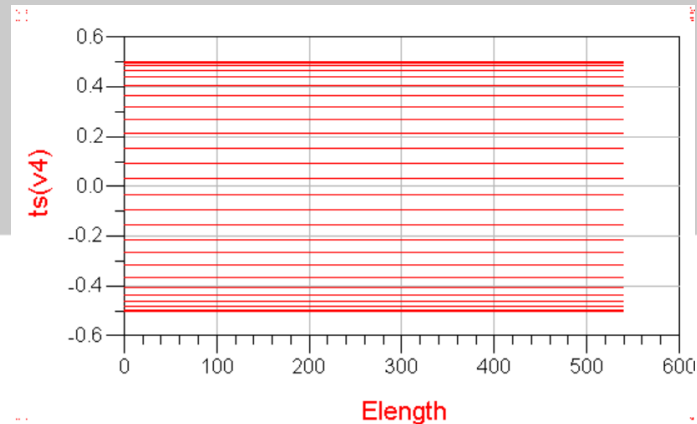Simulation ADS mag(V(z)) with time changing



Standing Waves -Short

Shorted Line ($Z_L=0$), we had

$$Z_{in} = jZ_o \tan \beta l, \quad \Gamma_L = -1, \quad s = \infty$$


■ So substituting in $V(z)$

$$V(z) = V^+ [e^{j\beta l} + (-1)e^{-j\beta l}]$$

$$V(z) = V^+ (2j \sin \beta l)$$


$$|V(z)| = |V^+| 2 \sin(\beta l)$$

$$|V(z)| = |V^+| 2 \sin\left(\frac{2\pi}{\lambda} l\right)$$

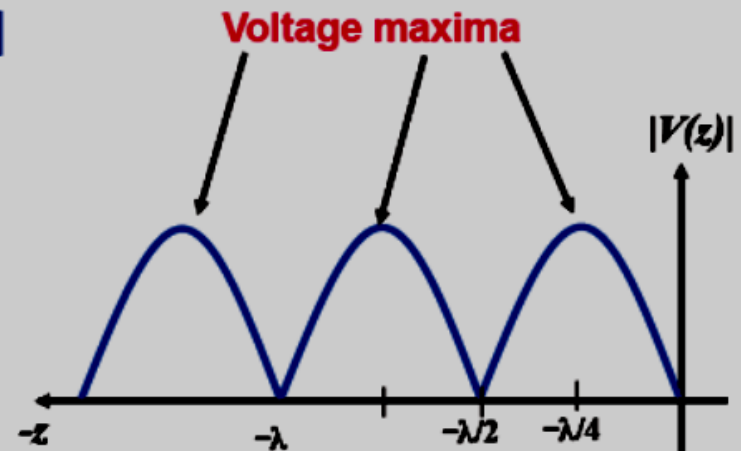

*Voltage **minima** occurs at same place that impedance has a **minimum** on the line

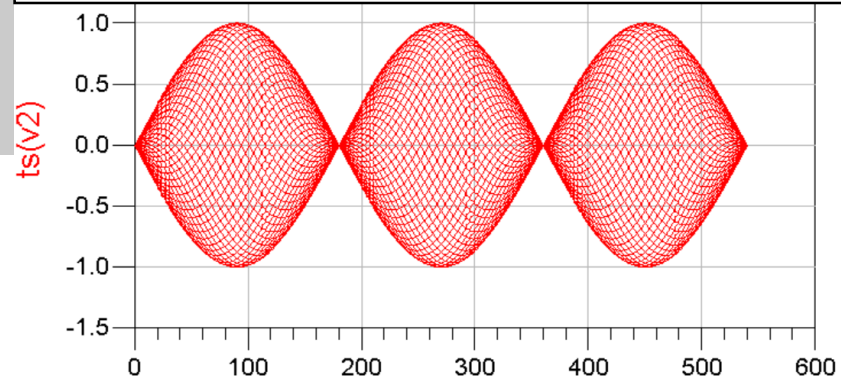Simulation with ADS time signal vs length



Length

Standing Waves - Open

Open Line ($Z_L = \infty$), we had

$$Z_{in} = -jZ_o \cot \beta l, \quad \Gamma_L = +1, \quad s = \infty$$


■ So substituting in $V(z)$

$$V(z) = V^+ [e^{j\beta l} + (+1)e^{-j\beta l}]$$

$$V(z) = V^+ (2 \cos \beta l)$$

$$|V(z)| = |V^+| |2 \cos(\beta l)|$$

$$|V(z)| = |V^+| \left| 2 \cos\left(\frac{2\pi}{\lambda} l\right) \right|$$

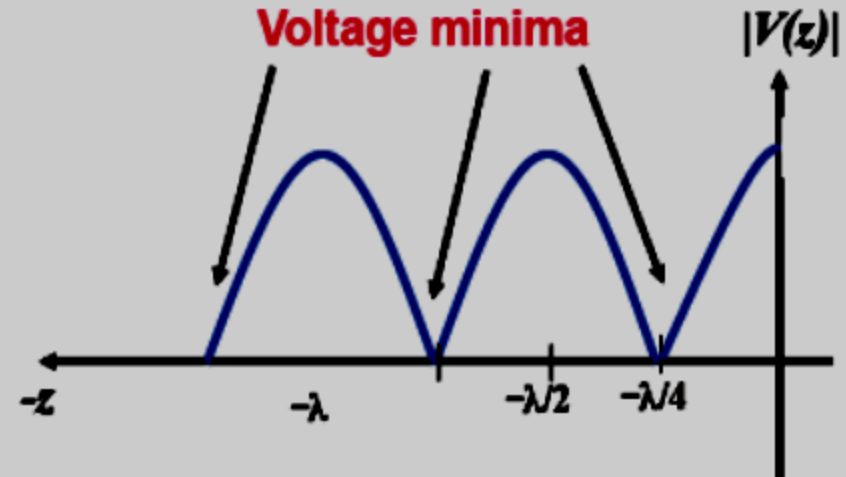

Simulation with ADS time signal vs length

