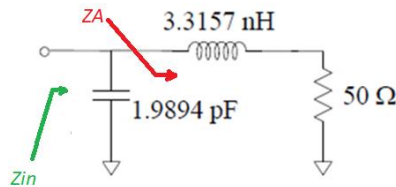





Sheet 5


- Using smith chart find  $Z_{in}$ ,  $\Gamma_{in}$ , VSWR for  $50 \Omega$  transmission line connected to the circuit below  
 $f=2.4\text{GHz}$



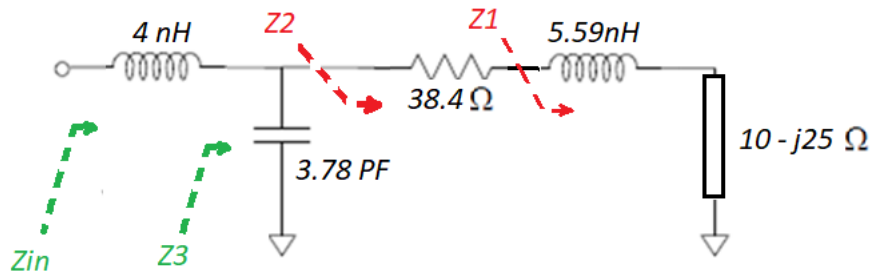- Using smith chart locate  $Z_1, Z_2, Z_3$  and  $Z_{in}$ , find  $\Gamma_{in}$ , VSWR for  $50 \Omega$  transmission line connected to the circuit below  
 $f=1\text{GHz}$



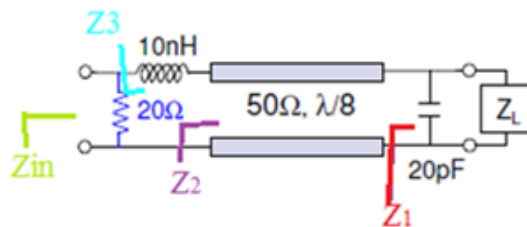- Compute the normalized impedance/admittance points ( $Z_L, Z_1, Z_2, Z_3$  and  $Z_{in}$ ) in figure below; locate these points on impedance/admittance Smith chart and show the solution track on smith. find  $Z_{in}$ ,  $\Gamma_{in}$ , VSWR.  
 $f=159\text{MHz}$




*Good Luck*

*Dr. Gehan Sami*


*Final solutions :*

*Note: all impedances/admittances are normalized, convert to un-normalized values by yourself.*


**Q1:**

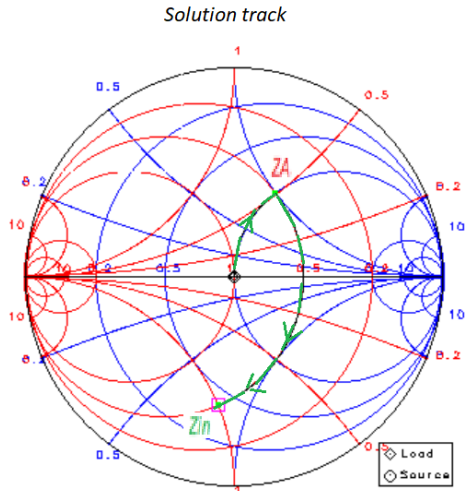

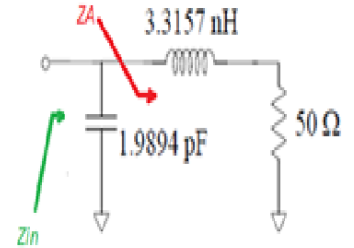$Z_A = 1 + j1$   
 $Z_{in} = 0.4 - j0.8$      $Y_{in} = 0.5 + j1$   
 input reflection coefficient  $0.62 \angle -97^\circ$   
 $VSWR = 4.27$




**Q2:**

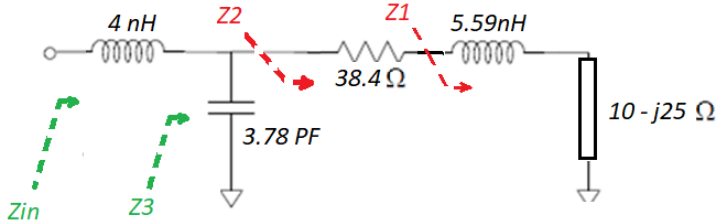


$Z_{Ln} = 0.2 - j0.5$   
 $Z_1 = 0.2 + j0.2$   
 $Z_2 = 0.97 + j0.2$      $Y_2 = 1 - 0.2j$   
 $Y_3 = 1 + j1$      $Z_3 = 0.5 - j0.5$   
 $Z_{in} = 0.5$

input reflection coefficient =  $0.324 \angle 180^\circ$   
 $VSWR = 1.96$

Get from smith

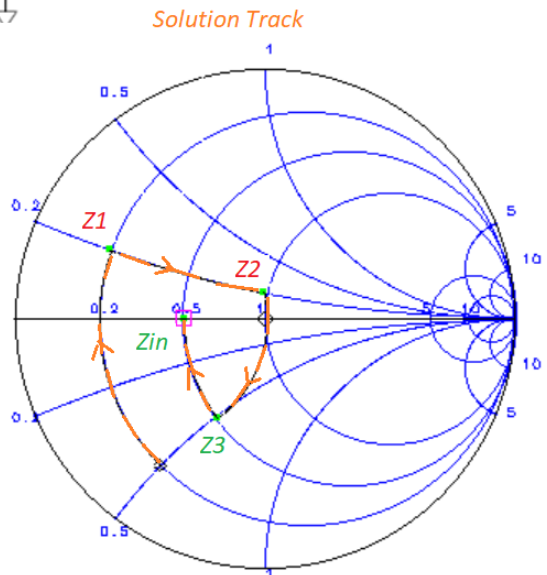

Q3:

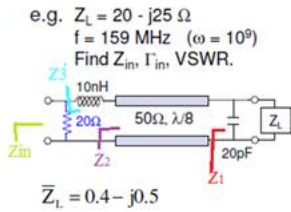

$$Y1 = 0.98 + j2.2 \quad Z1 = 0.166 - j0.378$$

$$Z2 = 0.172 + j0.43$$


$$Z3 = 0.172 + j0.63 \quad Y3 = 0.4 - j1.48$$

$$Y_{in} = 2.9 - j1.48 \quad Z_{in} = 0.27 + j0.139$$

$$Z_{in} = 50(0.28 + j0.13) = 14 + j7 \Omega$$

$$\Gamma_{in} = 0.57 (164^\circ)$$

### Solution Track

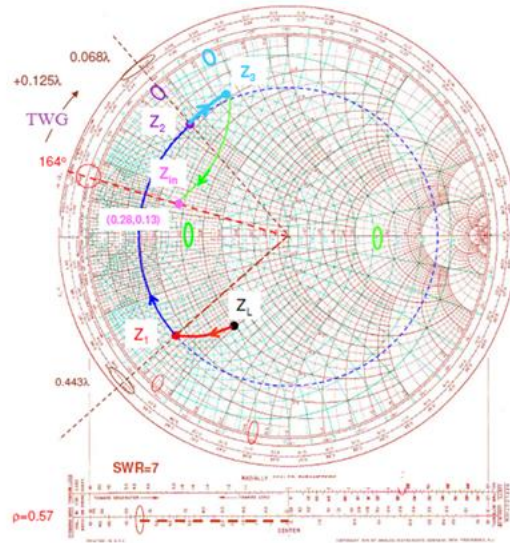

$$\bar{B} = \omega C / Y_0 = 0.02 Z_0 = 1$$

$$\bar{X} = \omega L / Z_0 = 10 / Z_0 = 0.2$$

$$\bar{G} = G / Y_0 = Z_0 / R = 50 / 20 = 2.5$$