

ECE 344


MICROWAVE FUNDAMENTALS PART1-Lecture 3

Dr. Gehan Sami

Many Slides from: ECE 5317_6351 Microwave Engineering Prof. David R. Jackson


ADS Examples: Characteristic impedance depend on dimension only


 $Z_o = \sqrt{Z_{sc}Z_{oc}}$

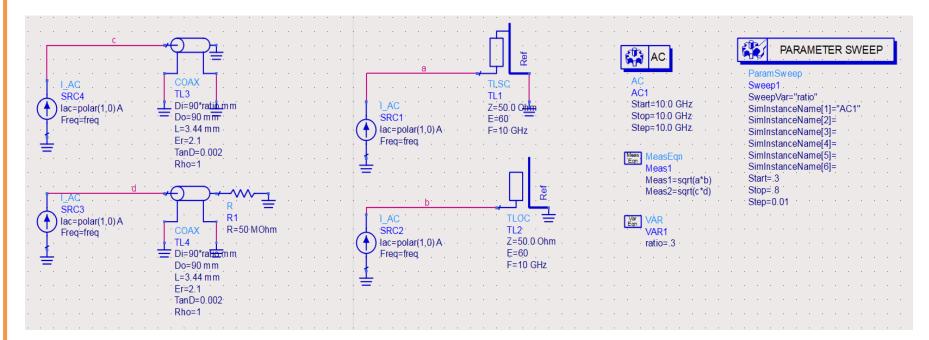

Note as I=1 V=Zin so points a,b,c,d measure input impedance

To get Zo=50Ω, a/b=26.87/90=.3

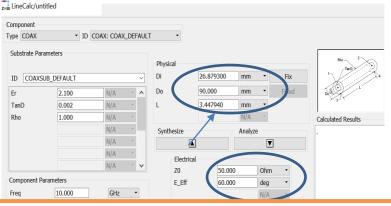

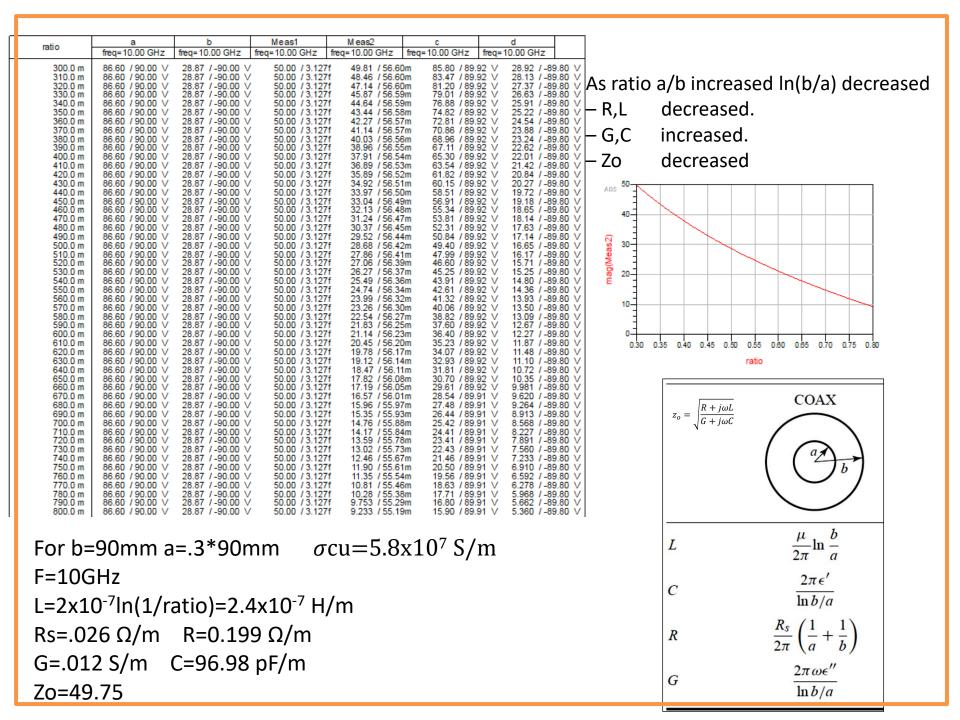

Compute Attenuation/m in Coaxial Using: Line Calc.

S parameter calc.


Equations

	· · · · · · · · · · · ·
	S-PARAMETERS
$\begin{array}{c} + & Term \\ \hline Term 1 \\ Num=1 \\ Z=50 \text{ Ohm} \\ \hline \\ = \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\ \\$	S_Param SP1 Start=10 GHz Stop=10.0 GHz Step=1.0 GHz
TanD=0.002 ^{··································}	

<u>Compute Attenuation/m in Coaxial Using: Line Calc.</u>

LineCalc/unt	itled									—		\times
ile Simulation	Options Hel	р										
🗋 📁 🔚 👜												
Component												
Type COAX	• ID	COAX: COAX_	DEFAULT	- -								
-Substrate Parar	meters			2 Physical						Rho	2	0
ID COAXSU	B_DEFAULT		×	Di	90*.3	mm	•	Fix		1Tan		×4
Er	2.100	N/A	~ /	Do	90.000	mm	•	Fixed		D.B.		
TanD 1	0.002	N/A	~	L	1.000	meter	•			3		
Rho	1.000	N/A	~			N/A	~			Calculated Re	sults	
		N/A	~	Synthesize		Analyze	5		_	A_DB = 2.67		
		N/A	~			3	▼					
		N/A	~	Electrical						Attenuati	on in dE	2
		N/A	- N	ZO	49	.814700	Ohm	-		2 Ittendari	JII III GI	·
Component Par	ameters			E_Eff		401.700000	deg	•				
Freq	10.000	GHz	•				N/A	~				
		N/A	~				N/A	~				
		N/A	~				N/A	-				
/alues are consist	tent								L			
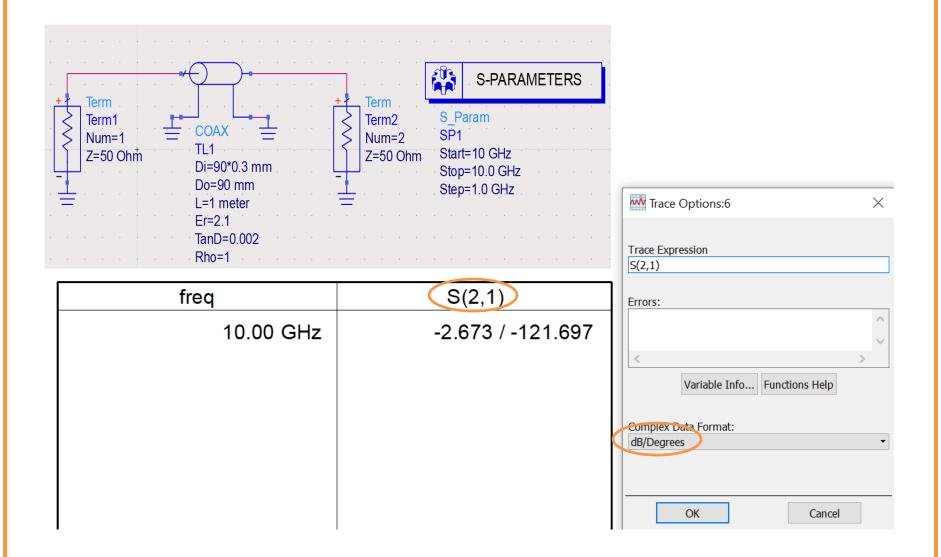
<u>Compute Attenuation/m in Coaxial Using: S parameter Calc.</u>



Using Equations
$$\sqrt{\frac{4m}{2\pi^2}}v_2 = v_3 = v_4 = v_5 = e^{-j\beta l}$$

$$S_{21} = \frac{V_2}{V_1}$$

$$= e^{-\alpha l} e^{-j\beta l} \frac{ind^3 }{20 \log l}$$

$$Gret \ll \beta from \qquad \forall = \sqrt{(R+jwL)(G+jwl)}$$

$$R = \frac{1}{2\pi \delta_{effer}} \left(\frac{1}{\alpha} + \frac{1}{b}\right) = \delta = \frac{1}{\sqrt{\pi} f\mu \sigma}$$

$$R = \frac{1}{2\pi \chi_{c-6} \chi_{5-8}} \left(\frac{1000}{0.5 \chi_{WS}} + \frac{1000}{45}\right) = 0.3954 \quad 52/m$$


$$G = \frac{2\pi \chi_{2\pi} \times 10^5 \times 6.002 \times 8.85 \times 10^{12} \chi_{2-1}}{(16\pi)^2} = 6.0(2.5 Mm) \left(\frac{14m}{6} S = \frac{6}{6}\right)$$

$$C = \frac{2\pi \chi_{8-8} 5 \times 10^{-12} \chi_{2-1}}{2\pi (16\sqrt{3})} = 2.41 \times 10^{-7} H/m$$

$$\begin{aligned} & & = \sqrt{(R+jwL)}(G+jwC) = 0.3+j303.12, \quad l=1 \\ & = |S_{2l}| = |e^{-\alpha l}-j\beta l| = -6.3 \\ & = e^{-6.3} \\ & = -6.3 \\ & = -2*61 \end{aligned}$$

Assume loss due to skin depth only


S-PARAMET	ERS			1.1																
Param P1 art=10 MHz op=30 GHz ep= 01 GHz	Term Term1 Num= Z=50 (1 W		mm	" + *	Nu	m m2 m=2 50 Oh			Term Term Num= Z=50	-3	- E=			m	•	•	+		Terr Terr Nur Z=5
	T : .				-4				-			17						-	μ.	
MSub ·	. .				. =	÷			ŧ									. E	= .	
MSUB																				
MSub1 H=20.0 mil																				
Er=2.1																				
Mur=1																				
Cond=5.96E+07																				
Hu=3.9e+034 mil																				
T=1.4 mil																				
TanD=0 Rough=0 mil																				
Bbase=																				
Dpeaks=																				
-																				1
IineCalc/untit															-				×	
File Simulation	Options Help	LIN: MLIN_	DEFAULT	7	•										-				×	
File Simulation	Options Help TID M eters	LIN: MLIN_	DEFAULT		vysical	1	.56985	50	mm						-			-	×	
File Simulation	Options Help TID M eters	LIN: MLIN_		Ph			.56985		mm	•					-	7		-	×	
File Simulation	Options Help ID M eters AULT		~	Ph W					mm N/A	•					- 7-2	7-		-	×	· · · · · · · · · · · · · · ·
File Simulation File Simulation Component Type MLIN Substrate Parame ID MSUB_DEF Er	Options Help ID M eters AULT 2.100	N/A	~	Ph W L	iysical		.97040	00	N/A	•	a	Iculate	d Rest	ults	-	7	7	-	×	in introduce on the second
File Simulation	Options Help	N/A N/A mil mil	× × ×	Ph W L	nysical	8	.97040		mm N/A N/A	•	K	Eff =	1.811		-	7		-	×	
File Simulation	Options Help	N/A N/A mil mil mil	× * *	Ph W L	iysical	8	.97040	00	N/A	•	K A	Eff = _DB =	1.811 0.012	2	- -	7		-	×	
File Simulation	Options Help ID M eters AULT 2.100 1.000 20.000 3.9e+34 1.400 5.96e7	N/A N/A mil mil N/A	× × • • •	Ph W L Syn	nysical	8	.97040	00	mm N/A N/A ze		K A	Eff =	1.811 0.012	2	-	7		-	×	
File Simulation	Options Help ID M eters AULT 2.100 1.000 20.000 3.9e+34 1.400 5.96e7 0.000 0.	N/A N/A mil mil mil	× * *	Ph W L Syn Eler Z0	nthesize	8	0.000	00 Analy	mm N/A N/A ze	1 * 1 * 1 *	K A	Eff = _DB =	1.811 0.012	2	-	7		_	×	
File Simulation	Options Help	N/A N/A mil mil N/A N/A		Ph W L Syn	nthesize	8	.97040	00 Analy	mm N/A N/A ze ▼ Ohn deg	n •	K A	Eff = _DB =	1.811 0.012	2	-	7		_	×	
File Simulation	Options Help ID M eters AULT 2.100 1.000 20.000 3.9e+34 1.400 5.96e7 0.000 0.	N/A N/A mil mil N/A N/A	> + + + > + + + +	Ph W L Syn Eler Z0	nthesize	8	0.000	00 Analy	mm N/A N/A Ze ▼ Ohn deg N/A	n •	K A	Eff = _DB =	1.811 0.012	2	5	7		-	×	
File Simulation	Options Help	N/A N/A mil mil N/A N/A		Ph W L Syn Eler Z0	nthesize	8	0.000	00 Analy	mm N/A N/A ze ▼ Ohn deg	n •	K A	Eff = _DB =	1.811 0.012	2	5	7		_	×	

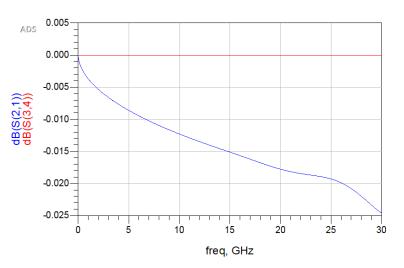

dbS21=-.025 dB 20logS21=-.025 S21=.997

As the frequency increase losses increase And S21 decreased

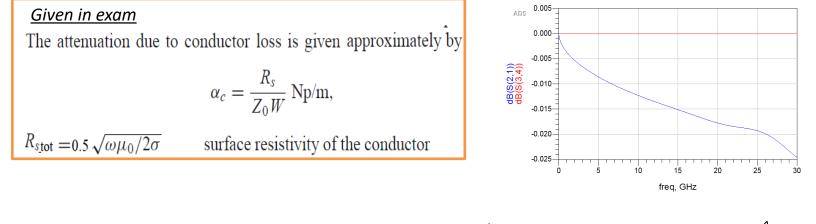 $v_{ph} = \omega/\beta$ for T.L. have $\varepsilon_{r_{eff}} - U_{ph} = \frac{3x_{10}^{\delta}}{\sqrt{1-8}} = 2.236 \times 10^{8}$ - ideal T.L. Uph = 3×10




|Sz1 = 20109e = - 0.015dB

Ideal transmission line component in ADS

Example

Figure shows an ideal transmission line in the ADS schematic window. The **E** in the figure represents the electrical length

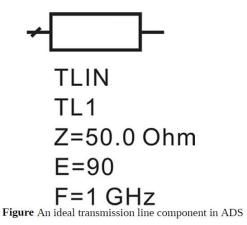

(1) If the wavelength at 1 GHz is denoted as λ_o , what is the length of the transmission line?

(2) What is the electrical length E at a frequency of 3 GHz?

Solutions

(1) Since

$$\theta = \beta l = \frac{2\pi l}{\lambda_o} = \frac{\pi}{2}$$

then the length is found to be $l = 0.25 \lambda_0$. physical length if fabricated=7.5 cm

(2) The electrical length is

$$\theta = \beta l = \frac{\omega l}{v_p} = \frac{2\pi l}{\lambda}$$

Now, keeping the phase velocity and length fixed, the electrical length is proportional to the frequency. Thus, at 3 GHz, $\mathbf{E} = 270^{\circ}$.