



**ECE 344**

# ***MICROWAVE FUNDAMENTALS***

## ***PART1-Lecture 4***

**Dr. Gehan Sami**

## Terminated TL


- Input impedance , two formula
- TL repeats mag. of Voltage, mag. of Current, Z every  $\lambda/2$
- EX1
  - Total voltage and current on terminated TL
  - $V_{max}$ ,  $I_{max}$ ,  $V_{min}$ ,  $I_{min}$
  - Reflection coefficient
- Ex2 terminated and sourced TL
- Equivalent input impedance for open circuit , short circuit and matched TL
- Equivalent TLs to lumped elements: inductors and capacitors.
- Input impedance for  $\lambda/2$  and  $\lambda/4$
- Quarter wavelength transformer
- Compute input impedance for TL with lumped elements or different connections.
- Voltage on TL
- SWR

# Terminated Transmission Line

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

Ampl. of voltage wave propagating in positive  $z$  direction at  $z = 0$ .

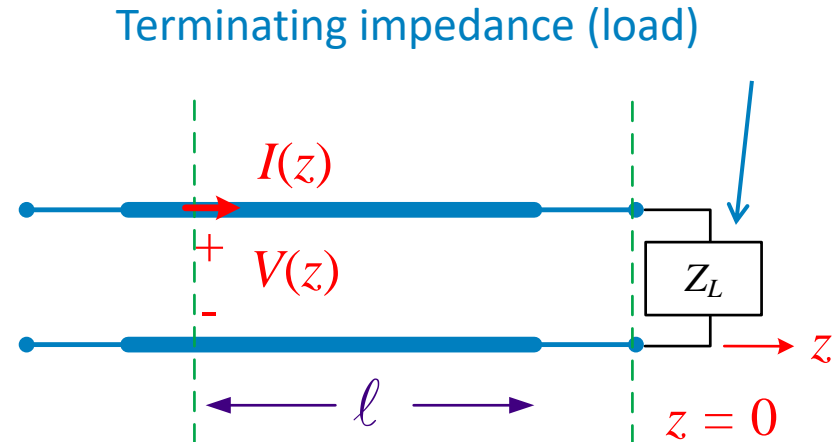Ampl. of voltage wave propagating in negative  $z$  direction at  $z = 0$ .



Where do we assign  $z = 0$ ?

The usual choice is at the load.

Note: The length  $l$  measures distance from the load:  $l = -z$

# Terminated Transmission Line (cont.)

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$


What is  $V(-\ell)$ ?

$$V(-\ell) = V_0^+ e^{\gamma \ell} + V_0^- e^{-\gamma \ell}$$

propagating forwards

propagating backwards

Terminating impedance (load)

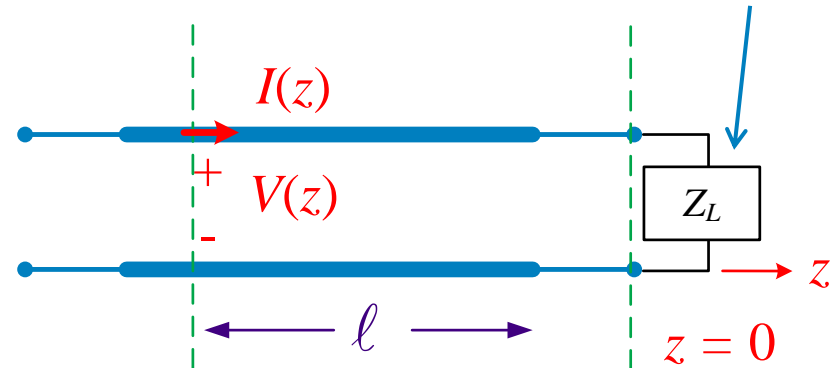


The current at  $z = -\ell$  is then

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma \ell} - \frac{V_0^-}{Z_0} e^{-\gamma \ell}$$

$\ell \equiv$  distance away from load

# Terminated Transmission Line (cont.)

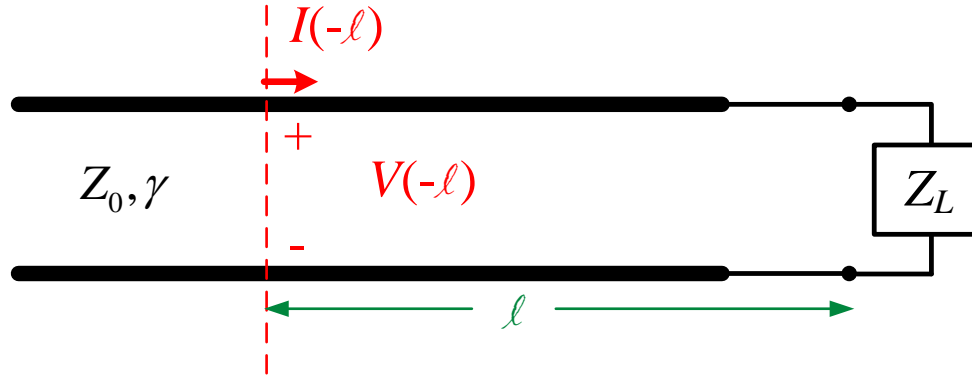

Total volt. at distance  $l$   
from the load

$$V(-l) = V_0^+ e^{\gamma l} + V_0^- e^{-\gamma l} = V_0^+ e^{\gamma l} \left( 1 + \frac{V_0^-}{V_0^+} e^{-2\gamma l} \right)$$

Ampl. of volt. wave prop.  
towards load, at the load  
position ( $z = 0$ ).

Ampl. of volt. wave prop.  
away from load, at the  
load position ( $z = 0$ ).

$\Gamma_L \equiv$  Load reflection coefficient


$\Gamma_l \equiv$  Reflection coefficient at  $z = -l$

$$= V_0^+ e^{\gamma l} (1 + \Gamma_L e^{-2\gamma l})$$

Similarly,

$$I(-l) = \frac{V_0^+}{Z_0} e^{\gamma l} (1 - \Gamma_L e^{-2\gamma l})$$


# Terminated Transmission Line (cont.)

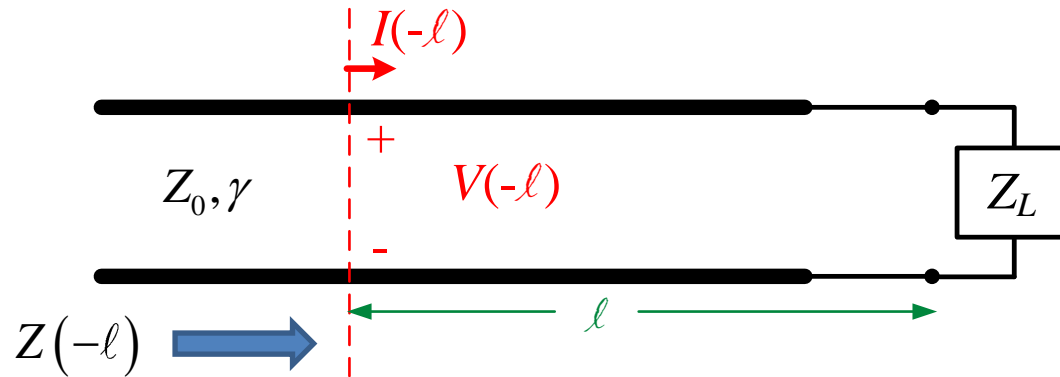

$$V(-l) = V_0^+ e^{\gamma l} (1 + \Gamma_L e^{-2\gamma l})$$

$$I(-l) = \frac{V_0^+}{Z_0} e^{\gamma l} (1 - \Gamma_L e^{-2\gamma l})$$
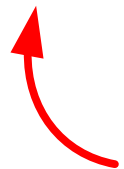
$$Z(-l) = \frac{V(-l)}{I(-l)} = Z_0 \left( \frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right)$$



Input impedance seen “looking” towards load at  $z = -l$ .

# Terminated Transmission Line (cont.)

At the load ( $\ell = 0$ ):

$$Z(0) = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \equiv Z_L \quad \Rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Recall  $Z(-\ell) = Z_0 \left( \frac{1 + \Gamma_L e^{-2\gamma\ell}}{1 - \Gamma_L e^{-2\gamma\ell}} \right)$

Thus,

$$Z(-\ell) = Z_0 \left( \frac{1 + \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}}{1 - \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}} \right)$$

# Terminated Lossless Transmission Line

$$\gamma = \cancel{\alpha} + j\beta = j\beta$$

$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$

$$Z(-\ell) = Z_0 \left( \frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right)$$

$$Z(-\ell) = Z_0 \left( \frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right)$$

Impedance is periodic  
with period  $\lambda_g/2$

tan repeats every  $\pi$

$$\beta\ell = \pi$$

$$\frac{2\pi}{\lambda_g} \ell = \pi$$


$$\Rightarrow \ell = \lambda_g / 2$$

$$\tan(\beta\ell) = \tan(\beta\ell + \pi)$$

$$\beta\ell_2 = \beta\ell_1 + \pi$$

$$\beta(\ell_2 - \ell_1) = \pi$$

$$\ell_2 - \ell_1 = \frac{\lambda}{2}$$

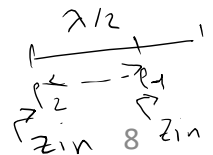






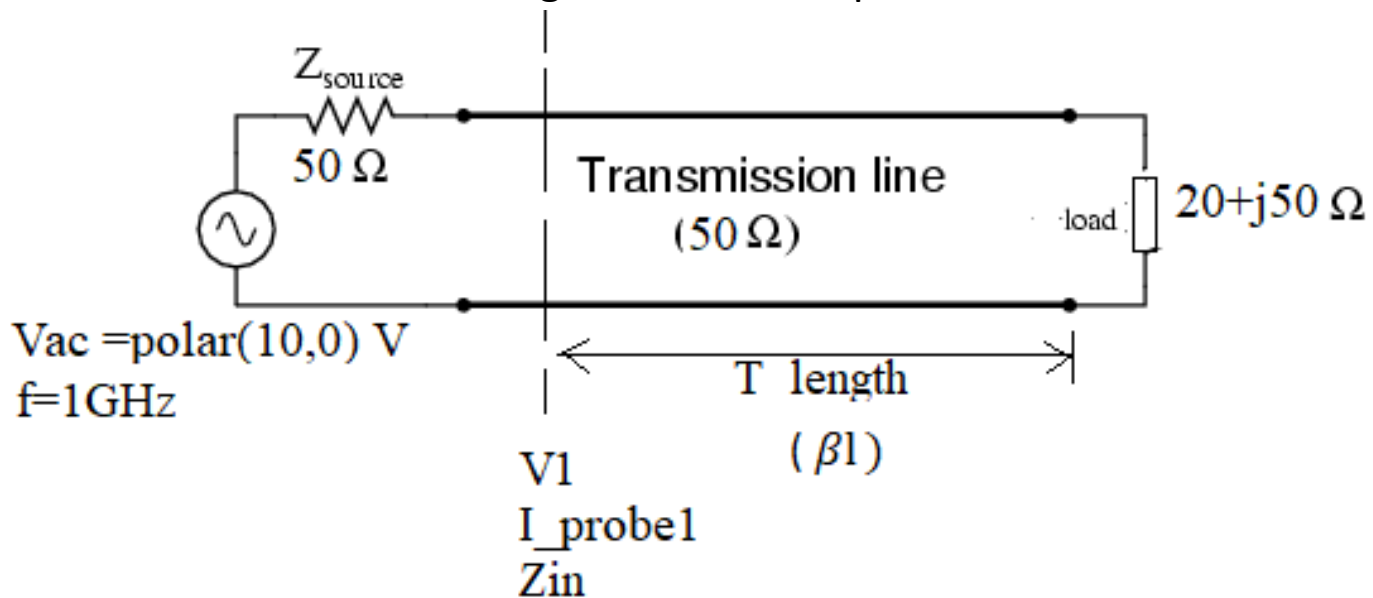
## Example 1

USE ADS to:


- draw magnitude voltage across the line  $\beta l = 2\pi$  or  $\ell = \lambda$
- draw magnitude current across the line
- draw impedance across the line
- observe  $\text{mag}(V), \text{mag}(I), Z$  every  $\ell = \lambda/2$**
- Compute magnitude of voltage, current at load.
- verify input impedance at load from voltage/current  
Equals load impedance.
- find max voltage value and its position
- find min voltage value and its position


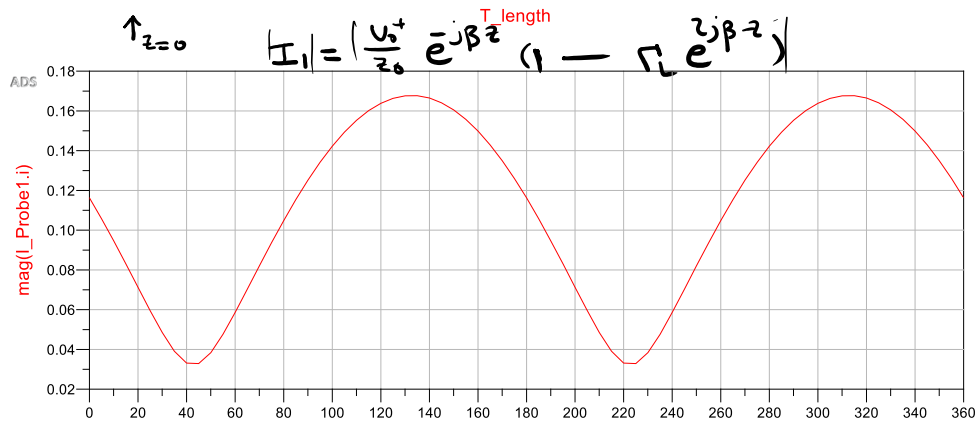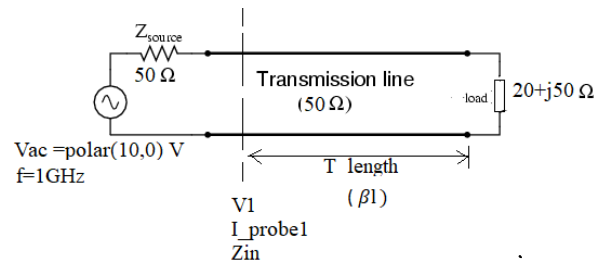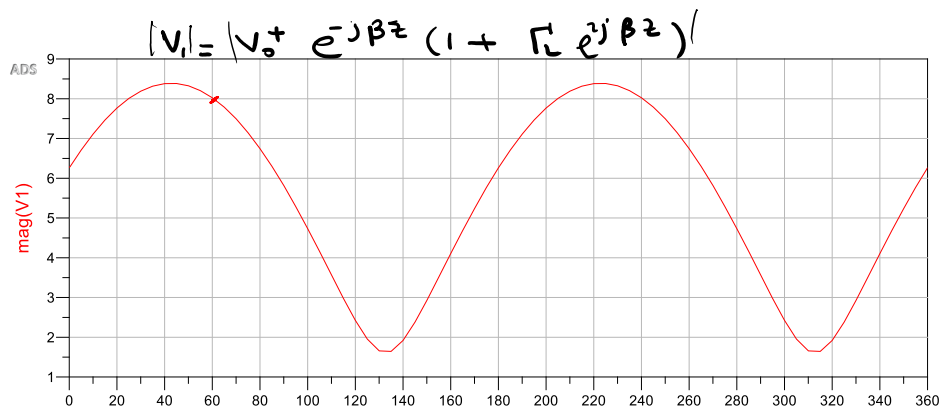
# Terminated transmission line repeats its voltage mag., current mag. and impedance each $\lambda/2$



$Z_1 = V_1 / I_1$

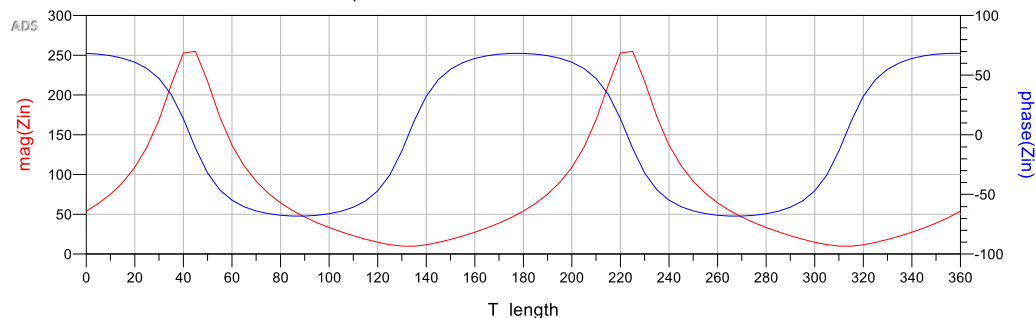

@  $z=0 \quad V_0^+ = 5 \text{ volt} \quad Z_0 = Z_0$

$V_1 = V_0^+ (1 + \Gamma), \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

$V_1 = 5 (1 + 0.678 \angle 85.43)$   
 $V_1 = 6.26 \angle 32.67$

$I_1 = \frac{V_0^+}{Z_0} (1 - \Gamma) = 0.116 \angle -35.53$

$Z_1 = V_1 / I_1 = 53.9 \angle 68.2$   
 $= Z_L$

$Z_L = 20 + j50 = 53.85 \angle 68.2$

$$\left. \begin{aligned} V(l + \lambda/2) &= -V(l) \\ I(l + \lambda/2) &= -I(l) \end{aligned} \right\} Z_{in}(l + \lambda/2) = Z_{in}(l)$$

$$V(l + \lambda) = V(l), \quad I(l + \lambda) = I(l)$$

for  $\beta l = 60^\circ$   $U_0^+ = 5$   $\Gamma_L = 0.678 \angle 85.43$

Find  $V(\beta l = 60)$ ,  $I(\beta l = 60)$ ,  $Z(\beta l = 60)$

Soln

$$V = U_0^+ e^{j\beta l} (1 + \Gamma_L e^{-2j\beta l})$$

$$= 5 \angle 60 (1 + 0.678 \angle 85.43 \angle -120)$$

$$= 5.56 + j5.79 = 8 \angle 46.13^\circ \text{ Volt}$$

$$I = \frac{U_0^+}{Z_0} e^{j\beta l} (1 - \Gamma_L e^{-2j\beta l})$$

$$= \frac{5}{50} \angle 60 (1 - 0.678 \angle 85.43 \angle -120)$$

$$= -0.011 + j0.057 = 0.0586 \angle 101$$

$$Z = \frac{V}{I} = \frac{8 \angle 46.13}{0.0586 \angle 101} = 78.48 - j111.7 = 136.6 \angle -54.9^\circ$$

$$V_o^+ = 5 \text{ Volt} \quad \Gamma_L = 0.678 \quad \underline{85.43}$$

$$|V| = |V_o^+| \left| 1 + |\Gamma_L| e^{j\phi} e^{-2j\beta l} \right|$$

$$|V_{\max}| = |V_o^+| (1 + |\Gamma_L|) = 5 \times 1.678 = 8.4 \text{ Volt}$$

$$|V_{\min}| = |V_o^+| (1 - |\Gamma_L|) = 5 \times 0.322 = 1.6 \text{ Volt}$$

$$\text{Max @ } \phi - 2\beta l = 0 \rightarrow \beta l = \frac{85.43}{2} = 42.7^\circ$$

$$\text{Min @ } \phi - 2\beta l = \pi \rightarrow \beta l = \frac{85.43 - 180}{2}$$

at  $l = \lambda/2 \quad \beta l = 180$

magnitude of voltage repeats every  $l = \frac{\lambda}{2}$

$$\Rightarrow |V(z + \lambda/2)| = |V(z)|$$


$$\text{or } \left| 1 + |\Gamma_L| e^{j\phi} e^{-2j\beta l} e^{-2j\beta \lambda/2} \right| = \left| 1 + |\Gamma_L| e^{j\phi} e^{-2j\beta l} \right|$$

$$= -47.28 + 180$$

$$= 132.7^\circ$$

ADS

$ts(V1)$

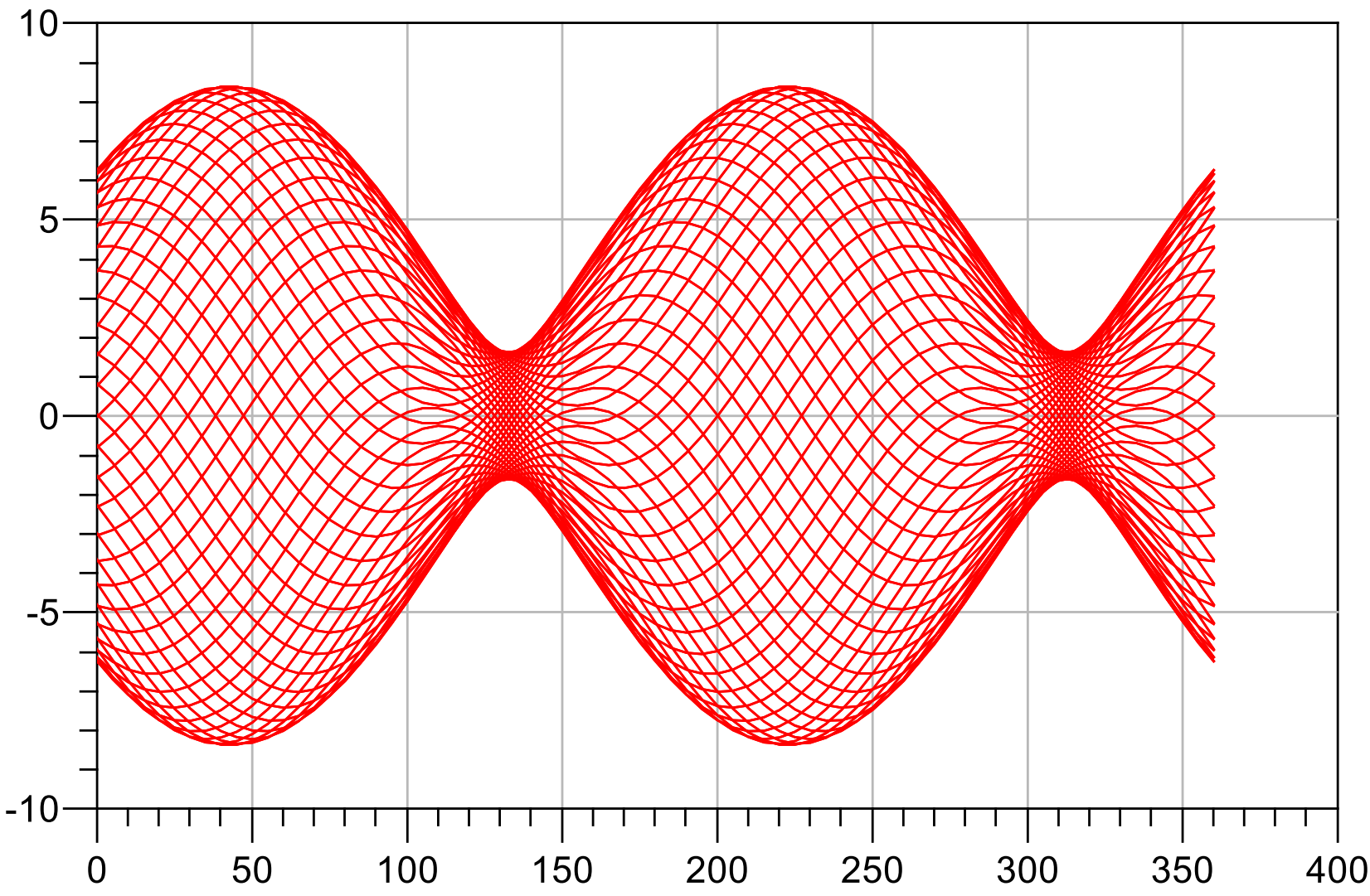

$T\_length$