



**ECE 344**

# ***MICROWAVE FUNDAMENTALS***

## ***PART1-Lecture 6***

**Dr. Gehan Sami**

## Examples on

- SWR for short circuit , open circuit Transmission line
- Slotted line and determination of unknown impedance
- Input impedance for Terminated TL with shunt element or equivalent stub.
- Coaxial, characteristic impedance and Attenuation.

### **Experiment 1**

- To determine the Standing Wave-Ratio and Reflection Coefficient

### **Experiment 2**

- To measure an unknown Impedance with Smith chart

### **Experiment 3**

- To determine the frequency & wavelength in a rectangular Waveguide working on TE<sub>10</sub> mode

## Previous lectures Equations

$$\gamma = [(R + j\omega L)(G + j\omega C)]^{1/2} = \alpha + j\beta$$

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\beta = \frac{2\pi}{\lambda_g}$$

$$v_p = \frac{\omega}{\beta}$$

$$\text{Attenuation in dB for matched TL} = 20 \log e^{-\alpha l}$$

$$Z_{in} = Z_o \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}} = Z_o \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}, \quad Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \quad \Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o}, \quad \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

short circuit load  $Z_{in} = jZ_o \tan \beta l$ , open circuit load  $Z_{in} = -jZ_o \cot \beta l$

$\lambda/4$  transformer  $Z_{in} = Z_{ch}^2 / Z_L$

$$V(z) = |V_o^+| e^{j\Phi^+} e^{-\alpha z} e^{-j\beta z} + |V_o^-| e^{j\Phi^-} e^{\alpha z} e^{j\beta z} \rightarrow \text{lossless} \quad V(z) = V_o^+ e^{-j\beta z} (1 + \Gamma_L e^{2j\beta z})$$

$$|V(z)| = |V_o^+| |(1 + |\Gamma_L| e^{j(\varphi - 2\beta l)})| \rightarrow |V_{\max}(z)| = |V_o^+| (1 + |\Gamma_L|), \quad |V_{\min}(z)| = |V_o^+| (1 - |\Gamma_L|)$$

$$\max \text{ at } \varphi - 2\beta l_{\max} = 0, \quad \min \text{ at } \varphi - 2\beta l_{\min} = \pi$$

# Standing Waves -Matched

Matched Line ( $Z_L = Z_o$ ), we had

$$Z_{in} = Z_o, \quad \Gamma_L = 0, \quad s = 1$$

■ So substituting in  $V(z)$


$$V(z) = V^+ [e^{j\beta l} + (0)e^{-j\beta l}]$$


$$V(z) = V^+ e^{j\beta l}$$

$$|V(z)| = |V^+| |e^{j\beta l}|$$

$$|V(z)| = |V^+|$$

$|V(z)|$  does not depend on  $z$

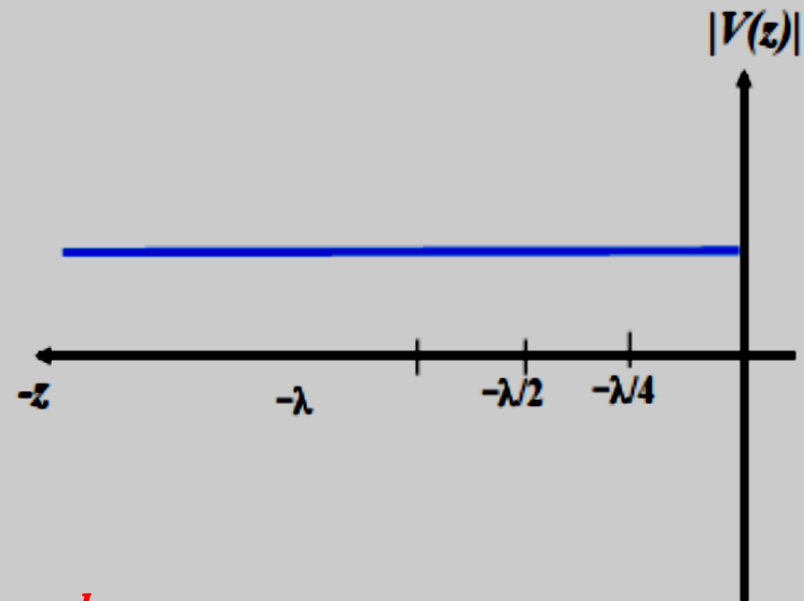

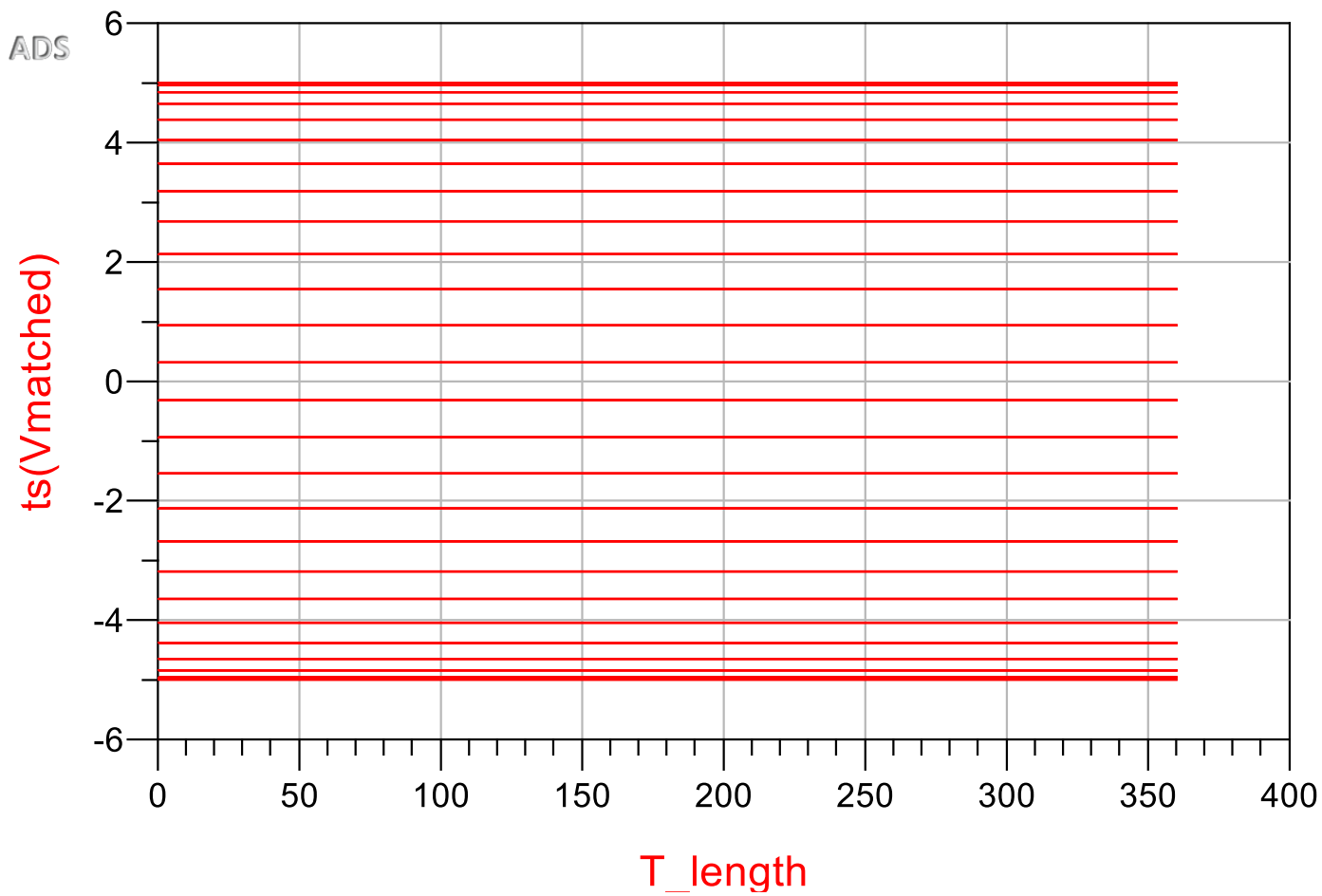

# Standing Waves -Short

Shorted Line ( $Z_L=0$ ), we had

$$Z_{in} = jZ_o \tan \beta l, \quad \Gamma_L = -1, \quad s = \infty$$


■ So substituting in  $V(z)$

$$V(z) = V^+ [e^{j\beta l} + (-1)e^{-j\beta l}]$$


$$V(z) = V^+ (2j \sin \beta l)$$

$$|V(z)| = |V^+| |2 \sin(\beta l)|$$

$$|V(z)| = |V^+| \left| 2 \sin \left( \frac{2\pi}{\lambda} l \right) \right|$$

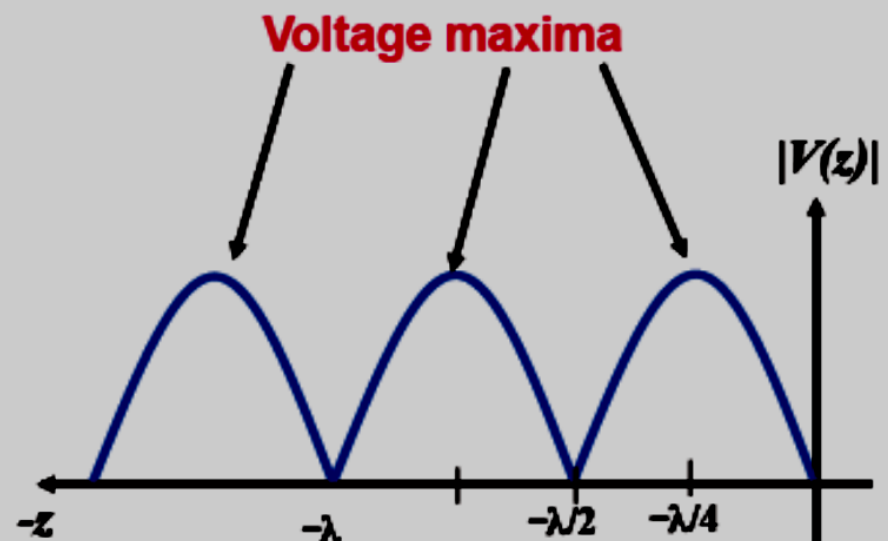

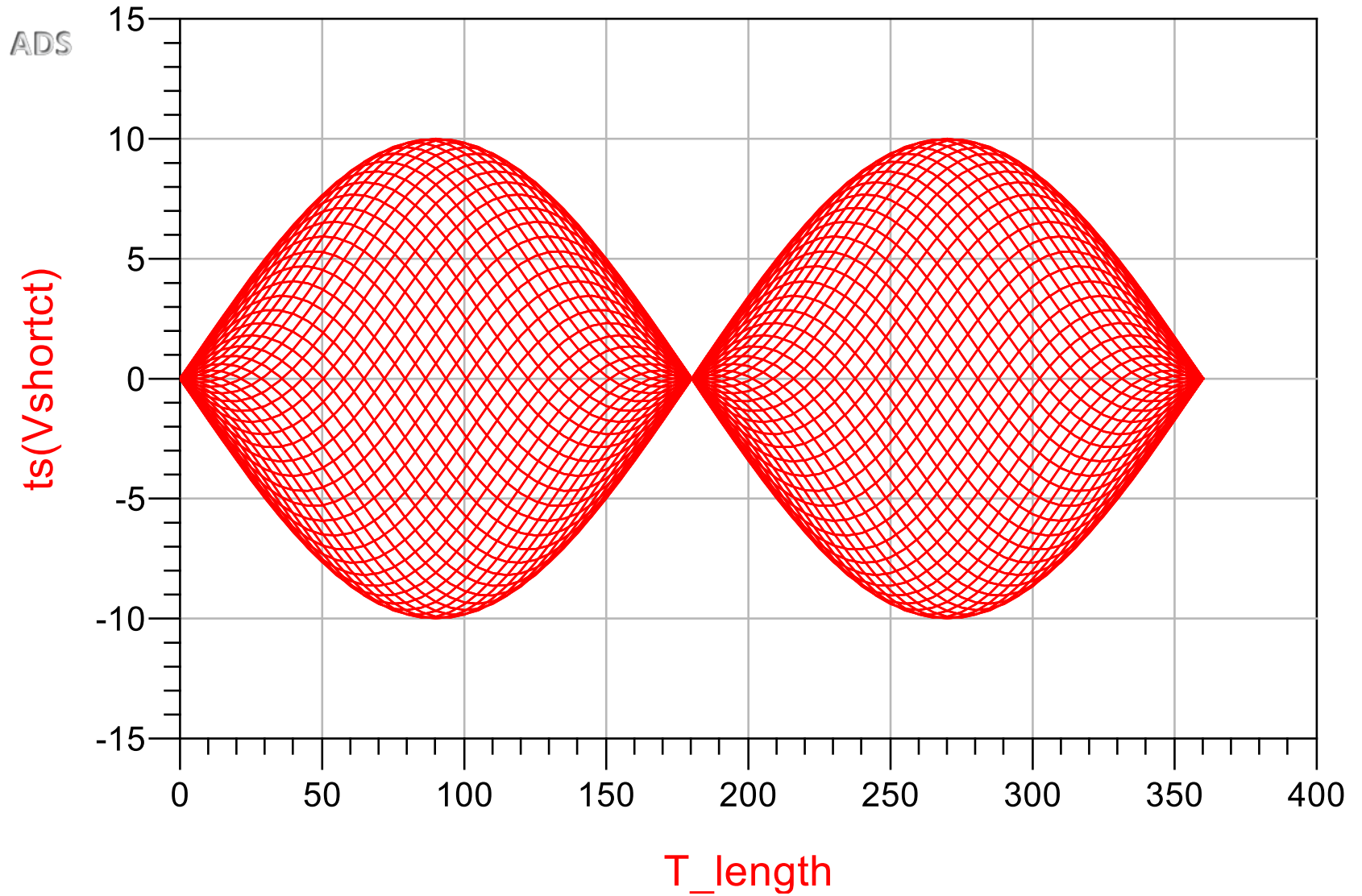\*Voltage **minima** occurs at same place that impedance has a **minimum** on the line



# Standing Waves - Open

Open Line ( $Z_L = \infty$ ), we had

$$Z_{in} = -jZ_o \cot \beta l, \quad \Gamma_L = +1, \quad s = \infty$$


■ So substituting in  $V(z)$

$$V(z) = V^+ [e^{j\beta l} + (+1)e^{-j\beta l}]$$


$$V(z) = V^+ (2 \cos \beta l)$$

$$|V(z)| = |V^+| |2 \cos(\beta l)|$$

$$|V(z)| = |V^+| \left| 2 \cos\left(\frac{2\pi}{\lambda} l\right) \right|$$

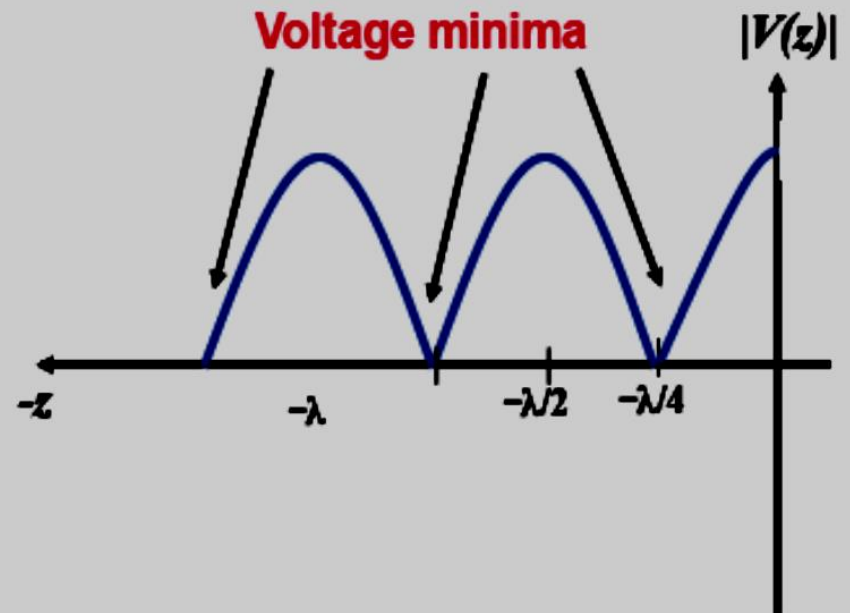



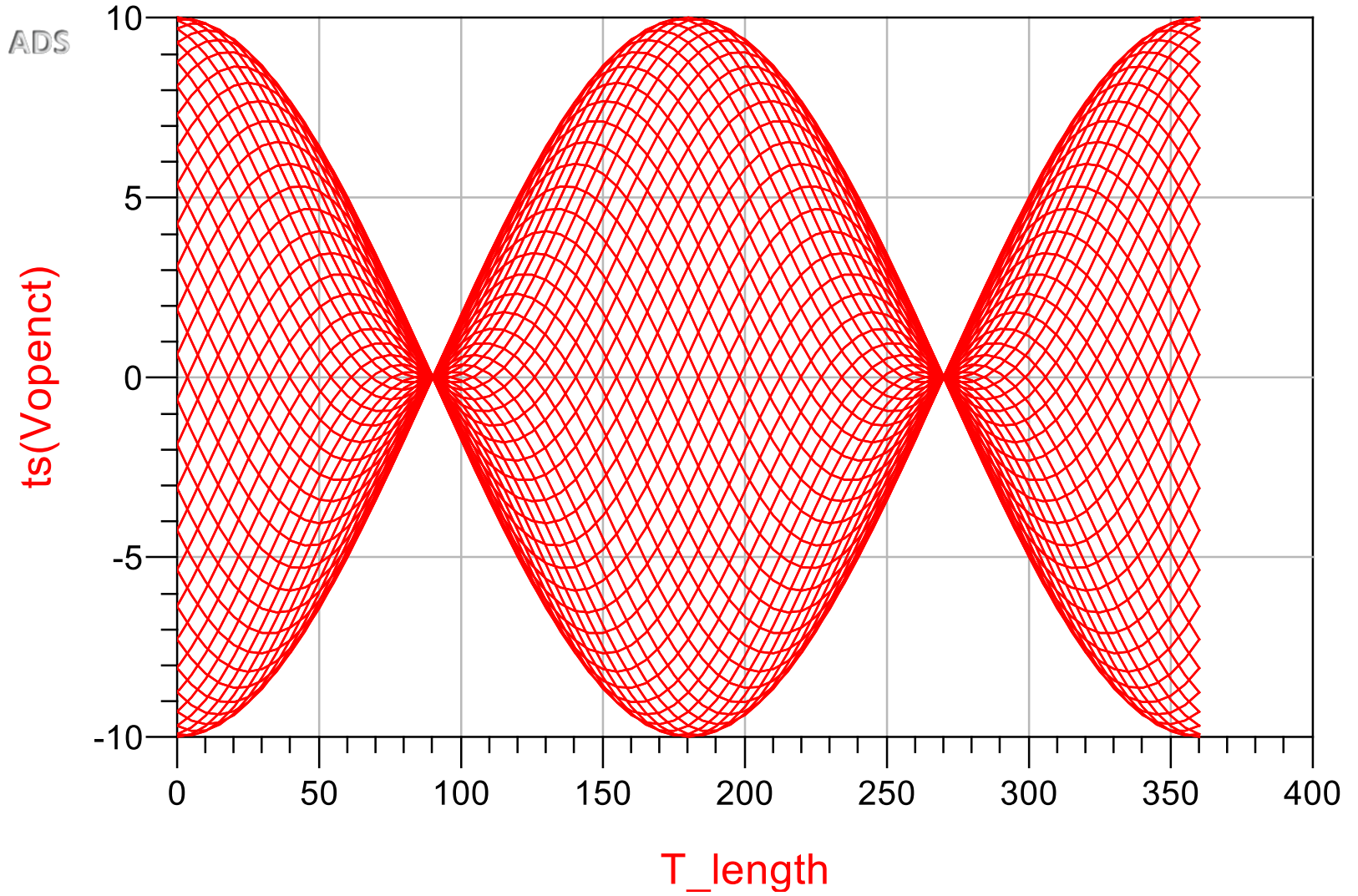

# VSWR

$$|V(z)| = |V_0^+| \left| (1 + |\Gamma_L| e^{j(2\beta z + \phi^- - \phi^+)}) \right|$$

$\theta = \phi^- - \phi^+$  is angle of reflection coeff. at load

max  $|V(z)|$  occurred at  $e^{j(2\beta z + \phi^- - \phi^+)} = 1$  (or  $2\beta z + \phi^- - \phi^+ = 2m\pi$  where  $m = 0, 1, 2$ )

$$|V(z)|_{\max} = |V_0^+| (1 + |\Gamma_L|)$$

min  $|V(z)|$  occurred at  $e^{j(2\beta z + \phi^- - \phi^+)} = -1$  (or  $2\beta z + \phi^- - \phi^+ = (2n + 1)\pi$  where  $n = 0, 1, 2$ )

$$|V(z)|_{\min} = |V_0^+| (1 - |\Gamma_L|)$$

$$\text{VSWR} = \frac{|V(z)|_{\max}}{|V(z)|_{\min}} = \frac{(1 + |\Gamma_L|)}{(1 - |\Gamma_L|)}$$

VSWR depend on mag of gamma only

**No reflection**  
( $Z_L = Z_0$ )


**Full reflection**  
( $Z_L = \text{open, short}$ )



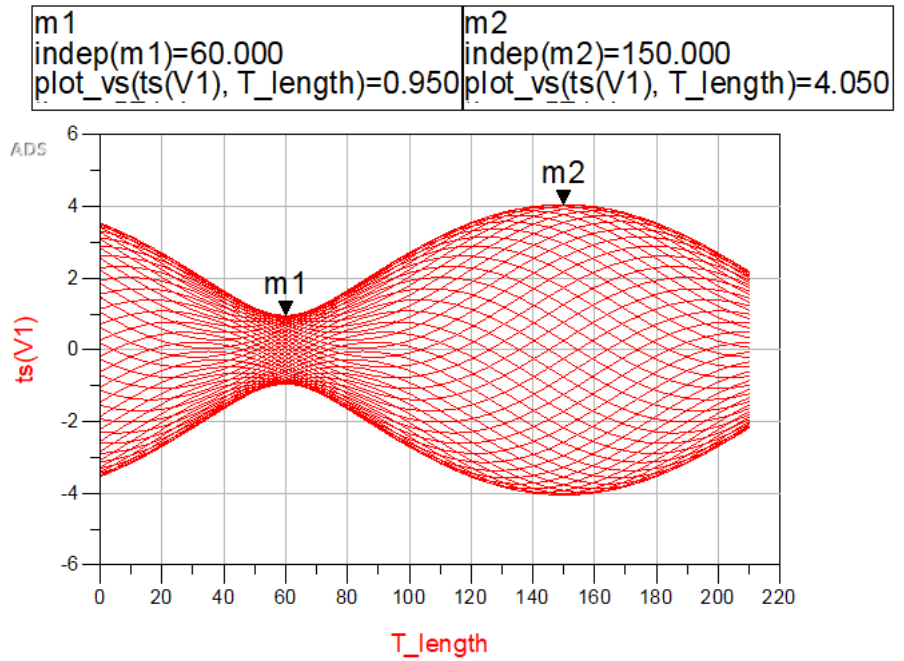
## Example:

The results of a slotted-line experiment are plotted in the following figure. The max at length of the line = 3.57 cm ;  
And the min at length 1.43cm.

- its characteristic impedance is  $50 \Omega$ . Find
- frequency of signal on the line
- the reflection coefficient at load
- the load impedance
- input impedance
- input reflection coefficient



solution

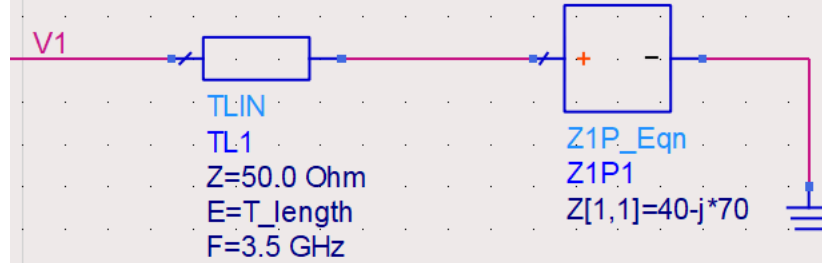

freq	$\Gamma_{load}$	$\Gamma_{in}$	Zin
3.500 GHz	0.620 / -60.255	0.620 / -120.255	30.742 / -60.128

Solution:  $P_{max} - P_{min} = \lambda/4 \rightarrow (3.57 - 1.43) \text{ cm} \times 4 = \lambda \rightarrow f = \frac{0.3 \text{ G}}{0.085 \text{ s}} = 3.5 \text{ GHz}$   
 $\lambda = 8.56 \text{ cm}$

- From Fig  $\frac{V_{max}}{V_{min}} = \frac{1+|\Gamma|}{1-|\Gamma|} \rightarrow \frac{4.05}{0.55} = \frac{1+|\Gamma|}{1-|\Gamma|} \rightarrow |\Gamma| = 0.62$

-  $\phi_L - 2\beta l_{min} = \pi \rightarrow \phi_L = \pi + 2 \times \frac{60}{180} \pi = \frac{5\pi}{3} = 300^\circ$

$\Gamma_L = 0.62 \angle 300 \rightarrow Z_L = 50 \times \frac{1 + 0.62 \angle 300}{1 - 0.62 \angle 300} = 40.3 - j70.2$

From Fig:

-  $\beta l = 210^\circ \therefore \Gamma_{in} = \Gamma_L e^{-2j\beta l} = 0.62 \angle 300 - 2 \times 210 = 0.62 \angle -120$


-  $Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{1 + 0.62 \angle -120}{1 - 0.62 \angle -120} = 15.4 - j26.79 = 30.87 \angle -60.17$

#
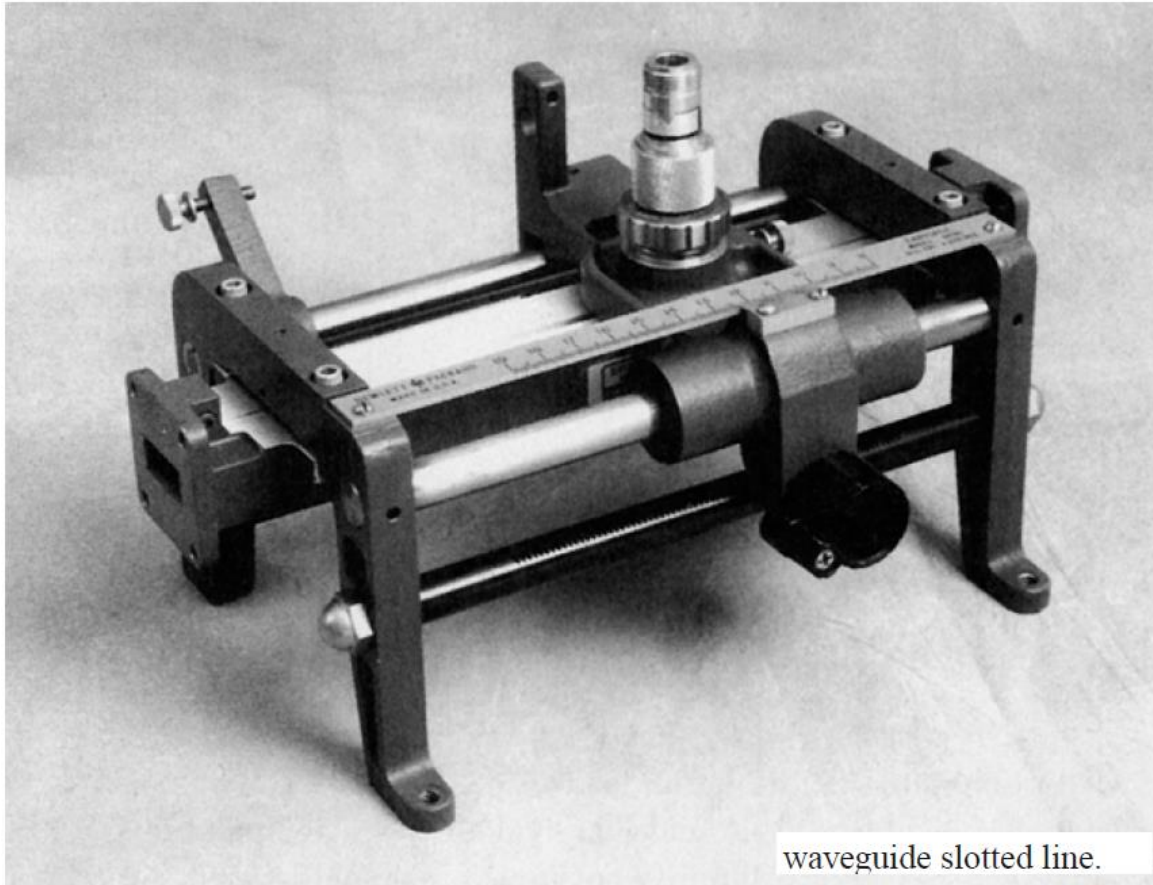
# The slotted line

slotted line is a transmission line configuration that allows sampling of the electric field amplitude of a standing wave on it when it is terminated by a load.

Measuring SWR and the distance of the first voltage minima from the load allows us to compute the unknown load.



waveguide slotted line.

## Using Slotted Line to Measure an Unknown Impedance:

1- From the SWR meter get :

$$|\Gamma_L| = \frac{SWR-1}{SWR+1}$$

2- Measure successive minima and maxima to get the frequency

$$l_1 - l_2 = \lambda/4 \rightarrow \beta = \frac{2\pi}{\lambda}$$

3- Use  $l_{\min}$  to get phase of reflection coefficient


$$\varphi - 2\beta l_{\min} = \pi \rightarrow \varphi$$

4- Compute  $Z_L$  or use smith chart to get  $Z_L$

$$\Gamma = |\Gamma|e^{j\varphi}$$

$$Z_L = Z_0 \frac{1+\Gamma}{1-\Gamma}$$

Ex.  $VSWR=1.5$ , find  $\Gamma_L$

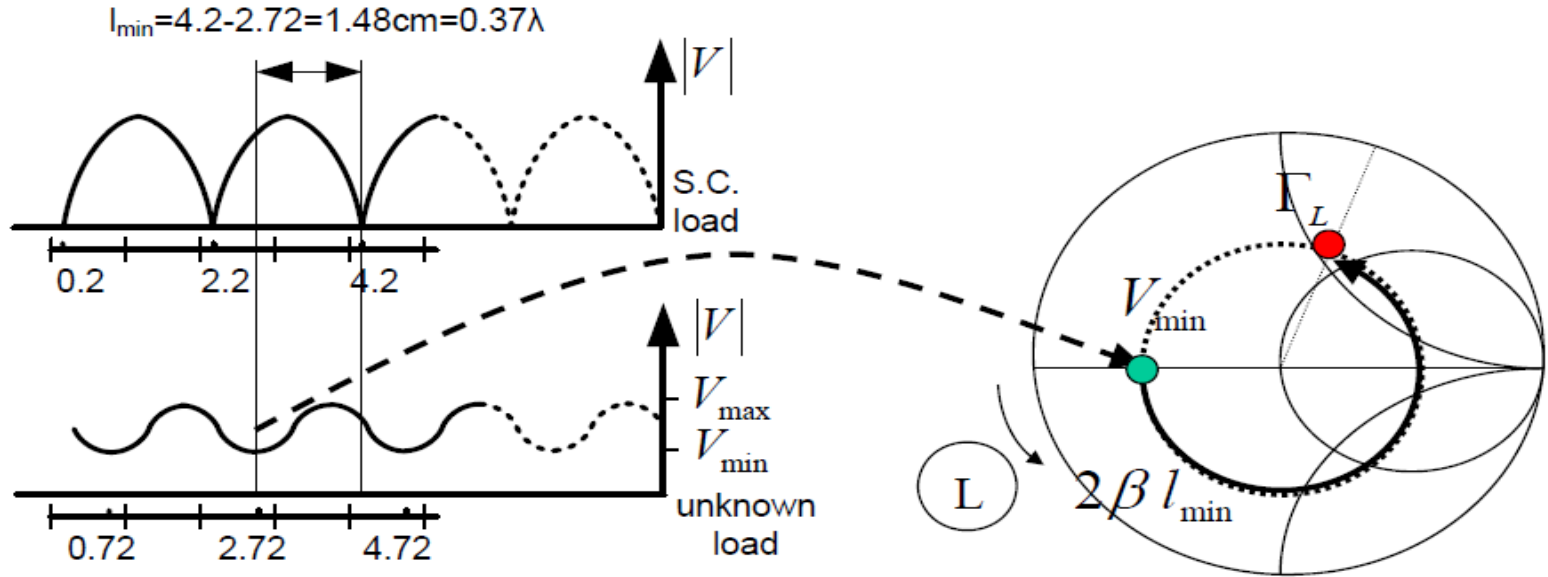

$$\frac{\lambda}{2} = 2\text{cm} \rightarrow \lambda = 4\text{cm}$$

$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \rightarrow |\Gamma_L| = \frac{VSWR - 1}{VSWR + 1} = \frac{1.5 - 1}{1.5 + 1} = 0.2$$

$$\angle \Gamma_L = 180^\circ + 2\beta l_{\min} = 180^\circ + 2 \frac{2 \times 180^\circ}{4} \times 1.48 - 360^\circ = 86.4^\circ$$

$$\Gamma = 0.2e^{j86.4^\circ} = 0.0126 + j0.1996.$$

The load impedance is then

$$Z_L = 50 \left( \frac{1 + \Gamma}{1 - \Gamma} \right) = 47.3 + j19.7\Omega.$$