




ECE 344

MICROWAVE FUNDAMENTALS



PART1-Lecture 8

Dr. Gehan Sami

Try to solve:

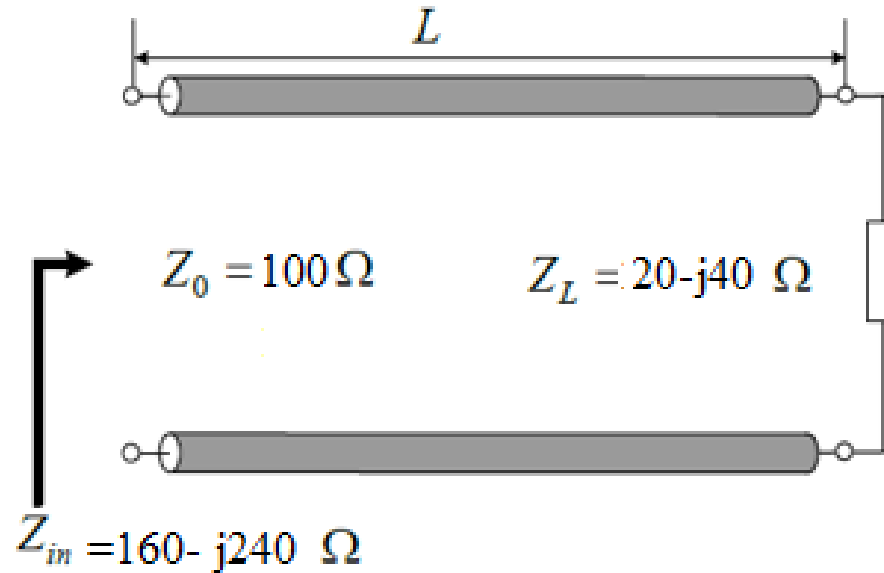

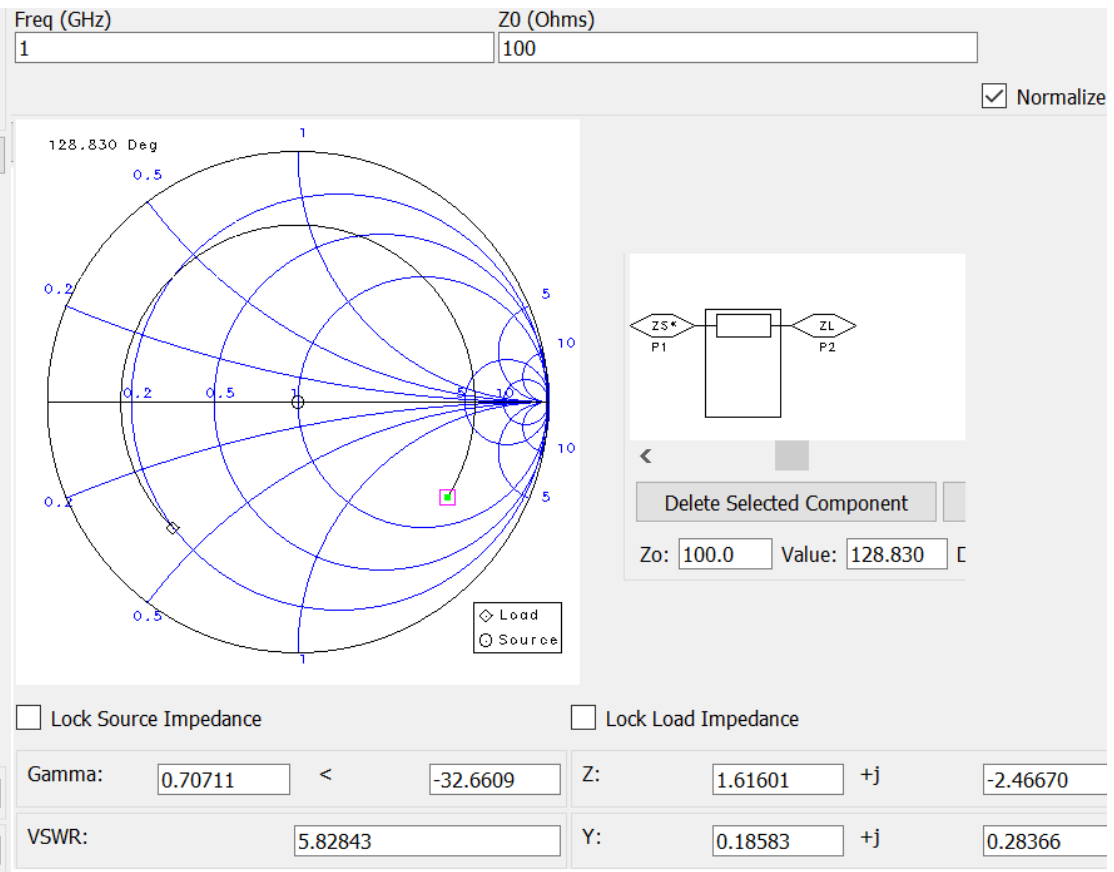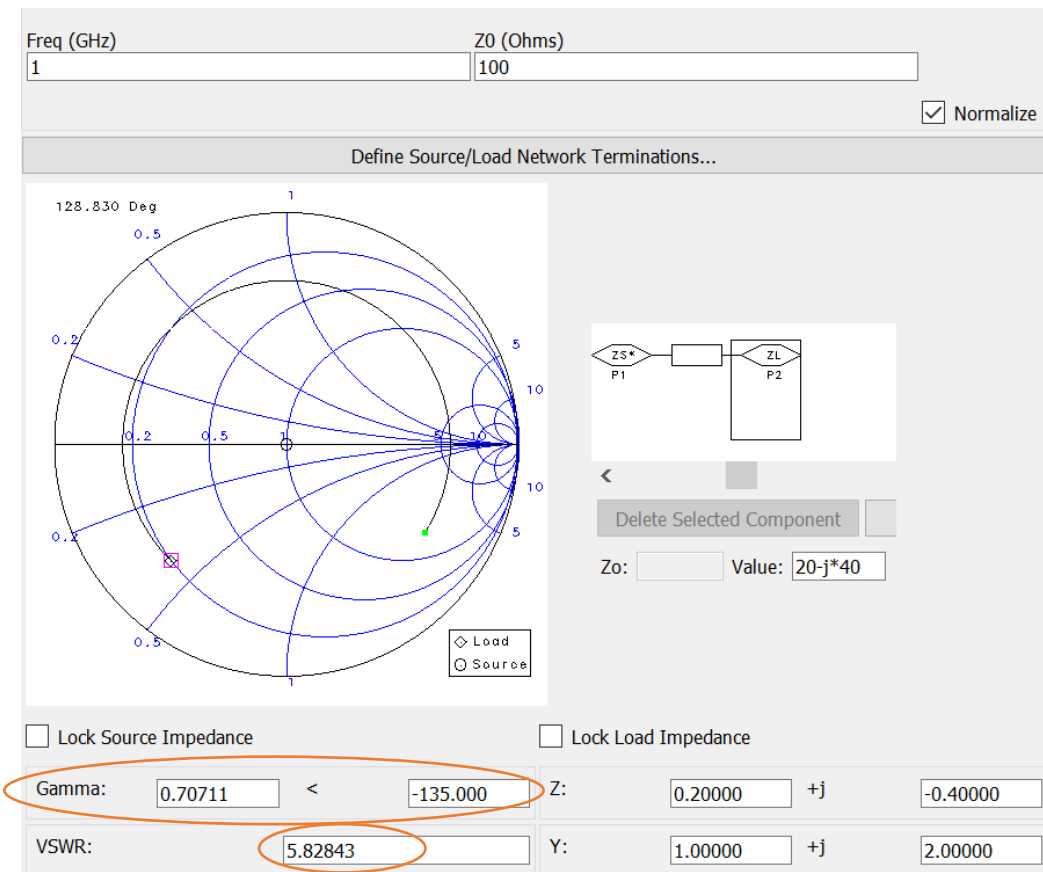- i. The SWR on the line.
- ii. The reflection coefficient at the load, and at the input of the line
- iii. The distance from load to the input impedance of the line.
- iv. The distance from the load to the first voltage minimum.
- v. The distance from the load to the first voltage maximum



At the load:

Swr=5.8

$\Gamma_{load}=0.7\angle-135^\circ$

At the input impedance:


$\Gamma_{input}=0.7\angle-32^\circ$

$\beta l=129^\circ$

$L = \lambda * 129/360 = 0.36\lambda$ on smith $\rightarrow (.5 - .438 + 0.296 = .36\lambda)$

$L_{min} = (0.5 - .438)\lambda = 0.062\lambda$ $\rightarrow \beta l = 22^\circ$

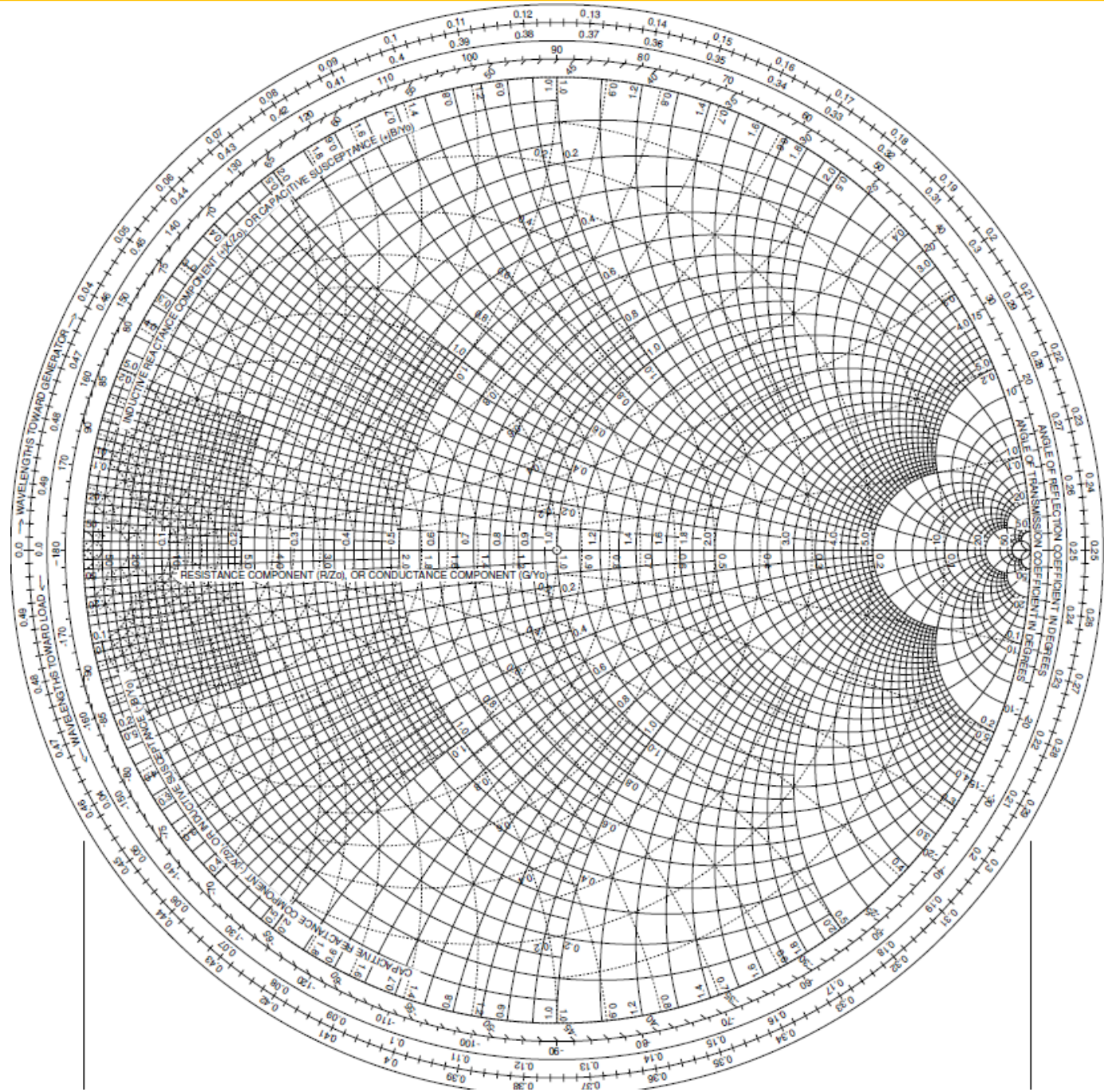$L_{max} = 0.312\lambda$ $\rightarrow \beta l = 112^\circ$



$$P = (0.5 - 0.438)\lambda + 0.296\lambda$$

$$= 0.358\lambda$$

$$P_{\min} = (0.5 - 0.438)\lambda$$

$$= 0.062\lambda$$


$$l_{\max} = P_{\min} + \lambda/4$$

$$= 0.312\lambda$$

$$\Gamma = 0.7 \angle -135^\circ$$

$$\Gamma_{in} = 0.7 \angle -33^\circ$$

$\Gamma \rightarrow$ Get $|\Gamma| = 0.7$
 $SWR = 5.8$

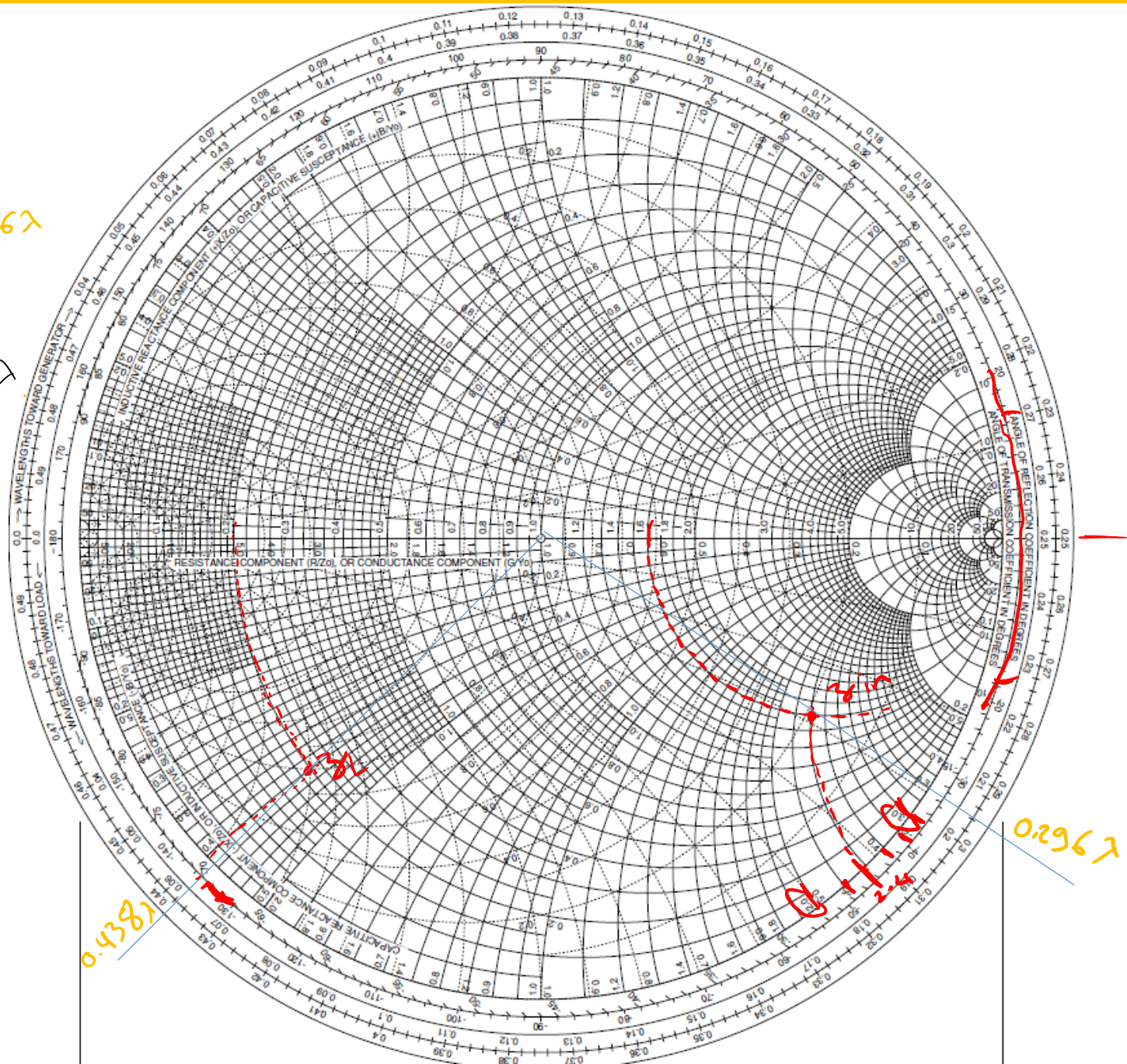

0.438λ

0.296λ

Admittance (Y) Calculations

Note:

$$Y(-\ell) = \frac{1}{Z(-\ell)} = \frac{1}{Z_0} \left(\frac{1 - \Gamma(-\ell)}{1 + \Gamma(-\ell)} \right)$$

$$= Y_0 \left(\frac{1 + (-\Gamma(-\ell))}{1 - (-\Gamma(-\ell))} \right) \quad Y_0 = \frac{1}{Z_0}$$

$$\Rightarrow Y_n(-\ell) = \frac{Y(-\ell)}{Y_0} = \left(\frac{1 + (-\Gamma(-\ell))}{1 - (-\Gamma(-\ell))} \right) = G_n(-\ell) + jB_n(-\ell)$$

Define: $\Gamma' = -\Gamma$

$$Y_n(-\ell) = \left(\frac{1 + \Gamma'}{1 - \Gamma'} \right)$$

Conclusion: The same Smith chart can be used as an admittance calculator.

Same mathematical form as for Z_n :

$$Z_n(-\ell) = \left(\frac{1 + \Gamma}{1 - \Gamma} \right)$$

Admittance (Y) Chart

As an **alternative**, we can continue to use the **original Γ plane**, and add admittance curves to the chart.

$$Y_n(-\ell) = \left(\frac{1 + (-\Gamma(-\ell))}{1 - (-\Gamma(-\ell))} \right) = G_n(-\ell) + jB_n(-\ell)$$

Compare with previous Smith chart derivation, which started with this equation:

$$Z_n(-\ell) = \left(\frac{1 + (\Gamma(-\ell))}{1 - (\Gamma(-\ell))} \right) = R_n(-\ell) + jX_n(-\ell)$$


If $(R_n X_n) = (a, b)$ is some point on the Smith chart corresponding to $\Gamma = \Gamma_0$,
Then $(G_n B_n) = (a, b)$ corresponds to a point located at $\Gamma = -\Gamma_0$ (**180° rotation**).

$\Rightarrow R_n = a$ circle, rotated 180°, becomes $G_n = a$ circle.
and $X_n = b$ circle, rotated 180°, becomes $B_n = b$ circle.


Side note: A 180° rotation on a Smith chart makes a normalized impedance become its reciprocal.

Admittance Smith Chart


Conductance Circles

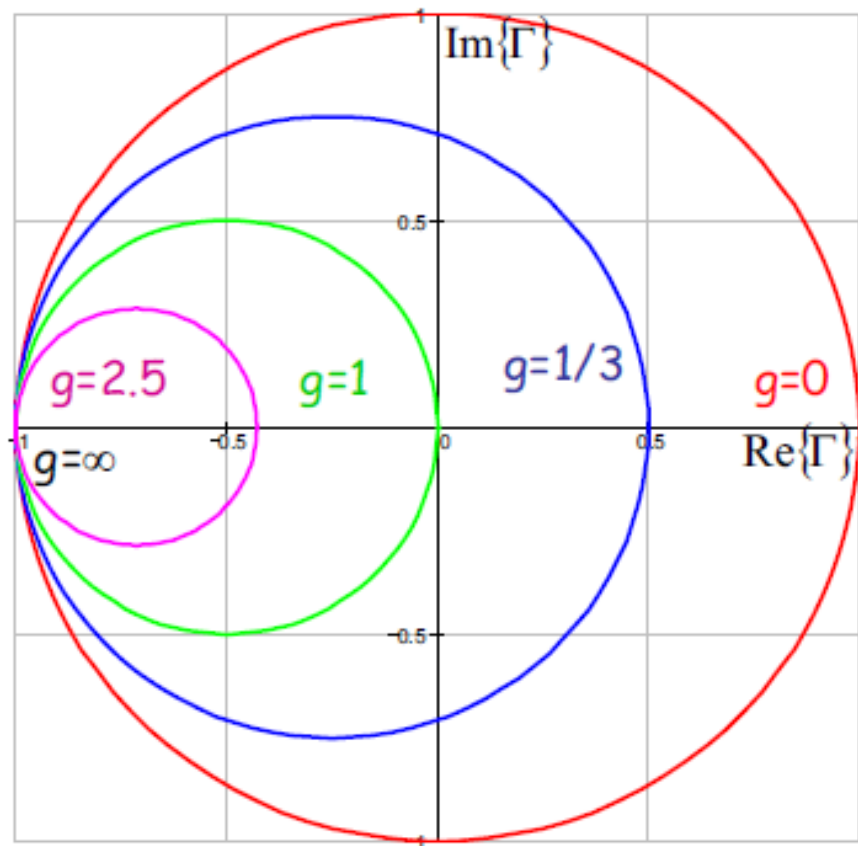

Susceptance Circles

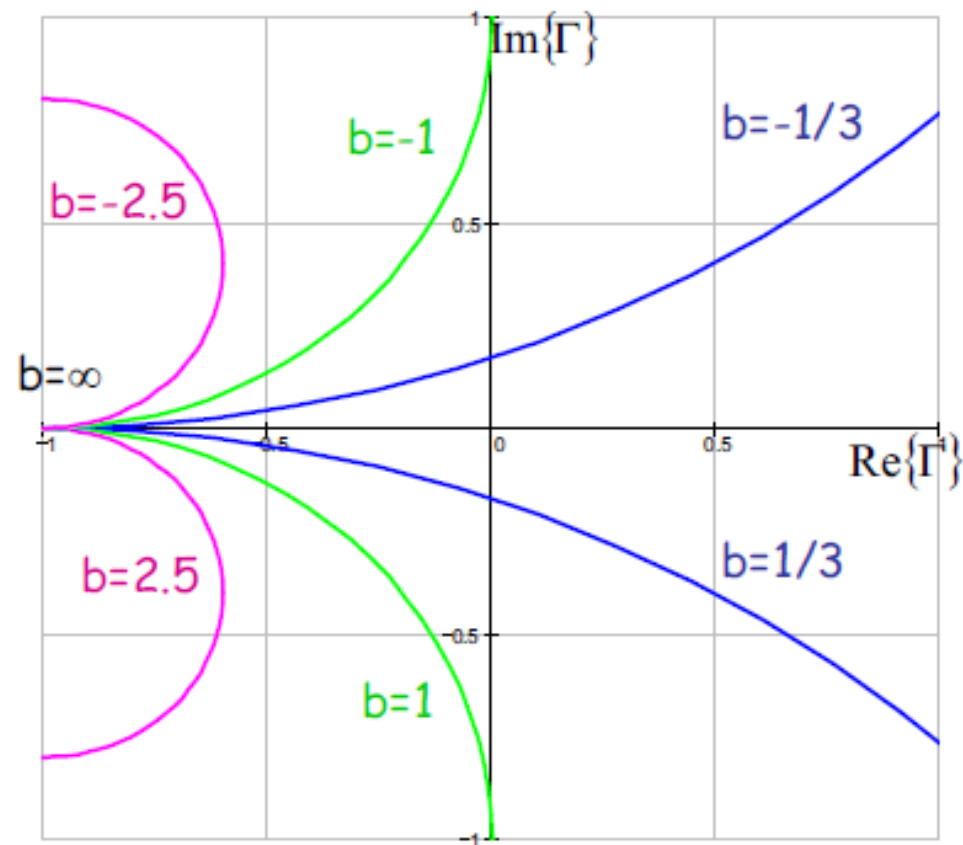


Admittance (Y) Chart (cont.)

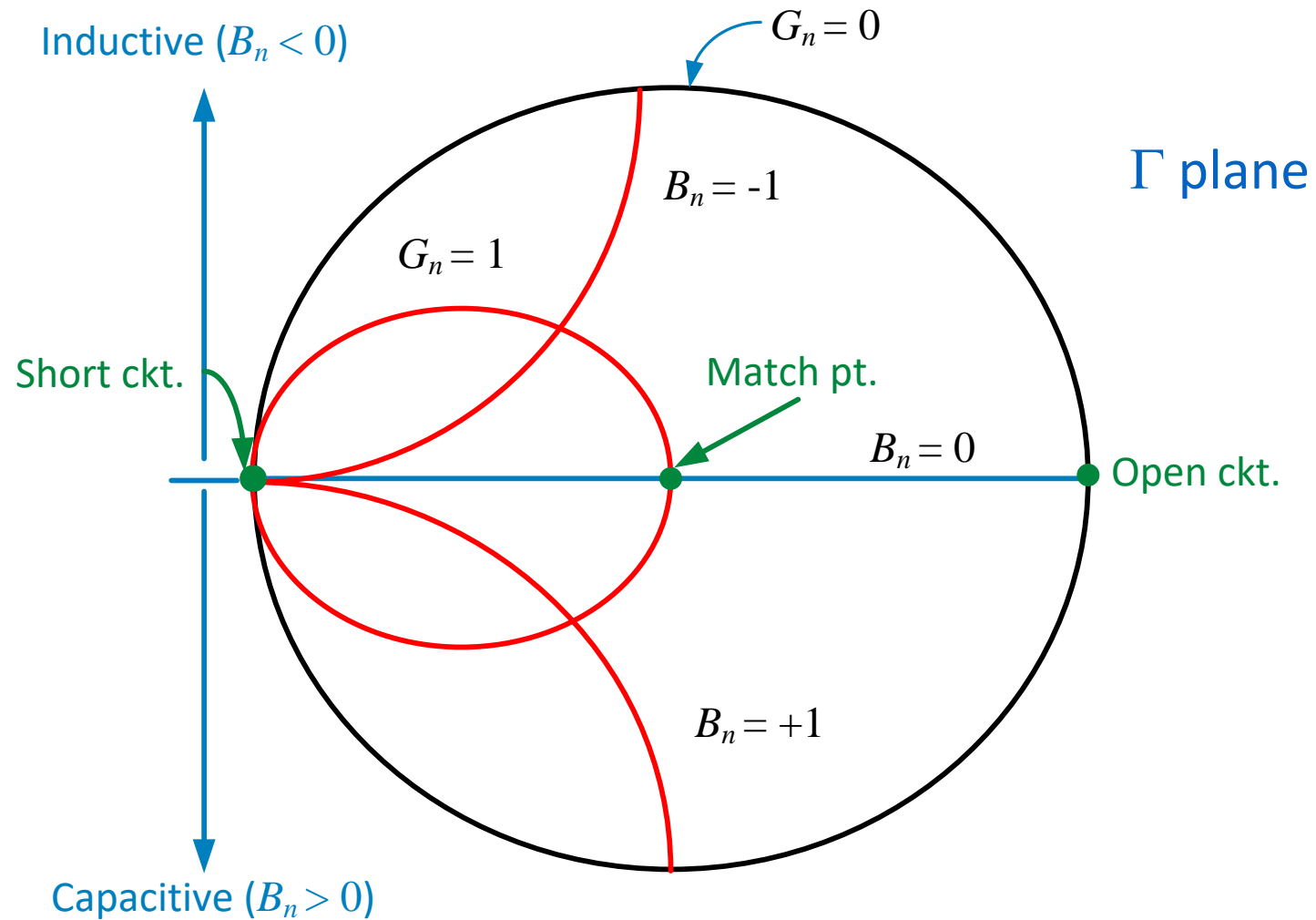


Impedance and Admittance (ZY) Chart

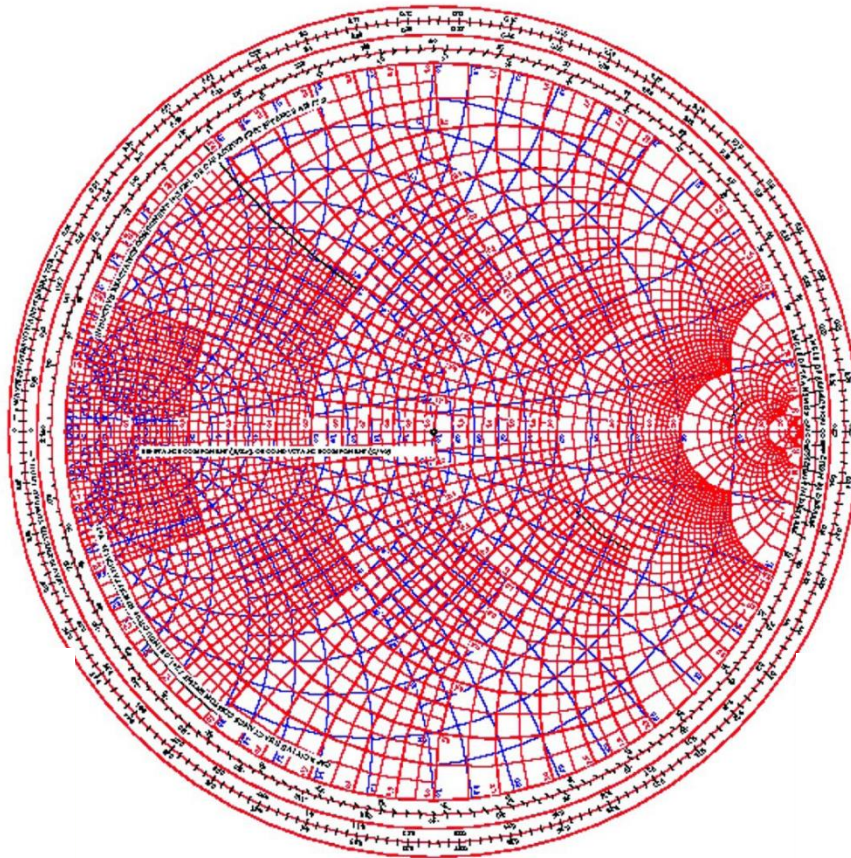NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Short-hand version

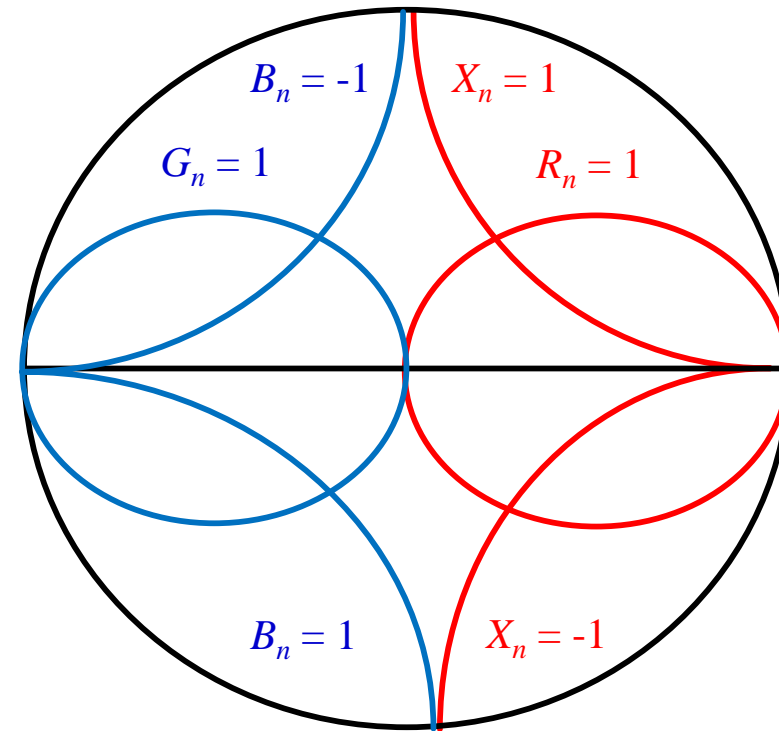

Γ plane


Example 6

$Y=1+j$
Find Z, Γ

1. Find y on Admittance chart
2. Read same point From corresponding Circles on impedance chart
3. Find Γ from ref coef degrees And REF coeff ruler

$\Gamma = 0.445 \angle -116^\circ$

$\angle -116^\circ$

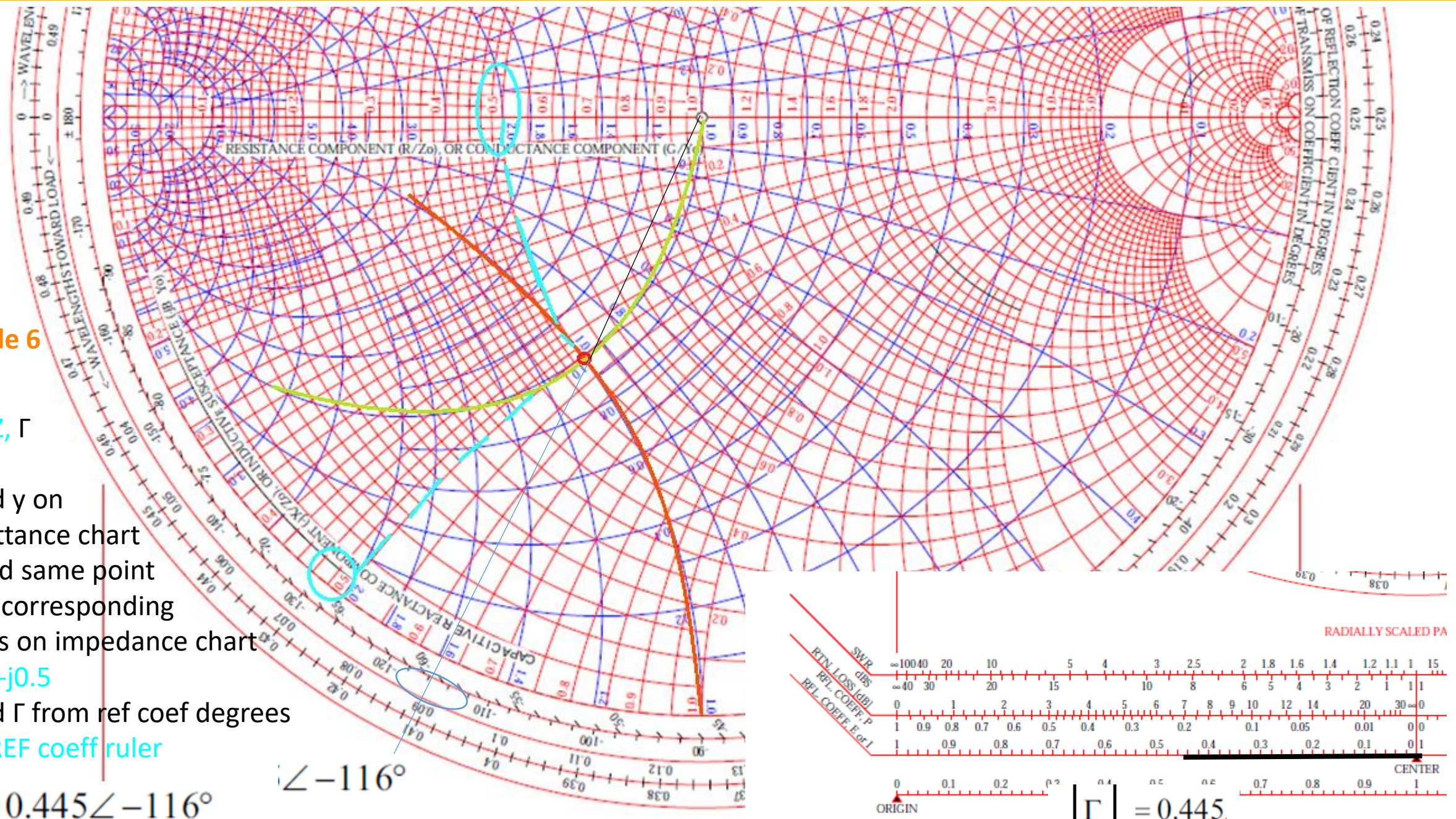

Using Impedance-Admittance Smith Chart

Example 7

Given:


$$\Gamma = 0.5 \angle +45^\circ \quad Z_0 = 50\Omega$$

Find Y

- Plot Γ
- Read coordinates on admittance chart

$$Y = \frac{1}{50\Omega} (0.38 - j0.36)$$
$$= (7.6 - j7.2) \cdot 10^{-3} \text{ S}$$

$$Z = 50 * (1.38 + 1.3j)$$

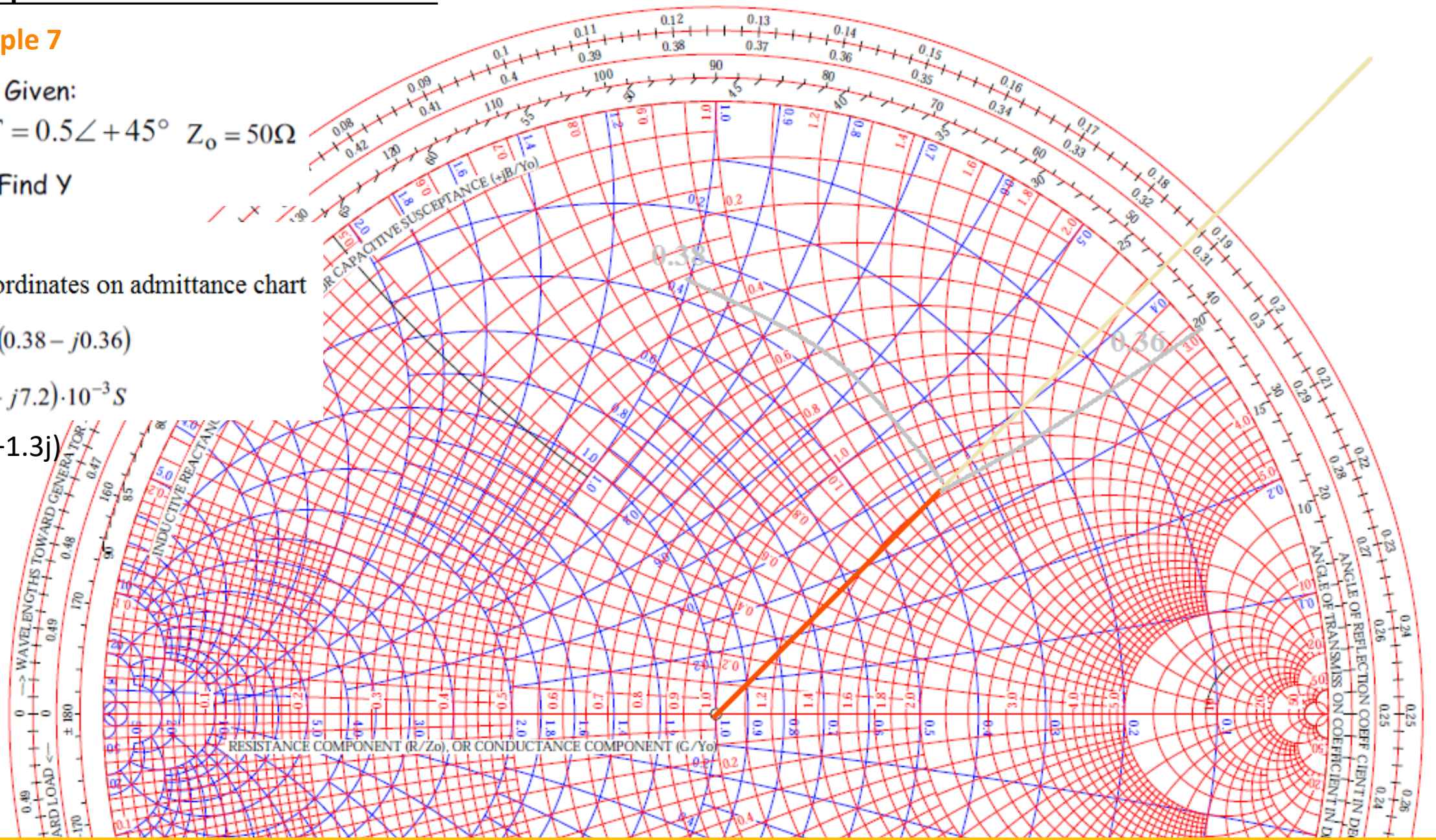

Adding Elements


Admittance

A matching network is going to be a combination of elements connected in series AND parallel.

Impedance is well suited when working with series configurations. For example:


$$V = ZI$$

$$Z_L = Z_1 + Z_2$$

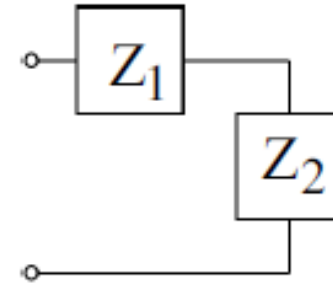

Impedance is NOT well suited when working with parallel configurations.

$$Z_L = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

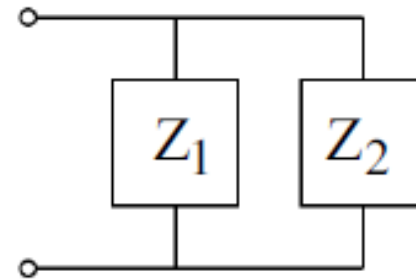


For parallel loads it is better to work with admittance.

$$I = YV$$

$$Y_1 = \frac{1}{Z_1}$$

$$Y_L = Y_1 + Y_2$$

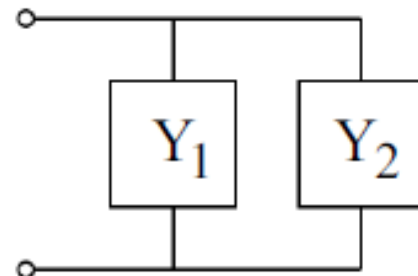

General Rules


Adding Series Components

→ Impedance Smith Chart





Adding Parallel (Shunt) Components



→ Admittance Smith Chart

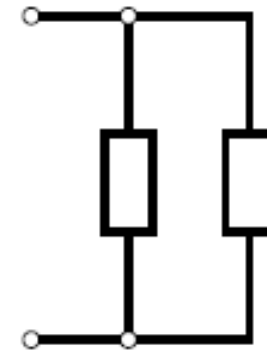



Navigation in the Smith Chart

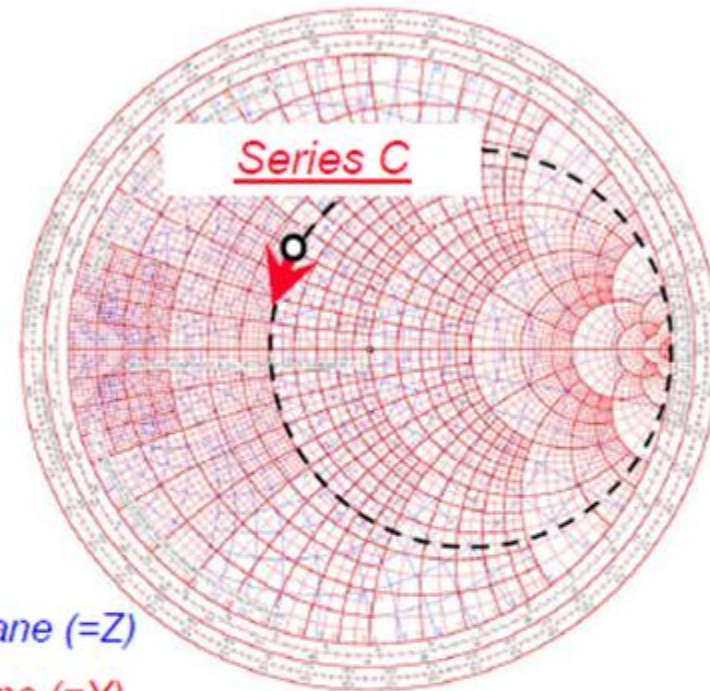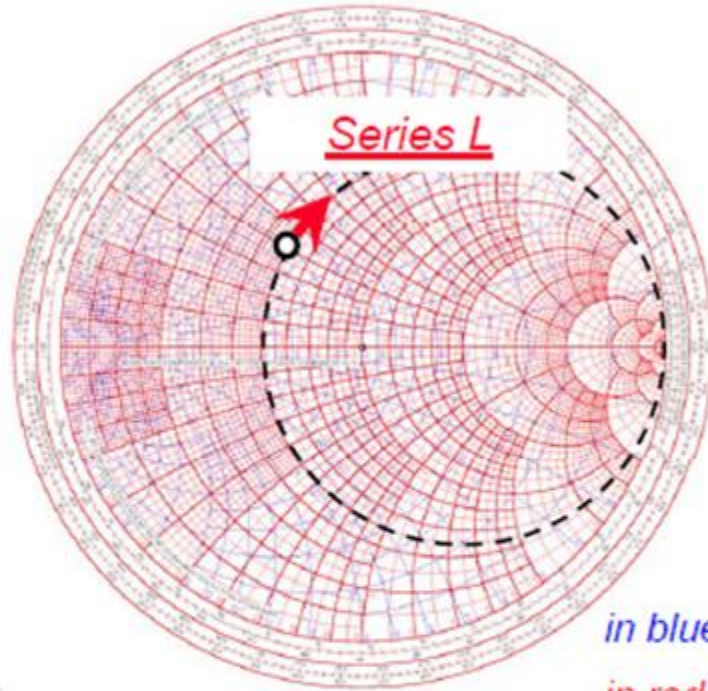

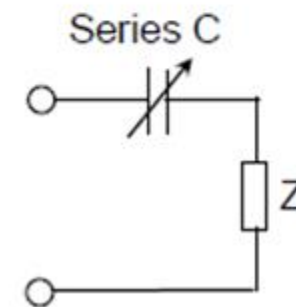
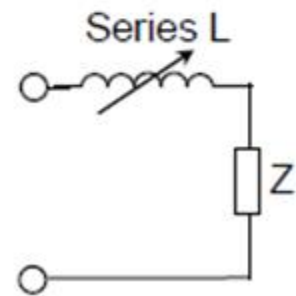
in blue: Impedance plane ($=Z$)
in red: Admittance plane ($=Y$)



Navigation in the Smith Chart (2)

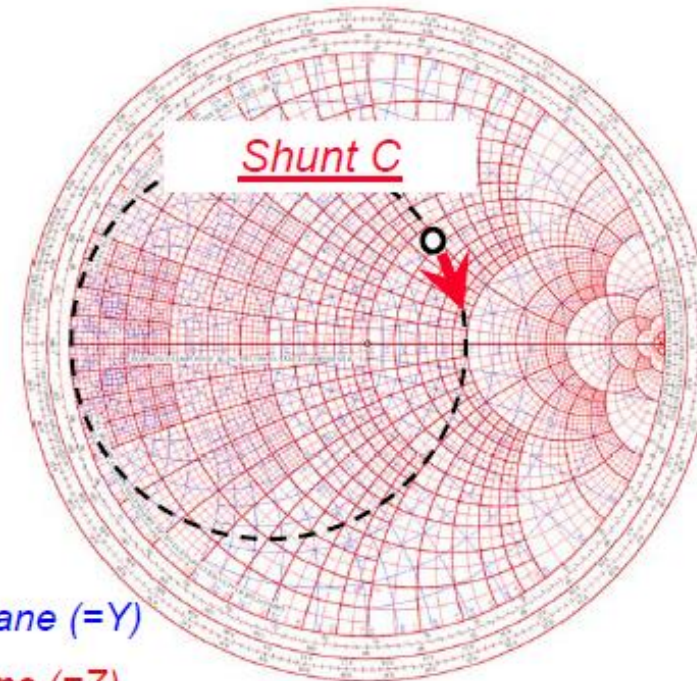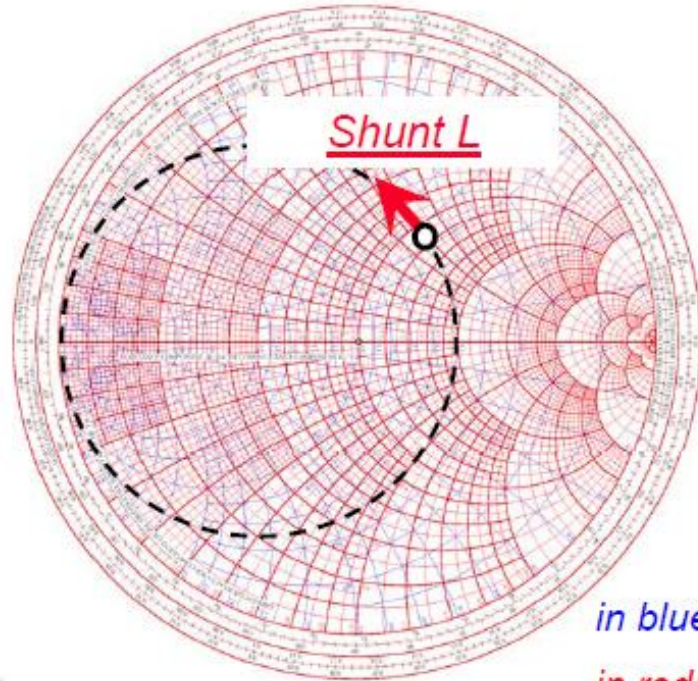


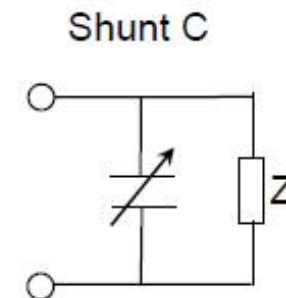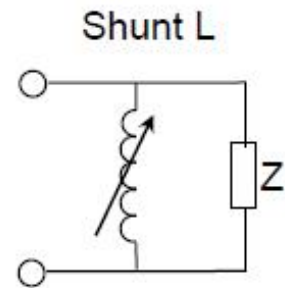in blue: Admittance plane (=Y)
in red: Impedance plane (=Z)




Series and Shunt Elements

Γ plane

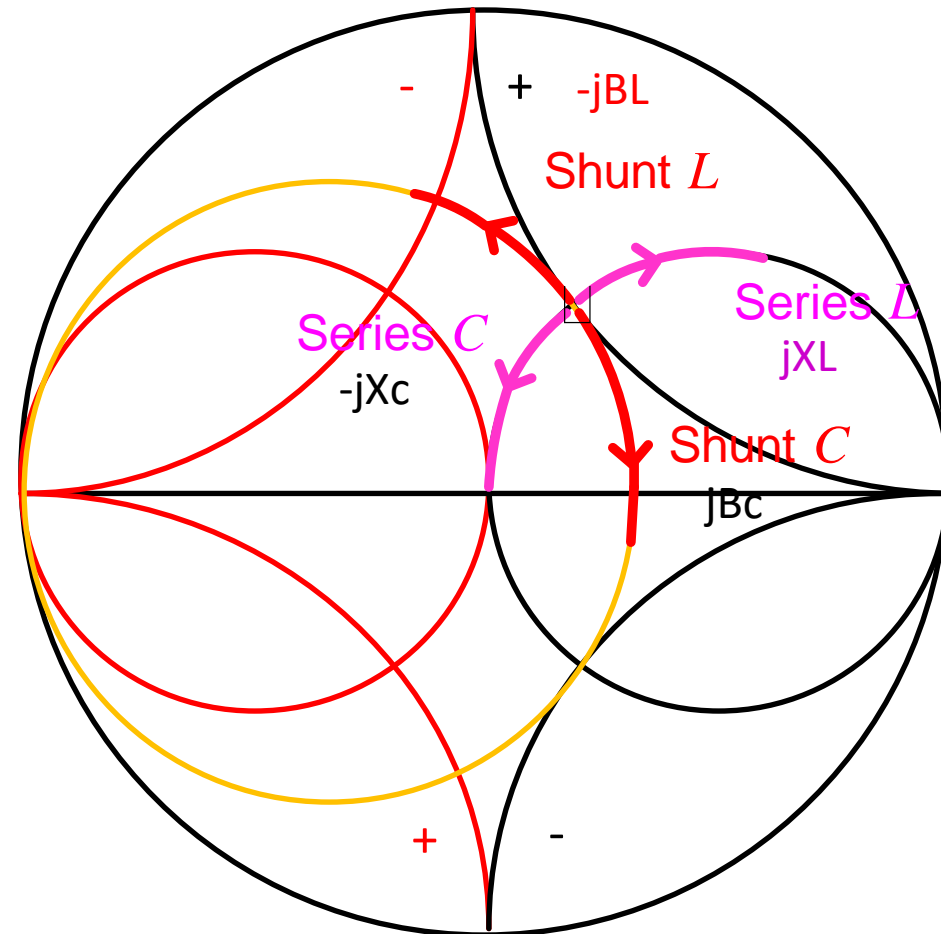

Note: The Smith chart is not actually being used as a transmission-line calculator but an impedance/admittance calculator. Hence, the normalizing impedance is arbitrary.

Adding a Series Capacitor

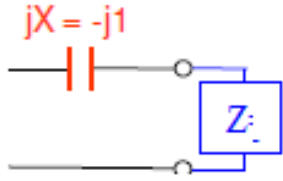

$$Z = 0.5 + j0.7$$

$$\begin{aligned} Z_1 &= 0.5 + j0.7 \\ \text{Adding } -j & \\ Z_2 &= 0.5 - j0.3 \end{aligned}$$

If we have initial impedance
 $Z = 0.5 + j0.7$

We add a series capacitor

Since resistance does not change
We move on constant circle from
 $j0.7$ to $-j0.3$

$$Z = 0.5 - j0.3$$


Values on ADS for $f = 1\text{GHz}$

$$Z = 25 + j35$$

$$Z_{in} = 25 - j15$$


$$1/\omega C = Z_{in} - Z = 50$$
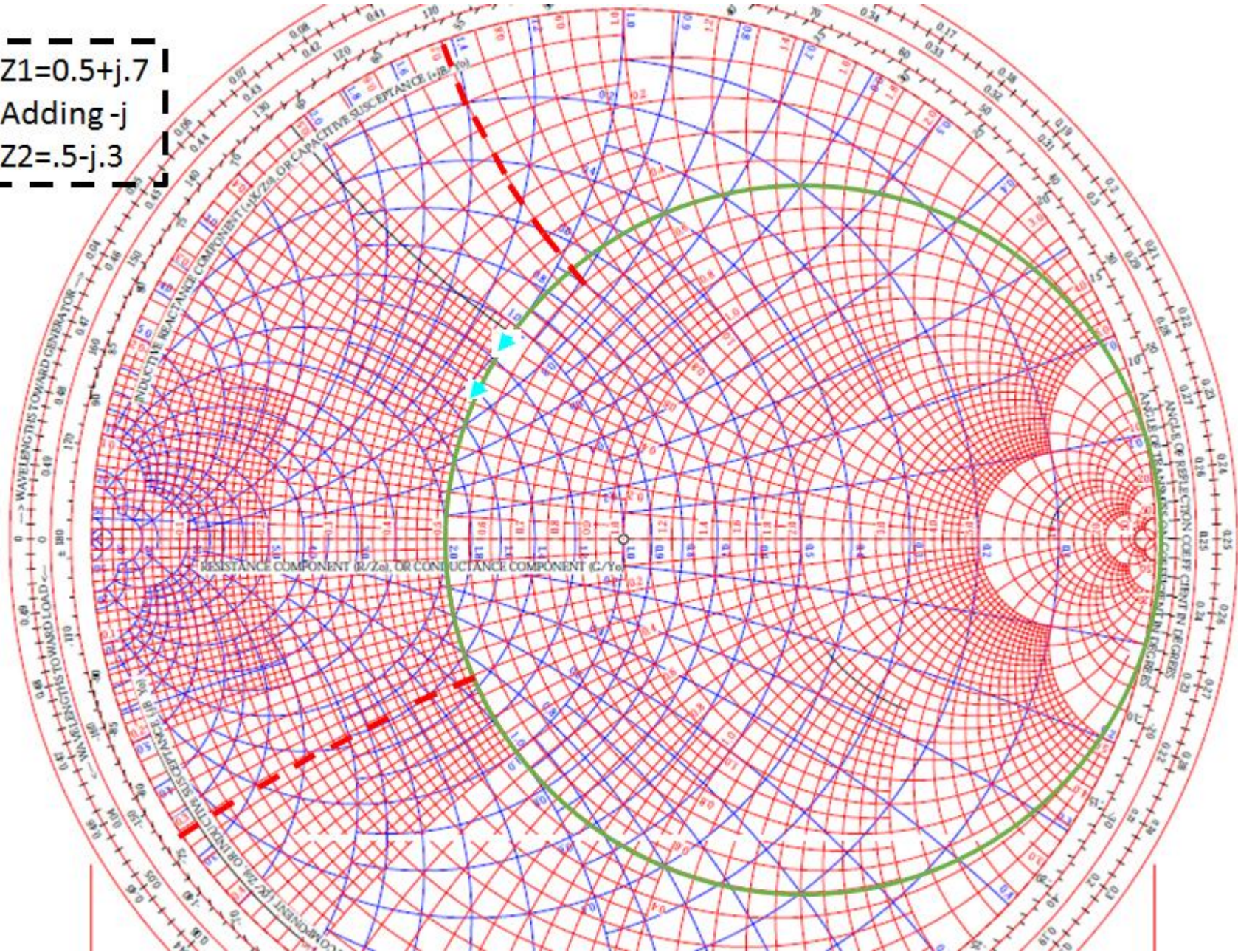
$$\text{so } C = 1/(50 * 2\pi) = 3.18\text{pF}$$



Adding a Series Inductor

$$jX = j1.4 = j\omega L/Z_c$$

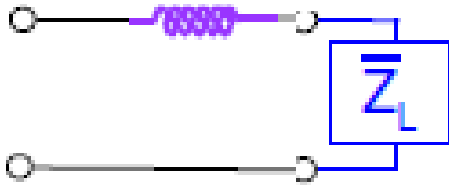

If we have $Z=0.5-j0.4$
We add series inductor
 $jX=j1.4$


We move on resistance circle
 $Z_{in}=0.5+j1.0$

Values on ADS


$$Z=25-j20$$

$$Z_{in}=25+j50$$
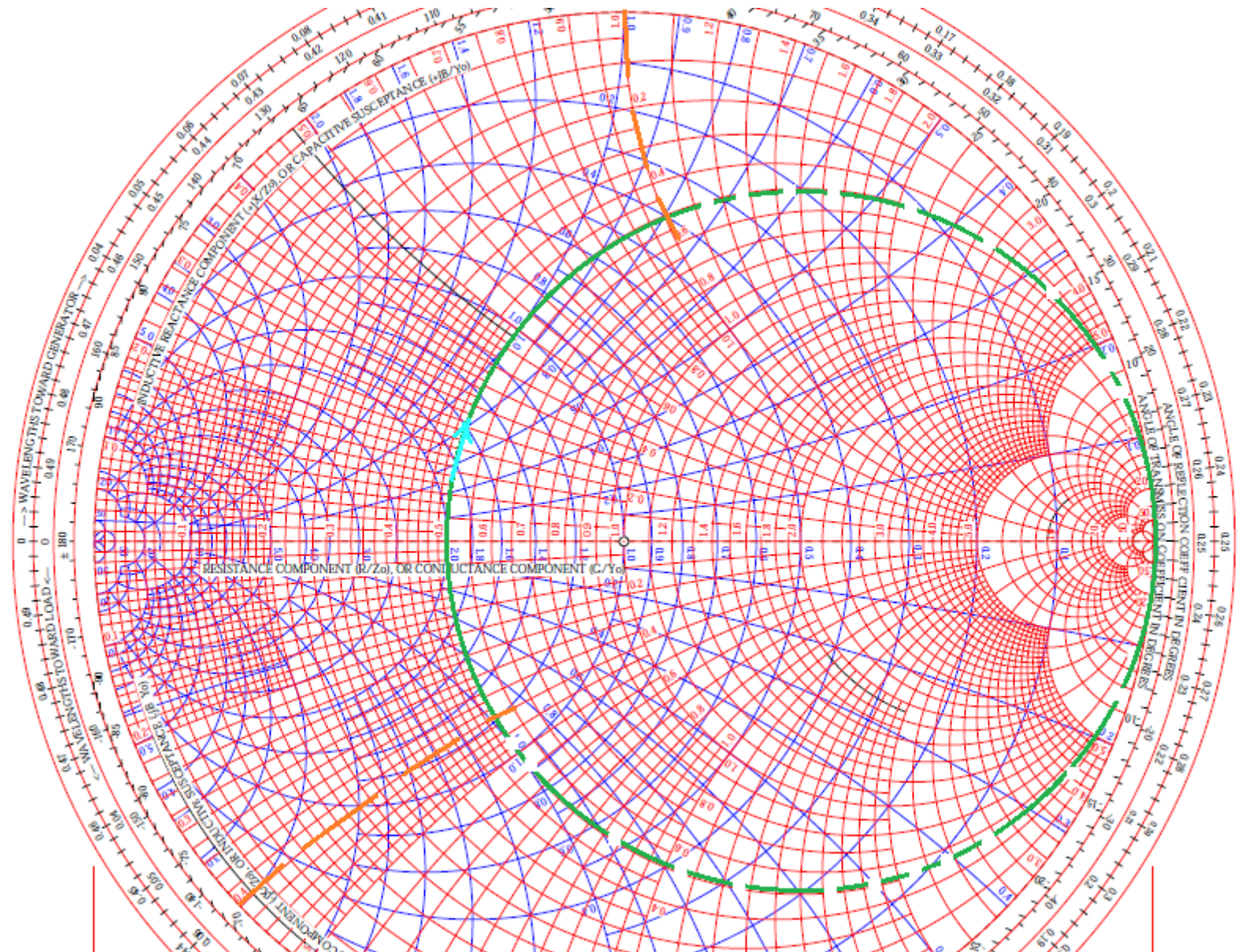
$$j\omega L=j70 \text{ so } L=70/(2\pi)=11.14\text{nH}$$



Adding a Shunt Capacitor

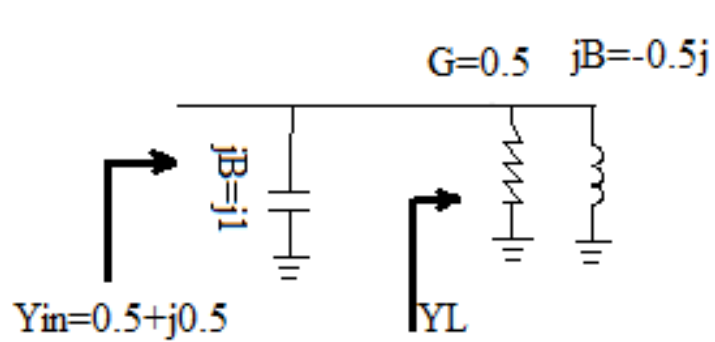

For $Z_L = 1 + j1.0$

On admittance chart

$Y_L = 0.5 - j0.5$


Adding shunt capacitor

With $jB = j1$


$Y_{in} = 0.5 + j0.5$

Read from impedance chart


$Z_{in} = 1 - j1.0$

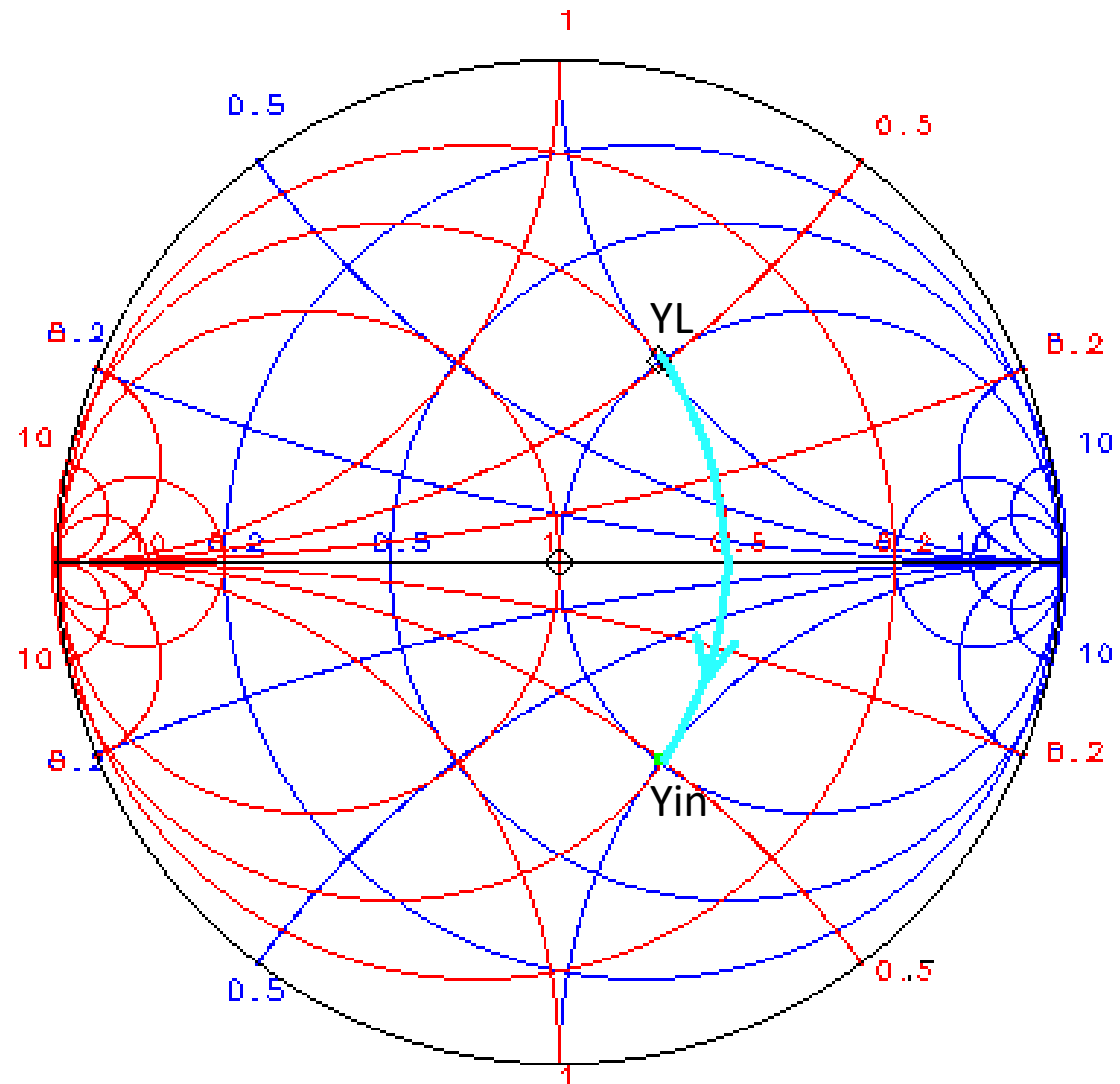


Adding Shunt Inductor

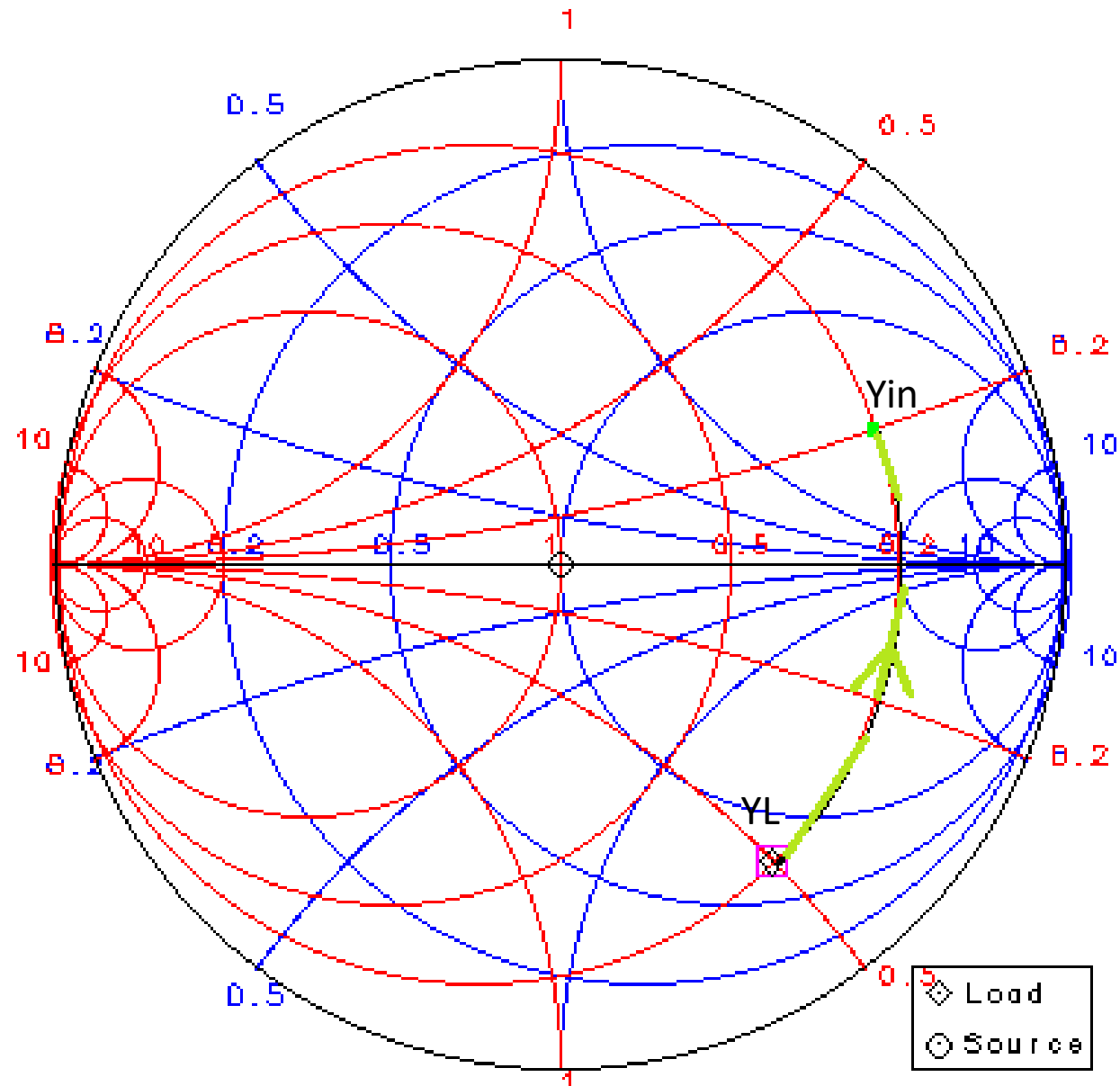

$$Y_L = 0.2 + j0.5$$

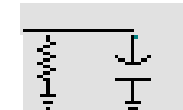

adding shunt inductor
with $J_B = -j0.7$

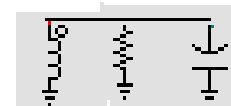


$$Y_{in} = 0.2 - j0.2$$

Read from impedance chart
 $Z_{in} = 2.4 + j2.5$

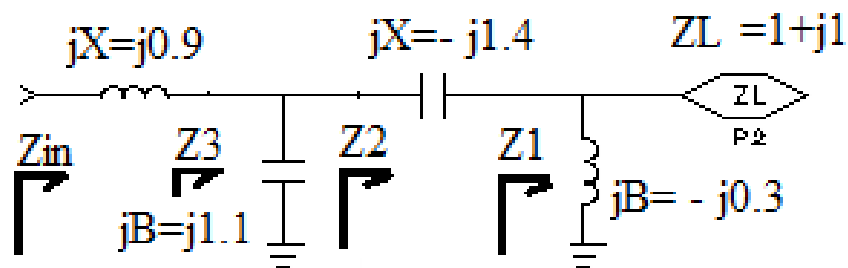
Example 8

what is the input impedance of network shown in Fig below




Solution :use impedance admittance smith chart

ZL			
Z:	1.00000	+j	1.00000
Y:	0.50000	+j	-0.50000
Z1,Y1			
Z:	0.55699	+j	0.89652
Y:	0.50000	+j	-0.80479
Z2,Y2			
Z:	0.55699	+j	-0.48811
Y:	1.01549	+j	0.88992
Z3,Y3			
Z:	0.20511	+j	-0.39989
Y:	1.01549	+j	1.97981
Zin,Yin			
Z:	0.20485	+j	0.49905
Y:	0.70391	+j	-1.71486

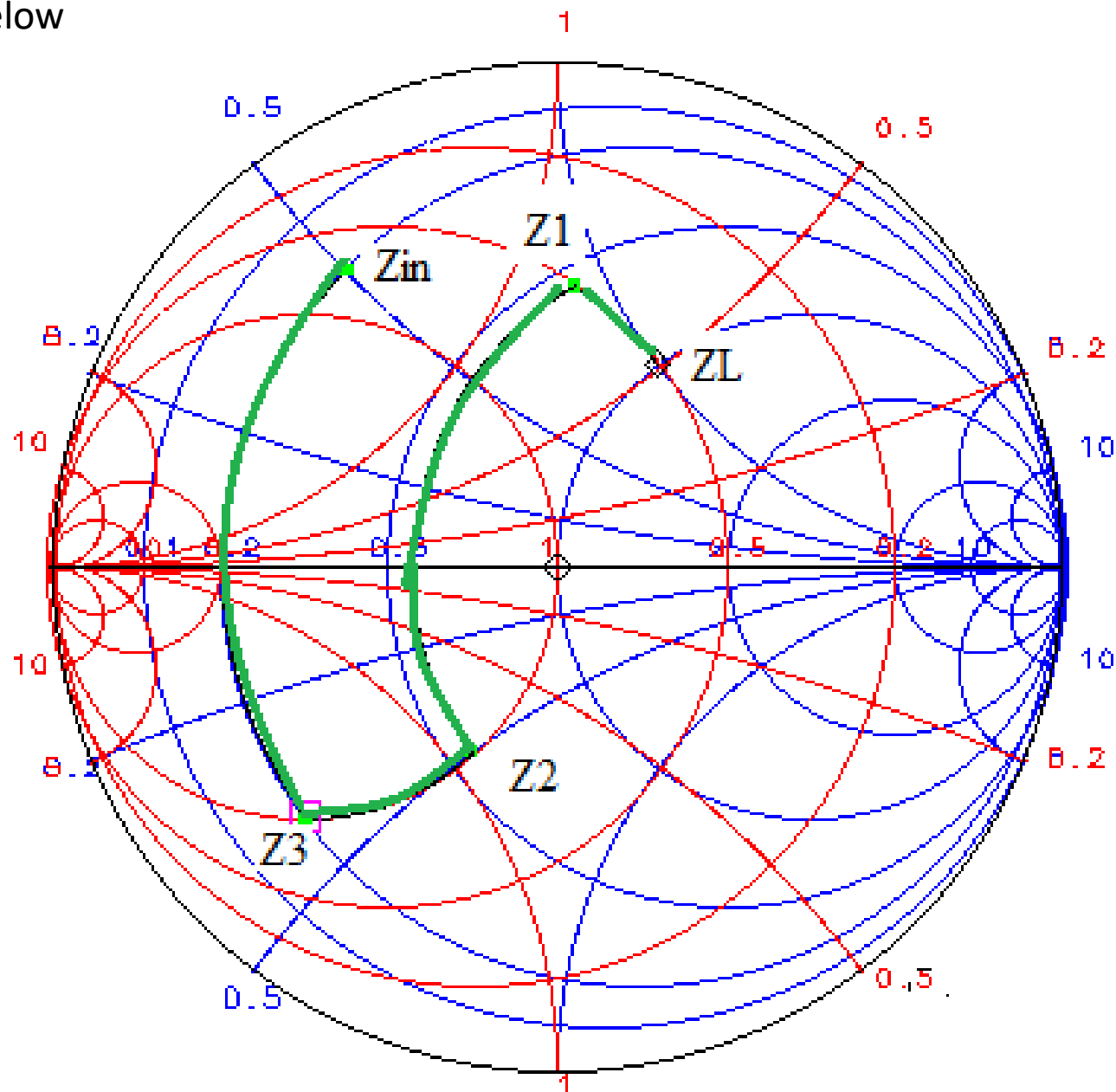

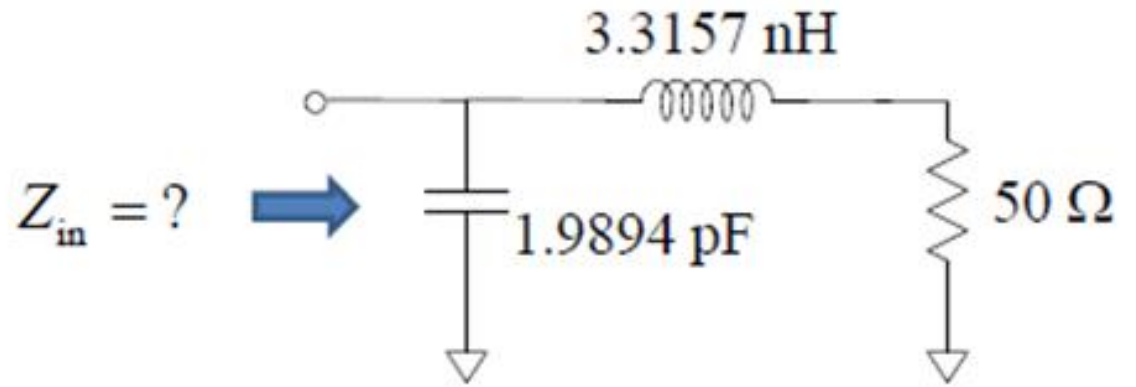Example 9

$$\begin{aligned} Z_{in} &= \frac{1}{j\omega C} \parallel (R + j\omega L) \\ &= \frac{\frac{1}{j\omega C}(R + j\omega L)}{\frac{1}{j\omega C} + (R + j\omega L)} \\ &= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC} \end{aligned}$$



$$f = 2.4 \text{ GHz}$$



$$Z_0 = 50 \Omega$$

$$\begin{aligned} &= \frac{50 + j(1.5080 \times 10^{10})(3.3157 \times 10^{-9})}{1 - (1.5080 \times 10^{10})^2 (3.3157 \times 10^{-9})(1.9894 \times 10^{-12}) + j(1.5080 \times 10^{10})(50)(1.9894 \times 10^{-12})} \\ &= 20 - j40 \Omega \end{aligned}$$

$$\Gamma = \frac{(20 - j40) - 50}{(20 - j40) + 50} = 0.62 \angle -98^\circ$$

$$\text{VSWR} = 4.2654$$

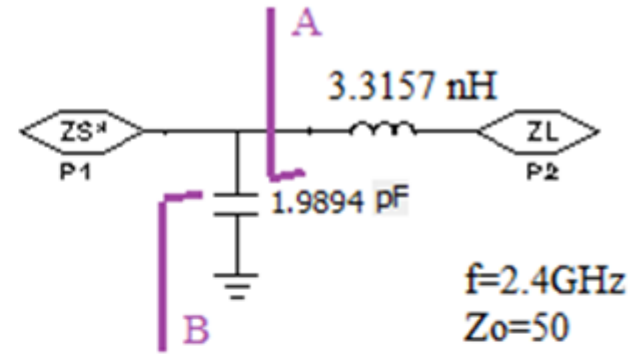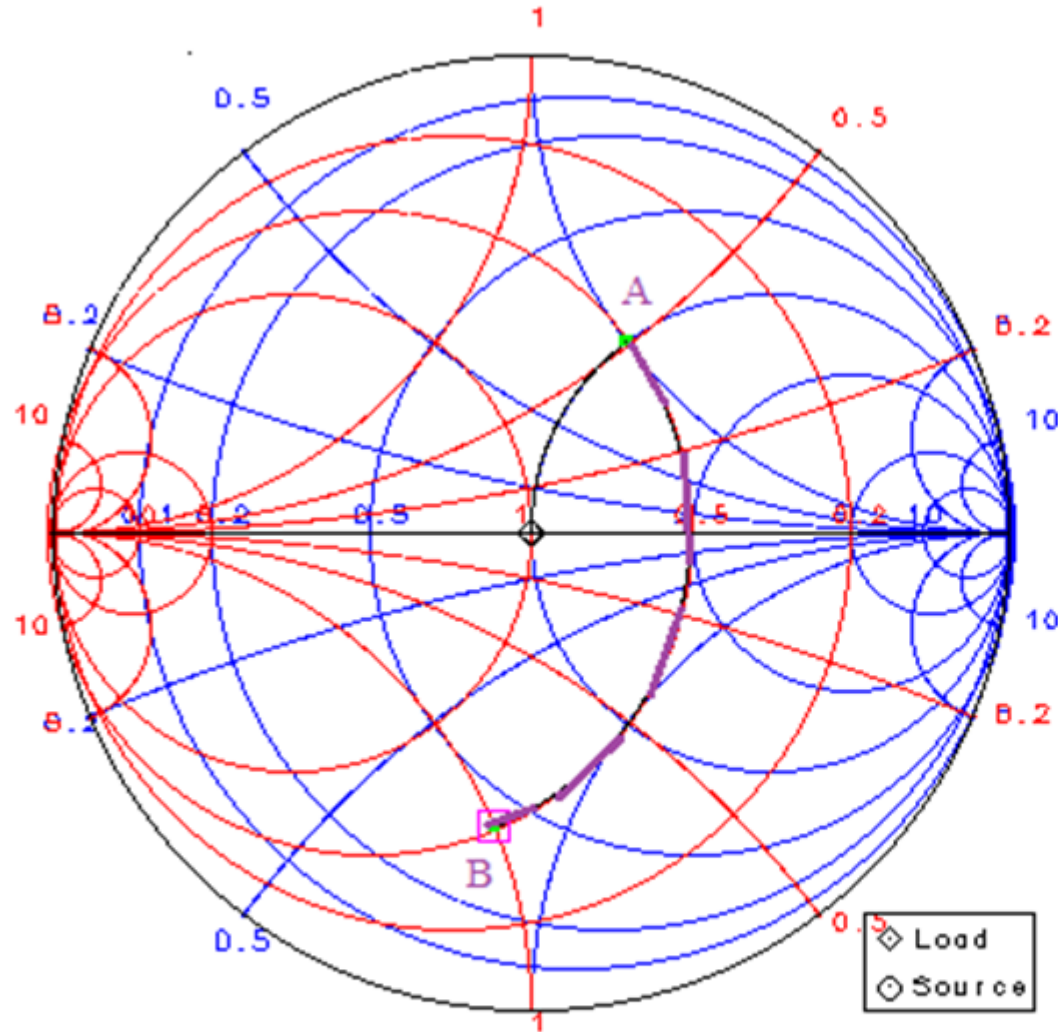Normalized value is used in impedance admittance smith chart (also using ADS smithchart)



$$Z_L = 50$$

$$Z_A = 50 + j2\pi \cdot 2.4 \cdot 3.3157$$

$$Z_A / Z_0 = 1 + j1$$


$$B_{cn} = 2\pi \cdot 2.4 \cdot 10^9 \cdot 1.9894 \cdot 10^{-12} \cdot 50 = 1.5$$

(B) Z, Y, and Gamma

Gamma:	0.62016	<	-97.1237	Z:	0.40002	+j	-0.80001	← ZB/Zo
VSWR:	4.26541			Y:	0.50000	+j	0.99997	ZB=20-j40

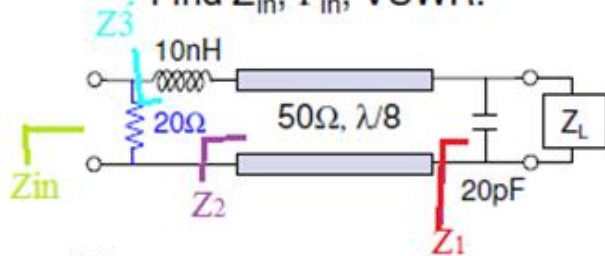Example 10 with shunt C, G, series L and TL

e.g. $Z_L = 20 - j25 \Omega$
 $f = 159 \text{ MHz}$ ($\omega = 10^9$)
 Find Z_{in} , Γ_{in} , VSWR.



$$\bar{Z}_L = 0.4 - j0.5$$

$$\bar{B} = \omega C / Y_0 = 0.02 Z_0 = 1$$

$$\bar{X} = \omega L / Z_0 = 10 / Z_0 = 0.2$$

$$\bar{G} = G / Y_0 = Z_0 / R = 50 / 20 = 2.5$$

$$Z_{in} = 50(0.28 + j0.13) = 14 + j7 \Omega$$

$$\Gamma_{in} = 0.57 (164^\circ)$$

