



ECE 344

MICROWAVE FUNDAMENTALS

PART1-Lecture 9

Dr. Gehan Sami

Matching Using TL and shunt stub:

Example 1


It is desired to match the load $Z_L=25+j50\Omega$ to 50Ω TL, $f=1\text{GHz}$

-use two lumped elements (four connections are possible, previous lecture)

-Use TL and shunt stub

Two solutions are possible , solve for minimum stub length. Declare stub end (s.c. or o.c.)

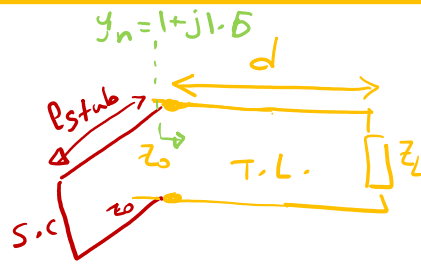-use TL and shunt limped elements (two solutions)



$$d = 0.428\lambda - 0.135\lambda = 0.293\lambda$$

$$\therefore y_n = 1 + j1.5$$


Added Element $y = -j1.5$ stub

$$l_{stub} = 0.09\lambda \text{ s.c}$$

if Added shunt o.c Stub


$$l_{stub} = (0.09 + 0.25)\lambda$$

$$o.c = 0.34\lambda$$

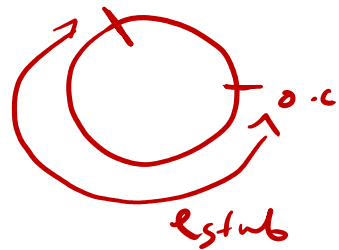



$l_{s.c}$

$l_{o.c}$

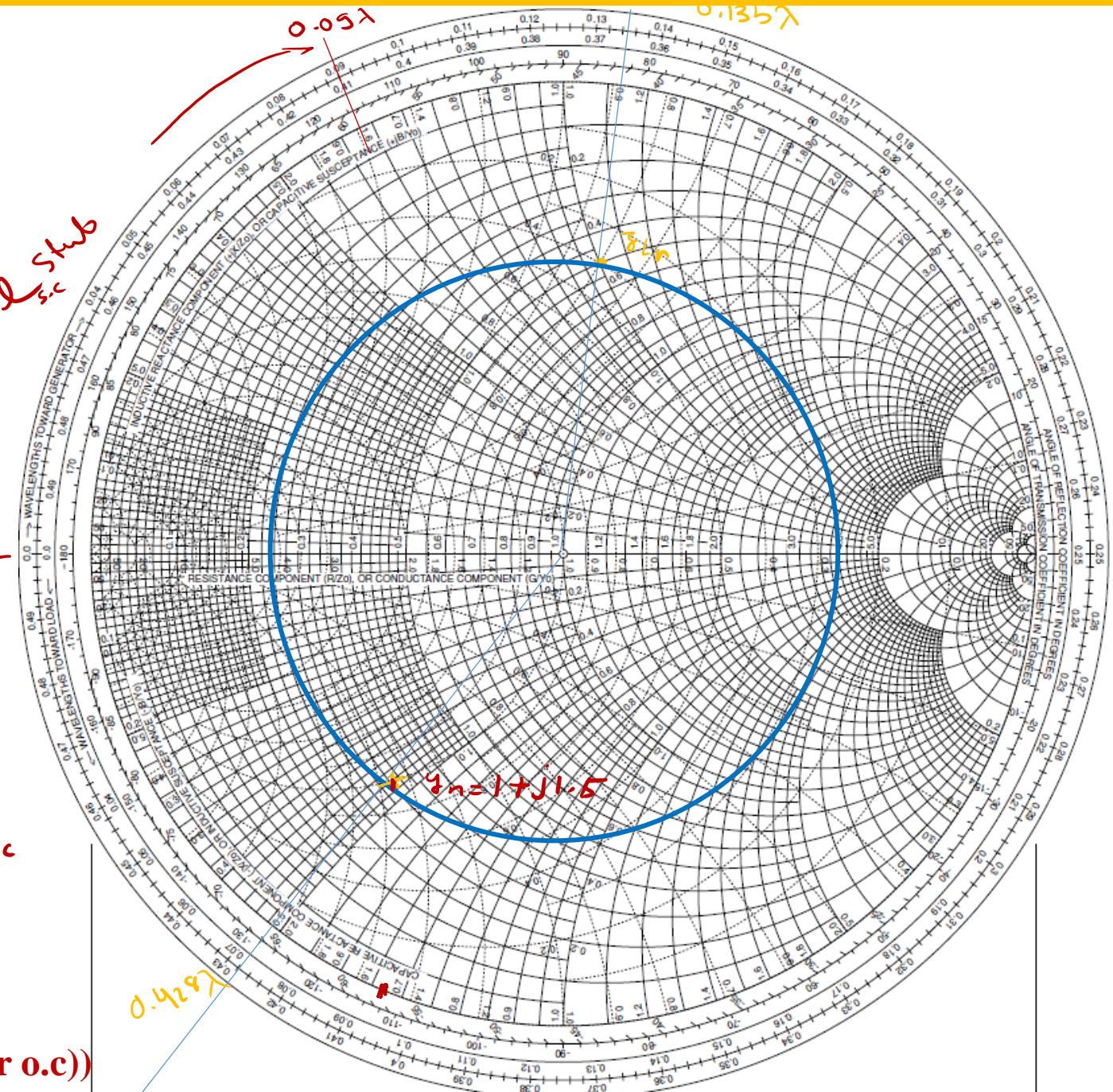

Using TL (small d then shunt stub (s.c or o.c))

Added Element: shunt L

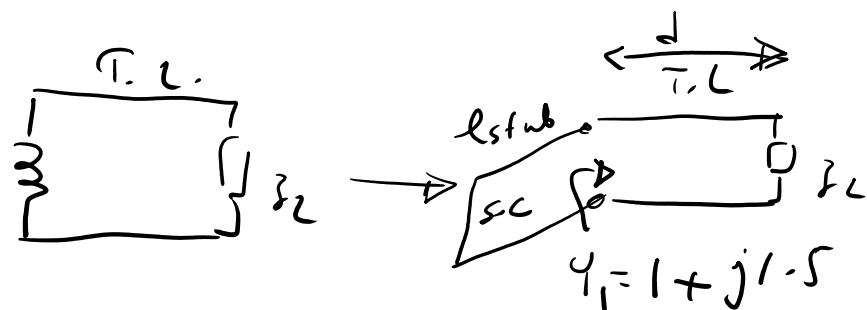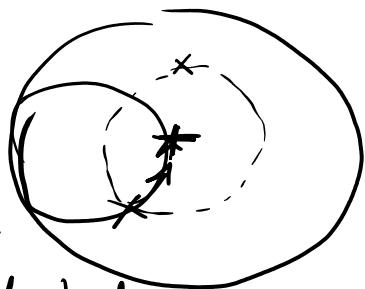

$$Y_{stub} = -j1.5 = \frac{1}{j\omega L / Z_0} = -j \cot \beta l$$


Compute l_{stub} by Equations:


$$Y_{stub} = -j1.5 = j \cot \beta l \rightarrow \beta l = \tan^{-1}\left(\frac{1}{1.5}\right) = 33.69^\circ \rightarrow l_{stub} = \frac{33.69}{360} \lambda = 0.0935 \lambda$$

if Matched Network $\Gamma \cdot L$ + lumped Element

Compute L
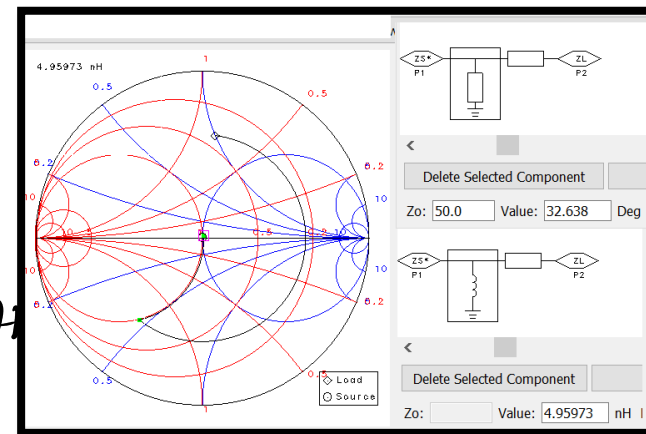
$$1.5 = \frac{1}{\omega L / Z_0} \rightarrow L = \frac{50}{1.5 \times 2\pi \times 10^9} = 5.3 \text{ nH}$$



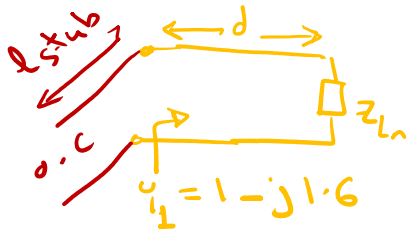

Using TL (large d then shunt stub (s.c or o.c))

$$d = (0.25 - 0.135)\lambda + 0.25\lambda + 0.072\lambda$$

$$= 0.437\lambda \rightarrow \beta l = 157.3^\circ$$

Added stub $Y_{\text{Stub}} = j1.6$

$$l_{\text{stub}} = 0.412\lambda - 0.25\lambda$$

o.c


$$= 0.162\lambda \rightarrow \beta l_{\text{Stub}} = 58.3^\circ$$

if we use s.c stub


$$l_{\text{stub}} = 0.162\lambda + \lambda/4$$

s.c


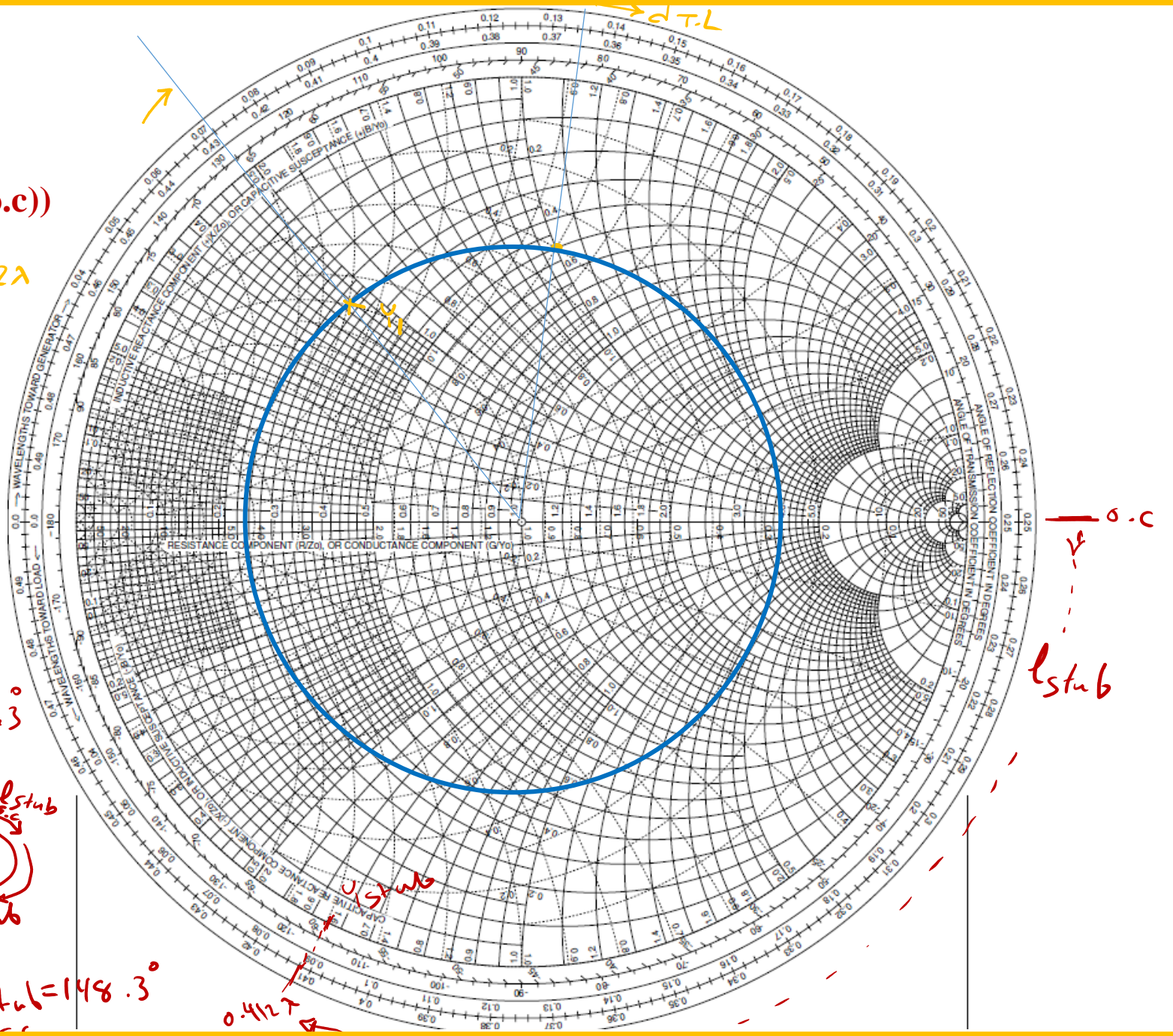
$$= 0.412\lambda \rightarrow \beta l_{\text{Stub}} = 148.3^\circ$$



Added Shunt
Element = C

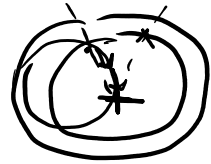

Compute l_{stub} by Equations:

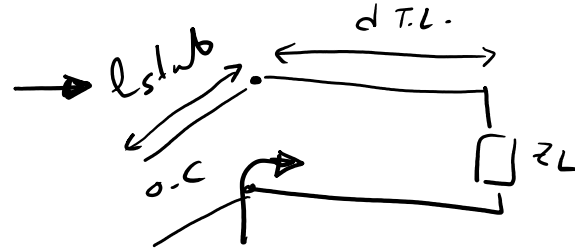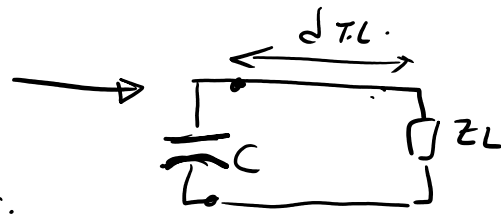

$$F = 1 \text{ GHz}$$

$$Z_0 = 50$$

$$Y_{stub} = j1.6 = Y_{o.c.} = j \tan \beta l$$

$$Y_1 = 1 - j1.6$$


$$Y_{stub} = j1.6$$

$$\therefore \beta l = \tan^{-1} 1.6 \Rightarrow l_{stub} = \frac{57.99}{360} \lambda = 0.161 \lambda$$

if Matched Network T.L. + Lumped Element :

Compute C

$$Y_{stub} = j1.6 = j\omega C Z_0 \rightarrow C = \frac{1.6}{2\pi \times 10^9 \times 50} = 5.09 \text{ pF}$$

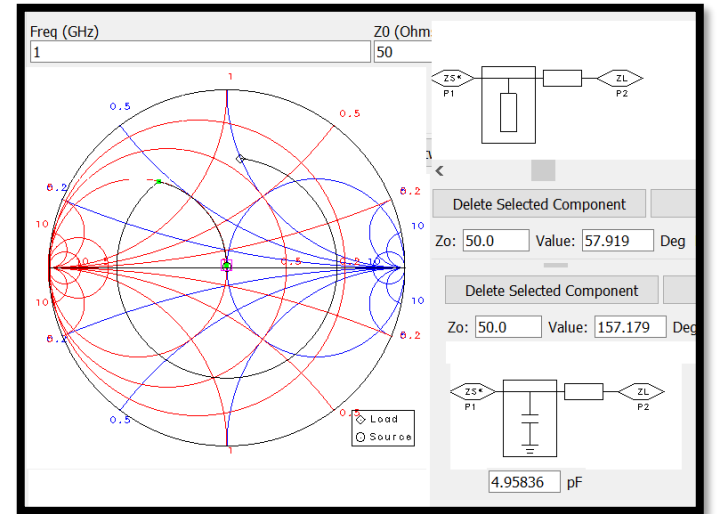



Example 2



build the circuit from the load
for giving track:

$$f = 1 \text{ GHz} \quad Z_0 = 50 \Omega$$

| ZL | | | |
|----------|---------|----|----------|
| Z: | 1.00000 | +j | 1.00000 |
| Y: | 0.50000 | +j | -0.50000 |
| Z1, Y1 | | | |
| Z: | 0.55699 | +j | 0.89652 |
| Y: | 0.50000 | +j | -0.80479 |
| Z2, Y2 | | | |
| Z: | 0.55699 | +j | -0.48811 |
| Y: | 1.01549 | +j | 0.88992 |
| Z3, Y3 | | | |
| Z: | 0.20511 | +j | -0.39989 |
| Y: | 1.01549 | +j | 1.97981 |
| Zin, Yin | | | |
| Z: | 0.20485 | +j | 0.49905 |
| Y: | 0.70391 | +j | -1.71486 |


Solution:

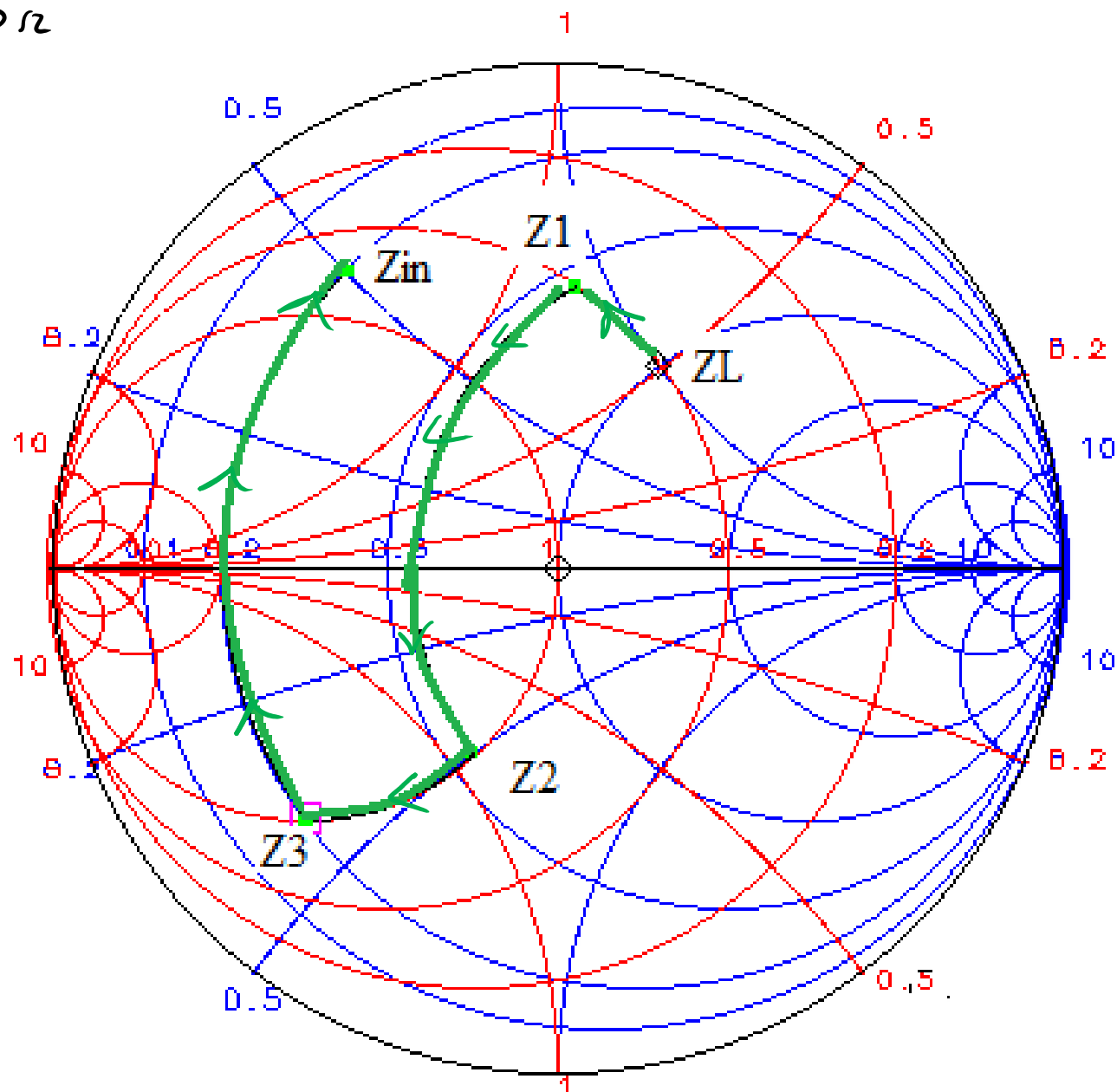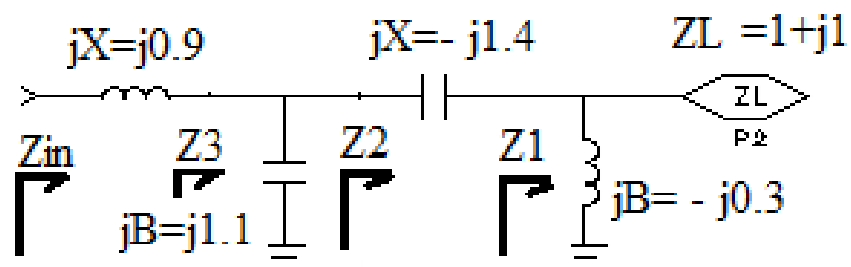

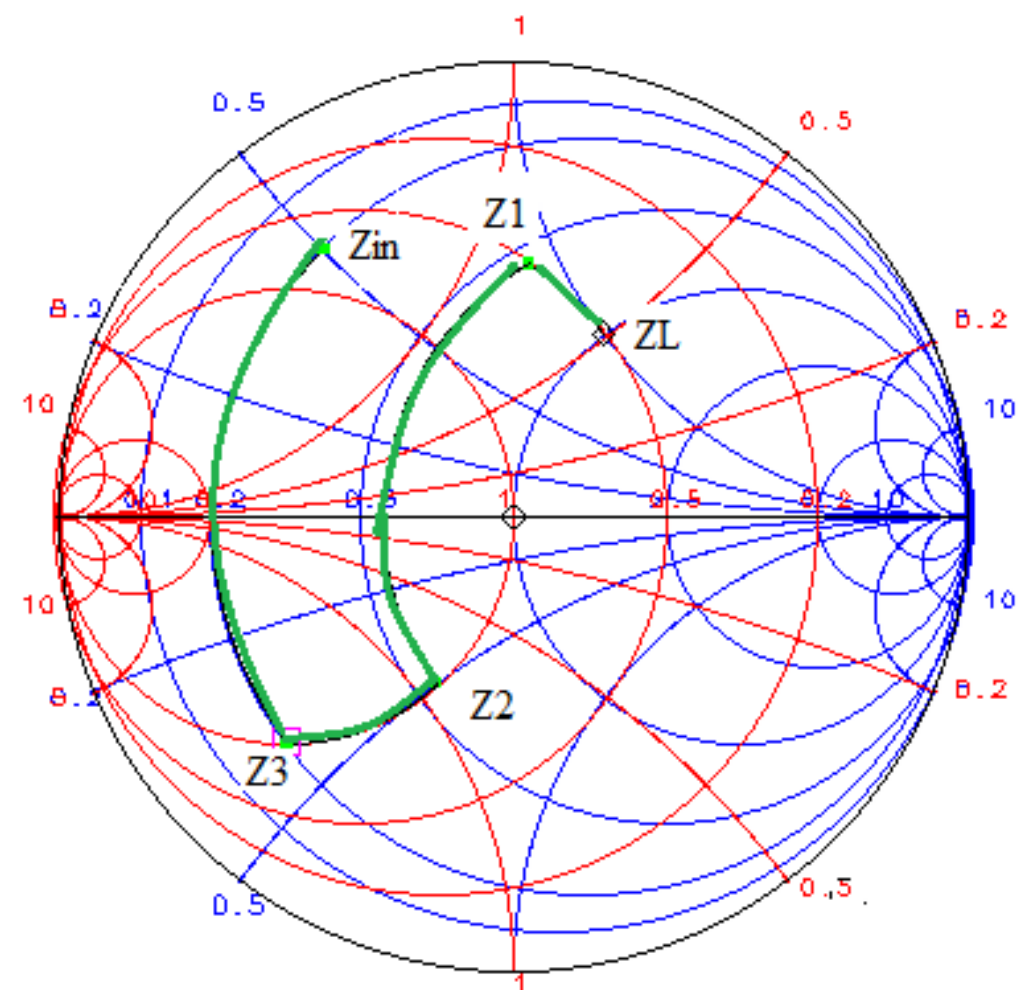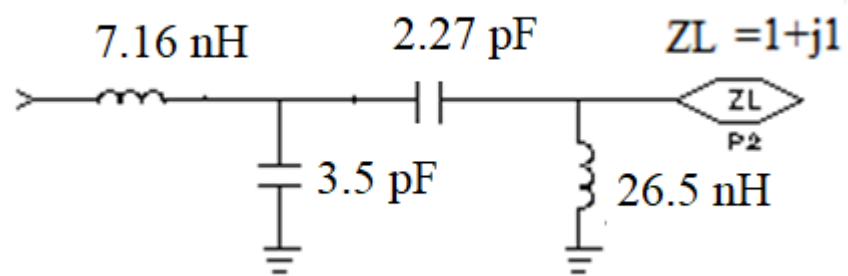

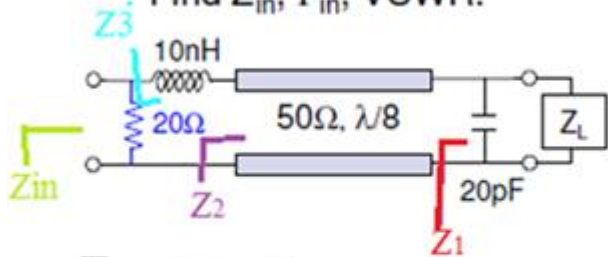Example 3 with shunt C, G, series L and TL

e.g. $Z_L = 20 - j25 \Omega$
 $f = 159 \text{ MHz}$ ($\omega = 10^9$)
 Find Z_{in} , Γ_{in} , VSWR.



$$\bar{Z}_L = 0.4 - j0.5$$

$$\bar{B} = \omega C / Y_0 = 0.02 Z_0 = 1$$

$$\bar{X} = \omega L / Z_0 = 10 / Z_0 = 0.2$$

$$\bar{G} = G / Y_0 = Z_0 / R = 50 / 20 = 2.5$$

$$\Gamma_{in} = 0.58 \angle 163^\circ$$

$$Z_{in} = 50(1 / (2.93 - j1.5j)) = 13.5 + j6.9 \Omega$$

