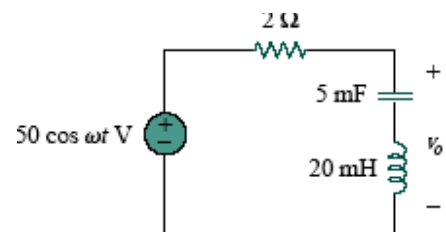





- (1) For each of the following voltage and current $v_s = 12 \sin(10^3 t + 24^\circ)$ V, $i_s = 8 \cos(500\pi t - 25^\circ)$ A, Find;
 (a) The angular frequency?
 (b) The frequency of the source?
 (c) Express v_s in cosine form.
 (d) Determine v_s and i_s at $t = 2.5$ ms
- (2) For the following pairs of sinusoids, determine which one leads and by how much.
 (a) $v(t) = 10 \cos(4t - 60^\circ)$, $i(t) = 4 \sin(4t + 50^\circ)$
 (b) $v_1(t) = 4 \cos(377t + 10^\circ)$, $v_2(t) = -20 \cos(377t)$
 (c) $x(t) = 13 \cos 2t + 5 \sin 2t$, $y(t) = 15 \cos(2t - 11.8^\circ)$
- (3) Transform the following sinusoids to phasors:
 (a) $-10 \cos(4t + 75^\circ)$ (b) $5 \sin(20t - 10^\circ)$ (c) $4 \cos 2t + 3 \sin 2t$
- (4) Obtain the sinusoids corresponding to each of the following phasors:
 (a) $V_1 = 60 \angle 15^\circ$, $\omega = 1$ (b) $V_2 = 6 + j8$, $\omega = 40$ (c) $I_1 = 2.8e^{-j/3}$, $\omega = 377$ (d) $I_2 = -0.5 - j1.2$, $\omega = 10^3$
- (5) Determine the current that flows through an $8\text{-}\Omega$ resistor connected to a voltage source $v_s = 110 \cos 377t$
- (6) What is the instantaneous voltage across a $2\text{-}\mu\text{F}$ capacitor when the current through it is:
 $i = 4 \sin(10^6 t + 25^\circ)$ A?
- (7) The voltage across a 4-mH inductor is $v(t) = 60 \cos(500t - 65^\circ)$ V Find the instantaneous current through it?
- (8) A current source of $i(t) = 10 \sin(377t + 30^\circ)$ A is applied to a single element load. The resulting voltage across the element is $v(t) = -65 \cos(377t + 120^\circ)$ V. What type of element is this? Calculate its value.


- (9) What value of ω will cause the voltage v_o in the figure to be zero?



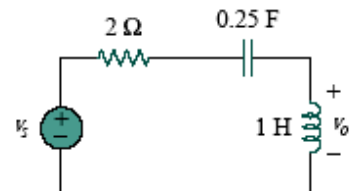- (10) If $v_s = 5 \cos 2t$ V in the figure. Find v_o using voltage divider rule.




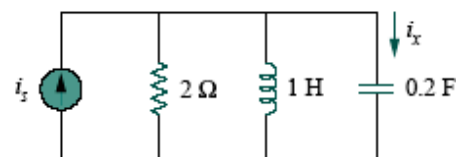- (11) Find i_x using current divider rule, when $i_s = 2 \sin 5t$ A is supplied to the circuit shown in figure.




Sheet No. 1

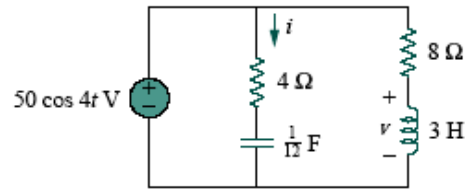
(12) Find $i(t)$ and $v(t)$ in the circuit shown, if the source frequency is 60 Hz.



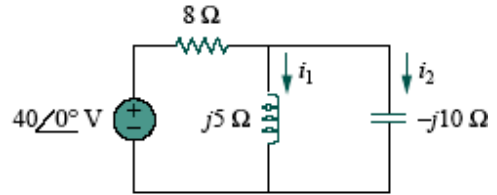
(13) In the circuit shown in fig. Calculate $i_1(t)$ and $i_2(t)$ using current divider rule.




(14) Find $v(t)$ in the RLC circuit

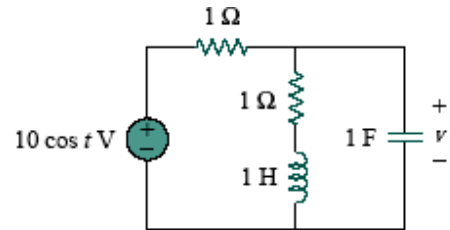

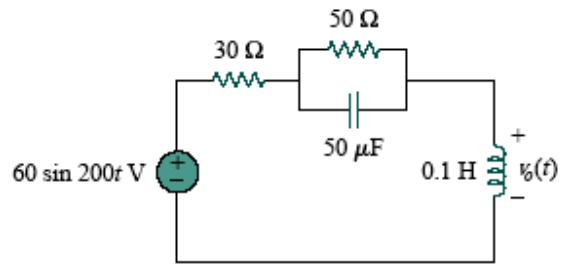
(15) In the circuit shown in fig. Calculate $v_o(t)$ using voltage divider rule.



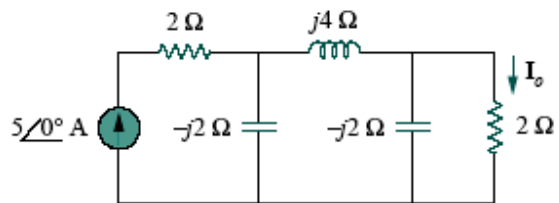
(16) Find current I_o in the network shown



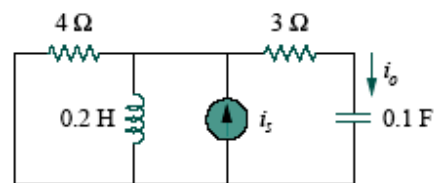(17) If $i_s = 5 \cos(10t + 40^\circ)$ A find i_o



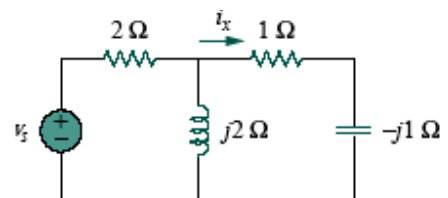(18) Find $v_s(t)$ in the circuit shown if the current i_x through the 1-Ω resistor is $0.5 \sin 200t$ A.



(19) If $V_o = 8 \angle 30^\circ$ V find I_s .

