
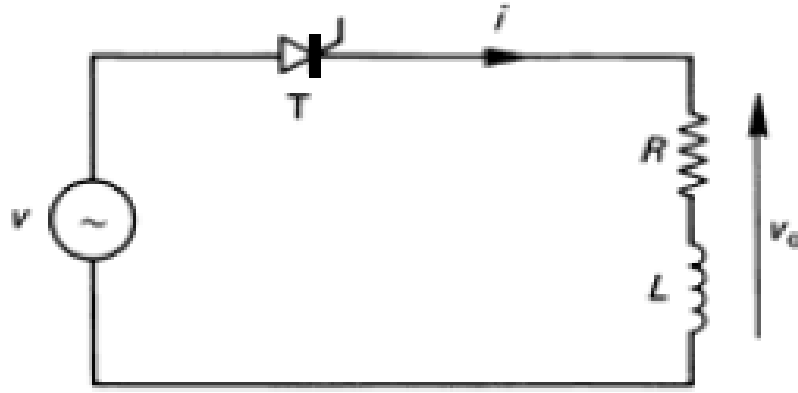


Willam Book Page 156

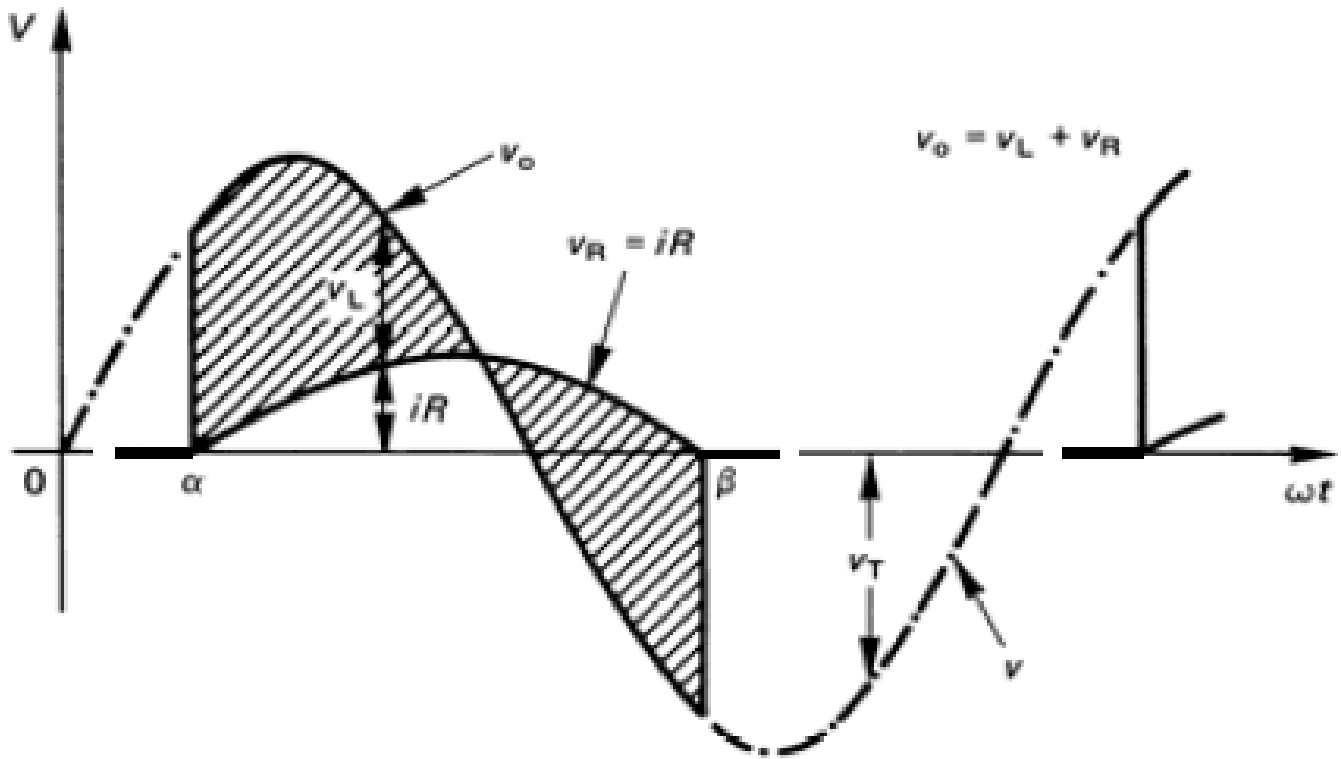**How To Calculate Beta in Ac Voltage Controller Has RL load
Using Curves**



(a)



(b)

Figure 11.6. Single-phase half-wave controlled converter:
(a) circuit diagram and (b) circuit waveforms for an inductive load.

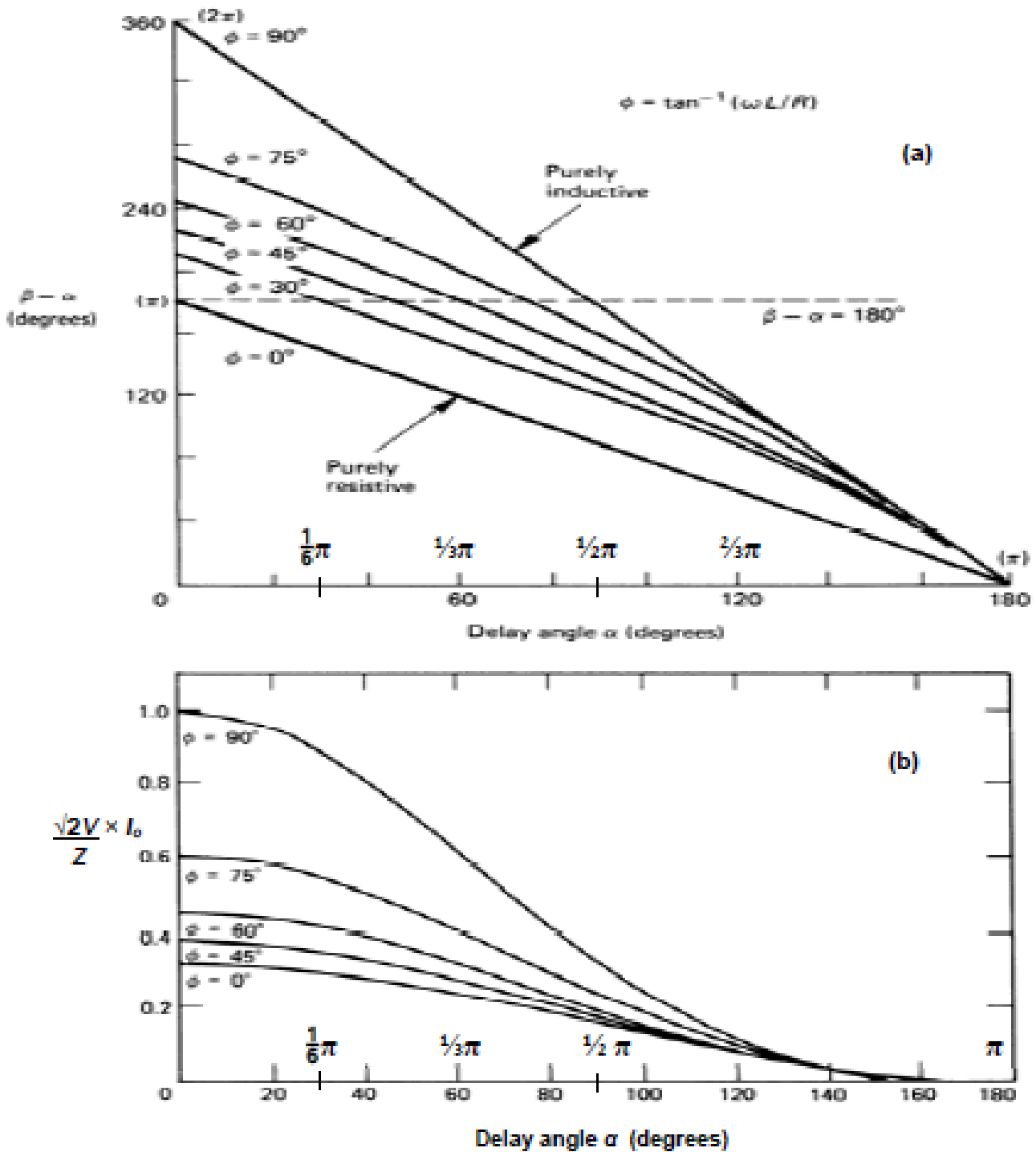


Figure 11.7. Half-wave, controlled converter thyristor trigger delay angle α versus: (a) thyristor conduction angle, $\beta - \alpha$, and (b) normalised mean load current.

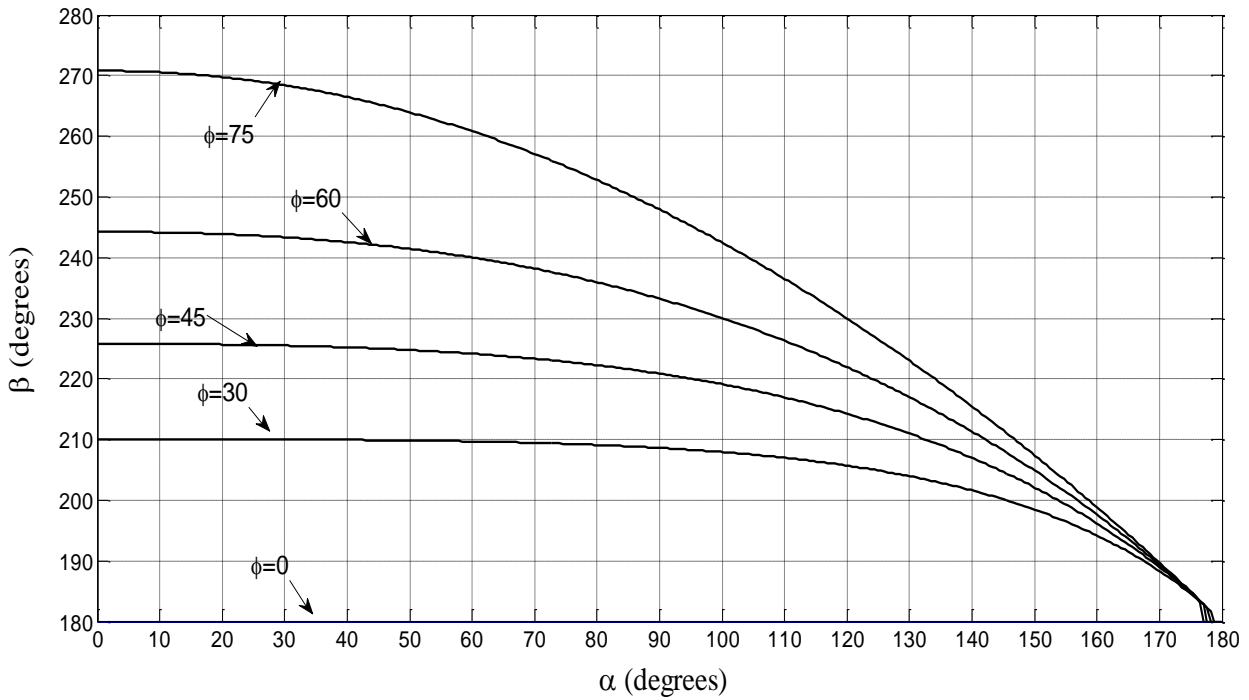


Fig. (1): Relation between *thyristor trigger delay angle* (α)
versus thyristor extinction angle (β)
(at using *RL load*)

Programs used to get Fig. (1) :
alpha_and_beta.m & BETA.m

Shepherd Book Page 331 & 334
How To Calculate Beta Using Curves
in AC Voltage Controller Has RL load

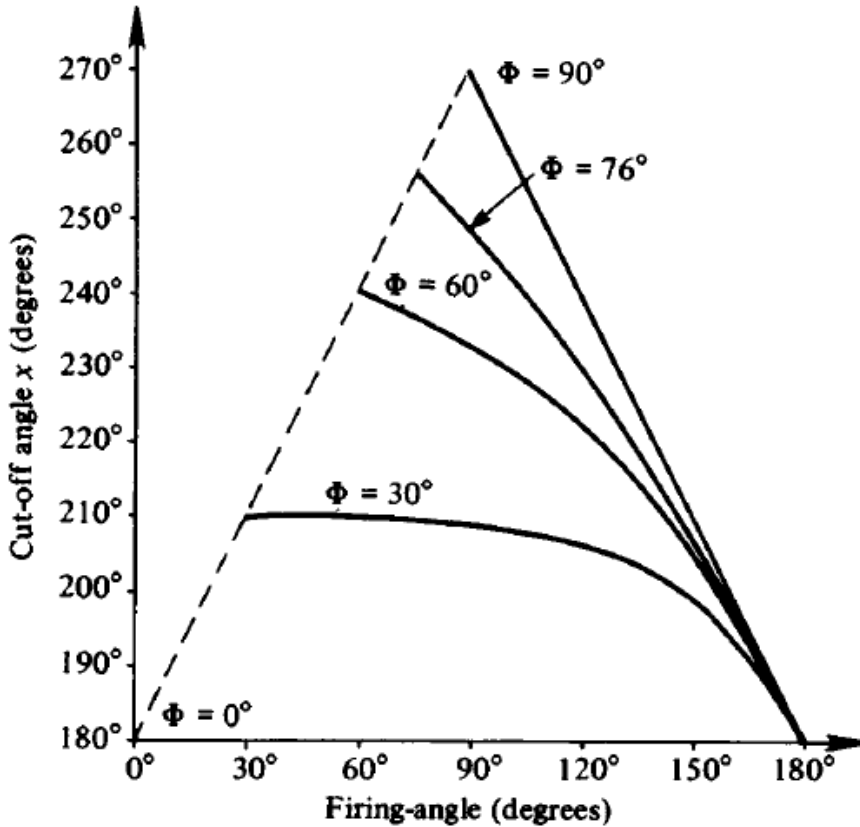


Fig. 8.15 Extinction angle versus firing-angle for single-phase controller. Series $R-L$ load.

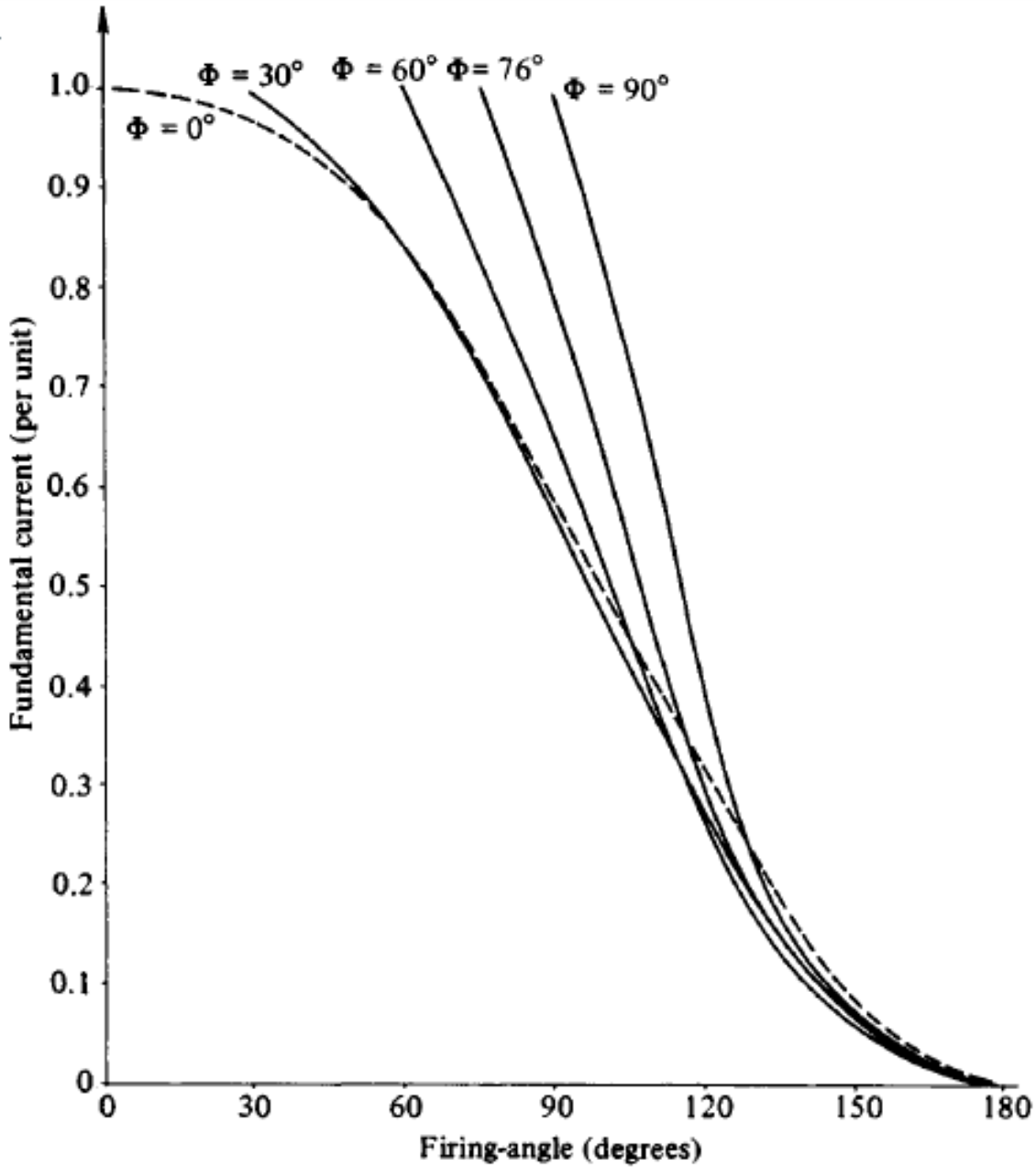


Fig. 8.18 Fundamental current versus firing-angle for single-phase controller. Series $R-L$ load.