



## Sheet (2)

- (1) (a) State and draw the types of AC-AC converters.  
(b) What is the control methods used with AC-AC converters?  
(c) What are the applications of AC-AC converters?  
(d) Draw the circuit and waveforms of a 1-phase AC voltage controller uses ON/OFF control technique; where  $n=2$  and  $m=1$ .  
(e) What are the disadvantages for using integral cycle control technique?
- (2) A heater of  $5\Omega$  is fed from an ac supply of 220V; 50Hz via a single-phase AC voltage controller uses ON-OFF control technique. The controller is ON for 2 cycles and OFF for 6 cycles. Determine:  
(i) The power consumed,  
(ii) The supply power factor.
- (3) A 1-phase AC voltage controller (ON-OFF control) supplying a  $4\Omega$  heating device. The input voltage is 220V, 50Hz and the power consumed by the heater is 2.42 kW, Determine:  
(i) The duty cycle,  
(ii) The turn-on and turn-off time,  
(iii) The maximum and RMS thyristor currents.
- (4) A 1kW electric heater is fed from an AC supply of 220V, 50Hz via 1-phase ON/OFF controller. The controller is turning OFF for 120ms, and the output power is 0.6kW. Determine:  
(i) The number of turning on cycles,  
(ii) Duty cycle to obtain 1kW output.
- (5) A single-phase AC voltage controller (use integral cycle control) supplying a  $4\Omega$  heating device. The input supply voltage is  $\sqrt{2} 208 \sin 2\pi 50t$ . If the average output power is 8kW. Determine:  
(i) Duty cycle,  
(ii) Supply power factor,  
(iii) The percentage power transferred compared to continuous AC operation,  
(iv) The thyristors maximum  $dv/dt$  and  $di/dt$  stresses.
- (6) A 220V, 50Hz electric boiler raises 1.7 liters of water from  $25^{\circ}\text{C}$  to  $100^{\circ}\text{C}$  in 5minutes. The boiler takes 12.5 minutes to raise the same amount of water in the same temperature conditions, when supplied from an on/off voltage controller. The specific heat capacity of water is  $4.18 \text{ kJ}/(\text{kg}\cdot^{\circ}\text{C})$ , assuming that the boiler is good thermally isolated. Determine:  
(i) Duty cycle,  
(ii) Boiler resistance,  
(iii) Output voltage.