



**Sheet (3)**

- (1) A single-phase half-wave AC controller has a resistive load of  $15\Omega$ . The input voltage is 220 V, 50 Hz. The firing delay angle is  $45^\circ$ . Determine:
- the rms output voltage,
  - the average and rms currents of the thyristor and the diode,
  - the average input current,
  - the input power factor, and
  - the maximum and minimum power factor.
- (2) A single-phase full-wave controller has a resistive load of  $10\Omega$ . The input voltage is 220V 50-Hz. If the desired output power is 2.5 kW, determine:
- the rms output voltage,
  - the firing angle,
  - the input power factor, and
  - the average and rms thyristor currents.
- (3) A resistive load of  $10\Omega$  is connected to a 220-V, 50-Hz AC source via a single-phase full-wave AC triac-voltage controller. The load power varies between the maximum value to  $\frac{1}{4}$  the max. value. Calculate the following:
- the control range of  $(\alpha)$ ,
  - the rms value of the load current for each extreme of the firing angle,
  - the average and rms values of triac current,
  - the supply power factor for the smaller power value.
- (4) A single-phase, full-wave, AC thyristors-voltage controller feeds power to a resistive load of  $10\Omega$  from a 220-V, 50-Hz AC source, at triggering angle  $\alpha = \pi/6$ . Determine:
- the rms value of the output voltage,
  - the output power and input power factor.
  - the value of the thyristor voltage at the instant of firing,
  - the ratio of the third harmonic to the fundamental components of the output voltage
  - the triggering angle at which the greatest forward or reverse voltage is applied to one of the thyristors and the magnitude of these voltages.
- (5) A single-phase, resistive load is supplied from 380-V, 50-Hz source through a fully-controlled AC voltage regulator. With no phase control the load power is 9.63 kW, find:
- the value of  $(\alpha)$  to reduce the average power to 3 kW,
  - the amplitude of the fundamental current for this value of  $(\alpha)$ , and
  - the amplitude of the third and fifth-order harmonic currents.