




=====

Sheet (5)

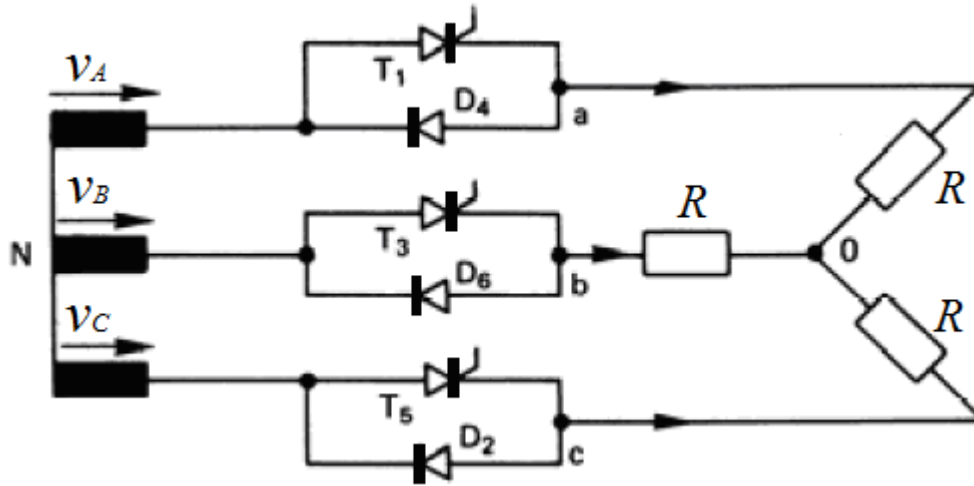- (1) If the instantaneous expression of the first phase (v_A); in three phase supply system, is:
 $v_A = 311 \sin(314t)$ V. Draw in the same figure; v_A , v_{AB} , v_{AC} .
- (2) If the instantaneous expression of the first phase (v_A); in three phase supply system, is:
 $v_A = 311 \sin(314t)$ V. Draw in the same figure; v_A , $0.5v_{AB}$, $0.5v_{AC}$.
- (3) A 3-phase, full-wave AC voltage controller feeds Y-connected resistive load of 5Ω per phase and is supplied from an AC source of 380V, 50 Hz. For each firing delay angles: 0° , 45° , 75° , 120° and 150° :
- Draw the waveform of the output phase voltage and current, v_{ao} and i_{ao}
 - Write the expression of the output phase voltage and current, v_{ao} and i_{ao}
 - Calculate the instantaneous phase voltage value (v_{ao}) at $wt = 0^\circ, 30^\circ, 45^\circ, 75^\circ, 90^\circ, 120^\circ, 150^\circ, 180^\circ, 210^\circ, 270^\circ, 330^\circ$ and 360° .
 - Calculate the rms value of output phase voltage,
 - Calculate the load power,
 - Calculate the source power factor,
 - Calculate the maximum applied voltage to the thyristor in the first phase.
- (4) A 3-phase, half-wave AC voltage controller feeds Y-connected resistive load of 10Ω per phase and is supplied from an AC source of 400V, 50 Hz. For each firing delay angles: 0° , 45° , 75° , 120° and 150° .
- Draw the waveform of the output phase voltage and current, v_{ao} and i_{ao}
 - Write the expression of the output phase voltage and current, v_{ao} and i_{ao}
 - Calculate the instantaneous phase voltage value (v_{ao}) at $wt = 0^\circ, 30^\circ, 45^\circ, 75^\circ, 90^\circ, 120^\circ, 150^\circ, 180^\circ, 210^\circ, 270^\circ, 330^\circ$ and 360° .
 - Calculate the rms value of output phase voltage,
 - Calculate the load power,
 - Calculate the source power factor, and
 - Calculate the maximum applied voltage to the thyristor in the first phase.
- (5) A Y-connected resistive load of 20Ω per phase is connected to 460V, 60-Hz, 3-phase supply. The load power varied from 9kW to 3kW by using a 3-phase full-wave AC voltage controller. Determine:
- The peak value of thyristor current,
 - The range of required firing delay angle, and
 - The range of supply power factor.
- (6) Repeat prob. (5) for 3-phase half-wave AC voltage controller.
- (7) Write a short note about soft starting of 3-phase induction motor using 3-phase ac voltage regulators.



Three Phase Half Wave AC Voltage Controller with Y connected Resistive Load



The expressions for RMS load phase voltage with resistive load are:

$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{4\pi} + \frac{3}{8\pi} \sin 2\alpha \right\}} \quad \dots\dots\dots 0^\circ \leq \alpha \leq 90^\circ$$

$$V_o = V_s \sqrt{\left\{ \frac{11}{8} - \frac{3\alpha}{2\pi} \right\}} \quad \dots\dots\dots 90^\circ \leq \alpha \leq 120^\circ$$


$$V_o = V_s \sqrt{\left\{ \frac{7}{8} - \frac{3\alpha}{4\pi} + \frac{3}{16\pi} \sin 2\alpha - \frac{3\sqrt{3}}{16\pi} \cos 2\alpha \right\}} \quad \dots\dots\dots 120^\circ \leq \alpha \leq 210^\circ$$

$$V_o = 0 \quad \dots\dots\dots \alpha \geq 210^\circ$$

Where V_s is the rms of the supply phase voltage



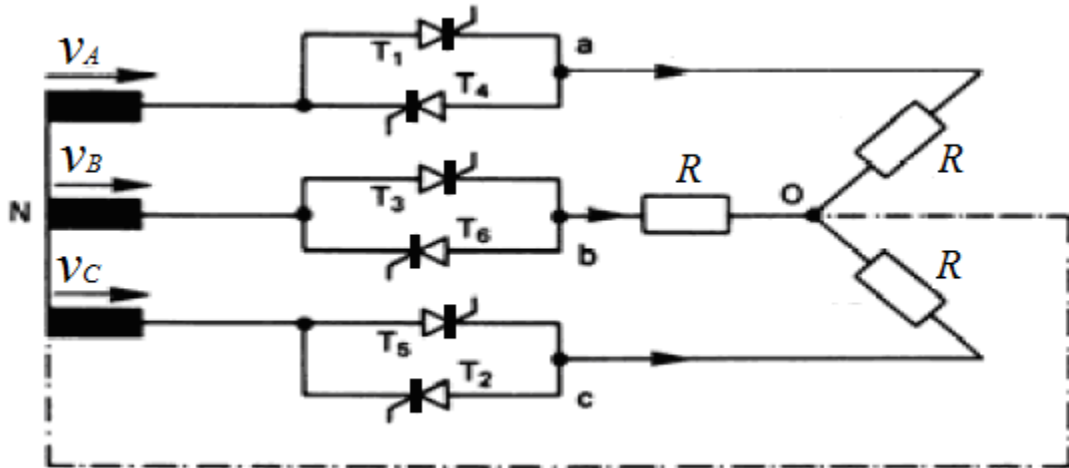Three Phase Full Wave AC Voltage Controller with Y connected Resistive Load



The expressions for RMS load phase voltage with resistive load are:

$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{2\pi} + \frac{3}{4\pi} \sin 2\alpha \right\}} \quad \dots\dots\dots 0^\circ \leq \alpha \leq 60^\circ$$

$$V_o = V_s \sqrt{\left\{ \frac{1}{2} + \frac{9}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}} \quad \dots\dots\dots 60^\circ \leq \alpha \leq 90^\circ$$

$$V_o = V_s \sqrt{\left\{ \frac{5}{4} - \frac{3\alpha}{2\pi} + \frac{3}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}} \quad \dots\dots\dots 90^\circ \leq \alpha \leq 150^\circ$$

$$V_o = 0 \quad \dots\dots\dots \alpha \geq 150^\circ$$

Where V_s is the rms of the supply phase voltage

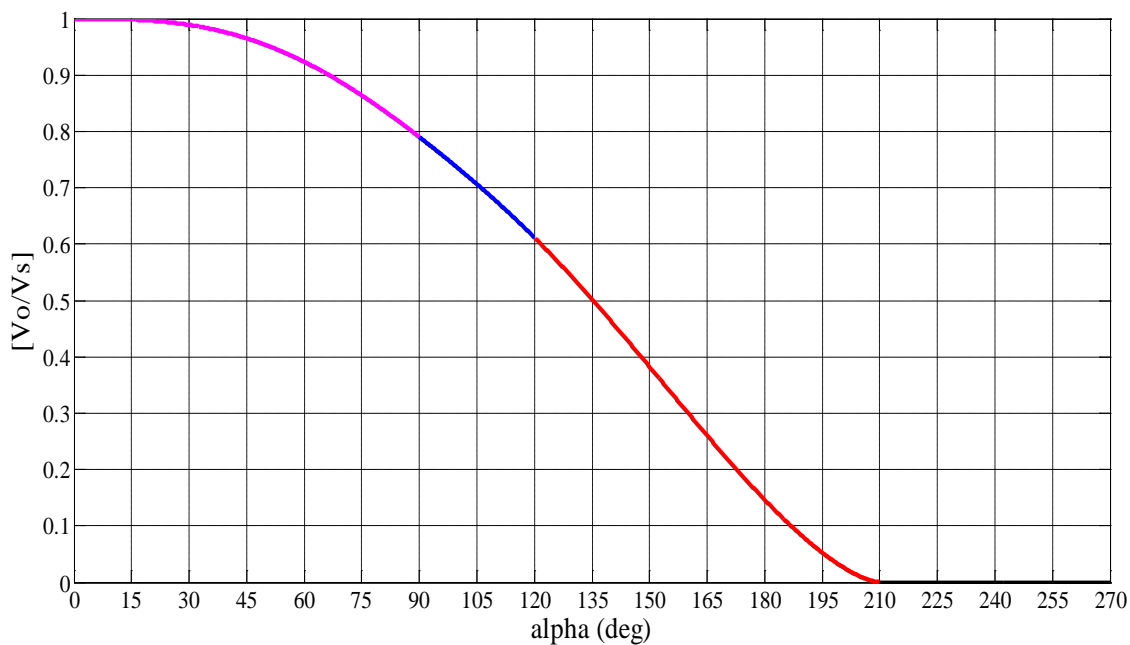


Fig. (1): $[V_o/V_s]$ versus [firing angle] for a Y- connected resistive load in 3-ph Half Wave AC Voltage Controller

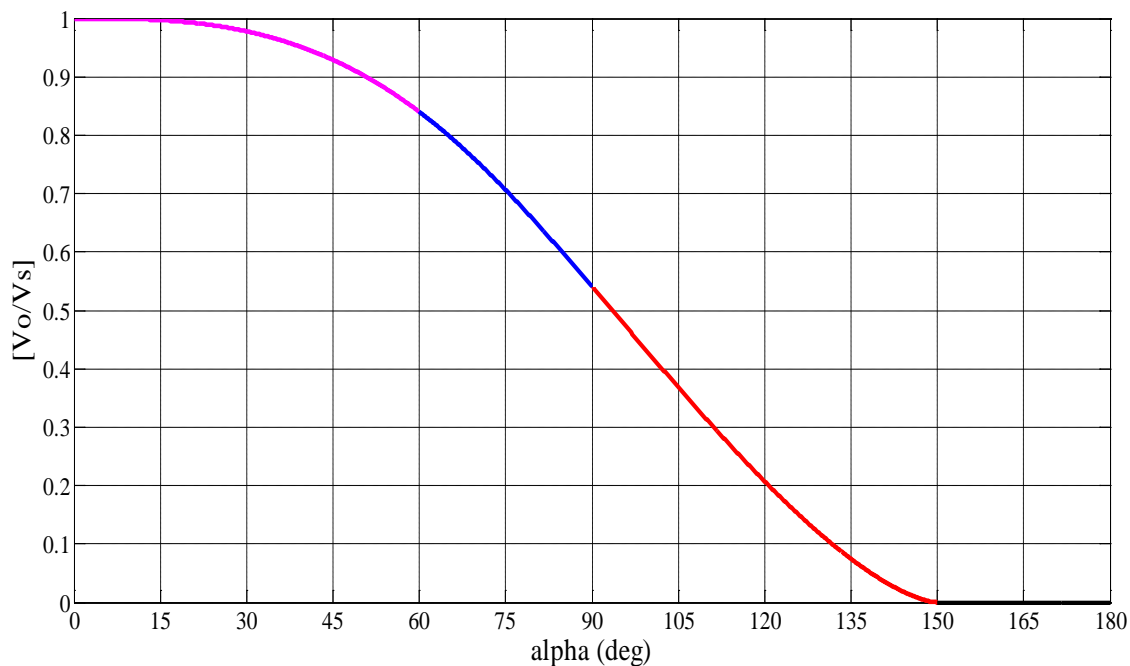


Fig. (2): $[V_o/V_s]$ versus [firing angle] for a Y- connected resistive load in 3-ph Full Wave AC Voltage Controller

