



Sheet (6)

- (1) From the review of the cycloconverter:
 - [a] What are the basic concept, construction and applications of the cycloconverter?
 - [b] Why the maximum output frequency is limited to $\frac{1}{3}$ of the input frequency?
 - [c] What are the basic forms of the cycloconverter?
- (2) Draw and explain; how can you use 1-ph cycloconverter to get an output voltage has a frequency of $16\frac{2}{3}$ Hz from a voltage source has a frequency of 50Hz?
- (3) Draw and explain; how can you use 1-ph cycloconverter to get an output voltage has a frequency of 10Hz from a voltage source has a frequency of 50Hz?
- (4) Make a comparison between VSI and matrix converter.
- (5) Draw the power circuit of the matrix converter, then:
 - [a] Write the mathematical expression of switching function,
 - [b] Determine the 27 switching state combinations.
- (6) Draw the possible discrete configurations of a bi-directional switch used in matrix converter. Write the merit and demerit of each of them.
- (7) Draw a diagram of the four-step commutation strategy used to commutate the switches of matrix converter when the current flows from the supply to the load.
- (8) Repeat problem (7), when the current flows from the load to the supply.
- (9) A 380V, 50Hz, nine-switch matrix converter feeding an inductive load. The output frequency is 100Hz. Determine:
 - [a] The minimum value of the switching frequency,
 - [b] The possible maximum output voltage.
- (10) A 3-phase inductive load is fed from a 3-ph, 380V and 50Hz supply via a matrix converter. The fundamental output phase voltage can be expressed as:

$$V_o = 120 \cos(628t) \quad \text{V}$$

Determine:

- [a] The output and the switching frequencies,
- [b] The modulation index.