

1. A 120-V, 60-Hz, 1-ph, half-wave AC voltage controller feeding a resistive load of 10Ω . The conduction period of the thyristor is $2\pi/3$. Calculate:
 - i. The rms output voltage.
 - ii. The source power factor.

2. A 220-V, 50-Hz, AC regulator feeds a highly inductive load of $\phi \approx \pi/2$. Determine:
 - a. the range of the triggering angle.
 - b. the extinction angle, at $\alpha = 135^\circ$.
 - c. the rms value of the fundamental phase voltage.

3. A three-phase, 380-V, 50-Hz, AC-regulator feeding a heater of a 100Ω resistance, at a triggering angle of 75° .
 - a. write the expression of the instantaneous output phase voltage.
 - b. the rms value of the output phase voltage.
 - c. draw the waveform of the output phase voltage.

Mid-Term 2015/2016 (PE2)

Q1)

$$\because \gamma = 2\pi/3; \rightarrow \alpha = \pi - 2\pi/3 = \pi/3 = 60^\circ$$

$$i) V_{orms} = V_s \sqrt{\frac{1}{2\pi} (2\pi - \alpha + \frac{\sin(2\alpha)}{2})} = 120 * \sqrt{\frac{1}{2\pi} (2\pi - \pi/3 + \frac{\sin(120)}{2})}$$

$$\therefore V_{orms} = 104.9V$$

$$ii) Pf = V_{orms}/V_s = 104.9/120 = 0.87$$

Q2)

i) Range of triggering angle= $90 < \alpha < 180$

ii) As $i(\beta) = 0 \rightarrow \sin(\beta - \Phi) - \sin(\alpha - \Phi) * e^{(\alpha - \beta)/\tan(\Phi)} = 0$

For highly inductive load $\Phi = 90$ so

$$\sin(\beta - 90) = \sin(\alpha - 90) \rightarrow \cos(\beta) = \cos(\alpha)$$

$\beta = \alpha$ neglected solution

or $\beta = 2\pi - \alpha$ where $\cos(\alpha) = \cos(2\pi - \alpha) = \cos(4\pi - \alpha)$ and so on

$$\text{at } \alpha = 135 \rightarrow \beta = 360 - 135 = 225^\circ$$

iii)


$$a_1 = \frac{220\sqrt{2}}{2\pi} (\cos(2 * 135) - \cos(2 * 225)) = 0V$$

$$b_1 = \frac{220\sqrt{2}}{2\pi} * (2 * (225 - 135) * \frac{\pi}{180} + \sin(2 * 135) - \sin(2 * 225)) = 56.5V$$

$$\therefore V_1 = \sqrt{a_1^2 + b_1^2} = 56.5V \rightarrow V_1 = \frac{56.5}{\sqrt{2}} \approx 40V$$

Q3)

c)

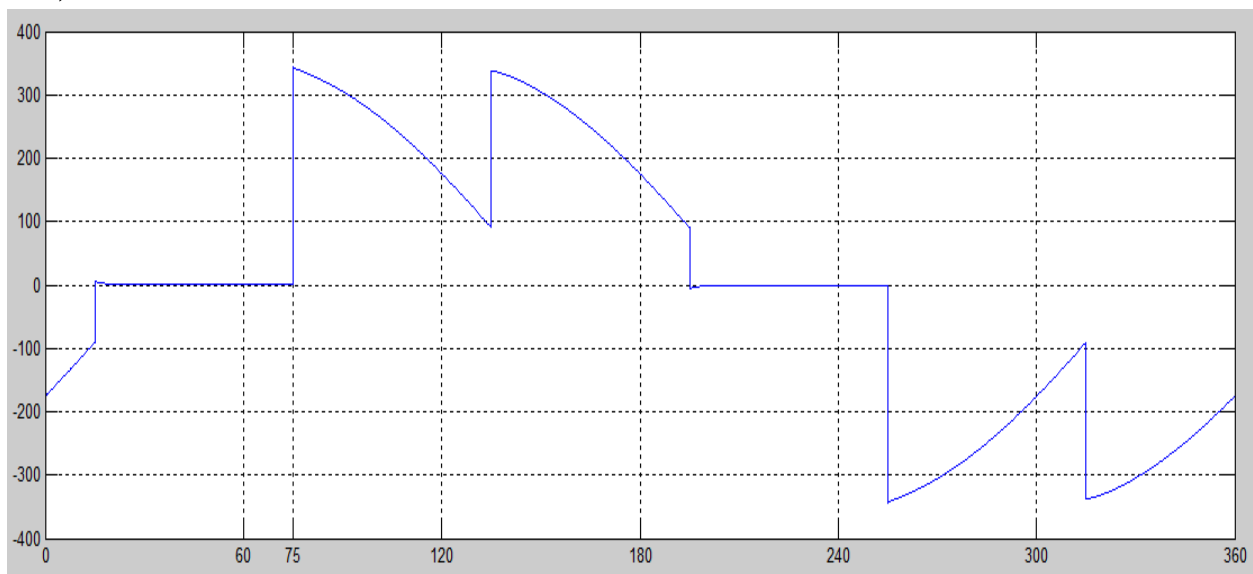

a) Instantaneous output voltage for phase a

$$v_a(\omega t) = \begin{cases} v_{ac} / 2 & 0^\circ < \omega t < 15^\circ \\ 0 & 15^\circ \leq \omega t < 75^\circ \\ v_{ab} / 2 & 75^\circ \leq \omega t < 135^\circ \\ v_{ac} / 2 & 135^\circ \leq \omega t < 195^\circ \end{cases}$$

b) V_o substitute in equation 2 by $\alpha=75$

$V_o =$

$$\begin{aligned} & 380/\sqrt{3} * \sqrt{1/(2 * \pi) * (\pi + 3 * \sqrt{3})/2 * \sin(30 + 150))} \\ & = 155V \end{aligned}$$