

CHAPTER 2


Laplace Transform, Transfer Function and Electrical Systems Modeling

By

Dr. Ayman Yousef

Modified By


Dr. Emad Sami

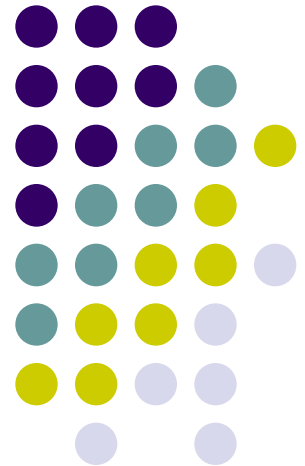




Transfer Function

Transfer Function (TF)

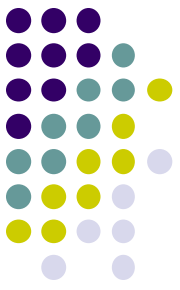


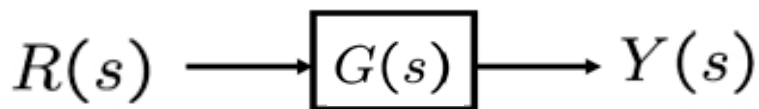- * Is a mathematical model that defines the relationship between the output and the input of a linear system. It is usually expressed as the ratio of the Laplace transform of the output function divided by the Laplace transform of the input function.
- * The order of the numerator must not exceed that of the denominator.



$$G(s) = \frac{Y(s)}{R(s)}$$

Transfer function

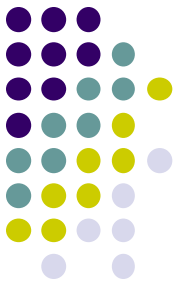


- A **transfer function** is defined by $G(s)$

$$G(s) = \frac{Y(s)}{R(s)}$$


Laplace transform of system output (pointing to $Y(s)$)

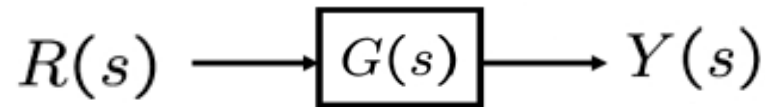Laplace transform of system input (pointing to $R(s)$)




$$Y(s) = G(s)R(s)$$

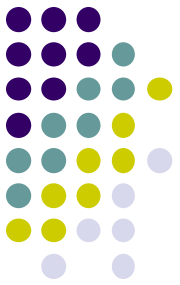- A system is assumed to be at rest. (Zero initial condition)




Electrical Systems Modeling

Models of electrical elements

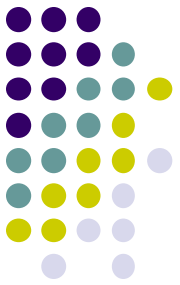

Resistance

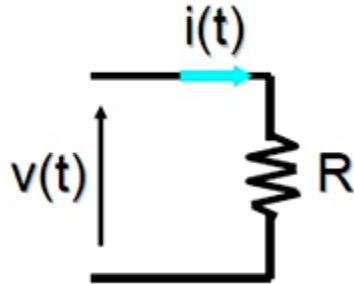


$$v(t) = Ri(t)$$

↓ Laplace transform

$$\frac{V(s)}{I(s)} = R$$

Inductance

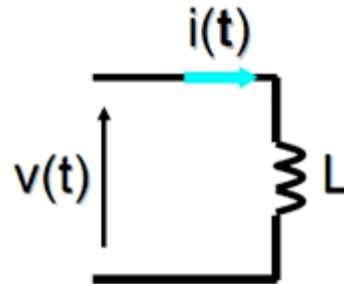


$$v(t) = L \frac{di(t)}{dt}$$

↓ ($i(0) = 0$)

$$\frac{V(s)}{I(s)} = sL$$

Capacitance

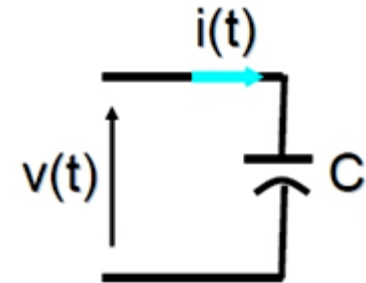


$$i(t) = C \frac{dv(t)}{dt}$$


↓ ($v(0) = 0$)

$$\frac{V(s)}{I(s)} = \frac{1}{sC}$$

Impedance Modeling

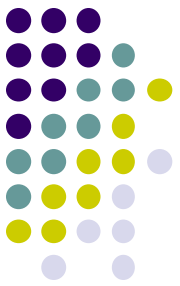

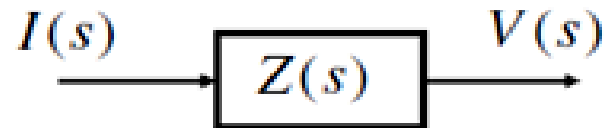In s - domain, $V(s) = Z(s) I(s)$ ($Z(s)$ - effective resistance)





Element	t – domain	s – domain	Impedance
Resistance	$v(t) = Ri(t)$	$V(s) = RI(s)$	R
Inductor	$v(t) = L \frac{di(t)}{dt}$	$V(s) = sL I(s)$	sL
Capacitor	$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$	$V(s) = \frac{1}{sC} I(s)$	$\frac{1}{sC}$

Impedance in series : $Z_{eff}(s) = Z_1(s) + Z_2(s) + \dots$

Impedance in *paralell* : $Z_{eff}(s) = \frac{1}{\frac{1}{Z_1(s)} + \frac{1}{Z_2(s)} + \dots}$

Modeling example

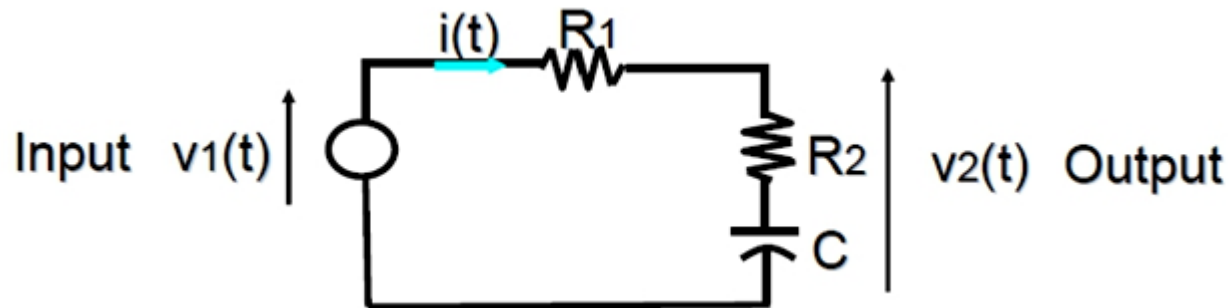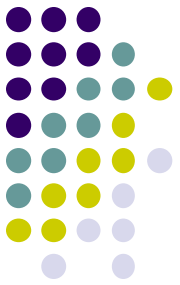



- **Kirchhoff voltage law** (with zero initial conditions)

$$\begin{aligned}v_1(t) &= (R_1 + R_2)i(t) + \frac{1}{C} \int_0^t i(\tau) d\tau \\v_2(t) &= R_2 i(t) + \frac{1}{C} \int_0^t i(\tau) d\tau\end{aligned}$$

- **By Laplace transform,**

$$\begin{aligned}V_1(s) &= (R_1 + R_2)I(s) + \frac{1}{sC}I(s) \\V_2(s) &= R_2 I(s) + \frac{1}{sC}I(s)\end{aligned}$$

Modeling example (cont'd)

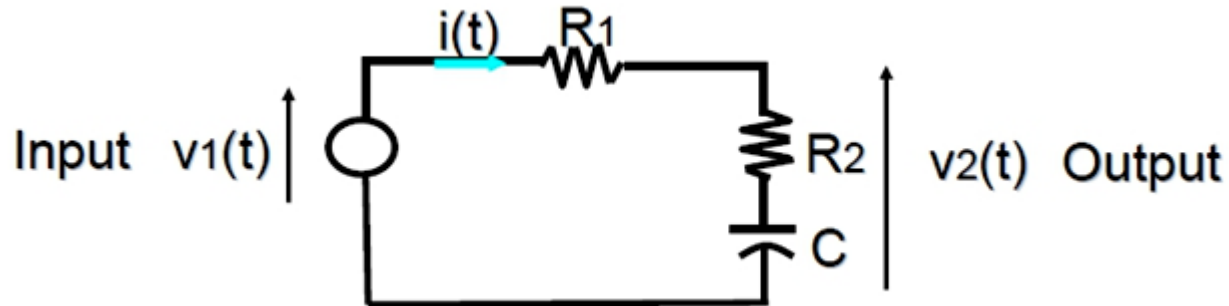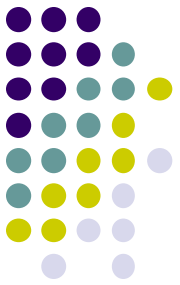


Transfer function

$$\begin{aligned} G(s) &= \frac{V_2(s)}{V_1(s)} = \frac{R_2 + \frac{1}{sC}}{(R_1 + R_2) + \frac{1}{sC}} \\ &= \frac{R_2Cs + 1}{(R_1 + R_2)Cs + 1} \\ &\quad \text{(first-order system)} \end{aligned}$$

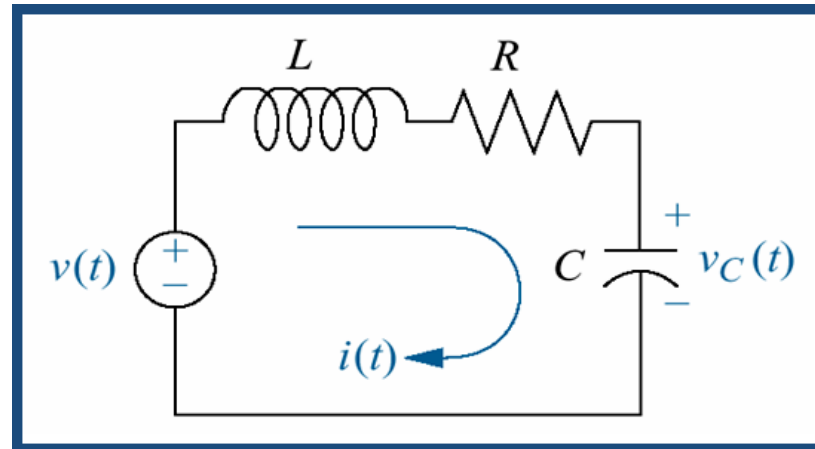Example 2


Find the transfer function relating the $v_c(t)$ to the input voltage $v(t)$.



Summing the voltages around the loop, assuming zero initial conditions, yields the integro-differential equation for this network as


$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

Example 2 (Cont'd)

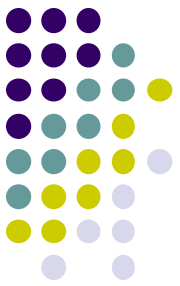

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

$$i(t) = C \frac{dv_C}{dt}$$

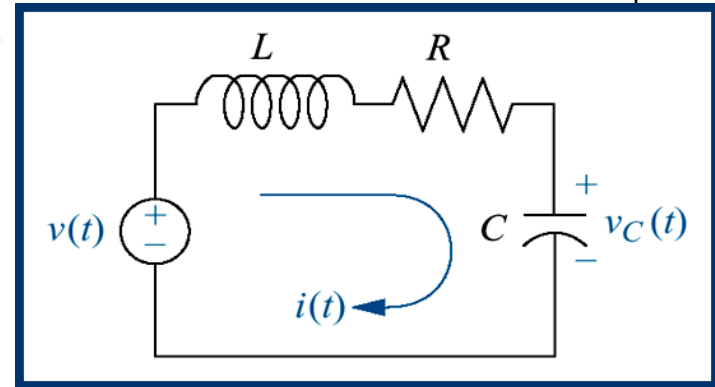

Taking Laplace $I(s) = C s v_C(s)$

substitute in above eq.




$$(LCs^2 + RCs + 1)V_C(s) = V(s) \quad \longrightarrow \quad \frac{V_C(s)}{V(s)} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Example 3

Repeat Example 2 using the transformed circuit.

Solution

using voltage division

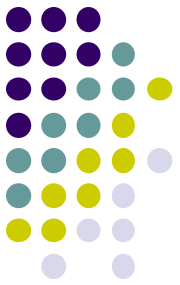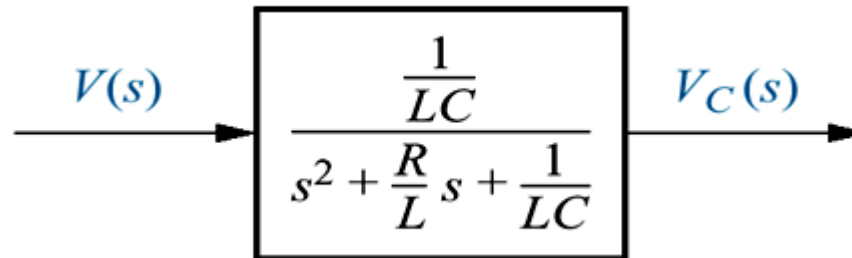
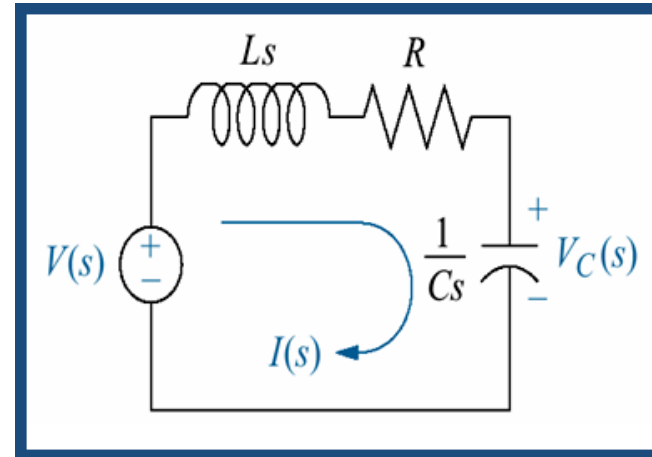


Example 4

Find the T.F $I_2(s)/V(s)$


Solution

Using mesh current

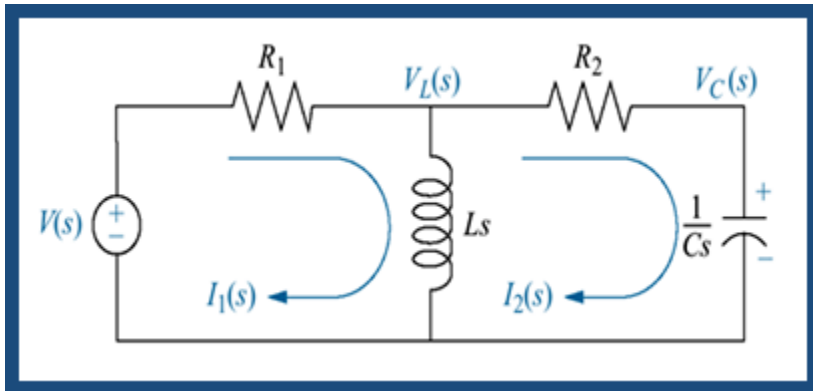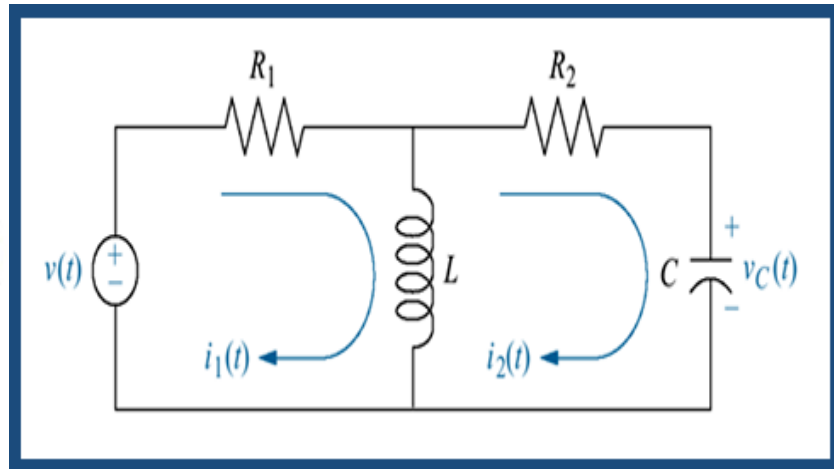

$$(R_1 + LS)I_1 - LSI_2 = V(s)$$

$$-LSI_1 + (R_2 + LS + 1/CS)I_2 = 0$$

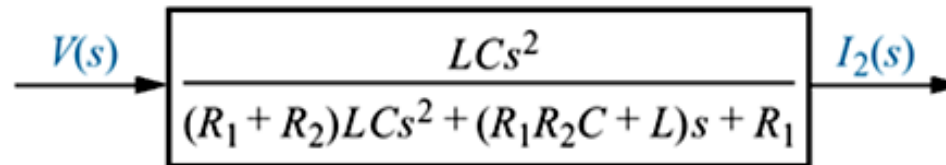


Example 5

Obtain the transfer function $V_o(s)/V_i(s)$



$$V_i(s) = (10 + 2 + (1/(\frac{s}{8}))) * I(s)$$

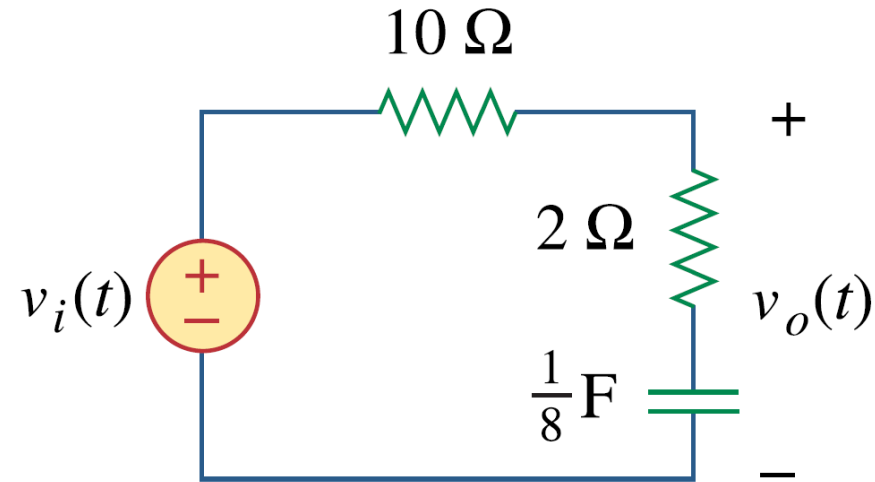
$$V_o(s) = (2 + (1/(\frac{s}{8}))) * I(s)$$



$$\frac{V_o(s)}{V_i(s)} = \frac{(2 + (1/(\frac{s}{8})))}{(10 + 2 + (1/(\frac{s}{8})))} = \frac{s + 4}{6s + 4}$$

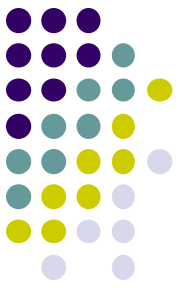
Example 5: continued

Obtain the transfer function $V_o(s)/V_i(s)$



Using:


Voltage Divider Rule

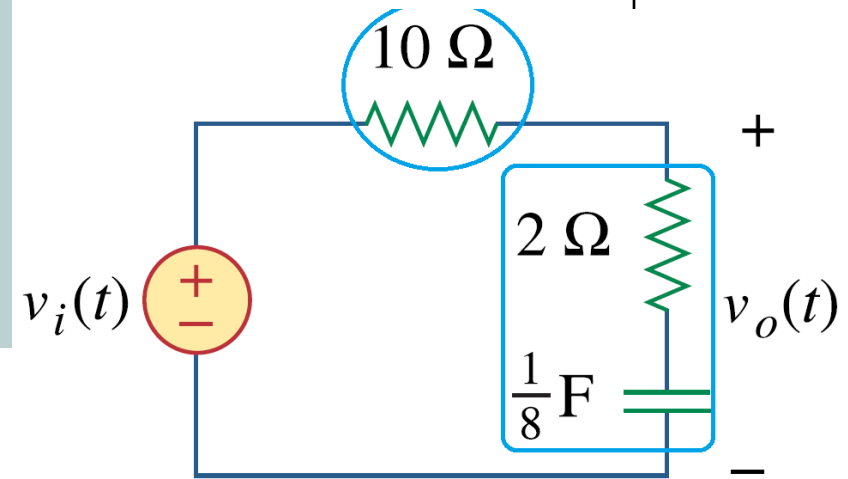

$$\frac{V_o(s)}{V_i(s)} = \frac{(2 + (1/(\frac{s}{8})))}{(10 + 2 + (1/(\frac{s}{8})))} = \frac{s + 4}{6s + 4}$$

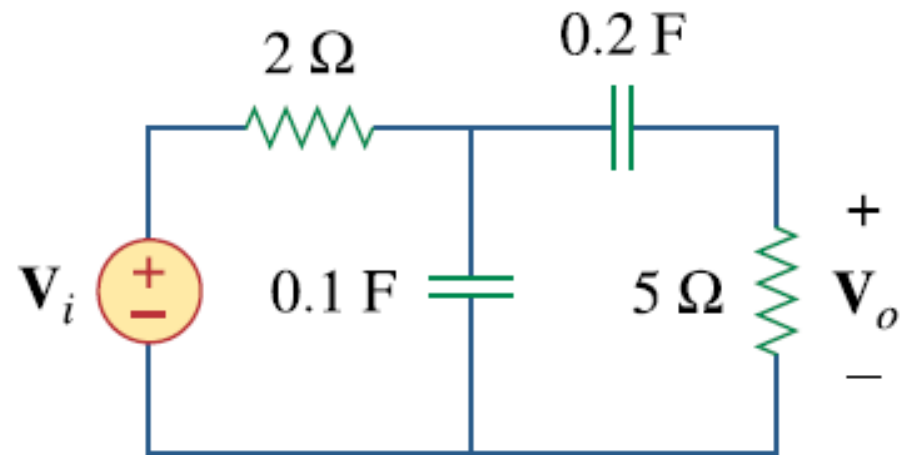Example 6


Obtain the transfer function $V_o(s)/V_i(s)$




Solution

$$0.2F \longrightarrow \frac{1}{Cs} = \frac{1}{(0.2)s} = \frac{5}{s}$$

$$0.1F \longrightarrow \frac{1}{(0.1)s} = \frac{10}{s}$$

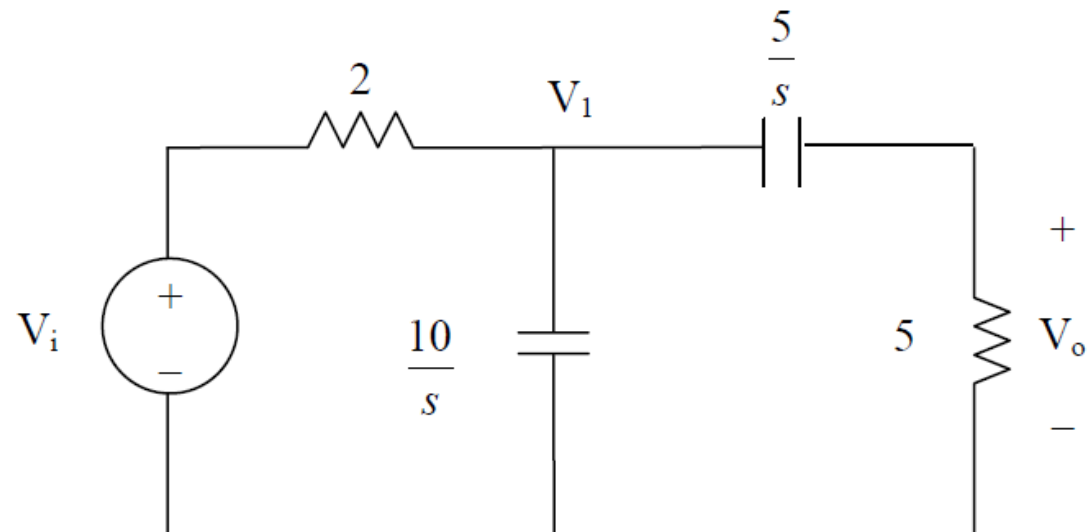

Example 6: (Continued)

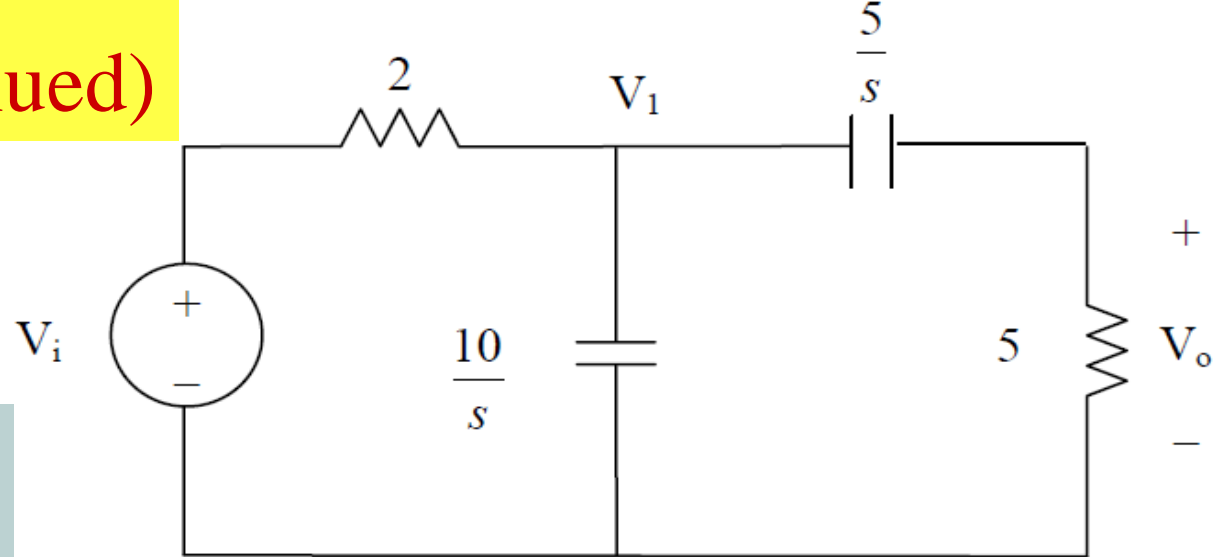

Using:

Voltage Divider Rule

$$Z = \frac{10}{s} \parallel \left(5 + \frac{5}{s}\right) = \frac{\frac{10}{s} \left(5 + \frac{5}{s}\right)}{5 + \frac{15}{s}} = \frac{\frac{10}{s} 5 \left(\frac{1+s}{s}\right)}{\frac{5}{s} (3+s)} = \frac{10(s+1)}{s(s+3)}$$



$$\frac{V_1}{V_i} = \frac{Z}{Z+2} \longrightarrow V_i = \frac{Z+2}{Z} V_1$$

$$\frac{V_o}{V_1} = \frac{5}{5 + 5/s} \longrightarrow V_o = \frac{5}{5 + 5/s} V_1$$


$$\frac{V_o}{V_i} = \frac{5s}{s^2 + 8s + 5}$$

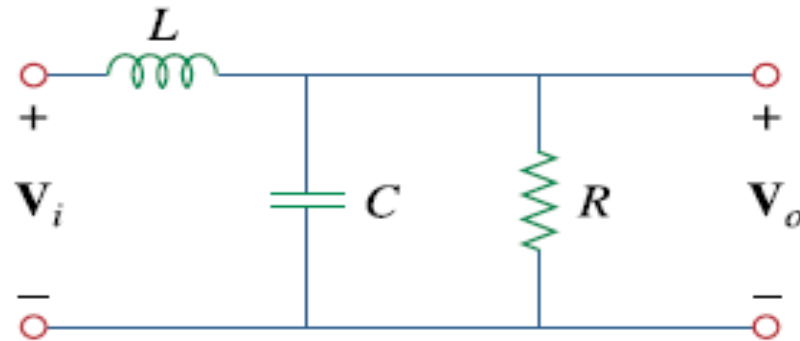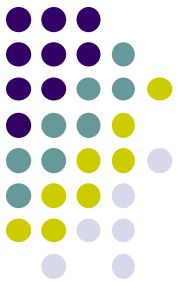Example 7

Obtain the transfer function $V_o(s)/V_i(s)$



(a)

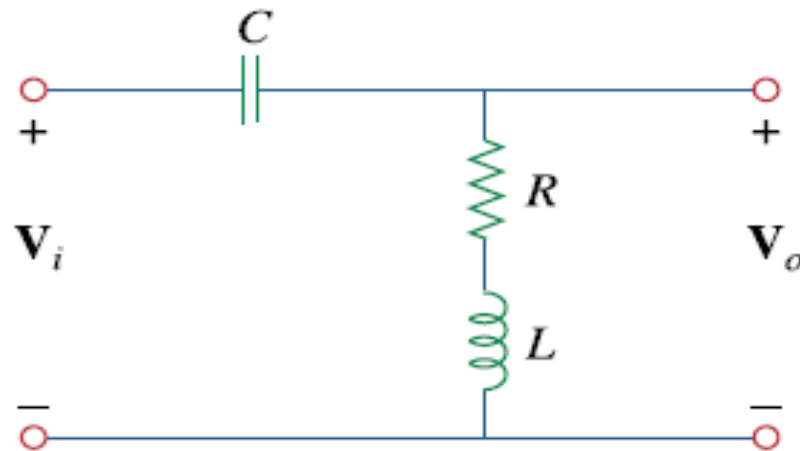


(b)

Example 7


Obtain the transfer function $V_o(s)/V_i(s)$

Solution
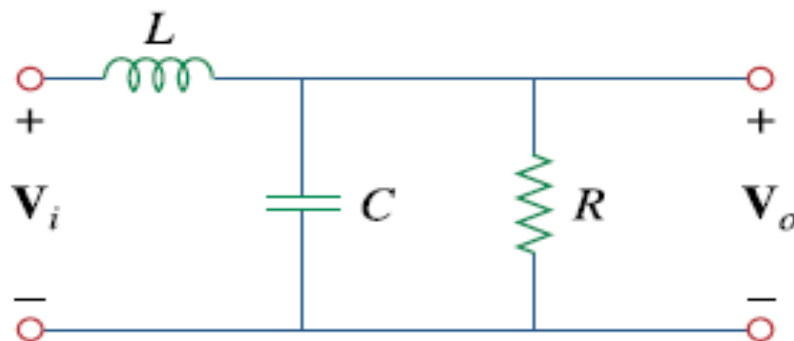
$$\frac{V_o(s)}{V_i(s)} = \frac{R}{RLC S^2 + LS + R}$$




$$\frac{V_o(s)}{V_i(s)} = \frac{LCS^2 + RCS}{LCS^2 + RCS + 1}$$

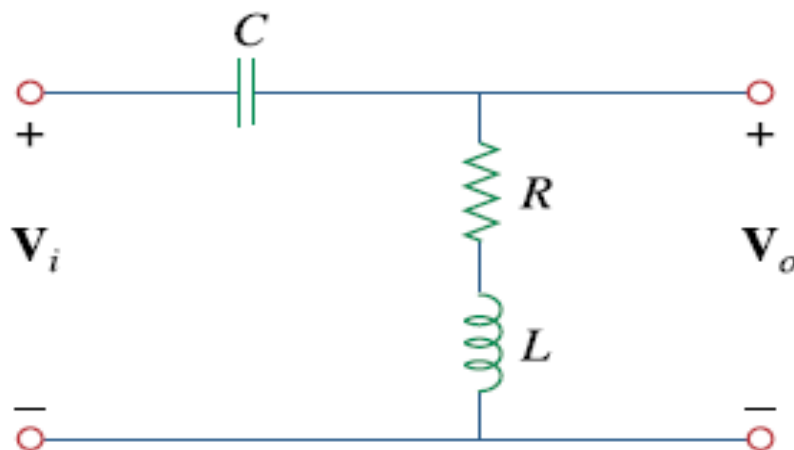


Example 8




For the following circuits e_i and e_o are in time domain, Determine the transfer function $E_o(s)/E_i(s)$ of each circuit and draw its block diagram.

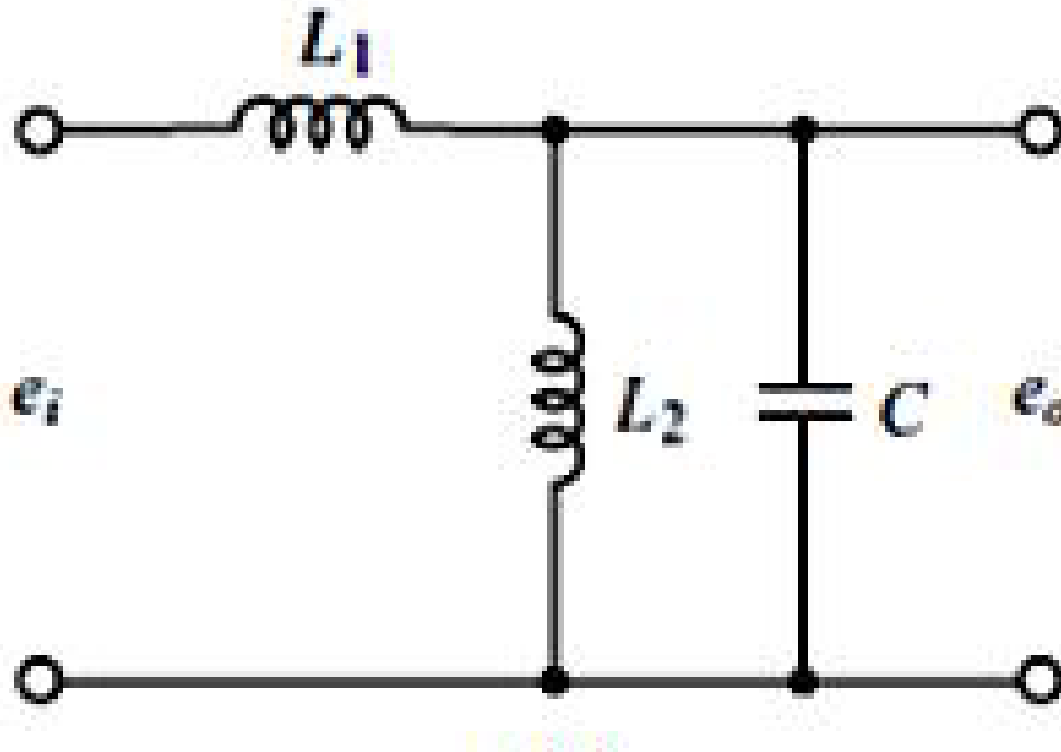

Example 8: (continued)

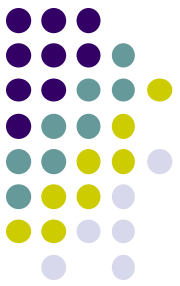

Solution

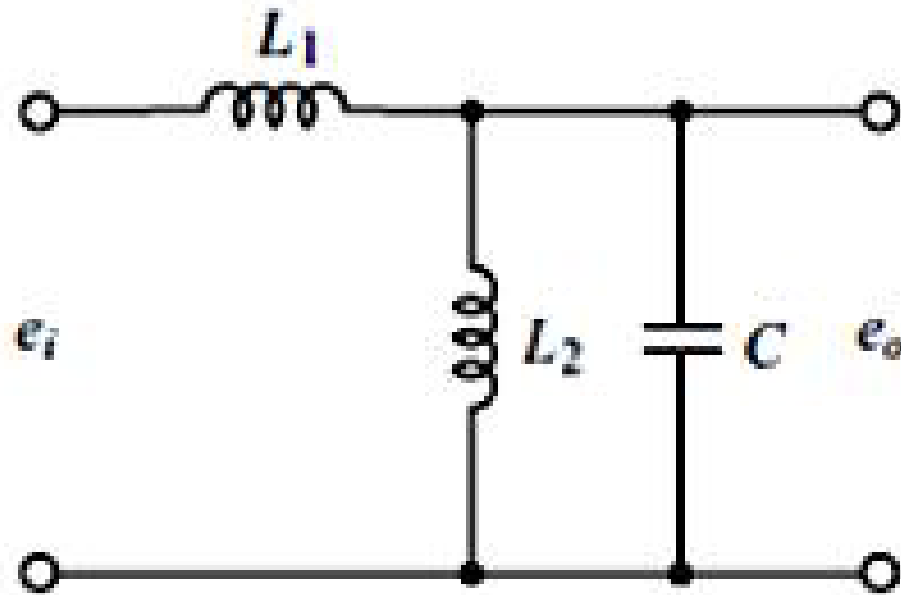

$$\frac{E_o(s)}{E_i(s)} = \frac{L_2 C S^2}{L_1 L_2 C S^3 + L_2 C S^2 + L_1 S}$$

Summary



- Introduction:
 - Laplace transform
 - Transfer function
 - Modeling of electrical systems

Next Lecture:

Block diagrams and Signal flow graphs