



For the control system shown in the figure; deduce the transfer function $E_o(s)/E_i(s)$ as function of the circuit elements.

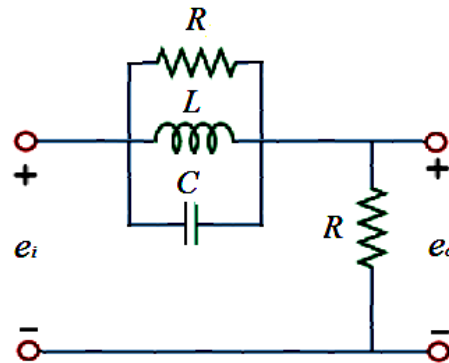


Fig. (1)

Answer

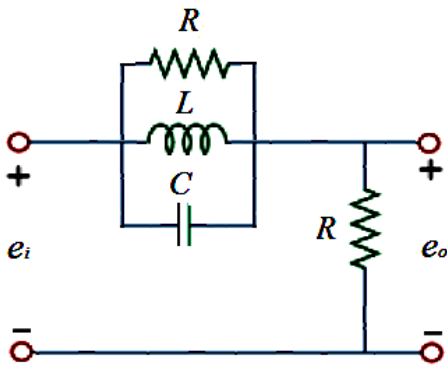


Fig. (1) circuit in t- domain

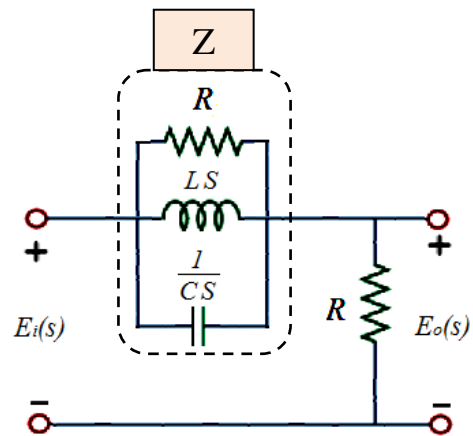


Fig. (2) circuit in S-domain

From S-domain circuit in Fig. (2):

- Total impedance Z of the components $R // (1/CS) // LS$ is as follows:

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{LS} + \frac{1}{1/CS}$$

$$Z = 1 / \left(\frac{1}{R} + \frac{1}{LS} + \frac{1}{1/CS} \right) = \frac{RLS}{RLCS^2 + LS + R}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{R}{Z + R} = \frac{R^2LCS^2 + RLS + R^2}{R^2LCS^2 + 2RLS + R^2}$$

Note that: you can get Z by:
 First Obtain $R//LS$ as Z_1
 Second Obtain $Z_1//(1/CS)$ as Z
 Then: $Z = \frac{RLS}{RLCS^2 + LS + R}$