

# Tests of 3-ph Induction "Asynchronous" Motor

dc Test      Short circuit      open circuit


Given 3-φ IM squirrel cage type

Nameplate:

Y-Conn.: 380V

Δ-Conn.: 220V, 2.1A

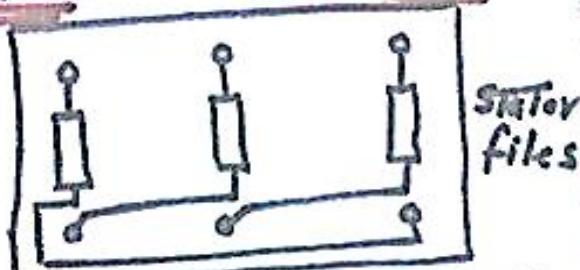يتمدد عند توصيل ملفات الـ STATOR  
 يجب تلبية الشروط المذكورة هنا





Motor Connection Box



Squirrel Cage Rotor

Objective: Determine Values of Motor Parameters:

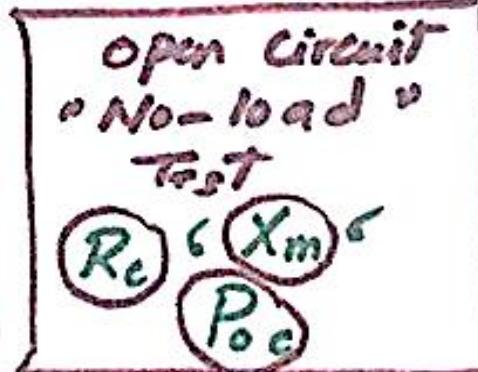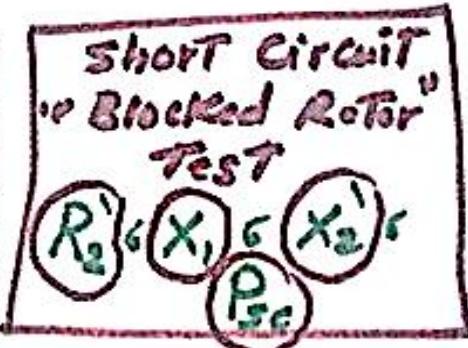- $R_1$ : Stator resistance/ph.
  - $X_1$ : " reactance/ph.
  - $R_2'$ : Rotor resistance/ph.  
referred to STATOR side
  - $X_2'$ : " reactance /ph.  
referred to STATOR side
  - $P_{sc}$ : short circuit losses "motor Co. losses".
  - $P_{oc}$ : open circuit losses "hysteresis & eddy current losses"
- Re: magnetization resistance  
"due to hysteresis & eddy cur."
- Xm: magnetization reactance





## DC Test

Objective:  $R_1$

Components:

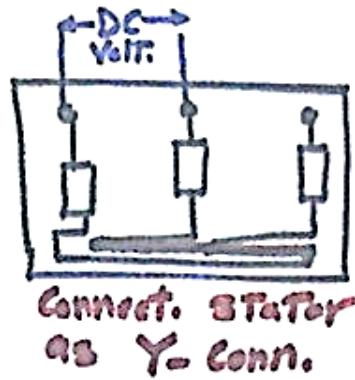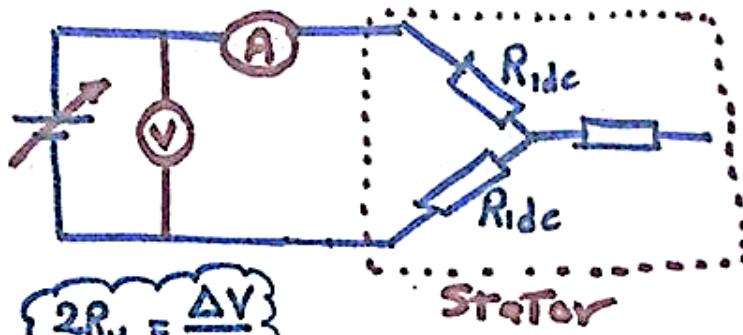- Ammeter
- Voltmeter
- Variable DC supply
- Connection cables.



Steps:

- ① Connect stator terminals as Y-connection.
- ② Make sure that you adjust the supply at 0V.
- ③ Connect the circuit to the supply as shown above.
- ④ Complete the following Table by varying supply voltage.

The final value "V<sub>\*</sub>" you apply from supply must be less than 10% of the rated voltage at Y-connection:

V <sub>dc</sub> applied Voltage	0V	5V	10V	.....	V <sub>*</sub>
I <sub>dc</sub> applied current	...	A	A	....	A

$$V_* \leq 10\% * 380 \rightarrow 32V$$

- ⑤ draw the relation betw V<sub>dc</sub> & I<sub>dc</sub> is straight line.


$$\therefore 2R_{idc} = \frac{\Delta V}{\Delta I} = \dots \Omega$$

but  $R_{iac} = 1.2 R_{idc} = \dots \Omega$

"Value of  $R_1$  is  $R_{iac}$ ".

$(R_1 = R_{iac}) > (R_{idc})$  due to Skin Effect.

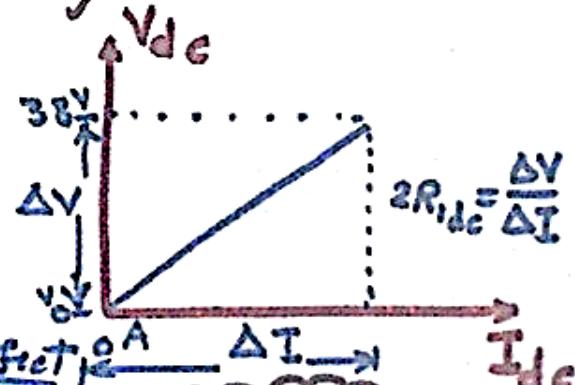مسافة القطع التي تغدو متر التيار في الاتجاه المعاكس (dc) اقل من المسافة التي تغدو متر التيار في الاتجاه المترافق (ac).





$$R = \frac{S \cdot L}{A}$$

## Short-Circuit OR Blocked Rotor Test

Objective:  $R_2 < X_1 < X_2 < P_{Sc}$

Components: • Ammeter & Voltmeter & Wattmeter  
• Variable 3- $\phi$  ac supply.

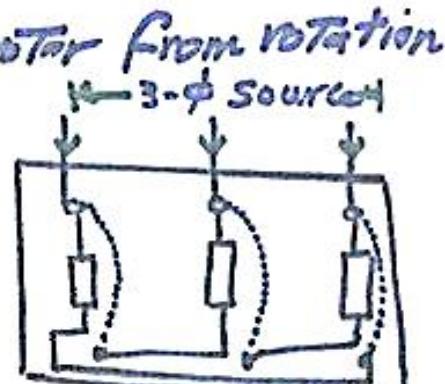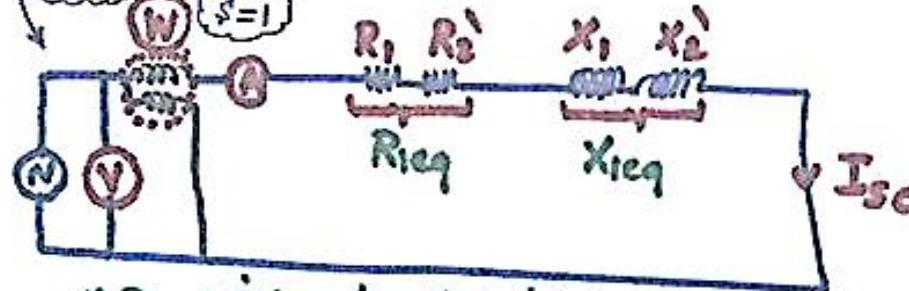Motor eq't circuit  
per phase referred  
to stator side at  
 $S=1$



" $R_e \parallel jX_m$  is very high so it is open"       $\Delta$ -Conn. STATOR

Steps:

- ① Connect The Stator Terminals as  $\Delta$ , Block The Rotor Using Iron Rod
- ② Make sure That You supply voltage is 0V.
- ③ Connect The Circuit of The motor as above
- ④ Increase Supply Voltage until The Short circuit current value is passes Through The motor.  $I_{Sc} = \frac{I_r}{\sqrt{3}} = \frac{2.1A}{\sqrt{3}} = 1.2A$
- ⑤ Complete The following Table:

$$\therefore P_{Sc} = 3 V_{Sc} I_{Sc} \cos \phi_{Sc}$$

$\therefore \cos \phi_{Sc} = \dots$

$$P_{Sc} = 3 I_{Sc}^2 \cdot R_{Sc} \quad \therefore R_{Sc} = \dots \Omega = R_{req}$$

$$\therefore R_{req} = R_1 + R_2$$

De Test

$$Z_{req} = \frac{V_{Sc}}{I_{Sc}} = \dots \Omega \longrightarrow \therefore R_2' = \dots \Omega \quad \therefore P_{Sc} = \dots \text{Watt}$$

$$X_{req} = \sqrt{Z_{req}^2 - R_{req}^2} = \dots \Omega$$

$$X_{req} \approx 2X_1 \approx 2X_2 \quad \text{"i.e.: } X_1 = X_2 \text{"}$$

$$X_1 = X_2' = \frac{X_{req}}{2} = \dots \Omega$$

Note:  $S = \frac{N_s - N_r}{N_s} = \frac{N_s}{N_s} = 1$


# open-circuit = No-load Test

objective:  $R_c < X_m < P_{oc}$


Components : • Ammeter & Voltmeter & Wattmeter  
• Variable 3- $\phi$  ac supply.

eq't circuit per phase referred to stator side  
at  $S=0$

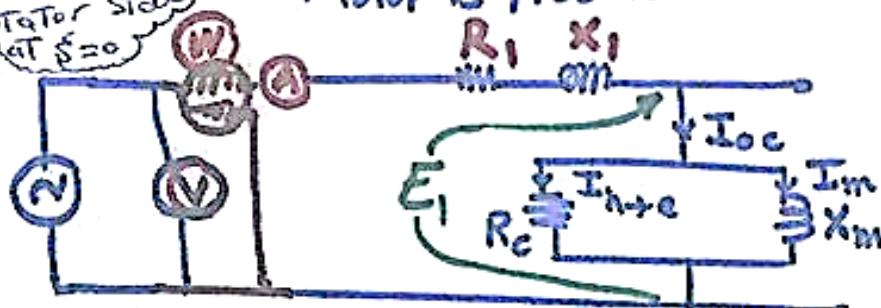- Connection Cables
- Motor is free to rotate & has no-load.


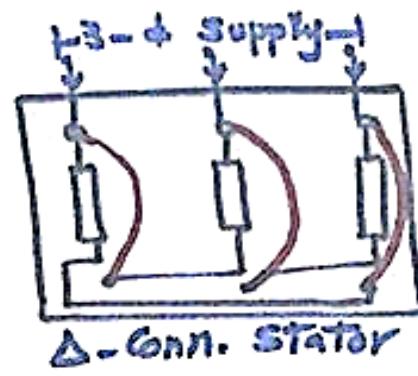
$$S = \frac{N_s - N}{N_s} = \frac{0}{N_s} \Rightarrow \frac{R_2}{S} \approx 0 \text{ "o.c."}$$



Steps :

- ① Connect stator terminals as  $\Delta$ , rotor is free to rotate and has no-load.
- ② Make sure that your supply voltage is 0V.
- ③ Connect the circuit as above.
- ④ Increase supply voltage until the applied voltage from supply is 220V.
- ⑤ Complete the following table.

Ammeter reading (A)	Voltmeter reading (V)	Wattmeter reading (Watt)
$I_{oc} = \dots A$	$V_{oc} = 220V$	$P_{oc} = \dots \text{Watt}$

$$P_{oc} = 3 V_{oc} I_{oc} \cos \phi_{oc}$$

$$\therefore \cos \phi_{oc} = \dots \quad \sin \phi_{oc} = \dots \quad \phi_{oc} = \dots$$

$$I_{cc} = |I_{oc}| \angle -\phi_{oc} = \dots \angle \dots A$$

$$P_{oc} = \dots \text{Watt}$$

$$E_1 = \overline{V_{oc}} - \overline{I_{oc}} (R_1 + jX_1) \rightarrow R_1 < X_1 \text{ from short circuit test}$$

$$= 220 \angle 0^\circ - |I_{oc}| \angle -\phi_{oc} (R_1 + jX_1)$$

$$= |E_1| \angle \dots^\circ \text{ Volts}$$

$$R_c = \frac{E_1}{I_{h+e}} \quad X_m = \frac{E_1}{I_m}$$

$$\therefore I_{h+e} = I_{oc} \cos \phi_{oc} \dots A$$

$$\therefore I_m = I_{oc} \sin \phi_{oc} \dots A$$


**Example:** A dc test is performed on a 460V,  $\Delta$ -connected 100hp induction motor. If  $V_{DC}=24V$  and  $I_{DC}=80A$ , what is the ac stator resistance  $R_1$ .

## Answer

$$R_{tot} = \frac{2R_{DC} \times R_{DC}}{R_{DC} + R_{DC} + R_{DC}} = \frac{2R_{DC}}{3}$$

$$V_{DC} = \frac{2R_{DC} \times I_{DC}}{3} \rightarrow 24 = \frac{2R_{DC}}{3} \times 80 \rightarrow R_{DC} = 0.45$$
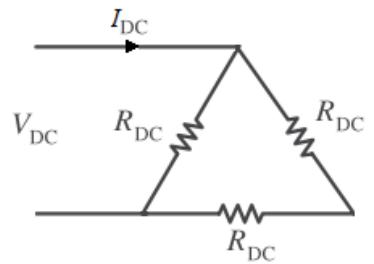
$$R_1 = 1.2 \times R_{DC} = 1.2 \times 0.45 = 0.54\Omega$$



**Example:** A 208V, 60Hz, six-pole, Y-connected 25hp design class B induction motor is tested in the laboratory, with the following results:

No load : 208 V, 22.0 A, 1200 W, 60 Hz

Locked rotor: 24.6 V, 64.5 A, 2200 W, 15 Hz

DC test : 13.5 V, 64 A

Find the equivalent circuit parameters:  $R_1, X_1, R_2^\backslash, X_2^\backslash, R_c, X_M$   
(assume:  $R_1 = 1.2 R_{DC}$ ,  $X_1 = X_2^\backslash$ )

## Answer

DC test: (Y - connected stator)

$$2R_{DC} = \frac{V_{DC}}{I_{DC}} = \frac{13.5}{64} \rightarrow R_{DC} = 0.1055\Omega \rightarrow R_1 = R_{DC} = 0.1055\Omega$$

Short - circuit :

$$\because P_{sc} = 3I_{sc}^2 R_{1eq}$$

$$2200 = 3 \times 64.5^2 \times R_{1eq}$$

$$R_{1eq} = 0.1763 = R_1 + R_2^\backslash \rightarrow 0.1763 = 0.1055 + R_2^\backslash \rightarrow R_2^\backslash = 0.071\Omega$$

$$\therefore Z_{1eq} = \frac{V_{sc}}{I_{sc}} = \frac{24.6/\sqrt{3}}{64.5} = 0.2202\Omega$$

$$X_{1eq} = \sqrt{Z_{1eq}^2 - R_{1eq}^2} = \sqrt{0.2202^2 - 0.1763^2} = 0.132\Omega \rightarrow X_1 = X_2^\backslash = \frac{0.132}{2} = 0.066\Omega$$

Open - circuit :

$$\because P_{oc} = 3V_{oc} I_{oc} \cos \phi_{oc}$$

$$1200 = 3 \times \frac{208}{\sqrt{3}} \times 22 \times \cos \phi_{oc} \rightarrow \cos \phi_{oc} = 0.154 \text{ and } \phi_{oc} = 81.3^\circ \text{ and } \cos \phi_{oc} = 0.988$$

$$\therefore \overline{I_{oc}} = I_{oc} \angle -\phi_{oc} = 22 \angle -81.3^\circ A$$

$$\therefore \underline{I_{h+e}} = I_{oc} \cos \phi_{oc} = 22 \times 0.154 = 3.3308A \text{ and } I_M = I_{oc} \sin \phi_{oc} = 22 \times 0.988 = 21.736A$$

$$\therefore \overline{E_1} = \overline{V_{oc}} - \overline{I_{oc}}(R_1 + jX_1)$$

$$= 220 \angle 0^\circ - 22 \angle -81.3^\circ (0.1055 + j0.066)$$

$$= 220 \angle 0^\circ - 2.728 \angle -49.3^\circ$$

$$= 118.22 \angle -2.1^\circ V$$

$$\therefore R_c = \frac{E_1}{I_{h+e}} = \frac{118.22}{3.3308} = 35.3\Omega$$

$$\therefore X_M = \frac{E_1}{I_M} = \frac{118.22}{21.736} = 5.44\Omega$$