

- (1) In a 3-phase, slip-ring induction motor, the open-circuit voltage across slip-rings is measured to be 110V with normal voltage applied to the stator. The rotor is Y-connected and has a resistance of 1Ω and reactance of 4Ω at standstill condition. Find the rotor current when the machine is:
- (a) at standstill with slip-rings joined to Y-connected starter with a resistance of 2Ω per phase and negligible reactance.
- (b) running normally with 5% slip. [answer: (a) 12.7A (b) 3.11A]
- (2) A 4-pole, 50-Hz induction motor has a full-load slip of 5%. Each rotor phase has a resistance of 0.3Ω and a standstill reactance of 1.2Ω . Find the ratio of Maximum Torque to full-load torque. Also, the speed at which maximum torque occurs. [ans.: 2.6 - 1125rpm]
- (3) A 3-phase, 4-pole, 50-Hz induction motor has a Y-connected rotor. The voltage of each rotor phase at standstill and on open-circuit is 121V. The rotor resistance per phase is 0.3Ω and the reactance at standstill is 0.8Ω . If the rotor current is 15A. Calculate:
- (a) the speed at which the motor is running [ans. (a) 1402 rpm]
- (b) the speed at which the torque is maximum. [ans. (b) 938 rpm]
- (4) A 50-Hz, 3- ϕ , 8-pole induction motor has a full-load slip of 4%. The rotor resistance is 0.001Ω per phase and standstill reactance is 0.005Ω per phase. Find:
- (a) Ratio of Maximum Torque to full-load torque. [ans.: 2.6 - 600rpm]
- (b) speed at which maximum torque occurs.

(5) A 3- ϕ , 50-Hz induction motor with its rotor Y-connected gives 500V (rms) at standstill between slip-rings on open-circuit. Calculate the current and power factor in each phase of the rotor windings at standstill when joined to Y-connected circuit, each limb of which has a resistance of $10\ \Omega$ and an inductance of 0.03H . The resistance per phase of the rotor windings is $0.2\ \Omega$ and inductance 0.03H . Calculate also the current and power factor in each rotor phase when the rings are short-circuited and the motor is running with slip of 4%.

[Answer: $13.5\text{A} - 0.48\text{Lag}$
 $27\text{A} - 0.47\text{Lag}$]


(6) Deduce the three phase induction motor under running condition.

[Answer: deduce: $T_r = \frac{3}{2\pi N_s} \frac{SE_2^2 R_2}{R_2^2 + (SX_2)^2}$]


(7) Deduce the 3-phase induction motor running torque. Also, what is the value of slip?

[Answer: $T_{r(\max)} = \frac{K_1 s}{2R_2} = \frac{K_1}{2X_2}$, $s = \frac{R_2}{X_2}$]

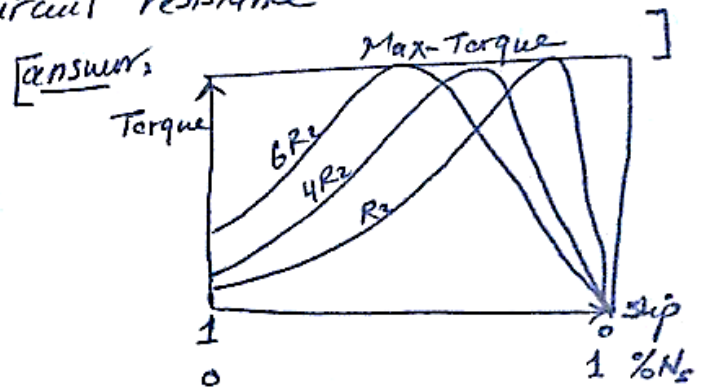(8) Draw the torque-slip characteristics for induction motor at different values of rotor circuit resistance.



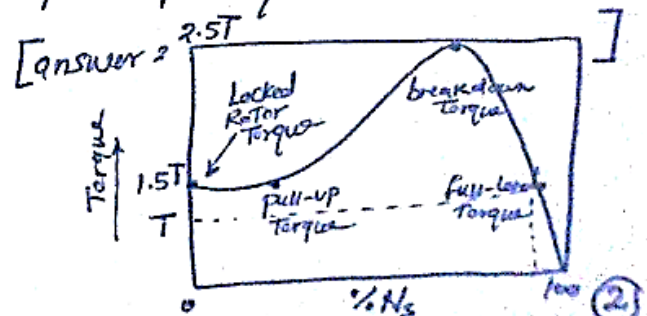(9) Draw the torque-speed characteristics for induction motor. Showing the points of: Full-load Torque - breakdown Torque - Locked Rotor Torque - Pull-up Torque on the curve.



(10) What is The induction motor speed regulation. Write The Equation. Why The induction motor is classed as a Constant-speed motor.

(11) What are The factors affects on speed of induction Motor ?

[answer f , P , s]
supply freq. \leftarrow f \downarrow P s
stator poles