

Sheet (5)

Electrical Machines IV - 2016/2017

1 A 3-phase, Y-Connected, 400V, 50 Hz, 4-pole induction motor has the following per phase parameters in Ohms referred to stator side: $R_1 = 0.15$, $X_1 = 0.45$, $R_2' = 0.12$, $X_2' = 0.45$, $X_m = 28.5$. Compute the stator current and power factor when the motor is operated at rated voltage and frequency with slip = 0.04.
[Answer: $71.058 \angle -21.47^\circ$, $\text{Pf} = 0.93$ lagging]

2 A 220V, 3- ϕ , 4-pole, 50 Hz, Y-Connected induction motor is rated 3.73 kW. The equivalent circuit parameters are: $R_1 = 0.45 \Omega$, $X_1 = 0.8 \Omega$, $R_2' = 0.4 \Omega$, $X_2' = 0.8 \Omega$, $X_m = 30 \Omega$. The stator core loss is 50 Watt and the rotational losses is 150 Watt. For a slip of 0.04, find:
(i) input current.
(ii) Power factor at input.
(iii) air-gap power "i.e.: rotor power".
(iv) mechanical power.
(v) electro-magnetic torque "i.e.: gross torque".
(vi) output power, and
(vii) Efficiency.
[Answer:
(i) $12.7 \angle -25.8^\circ$ A
(ii) 0.9 Lag
(iii) 4125 Watt
(iv) 3960 Watt
(v) 26.3 Nm
(vi) 3210 Watt
(vii) 87.8%]

3 A 115V, 60 Hz, 3-phase, Y-Connected, 6-pole induction motor has the following parameters of approximate equivalent circuit referred to the stator side:
 $R_1 + jX_1 = 0.07 + j0.3 \Omega$, $R_2' + jX_2' = 0.08 + j0.3 \Omega$
 $R_c = 45.45 \Omega$, $jX_m = j6.33 \Omega$: For a slip of 2%.
Find:
(a) Secondary current. (b) Primary current (c) Primary Pf.
(d) output power (e) gross torque (f) input power.
(g) Efficiency. [Answer: (a) $16.15 \angle -8.4^\circ$ A (d) $P_{\text{load}} = 3067$ Watt
(b) $21.66 \angle -36.4^\circ$ A (e) 24.9 Nm
(c) 0.805 Lag (f) 3470 Watt, (g) 88.3%]



4] A 3-phase, 400 V, Y-connected induction motor has the following parameters of approximate equivalent circuit referred to the stator side:

$$R_1 = 1\ \Omega, \quad X_1 = 2\ \Omega, \quad R_2' = 1.2\ \Omega, \quad X_2' = 1.5\ \Omega, \quad Z_{Mag} = 4 + j40\ \Omega$$

For a slip of 5%. Find:

- Rotor current, input current.
- Efficiency.
- input power factor.
- output power

Assume friction loss of 250 Watt

[Answer:

- $9.15 \angle -7.97^\circ\text{ A}$
 $11.9 \angle -36^\circ\text{ A}$
- 82%
- 0.81
- 5477 Watt]

5] A 3-phase, 400 V, 6-pole, 19 kW induction motor has the following parameters of its approximate equivalent circuit:

$$R_1 = 1.4\ \Omega \quad \text{and} \quad R_2' = 0.6\ \Omega$$

$$X_1 = 2\ \Omega \quad \text{and} \quad X_2' = 1\ \Omega$$

$$X_m = 50\ \Omega \quad \text{and} \quad f = 50\text{ Hz}$$

The rotational losses is 275 W. For a slip of 0.03: determine

- The line current, pf and power input.
- The shaft torque and mechanical output power.
- The efficiency.

[Answer = (a) $12.2 \angle -30^\circ$, 0.866 lag, 7320 W
(c) $T_{sh} = 62.9\text{ Nm}$, $P_{mech(tot)} = 6663\text{ W}$, $P_{mech(net)} = P_{out} = 6388\text{ W}$
(d) $\% \eta = 87.3\%$]

6] A 460 V, 25 hp, 60 Hz, 4-pole Y-connected induction motor has the following parameters in Ohms referred to the stator side for an exact equivalent circuit per phase:

$$R_1 = 0.641\ \Omega, \quad R_2' = 0.332\ \Omega, \quad X_1 = 1.106\ \Omega, \quad X_2' = 0.464\ \Omega, \quad X_m = 26.3\ \Omega$$

The total rotational losses are 1100 W. For a rotor slip of 2.2% at the rated voltage and rated frequency: Find:

- rotor speed
- stator current
- input power factor
- rotor current, rotor power, mechanical power, net output power.
- gross torque, load torque
- Efficiency

[Answer: (a) 1760 rpm (b) $18.9 \angle -33.6^\circ$ A (c) 0.833 Lag
 (d) $16.3 \angle -4.32^\circ$ A $\hookrightarrow P_{rotor} = 11956$ W $\hookrightarrow P_{mech} = 11693$ W $\hookrightarrow P_{net} = 10590$ W
 (e) $T_{gross} = \frac{P_{rotor}}{\omega_s} = 63.4$ Nm $\hookrightarrow T_{load} = T_{shaft} = \frac{P_{net}}{\omega} = 57.5$ N.m
 (f) $\% \eta = 84.4\%$]

- [7] A 208 V, Two-pole, 60 Hz Y-connected wound-rotor induction motor is rated at 15 hp. The Exact Equivalent circuit has the following parameters per phase referred to the stator side:
 $R_1 = 0.2 \Omega$ $\hookrightarrow R_2 = 0.12 \Omega$ $\hookrightarrow X_M = 15 \Omega$ $\hookrightarrow X_1 = 0.41 \Omega$ $\hookrightarrow X_2 = 0.41 \Omega$
 $P_{(fr+wd)} = 250$ W $\hookrightarrow P_{core(stator)} = 180$ W. For a slip of 0.05. find:
- (a) The Line Current
 - (b) The stator copper losses.
 - (c) The air-gap power
 - (d) mechanical power
 - (e) Gross Torque
 - (f) output power and Load Torque.
 - (g) Efficiency
 - (h) rotor speed in rpm & rad/sec.

[Answer: (a) $44.8 \angle -25.4^\circ$ A (b) 1205 W (c) 13195 W
 (d) $P_{mech} = 12535$ W (e) 35 Nm (f) 12290 W \hookrightarrow 34.3 N.m
 (g) $\% \eta = 84.3\%$ (h) 3420 rpm \hookrightarrow 358 rad/sec]