

1 A square-wave 1- ϕ bridge inverter has an RL Load with $R = 15\Omega$, $L = 10mH$. The inverter output frequency is 400 Hz.

Determine:

- (i) Value of dc source voltage required to establish a load current which has a fundamental frequency current component of 10 A (rms).
- (ii) THD per output voltage.

[Answer: $325V - 0.483$]

2 A single-phase H-bridge inverter has $R = 2.4\Omega$ (load) and the dc input voltage is $V_s = 48V$. Determine:

- (i) RMS output voltage at fundamental frequency.
- (ii) Inverter output power.
- (iii) Average and peak current of each Transistor.
- (iv) Peak Reverse blocking Voltage of " "
- (v) THD, DF of output voltage and current.

[Answer: (i) $43.2V$ - (ii) $P_o = 960W$ -
 (iii) $I_{peak} = 20A > I_{avg} = 10A$
 (iv) $V_{BR} = 48V$ - (v) $THD_v = 48.34\%$
 $THD_i = 48.34\%$, $DF_v = 90\%$,
 $DF_i = 90\%$.]

3 Single-phase H-bridge inverter has: RL Load, where:
 dc source voltage = $200V$, $R = 20\Omega$, $L = 50mH$, $f_{sw} = 80Hz$
 find: Iforms, P_o , THD_v , THD_i

[Answer: $7.216A - 1040W - 48.43\% - 18.15\%$.]

4] Full-bridge inverter (1-phase) has a RLC Load: $R = 10\Omega$, $L = 31.5\text{ mH}$ and $C = 112\mu\text{F}$. The inverter frequency is $f_0 = 60\text{ Hz}$ and The dc input voltage is 220 V . Find:

- (a) Express The instantaneous load Current in Fourier Series.
- (b) RMS load Current at fundamental Frequency.
- (c) THD of Load Current.
- (d) The power absorbed by The Load & The fundamental Power.
- (e) The rms current of dc Supply.
- (f) RMS & Peak Current of each Transistor.
- (g) Actual conduction time of each Transistor.
- (h) Actual conduction time of each diode.

Answer: (a) $i_o(t) = 18.1 \sin(377t + 49.74^\circ) + 3.17 \sin(3 \cdot 377t - 70.17^\circ)$
 $+ 3 \sin(5 \cdot 377t - 79.63^\circ) + 0.5 \sin(7 \cdot 377t - 82.85^\circ)$
 $+ 0.3 \sin(9 \cdot 377t - 84.52^\circ) + \dots$

(b) $I_{o,\text{rms}} = 12.8\text{ A}$

(c) $\text{THD}_i = 18.6\%$

(d) $P_o = 1695\text{ Watt}$ & $P_d = 1638\text{ Watt}$

(e) $I_s = \frac{P_o}{V_s} = 7.7\text{ A}$ (assuming op power = input power for inverter)

(f) $I_{peak} = 18.41\text{ A}$ & $I_{rms} = \frac{I_{peak}}{\sqrt{2}} = 9.205\text{ A}$

(g) $t_{sw} = 6027.3\mu\text{sec.}$

(h) $t_{diode} = 2302\mu\text{sec.}$]

5] What is meant by inverter, typical source of The inverter, typical output of The inverter?

6] What are inverter types according to no. of load phases?

7] What are inverter types according to its input?

8] What are inverter Applications?

9] What are Disadvantages of H-Bridge inverter?

10] What is The effect of harmonics of inverter?

11] How can you solve inverter harmonics?

[12] The square-wave Inverter of Fig.1 has $V_{dc} = 125V$, an output frequency of 60 Hz, and a resistive load of 12.5Ω .

* Sketch The currents in The Load, each switch, and The Source.

* Determine The average and rms values of each waveform

[ans.: O/P Voltage:
 $\bullet V_{rms} = 125V$
 $\bullet V_{dc} = 0$

O/P Current:
 $\bullet I_{rms} = 10A$
 $\bullet I_{dc} = 0$

Source Current
 $\bullet I_{srms} = 10A$
 $\bullet I_{sav} = 10A$

Switch Current
 $\bullet I_{sw(rms)} = 7.07A$
 $\bullet I_{sw(av)} = 5A$]

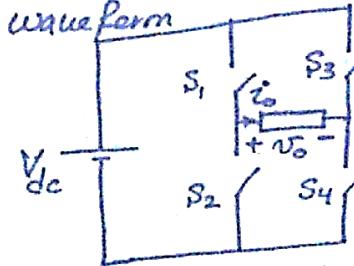


Fig.1: Full-bridge Inverter

[13] A square-wave inverter has an RL Load with $R = 15\Omega$ and $L = 10mH$.

The inverter output frequency is 400 Hz. Determine:

(a) The dc Source Voltage required to establish a fundamental Component of load current of 8A (rms).

(b) THD of load voltage and load current.

[ans.: (a) 260V
(b) $THD_v = 48.34\%$
 $THD_i = 13.7\%$.]

[14] The full-bridge inverter has a switching sequence that produces a square-wave voltage across a series RL load. The switching frequency is 60 Hz, $V_{dc} = 100V$, $R = 10\Omega$ and $L = 25mH$.

Determine: (a) an expression of o/p current using Fourier Series-
(b) an expression of o/p voltage " " "

(c) RMS value of o/p current, RMS value of o/p voltage.
(d) THD of o/p current, THD of o/p voltage.

(e) THD of o/p current, THD of o/p voltage.

(f) DF of o/p current, DF of o/p voltage.

(g) Power absorbed by the load.

(h) average current of dc supply.

(i) peak and average current of each Transistor

(j) actual conduction time of each Transistor
" " " diode.

(k) " " "

[ans.: (d) 6.64A, 100V
(e) 16.2%, 48.39%
(f) 98.93%, 70.7%]

(g) 441 Watt

(h) 4.41A

(i) 9.39A, 4.695A

(j) 6.329 ms]

(k) 2.005 ms]