

## Task 1:

(1)

(A)

$$Z_{\text{internal}} = 10 + j10 \\ = r + jx$$

(a) if pure R used as a load

$$R = \sqrt{10^2 + 10^2} = 14.14 \Omega.$$

(b) For complex load

1. For R var & X var

$$\therefore R = r = 10 \Omega \quad \& \quad X = -x = -j10$$

2. For R var & X Fixed

$$\text{let } X = -j2$$

$$\therefore R = \sqrt{10^2 + (10 + 2)^2} = 15.62 \Omega$$

$$\therefore R = 15.62 \Omega \quad \& \quad X = -j2$$

---

(B)


Let  $i_s(t) = 1 A_p \angle 0^\circ$

$v_s(t) = 10 V_p \angle 0^\circ$


$R_1 = 100 \Omega$

$R_2 = 10 \Omega$

$R_3 = 10 \Omega$

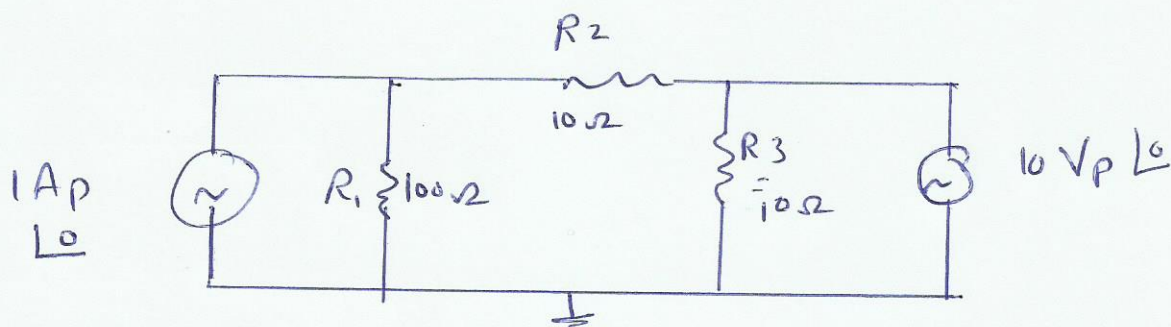


using Simulation

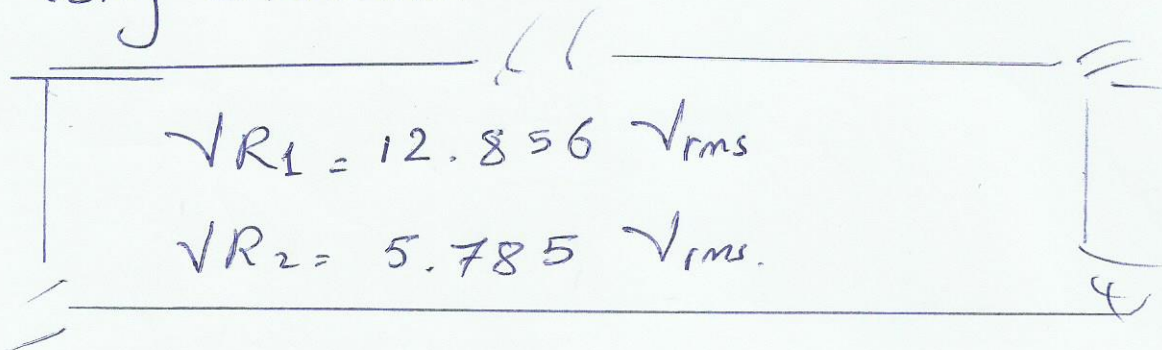

using Superposition.

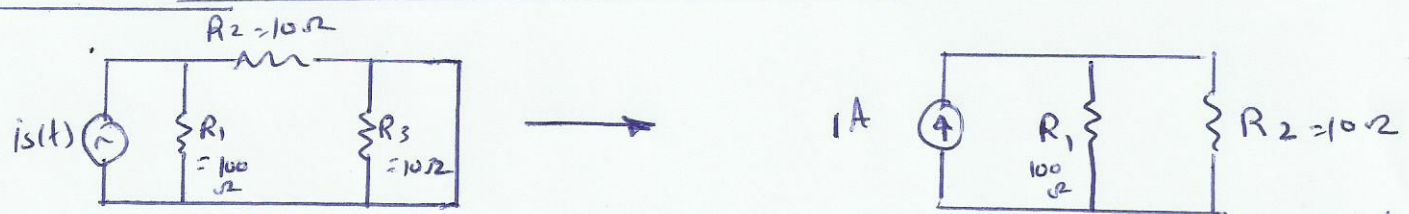(1) short of  $v_s(t)$  & use only  $i_s(t)$




$\therefore i_1 = 1 \times \frac{10}{110} = 91 \text{ mA peak} = 64.34 \text{ mA rms}$   
 $i_2 = 909 \text{ mA peak} = 642.76 \text{ mA rms}$

Simulation
64.28 mA
642.8 mA
rms

open circuit is (1)

3

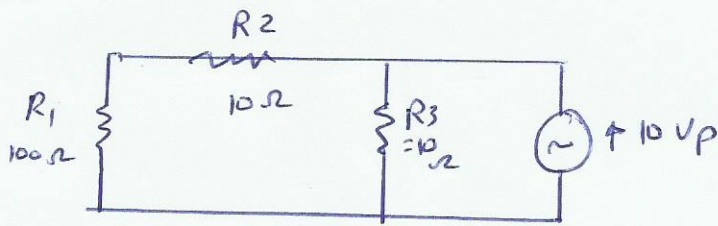

Simulation

$$V_{R1} = 6.428 \text{ Vrms}$$

$$V_{R2} = 0.642 \text{ Vrms}$$

✓

$$\therefore V_{R1} = 10 \times \frac{100}{110} = 9.09 \text{ Vpeak} = 6.428 \text{ Vrms}$$

$$V_{R2} = 10 \times \frac{10}{110} = 0.909 \text{ Vp} = 0.6428 \text{ Vrms}$$

Total Voltage.

$$V_{R1} = 6.428 \text{ V} + 642.8 \text{ mA}(100) = 12.856 \text{ Vrms}$$

$$V_{R2} = \frac{909 \text{ mA}}{\sqrt{2}} \times 10 = 0.642 \text{ mV rms}$$

$$= 5.786 \text{ Vrms}$$

which are the same like Simulation

Task 2

(a) Simulation File included.

(b) The Table "Results" as well as the graph also included in "Excel File".

From Fig,  $F_r \approx 2500 \text{ Hz}$

calculated  $F_r$

14

not Req in The Exam but just as a check

$$F_r = \frac{1}{2\pi} \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}} = 2640 \text{ Hz}$$

$$(c) R_d = \frac{L}{R_c} = \frac{12 \times 10^{-3}}{20 \times 300 \times 10^{-9}} = 2 \text{ K}\Omega$$

$$(d) Q_r = \frac{\omega_r L}{R} = \frac{12 \times 10^{-3} \times 2500}{20} = 1.5$$

$$(e) Q_r = \frac{F_r}{B_w}$$

$$\therefore B_w = \frac{F_r}{Q_r} = \frac{2500}{1.5} = 1666 \text{ Hz}$$


(f) not selective since

$$\underline{B_w > 20\% \cdot F_r}$$

### Task (3)

5

(A)

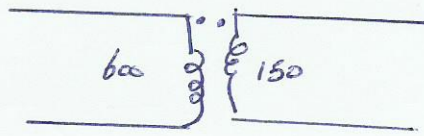

This transformer consists of a Primary winding of 600 turns  
" " " secondary " " 150 "

The  $V_{sec}$  will relate to  $V_{prim}$  by The Turns ratio as The relation

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

while The currents will reversaly proportional and given by

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}$$

The Total power of primary will equal to secondary  
For ideal Transformer (No Losses)

$$P_P = P_S$$

$$P_P = I_P V_P = P_S = I_S V_S$$



$$N_1 = 600 = N_P \quad \& \quad N_s = N_2 = 150$$

$$Z_P = 0.25 + j1 \quad \Omega$$

$$Z_S = 0.01 + j0.04 \quad \Omega$$

$$\text{Turns ratio} = a = \frac{N_P}{N_S} = \frac{600}{150} = 4$$

Z equivalent

(a)  $R'$  : Equivalent referred to primary

$$= a^2 R_{sec} = 4^2 \cdot 0.01 = 0.16 \quad \Omega$$

(b)  $X_L'$  : equivalent " " "

$$= X_{Lsec} + a^2 = 4^2 \cdot 0.04 = 0.64 \quad \Omega$$

(c)  $Z_L' = a^2 Z_{Lsec}$

$$= a^2 (0.01 + j0.04) = 0.16 + j0.64 \quad \Omega$$

(B)

mutual inductance

+ مبادی الحثیه

when two coils are placed close to each other a changing flux in one coil will cause an induced voltage in the second coil. The coils are said to have mutual inductance  $M$

For series inductors

7

$$L_{\text{total}} = L_1 + L_2 + 2M$$

---

$$V = iR + L \frac{di}{dt}$$

$$= iR + L \frac{di}{dt}$$

$$240 = 5(10+15) + L(10)$$

$$\begin{aligned} \therefore L = 11.5 \text{ H} &= L_x + L_y + 2M \\ &= 3 + 1.2 + 2M \end{aligned}$$

$$\therefore M = 3.65 \text{ H}$$

$$K = \frac{M}{\sqrt{L_x L_y}} = 1.923$$

---

(c) Same analysis of A

$$K = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.1}{\sqrt{0.2 \times 0.4}} = 0.353$$

$$I = \frac{F_s}{\pi} = 23.88 \quad \leftarrow \text{Simulation file appended}$$

$$\begin{aligned} I_1 &= 912.8 \text{ mA rms} \\ I_2 &= 183.137 \text{ mA rms} \end{aligned}$$

Task (4) (M1.2)

A) Three solution here

- # Simple solution
  - # using Mesh
  - # " Nodal
  - + Simulation
- only one solution Req  
(Sim Power)

$$R_3 = 1k\Omega$$


$$X_{C2} = -j \frac{1}{2\pi f C} = -j3980 \Omega$$

$$X_{L2} = j\omega L_2 = j2\pi \times 2 \times 10^3 \times 10 \times 10^{-3} = j125.6 \Omega$$

$$R_1 = 50 \Omega$$

$$Z_{11} \Rightarrow \frac{1}{Z_{11}} = \left[ \frac{1}{1k} + \frac{1}{j125.6} + \frac{1}{-j3980} \right]$$
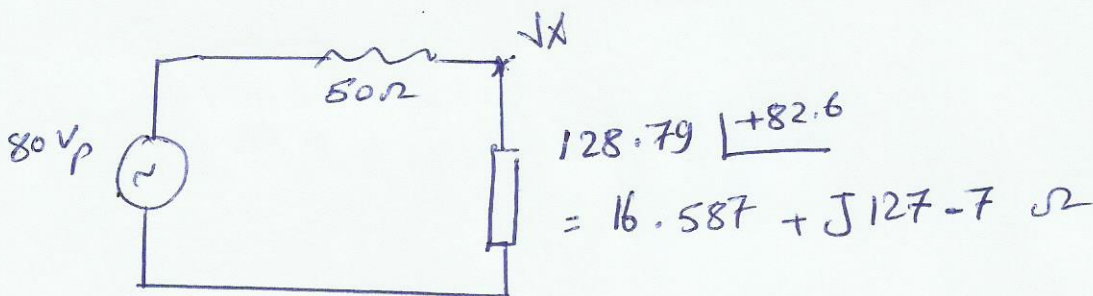
$$\therefore Z_{11} = 128.79 \angle +82.6 \Omega$$



$$\therefore Z_T = 66.587 + j127.7 = 144.01 \angle +62.46 \Omega$$

$$i_t = \frac{80V}{144.01 \angle 62.46} = 0.555 \angle -62.46 = 0.256 - j0.49 A_p$$



$$V_X = 80 - i_t(50) = 80 - 0.555 \angle -62.46 + 50$$

$$= 67.17 + j24.6$$

$$= 71.532 \angle 20.11 \text{ peak V}$$

$$V_X = 50.58 \text{ V}_{rms}$$

$\therefore i_{L2}$  " current in 10 mH coil

$$i_{L2} = \frac{V_X}{X_{L2}} = \frac{71.532 \angle 20.11}{j125.6} = 0.569 \angle -69.89$$

$$= 0.195 - j0.53 \text{ A peak}$$

$$i_{C2} = \frac{71.532 \angle 20.11}{-j3980} = 1.89 \times 10^{-3} \angle 110.11 \text{ A peak}$$

$$= -6.498 \times 10^{-4} + j1.77 \times 10^{-3} \text{ A peak}$$

$$i_{R3} = \frac{71.532 \angle 20.11}{3980 \angle -90} = \frac{71.532 \angle 20.11}{1000} = 71.532 \times 10^{-3} \angle 20.11$$

$$= 0.0671 + j0.0245 \text{ A peak}$$

$$V_{\text{across } R3} = V_X = 71.532 \angle 20.11$$


Verification  $i_t = i_{L2} + i_{C2} + i_{R3}$  "Phasor sum"

$$= 0.195 - j0.53 - 6.498 \times 10^{-4} + j1.77 \times 10^{-3} + 0.0671 + j0.0245$$

$$= 0.261 - j0.503 \approx i_t \approx 0.256 - j0.499$$

using Mesh

10

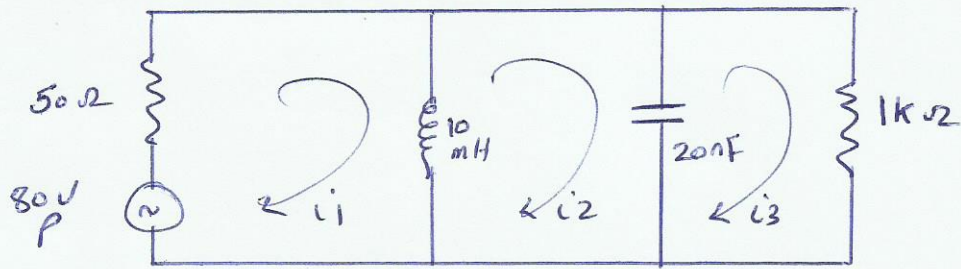

$$X_{L1} = 10 \times 10^{-3} \times 2\pi \times 2 \times 10^3 = j125.6 \Omega$$

$$X_C = -j \frac{1}{2\pi f C} = -j3980 \Omega$$

Loop 1

$$80 = 50 i_1 + (i_1 - i_2) j125.6$$

$$80 = i_1 (50 + j125.6) - i_2 j125.6 + 0 \rightarrow \textcircled{1}$$

Loop 2

$$0 = i_2 (j125.6 - j3980) + j3980 i_3 - i_1 (j125.6)$$

$$0 = i_2 (-j3855) + j3980 i_3 - i_1 j125.6$$

$$0 = -j125.6 i_1 - j3855 i_2 + j3980 i_3 \rightarrow \textcircled{2}$$

Loop 3

$$0 = i_3 (1000 - j3980) + i_2 j3980 \rightarrow \textcircled{3}$$

by solving (1/2/3)

$$i_1 = 0.26 - j0.09 = 0.554 \angle -62^\circ \text{ A peak}$$

$$i_2 = 0.06 + j0.04 = 0.0721 \angle 33.7^\circ \text{ A peak}$$

$$i_3 = 0.07 + j0.02 = 0.0728 \angle 15.94^\circ \text{ A peak}$$

$$\underline{i_1 = i_{\text{total}}}$$

$$= 0.26 - j0.49 = \boxed{0.554 \angle -62} \text{ A-peak}$$

$$\underline{i_2 = i_1 - i_2}$$

$$= 0.026 - j0.49 - 0.06 - j0.04 = 0.2 - j0.53 = \boxed{0.566 \angle -69} \text{ A-peak}$$

$$\underline{i_C = i_2 - i_3}$$

$$= 0.06 + j0.04 - 0.07 - 0.02 = -0.01 + j0.02$$

$$= \boxed{0.022 \angle 116.5} \text{ A-peak}$$

$$\underline{i_{R_3} = i_3}$$

$$= 0.07 + j0.02 = \boxed{0.728 \angle 15.19} \text{ A-peak}$$

note that:

Required

$$i_L = 0.566 \angle -69 = 0.195 - j0.53 \text{ A-peak}$$

$$= \underline{0.402} \angle -69$$

$\downarrow$   
A<sub>rms</sub>

$$V_{R_3} = i_{R_3} \times 1000 = 71.532 \angle 20 \text{ V-peak}$$

$$= 50.57 \text{ V}_{\text{rms}}$$

using Nodal only single node "Vx"

$$\frac{80 - Vx}{50} = \frac{Vx}{j125.6} + \frac{Vx}{-j3980} + \frac{Vx}{1000}$$

$$\frac{80}{50} = Vx \left[ \frac{1}{j125.6} - \frac{1}{j3980} + \frac{1}{1000} + \frac{1}{50} \right]$$

$$\therefore Vx = VR_3 = 71.54 \angle 20.13^\circ \quad V_{peak}$$

$$i_{L2} = \frac{Vx}{j125.6} = \frac{71.74 \angle 20.13^\circ}{125.6 \angle 90^\circ} = 0.571 \angle -69^\circ \quad A_{peak}$$

Summary of Result compared To Simulation

$$i_t = 0.555 \angle -62.46^\circ \text{ peak} = 0.256 - j0.49 \text{ A peak} \\ = 0.392 \text{ Arms}$$

$$i_{L2} = 0.566 \angle -69^\circ = 0.195 - j0.53 \text{ A peak} \\ = 0.402 \text{ Arms}$$

$$i_{L2} = 1.9 \times 10^{-3} \angle 110^\circ = -6.498 \times 10^{-4} + j1.77 \times 10^{-3} \text{ A peak} \\ = 1.34 \times 10^{-3} \text{ Arms}$$

$$i_{R3} = 71.532 \times 10^{-3} \angle 20.11^\circ = 0.0671 + j0.0245 \text{ A peak} \\ = 50.58 \times 10^{-3} \text{ Arms}$$

$$Vx = VR_3 = 71.53 \angle 20.11^\circ \text{ V peak} = 50.57 \text{ V rms}$$

$$VR_1 = 80 \angle 0^\circ - Vx = 80 - 71.53 \angle 20.11^\circ = 80 - [67.17 + j24.6] \\ = 12.83 - j24.6 = 27.74 \angle -62.45^\circ = 19.6 \text{ V rms}$$

تقریباً " " کے طور پر (Simulation میں) (Sim)

M1.2 B

13

$$L_1 = 10 \text{ mH} \rightarrow X_{L1} = 2\pi \times 1 \times 10^3 \times 10 \times 10^{-3} = \boxed{J62.8 \Omega}$$

$$\underline{Z_1 = 100 + J62.8 \Omega = 118.08 \angle 32.12^\circ \Omega}$$

$$L_2 = 5 \text{ mH} \rightarrow X_{L2} = J31.4 \Omega$$

$$\underline{Z_2 = 200 + J31.4 = 202.44 \angle 8.9^\circ \Omega}$$

$$L_3 = 15 \text{ mH} \rightarrow X_{L3} = J94.2 \Omega$$


$$C_2 = 50 \text{ nF} \rightarrow X_{C2} = -J3184 \Omega$$

$$\underline{Z_3 = X_{L3} + X_{C2} = -J3090 = 3090 \angle -90^\circ \Omega}$$

$$C_1 = 100 \text{ nF} \rightarrow X_{C1} = -J1592 \Omega$$

$$\underline{Z_4 = 200 - J1592 = 1604 \angle -82.84^\circ \Omega}$$

using Mesh

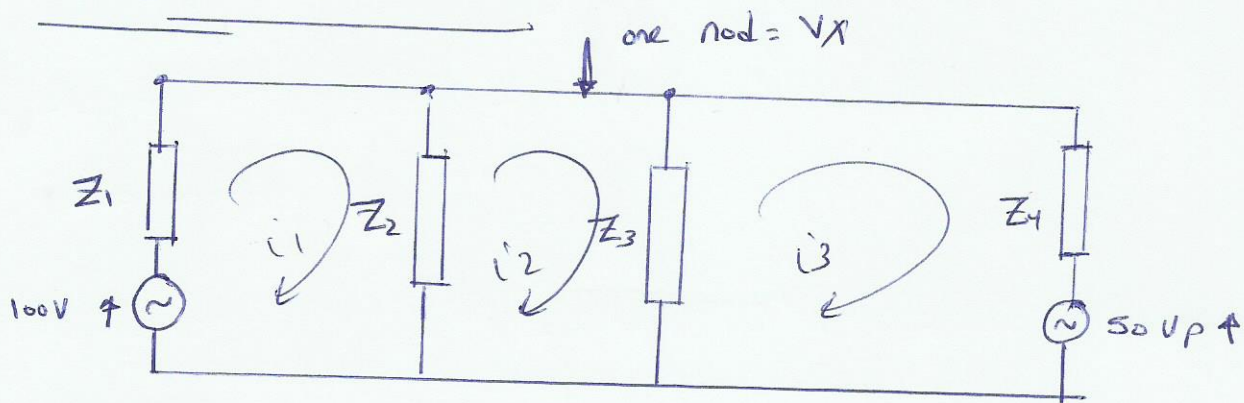

Loop (1)

$$100 = i_1 (300 + J94.2) - i_2 (200 + J31.4) + 0$$

Loop (2)

$$0 = -i_1 (200 + J31.4) + i_2 (200 - J3058.6) + J i_3 3090$$

Loop (3)

$$-50 = 0 + i_2 (J3090) + i_3 (200 - J4682)$$

## Solving 1, 2, 3

115

### Currents

$$i_1 = 0.314 - j0.079 \text{ A peak}$$

$$i_2 = 0.012 + j0.028 \text{ A peak}$$

$$i_3 = 0.008 + j0.008 \text{ A peak}$$

### current in (R<sub>1</sub>, L<sub>1</sub>) Branch = I<sub>1</sub>

$$= 0.314 - j0.079 = 323 \times 10^{-3} \angle -14.12^\circ \text{ A peak}$$

$$= 228.4 \text{ mA rms} \approx \text{Simulation (228.604 Arms)}$$

### current in (R<sub>2</sub>, L<sub>2</sub>) Branch

$$= i_1 - i_2 = 0.314 - j0.079 - [0.012 + j0.028]$$

$$= 0.302 - j0.106 = 0.320 \angle -19.34^\circ \text{ A peak}$$

$$\approx 0.226 \text{ Arms} \approx \text{Simulation 226 mA rms}$$

### current in (C<sub>1</sub>, R<sub>3</sub>) Branch

$$= i_3 = 0.008 + j0.008 = 11.313 \angle 45^\circ \text{ mA peak}$$

$$\approx 8 \text{ mA rms} \approx \text{Simulation (8.1 mA rms)}$$

### current in (C<sub>2</sub>, L<sub>3</sub>) Branch = i<sub>2</sub> - i<sub>3</sub>

$$= 0.012 + j0.028 - [0.008 + j0.008] = 4 \times 10^{-3} + 20 \times 10^{-3} j$$

$$= 20.39 \times 10^{-3} \angle 78.69^\circ \approx 14.41 \text{ mA rms}$$

$$\approx \text{Simulation (15.022 Arms)}$$

Voltage across each component

16

$$R_1 = 100 \Omega$$

$$V_{R_1} = 100 * 323 m \angle_{-14.12} = 32.3 V_p \angle_{-14.12} \approx 22.84 V_{rms}$$

$$\approx \text{Sim}(22.86 V_{rms})$$

$V_{L_1}$

$$= 323 m \angle_{-14.12} * \overset{X_{L_1}}{\downarrow} j62.8 = 20.28 \angle_{75.88} V_{peak}$$

$$= 14.34 V_{rms} \approx \text{Sim}(14.55 V_{rms})$$

$V_{R_2}$

$$= 200 + 320 m \angle_{-19.34} = 64 \angle_{-19.34} V_{peak}$$

$$= 45.25 V_{rms} \approx \text{Sim}(45.2 V_{rms})$$

$V_{L_2}$

$$= 320 m \angle_{-19.34} * \overset{X_{L_2}}{\downarrow} 31.4 \angle_{90} = 10.048 \angle_{70.66}$$

$$= 7.105 V_{rms} \approx \text{Sim}(7.193 V_{rms})$$

$V_{C_2}$

$$= 20.39 m \angle_{78.69} * \overset{X_{C_2}}{\downarrow} 3184 \angle_{-90} = 64.92 \angle_{-11.31} V_{peak}$$
$$\approx 46.2 V_{rms} \approx \text{Sim}(47 V_{rms})$$

$V_{L_3}$

$$= 20.39 \times 10^{-3} \angle_{78.69} * \overset{X_{L_3}}{\downarrow} 94.2 \angle_{90} = 1.92 \angle_{168.69} V_{peak}$$

$$= 1.36 V_{rms} \approx \text{Sim}(1.43 V_{rms})$$

$V_{k1}$ 

$$X_{k1} = -j1592$$

$$= 11.313 \text{ m} \angle 45^\circ + 1592 \angle -90^\circ = 18 \angle -45^\circ \text{ V}_{\text{peak}}$$

$$= 12.7 \text{ V}_{\text{rms}} \approx \text{Sim}(12.725 \text{ V}_{\text{rms}})$$

 $V_{R3}$ 

$$= 11.313 \angle 45^\circ \times 200 = 2.262 \angle 45^\circ \text{ V}_{\text{peak}}$$

$$= 1.6 \text{ V}_{\text{rms}} \approx \text{Sim}(1.62 \text{ V}_{\text{rms}})$$

Using Nodalone node only  $V_X$ see Fig p(13 - solution)

$$\frac{V_X - 100}{118.08 \angle 32.12^\circ} + \frac{V_X}{202.44 \angle 8.9^\circ} + \frac{V_X}{3090 \angle -90^\circ} + \frac{V_X - 50}{1604 \angle 82.84^\circ}$$

by solving

$$V_X = 0.0647 \times 10^3 \angle -10.542^\circ \text{ V}_{\text{peak}}$$

$$= 45.749 \text{ V}_{\text{rms}} \approx \text{Sim}(45.761 \text{ V}_{\text{rms}})$$

Current Through each Branch $R_1, L_1$ 

$$= \frac{100 - V_X}{R_1 + jX_{L_1}} = 0.314 - 0.79j = 323 \text{ m} \angle -14.12^\circ \text{ A}_{\text{peak}}$$



R2, L2

18

$$\frac{V_X}{R_2 + jX_{L2}} = 0.302 - j0.106 = 0.320 \angle -19.34^\circ \text{ A peak}$$

C2, L3

$$\begin{aligned} &= \frac{V_X}{jX_{L3} - jX_{C2}} = 4 \times 10^{-3} + 20 \times 10^{-3} j \\ &= 20.39 \angle 78.69^\circ \text{ A peak} \end{aligned}$$

C1, R3

$$= \frac{V_X}{R_3 + jX_{C1}} = 0.008 + j0.008 = 11.313 \angle 45^\circ \text{ A peak}$$

all other values like Mesh solution

D1.2

Solution - Appended

Dr. Michael