

BENHA UNIVERSITY  
FACULTY OF ENGINEERING (SHOUBRA)  
ELECTRONICS AND COMMUNICATIONS ENGINEERING



# ECE 444

## Industrial Electronics

(2022 - 2023) 1<sup>st</sup> term

Lecture 4: Analog Signal Conditioning.

Dr. Ahmed Samir

<https://bu.edu.eg/staff/ahmedsaied>

# Outlines:



Analog Signal Conditioning.

Analog Signal Conditioning Categories.

Voltage Divider Circuit.

Wheatstone Bridge Circuit.

Design Guideline.

# Analog Signal Conditioning (S/C):

- Signal conditioning refers to **operation performed** on signals to **convert** them to a **form** that is **suitable to interface** with other elements in the process-control loop.
- A **sensor** measures a variable by **converting information** about that variable into a dependent **signal**.
- We often describe the effect of the **signal conditioning** by the term **transfer function**.
- Signal conditioning Categories:
  - 1) Signal Level and bias changes.
  - 2) Linearization.
  - 3) Conversion.
  - 4) Filtering.
  - 5) Impedance Matching.




# 1-Signal level and bias changes:

- One of the most common types of signal conditioning involves **adjusting the level** (magnitude) and **bias** (zero value) of some voltage representing a process variable.
- For example, some sensor output voltage may vary from 0.2 to 0.6 V equipment to which this sensor output must be connected perhaps requires a voltage that varies from 0 to 5 V for the same variation of the process:
  - ❑ subtracting 0.2  $\rightarrow$  a zero shift, or a bias adjustment (0 to 0.4)
  - ❑ multiply the voltage by 12.5  $\rightarrow$  amplification (0 to 5)
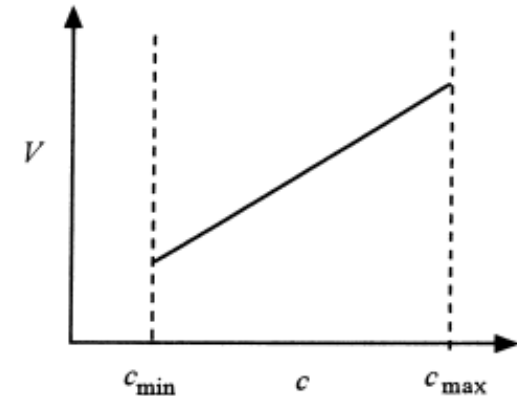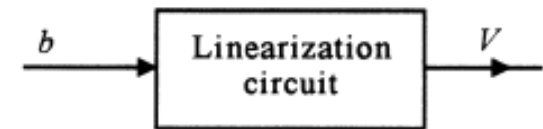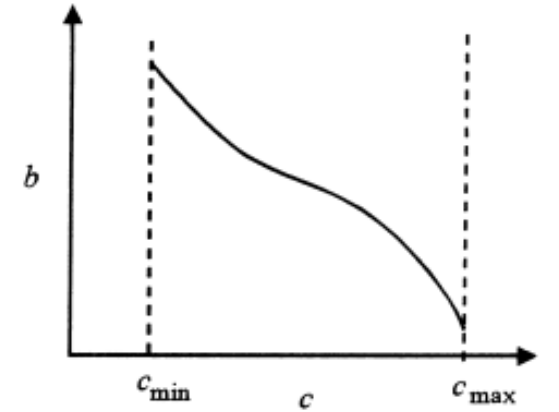
## 2. Linearization:

5

- The designer has a little choice of the characteristics of a sensor (Often has a nonlinear T.F.).
- A linearization circuit is difficult to design and has a narrow range.
- Now software based linearization techniques are used.



# 3. Conversion:


- To convert one type of electrical variation into another (e.g.  $\Delta R$  to  $\Delta V$  or  $\Delta I$  )
- For signal transmission (4-20 mA current loop) (**V to I** and **I to V**)
- For digital interface, The use of computers in process control requires conversion of **analog data into a digital format** by integrated circuit devices called analog-to-digital converters (**ADCs**). An analog signal conversion is usually required to **adjust the analog signal to match the input requirement of the ADC**
  - e.g. Sensor output 20 – 90 mV
  - ADC range 0 - 5 V

## 4. Filtering:

- Often, spurious signals of considerable strength are present in the industrial environment, such as the 60-Hz line frequency signals.
- Motor start transients may also cause pulses and other unwanted signals in the process-control loop.
- In many cases, it is necessary to use **high-pass, low-pass, Band-pass, band-reject** or **notch filters** to eliminate unwanted signals from the loop.
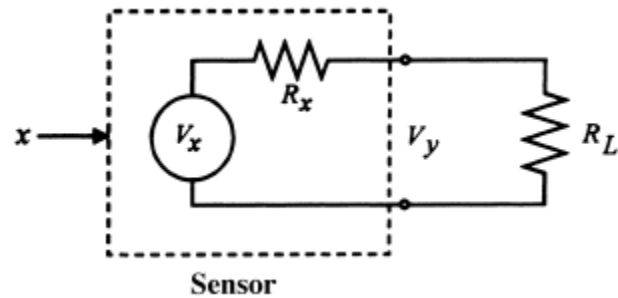
# 5. Impedance Matching:

- Impedance matching is an important element of signal conditioning when **transducer internal impedance** or **line impedance** can cause errors in measurement of a dynamic variable.
- Loading introduces uncertainty in the amplitude of a voltage as it is passed through the measurement process. (**Loading Effect**).



$$V_y = V_x \left( 1 - \frac{R_x}{R_L + R_x} \right)$$


- If loading is ignored, serious errors can occur in expected outputs of circuits and gains of amplifiers.



# Passive circuit:
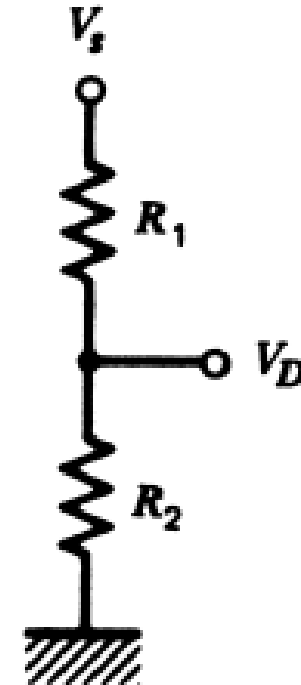
## Voltage Divider Circuit:

- The simple voltage divider can often be used to convert resistance variation into voltage variation.
- $V_D = V_s R_2 / (R_1 + R_2)$
- $R_1$  or  $R_2$  may be a sensor
- Notes:
  - Nonlinearity of the equation
  - Loading effect
  - $R_1$  &  $R_2$  power rating



# Voltage Divider Circuit:

10

**EXAMPLE 2** The divider of Figure 4 has  $R_1 = 10.0 \text{ k}\Omega$  and  $V_s = 5.00 \text{ V}$ . Suppose  $R_2$  is a sensor whose resistance varies from  $4.00$  to  $12.0 \text{ k}\Omega$  as some dynamic variable varies over a range. Then find (a) the minimum and maximum of  $V_D$ , (b) the range of output impedance, and (c) the range of power dissipated by  $R_2$ .

*Solution*


a. The solution is given by Equation (2). For  $R_2 = 4 \text{ k}\Omega$ , we have

$$V_D = \frac{(5 \text{ V})(4 \text{ k}\Omega)}{10 \text{ k}\Omega + 4 \text{ k}\Omega} = 1.43 \text{ V}$$

For  $R_2 = 12 \text{ k}\Omega$ , the voltage is

$$V_D = \frac{(5 \text{ V})(12 \text{ k}\Omega)}{10 \text{ k}\Omega + 12 \text{ k}\Omega} = 2.73 \text{ V}$$

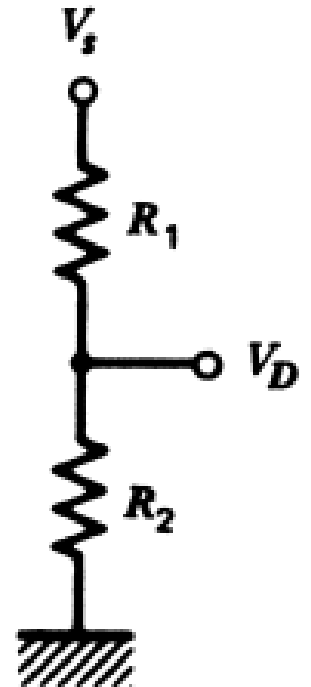- b. Thus, the voltage varies from  $1.43$  to  $2.73 \text{ V}$ .
- c. The range of output impedance is found from the parallel combination of  $R_1$  and  $R_2$  for the minimum and maximum of  $R_2$ . Simple parallel resistance computation shows that this will be from  $2.86$  to  $5.45 \text{ k}\Omega$ .
- d. The power dissipated by the sensor can be determined most easily from  $V^2/R_2$ , as the voltage across  $R_2$  has been calculated. The power dissipated varies from  $0.51$  to  $0.62 \text{ mW}$ .




# Wheatstone Bridge Circuit:

- To convert **impedance variations** into **voltage variations**.
- One of the advantages of the bridge for this task is that it can be designed so **the voltage produced varies around zero**.
- To measure impedance precisely.

- $\Delta V = V_a - V_b$  (voltage offset)  
 $= V_S \frac{(R_3 R_2 - R_1 R_4)}{(R_1 + R_3)(R_2 + R_4)}$

- Null condition:

$$R_3 R_2 = R_1 R_4$$

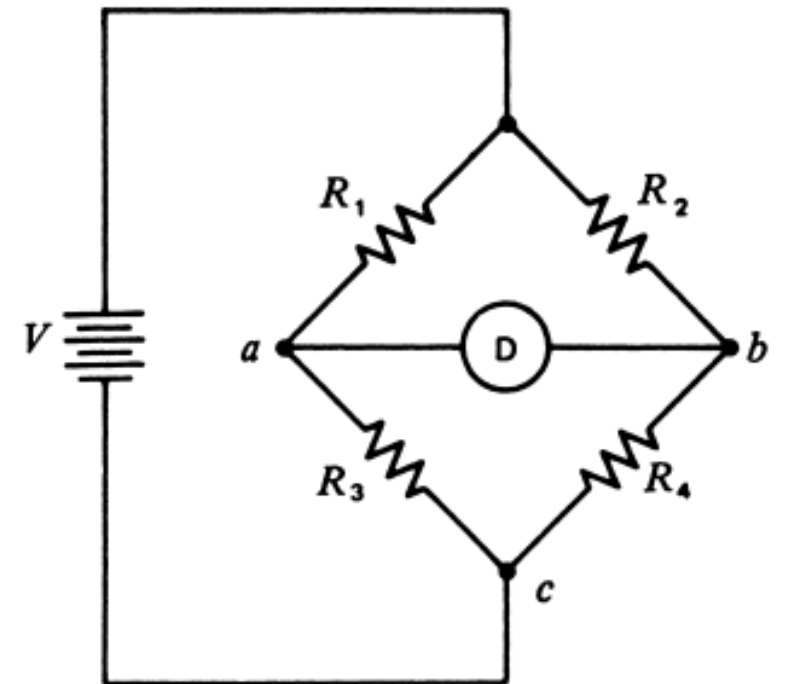

# Using Galvanometer to detect the offset:



12

- In some cases, a highly sensitive galvanometer with a relatively low impedance may be used
- When a galvanometer is used for a null detector, it is convenient to use the Thévenin equivalent circuit of the bridge

$$V_{Th} = V \frac{R_3 R_2 - R_1 R_4}{(R_1 + R_3)(R_2 + R_4)}$$

$$R_{Th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}$$

$$I_G = \frac{V_{Th}}{R_{Th} + R_G}$$

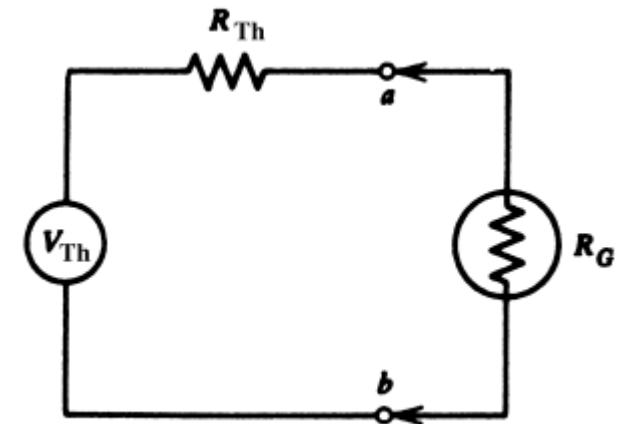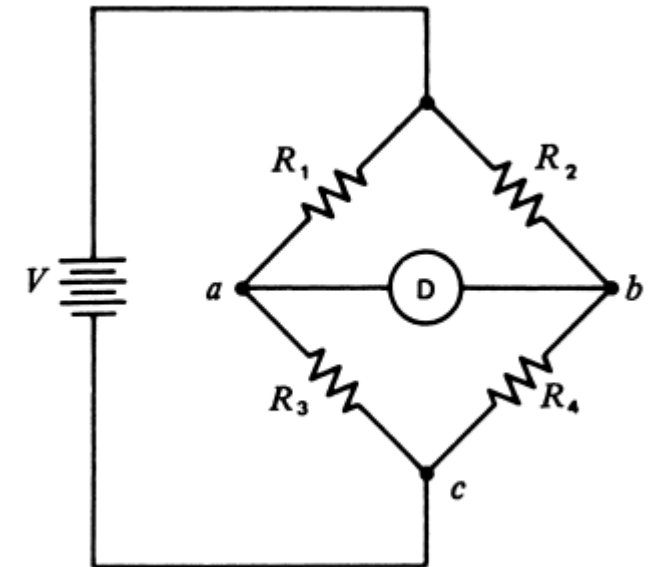

# Using Galvanometer to detect the offset:

13

**EXAMPLE 5** A bridge circuit has resistance of  $R_1 = R_2 = R_3 = 2.00 \text{ k}\Omega$  and  $R_4 = 2.05 \text{ k}\Omega$  and a 5.00-V supply. If a galvanometer with a  $50.0\text{-}\Omega$  internal resistance is used for a detector, find the offset current.

## *Solution*

From Equation (9), the offset voltage is  $V_{\text{Th}}$ .

$$V_{\text{Th}} = 5 \text{ V} \frac{(2 \text{ k}\Omega)(2 \text{ k}\Omega) - (2 \text{ k}\Omega)(2.05 \text{ k}\Omega)}{(2 \text{ k}\Omega + 2 \text{ k}\Omega)(2 \text{ k}\Omega + 2.05 \text{ k}\Omega)}$$
$$V_{\text{Th}} = -\mathbf{30.9 \text{ mV}}$$

We next find the bridge Thévenin resistance from Equation (10):

$$R_{\text{Th}} = \frac{(2 \text{ k}\Omega)(2 \text{ k}\Omega)}{(2 \text{ k}\Omega + 2 \text{ k}\Omega)} + \frac{(2 \text{ k}\Omega)(2.05 \text{ k}\Omega)}{(2 \text{ k}\Omega + 2.05 \text{ k}\Omega)}$$
$$R_{\text{Th}} = \mathbf{2.01 \text{ k}\Omega}$$

Finally, the current is given by Equation (11):

$$I_G = \frac{-30.9 \text{ mV}}{2.01 \text{ k}\Omega + 0.05 \text{ k}\Omega}$$
$$I_G = -\mathbf{15.0 \mu\text{A}}$$

- It is the resistance change in one arm of the bridge that causes an offset voltage (offset current) that is equal the resolution of the detector.
- Gives a limit to min. measurable resistance change.
- Seen as overall accuracy of the instrument

**EXAMPLE 6** A bridge circuit has  $R_1 = R_2 = R_3 = R_4 = 120.0\text{-}\Omega$  resistances and a 10.0-V supply. Clearly, the bridge is nulled, as Equation (8) shows. Suppose a  $3\frac{1}{2}$ -digit DVM on a 200-mV scale will be used for the null detector. Find the resistance resolution for measurements of  $R_4$ .

### *Solution*

On a 200-mV scale, the DVM measures from 000.0 to 199.9 mV, so the smallest measurable change is 0.1 mV, or  $100\ \mu\text{V}$ . So, we need to find out how much  $R_4$  has changed from  $120\ \Omega$  to create this much off null voltage.

We simply use Equation (6), with  $R_4$  changed to some unknown value so that  $100\ \mu\text{V}$  results:

$$100\ \mu\text{V} = \frac{(120\ \Omega)(10\ \text{V})}{120\ \Omega + 120\ \Omega} - \frac{R_4(10\ \text{V})}{120\ \Omega + R_4}$$

This equation is a bit of an algebraic challenge to solve, but eventually we find

$$R_4 = 119.9952\ \Omega$$



So the smallest change in resistance that can be measured is

$$\Delta R_4 = 120\ \Omega - 119.9952\ \Omega = 0.0048\ \Omega$$

A bridge offset of  $+100\ \mu\text{V}$  is caused by a reduction of  $R_4$ . It follows that a bridge offset of  $-100\ \mu\text{V}$  would be caused by an increase of  $R_4$ .
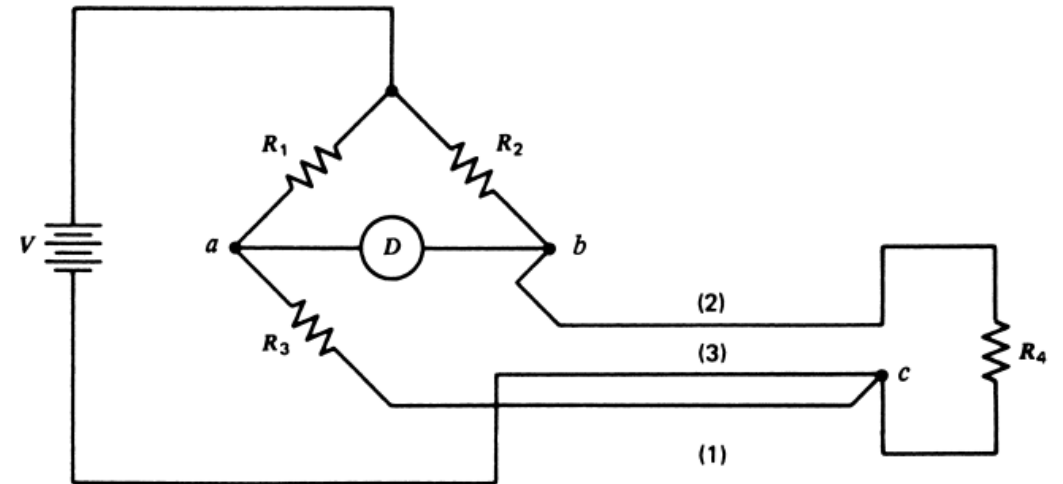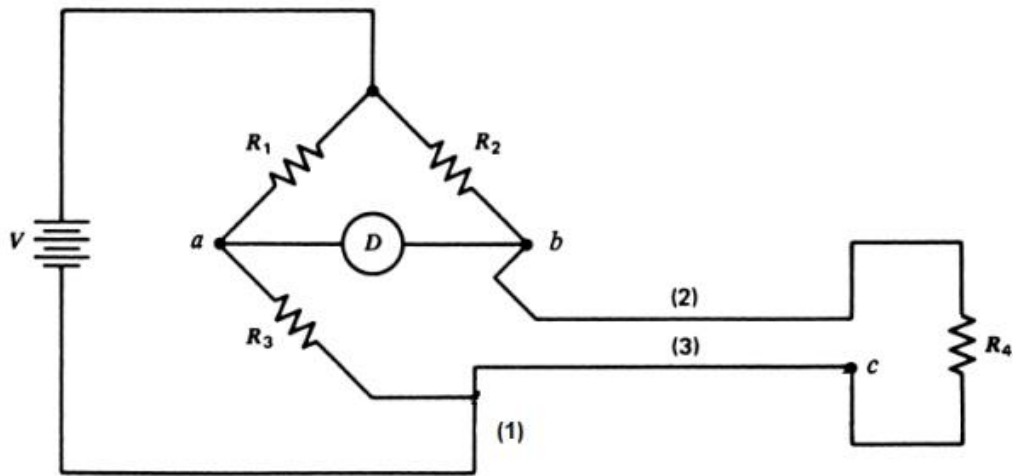
# Bridge Compensation:

- A Problem: In many process-control applications, a bridge circuit may be located at considerable distance from the sensor whose resistance changes are to be measured. The resistance of the wires (2) & (3) must be considered to minimize the error in measurement
- For remote sensor applications, this compensation system is used to avoid errors from lead resistance.






# Bridge Compensation:

- 9 A bridge circuit is used with a sensor located 100 m away. The bridge is not lead compensated, and the cable to the sensor has a resistance of  $0.45 \text{ } \Omega/\text{ft}$ . The bridge nulls with  $R_1 = 3400 \text{ } \Omega$ ,  $R_2 = 3445 \text{ } \Omega$ , and  $R_3 = 1560 \text{ } \Omega$ . What is the sensor resistance?
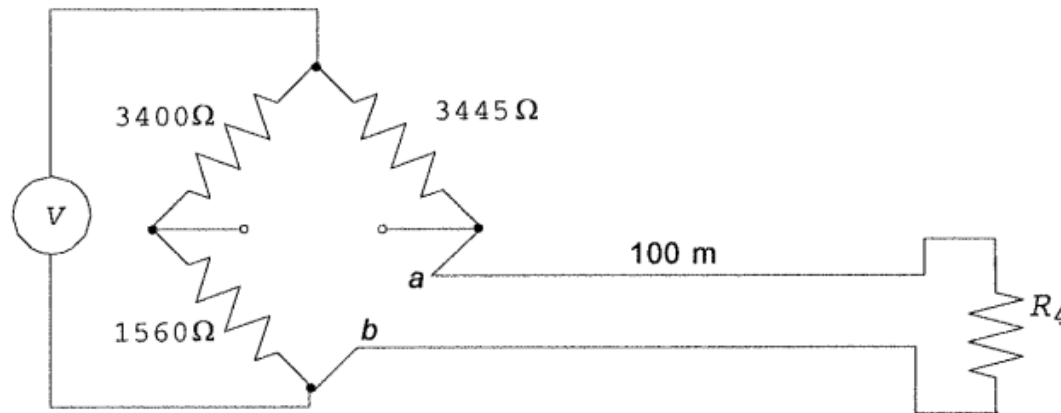
## Solution

A diagram will help you understand this problem. The circuit is,



If you use the null equation to find  $R_4$ , it will give the resistance from  $a$  to  $b$  in the schematic, which includes the two 100 m lead resistances. Thus these must be subtracted to find the actual sensor resistance.

$$R_{ab} = (3445 \text{ } \Omega)(1560 \text{ } \Omega)/(3400 \text{ } \Omega) = 1580.6 \text{ } \Omega$$

but the lead resistance is,


$$R_{\text{lead}} = 2(100 \text{ m})(0.3048 \text{ m/ft})(0.45 \text{ } \Omega/\text{ft}) = 295.3 \text{ } \Omega$$

So the actual sensor resistance is,

$$R_4 = 1580.6 \text{ } \Omega - 295.3 \text{ } \Omega = 1285.3 \text{ } \Omega$$


# OPERATIONAL AMPLIFIERS:

Differential Amplifier

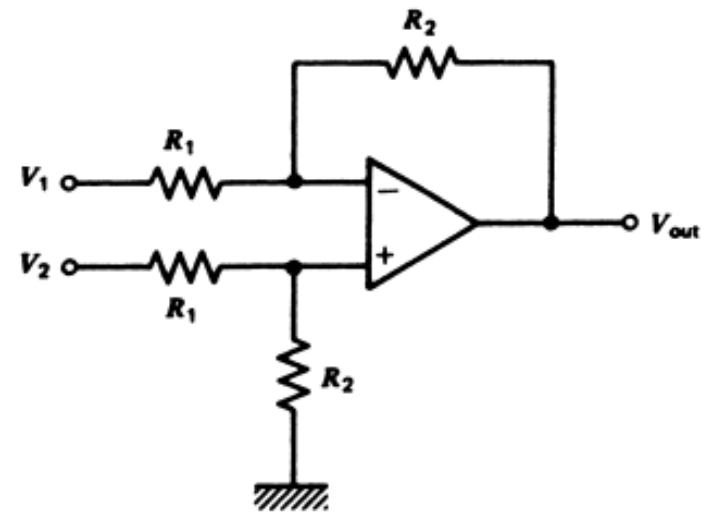


$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Instrumentation Amplifier

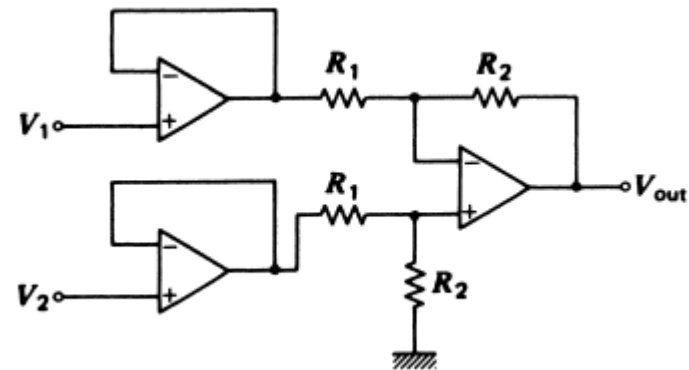

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


Instrumentation Amplifier

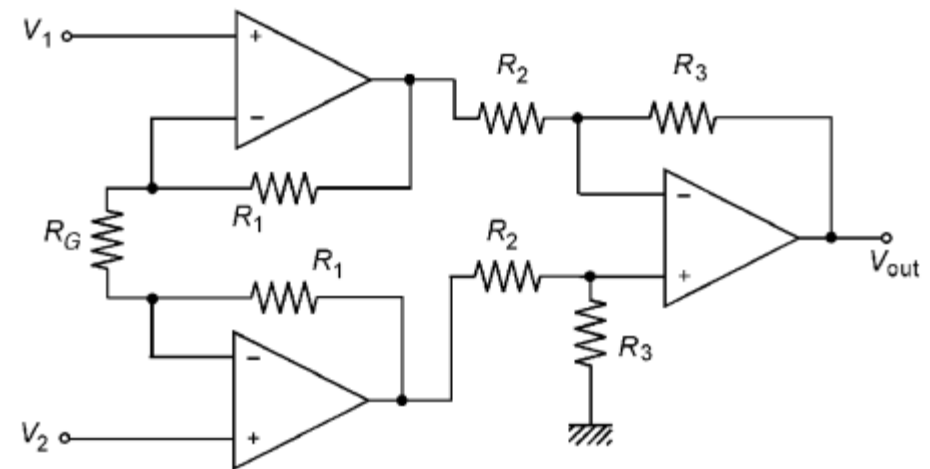


$$V_{out} = \left(1 + \frac{2R_1}{R_G}\right) \left(\frac{R_3}{R_2}\right) (V_2 - V_1)$$

# OPERATIONAL AMPLIFIERS:


### Voltage-to-Current Converter

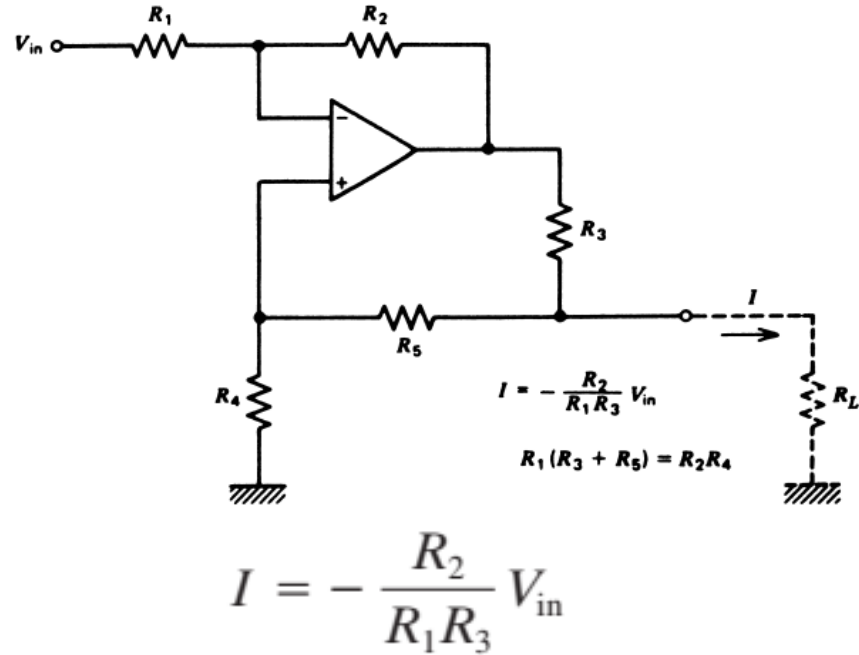


### Current-to-Voltage Converter

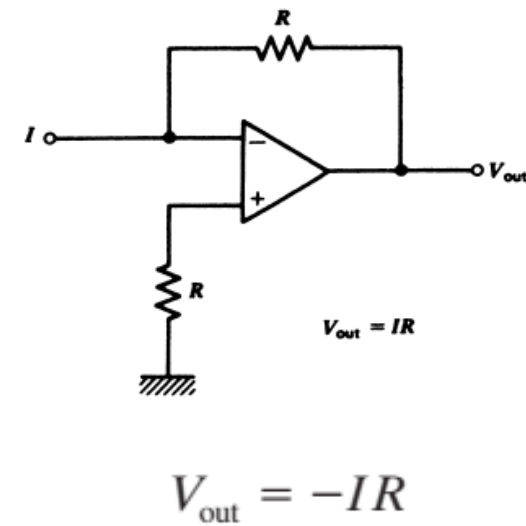

### Non-Inverting Amplifier

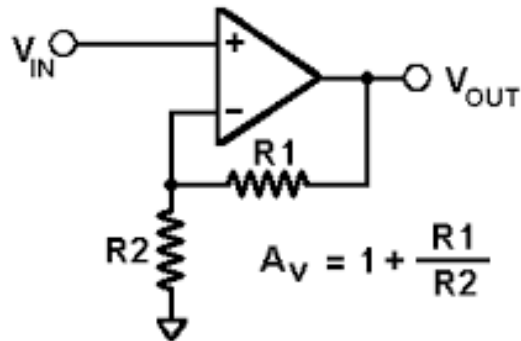

### Inverting Amplifier

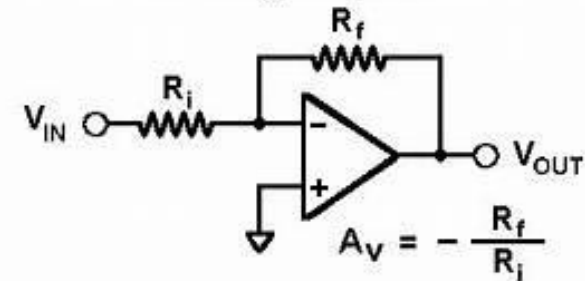

# OPERATIONAL AMPLIFIERS:

20

**EXAMPLE 20** A sensor outputs a range of 20.0 to 250 mV as a variable varies over its range. Develop signal conditioning so that this becomes 0 to 5 V. The circuit must have very high input impedance.

*Solution*

$$V_{\text{out}} = mV_{\text{in}} + V_0$$


$$0 = m(0.02) + V_0$$

$$5 = m(0.25) + V_0$$

We get  $m = 21.7$  and  $V_0 = -0.434$  V using standard algebra. The equation is

$$V_{\text{out}} = 21.7 V_{\text{in}} - 0.434$$
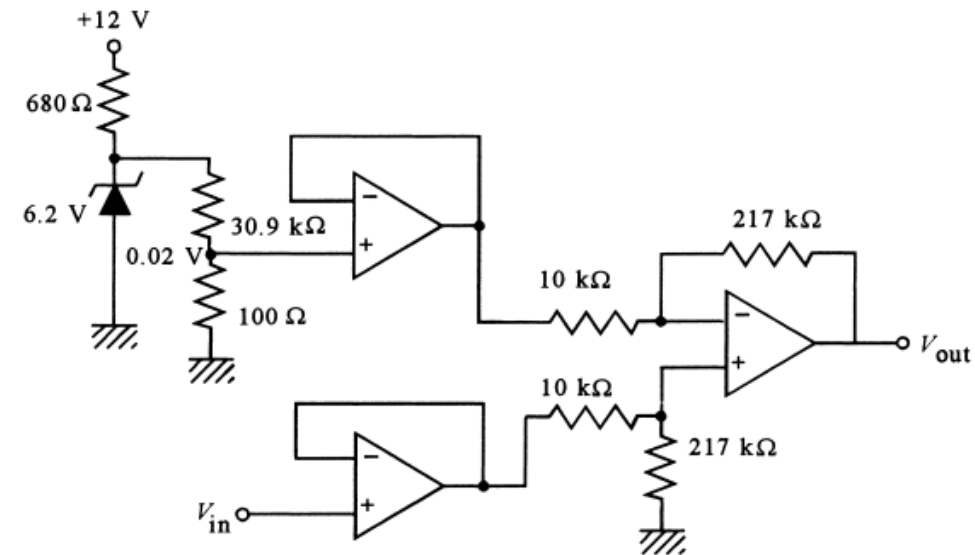
$$V_{\text{out}} = 21.7 (V_{\text{in}} - 0.02)$$



# OPERATIONAL AMPLIFIERS:

**EXAMPLE 24** A sensor outputs a voltage ranging from  $-2.4$  to  $-1.1$  V. For interface to an analog-to-digital converter, this needs to be  $0$  to  $2.5$  V. Develop the required signal conditioning.

**Solution**

$$V_{\text{out}} = mV_{\text{in}} + V_0$$



$$0 = -2.4m + V_0$$

$$2.5 = -1.1m + V_0$$

The transfer function equation is thus

$$V_{\text{out}} = 1.923 V_{\text{in}} + 4.615$$
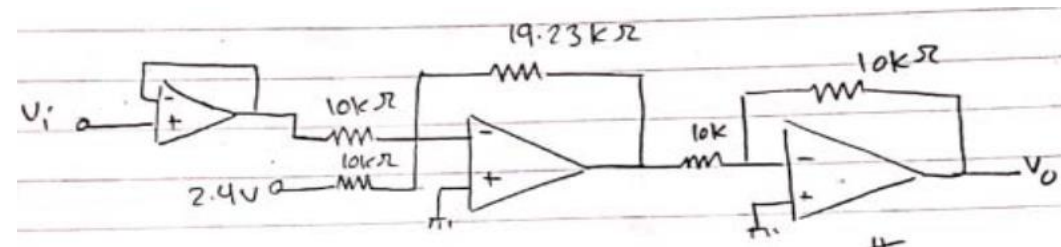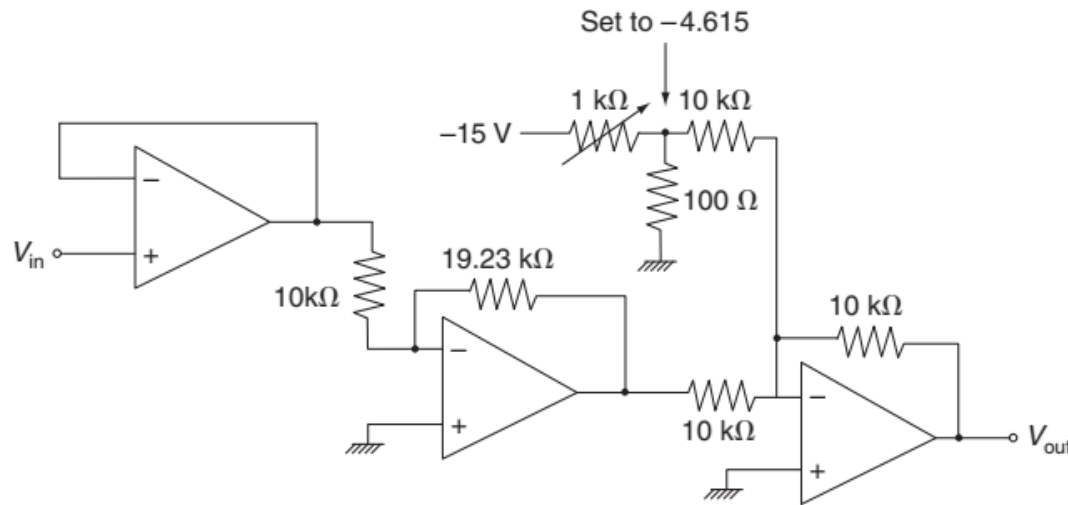
$$V_{\text{out}} = 1.923(V_{\text{in}} + 2.4)$$



# Design Guidelines:

22

## ➤ Measurement Objective:


- Parameter
- Range
- Accuracy
- Linearity
- Noise

## ➤ Select a Sensor:

- Parameter
- Range
- Transfer function
- Time response
- Power dissipation
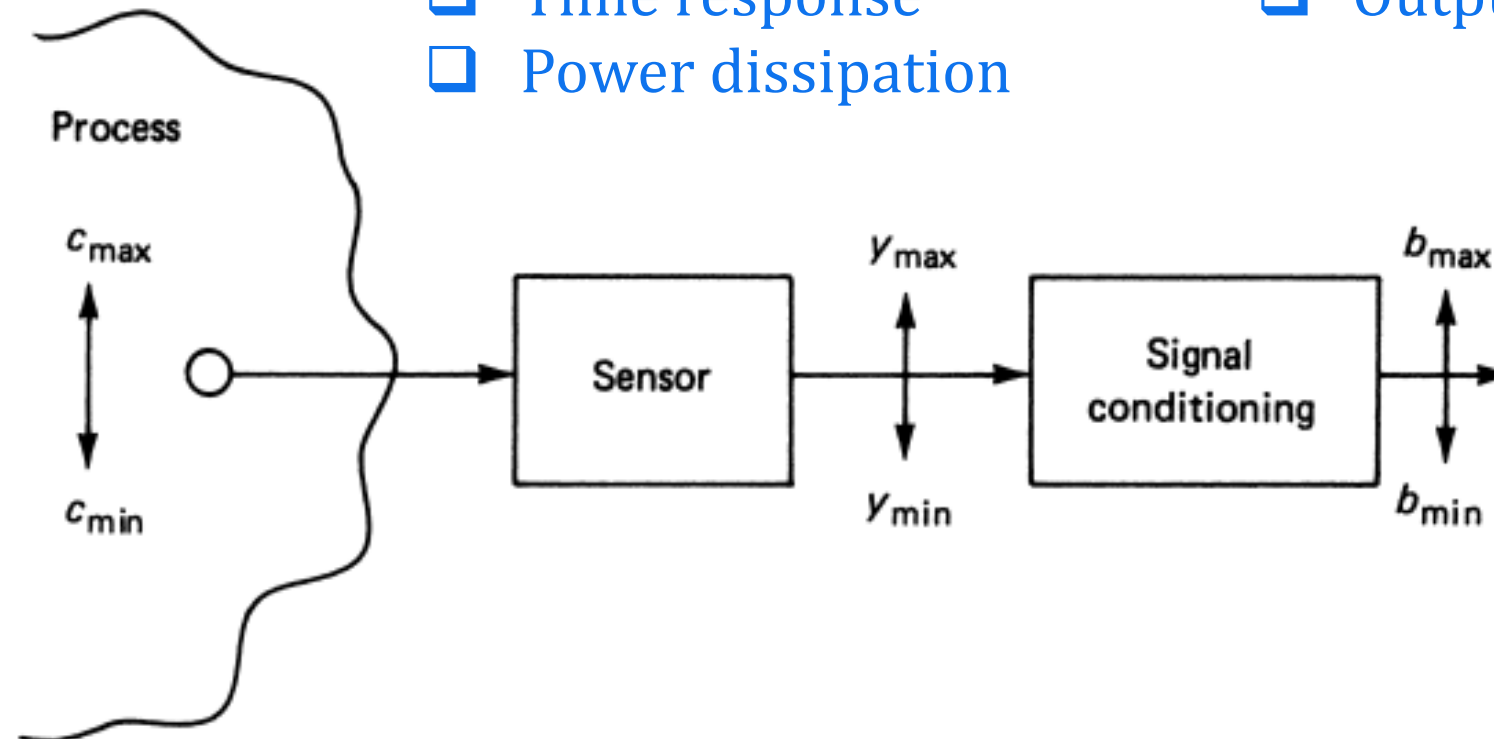
## ➤ Signal Conditioning:

- Parameter
- Range
- Input Impedance
- Output Impedance



# Design Guidelines:

**EXAMPLE 25** Temperature is to be measured in the range of 250°C to 450°C with an accuracy of  $\pm 2^\circ\text{C}$ . The sensor is a resistance that varies linearly from 280  $\Omega$  to 1060  $\Omega$  for this temperature range. Power dissipated in the sensor must be kept below 5 mW. Develop analog signal conditioning that provides a voltage varying linearly from  $-5$  to  $+5$  V for this temperature range. The load is a high-impedance recorder.

## *Solution*

Following the guidelines, let us first identify all the elements of the problem.

### *Measured Variable Parameter: Temperature*

*Range:* 250° to 450°C

*Accuracy:*  $\pm 2^\circ\text{C}$

*Noise:* unspecified

### *Sensor Signal*

*Parameter:* resistance

*Transfer function:* linear

*Time response:* unspecified

*Range:* 280  $\Omega$  to 1060  $\Omega$ , linear

*Power:* maximum 5 mW dissipated in sensor

### *Signal Conditioning*

*Parameter:* voltage, linear

*Range:*  $-5$  to  $+5$  V

*Input impedance:* keep power in sensor below 5 mW

*Output impedance:* no problem, high-impedance recorder

# Design Guidelines:

Solu:  $P = I^2 R$   $5 \times 10^{-3} = I^2 (280) \Rightarrow I = 4.2 \text{ mA}$   
 $\therefore I^2 (1000) \Rightarrow I = 2.17 \text{ mA}$

1) The design must always keep The Sensor Current below 2 mA

let we make it  $I_{max} = 1 \text{ mA}$

OR:  $280 \rightarrow 1000 \Omega$

$\Delta V: -5 \rightarrow 5 \text{ V}$  }  $\rightarrow$  linear relation


$V_{out} = m R_s + U$

$-5 = m(280) + U$  (I)


$5 = m(1000) + U$  (II)

}  $\Rightarrow m = 0.0128, U = -8.58$

$V_{out} = 0.0128 R_s - 8.58$

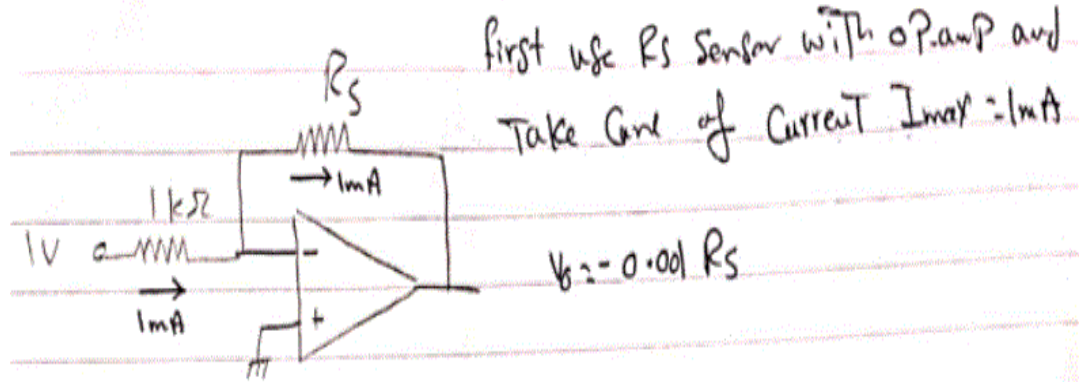

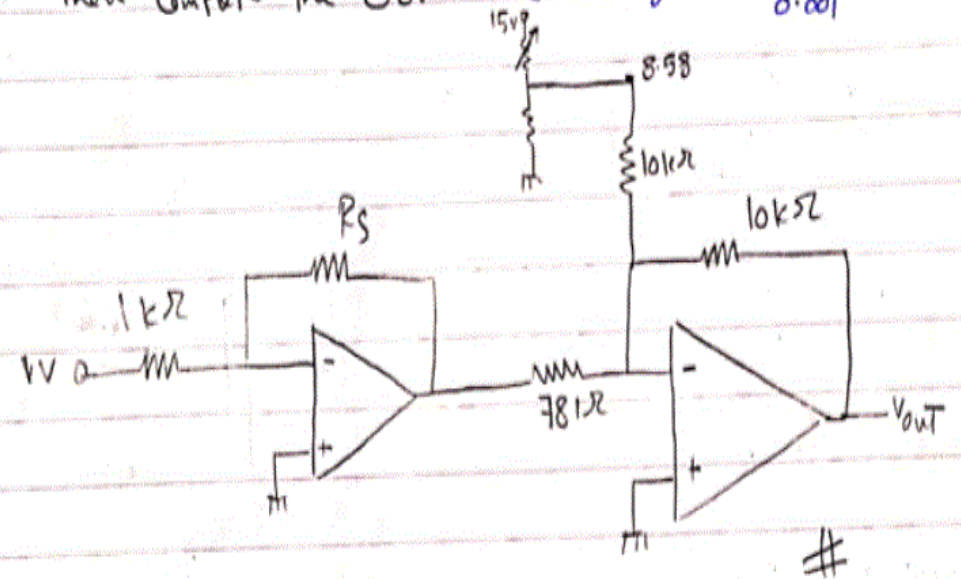Then Complete The Ct: The remain gain:  $\frac{0.0128}{0.001} = 12.8$







**END OF LECTURE**

**BEST WISHES**