



**BENHA UNIVERSITY**  
**FACULTY OF ENGINEERING (SHOUBRA)**  
**ELECTRONICS AND COMMUNICATIONS ENGINEERING**



**ECE 211**

**Measurements and Instrumentations**  
**(2022 - 2023) 1<sup>st</sup> term**

**Lecture 4: Electromechanical Instruments (part 2).**

**Dr. Ahmed Samir**

**<https://bu.edu.eg/staff/ahmedsaied>**

# Chapter Outline:


- 1) Permanent Magnet Moving Coil (PMMC).
- 2) Galvanometer.
- 3) **DC Ammeters**
- 4) DC Voltmeters
- 5) Ohmmeters
- 6) AC Voltmeters
- 7) AC Ammeters

## 3.3 DC Ammeters: Ammeter Circuit:

- ▶ The PMMC instrument can be used as an ammeter to **measure DC current**. However, the PMMC wire could be quickly **destroyed by large currents**.
- ▶ For large currents, a PMMC is modified by adding a **parallel (shunt) resistance**  $R_s$ .
- ▶ Most of the measured current will pass through  $R_s$  and a small portion of it will pass through the moving coil.

### Shunt Resistance

It is a **small resistance** connected in **parallel** with PMMC to allow measuring **large currents**. It is a **four-terminal** resistance to neglect the resistance of the current terminal.

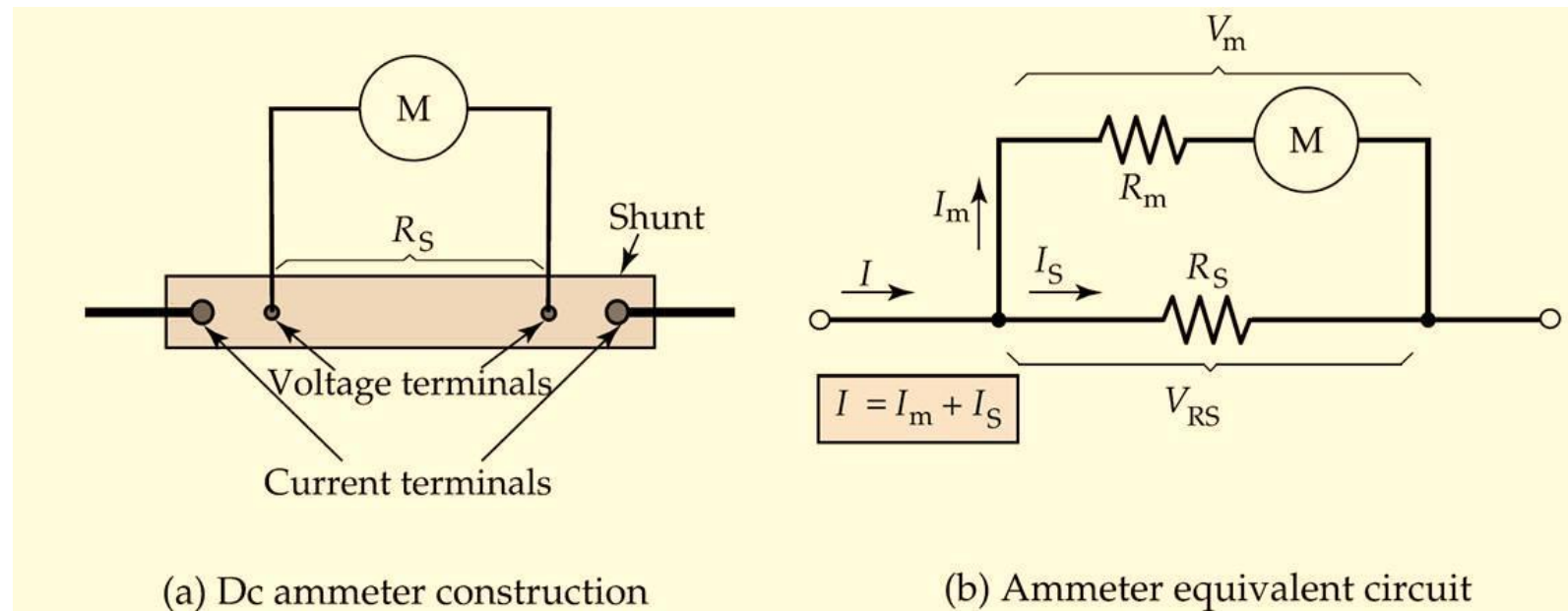


**Figure 4-1** A dc ammeter consists of a PMMC instrument and a low-resistance shunt. The meter current is directly proportional to the shunt current, so that the meter scale can be calibrated to indicate the total ammeter current.

## 3.3 DC Ammeter (Cont.)

### Example 3.3:

► An ammeter has a PMMC instrument with a coil resistance of  $R_m = 99 \Omega$  and full-scale deflection (FSD) current of 0.1 mA. Shunt resistance  $R_s = 1 \Omega$ . **Determine** the total current passing through the ammeter at:

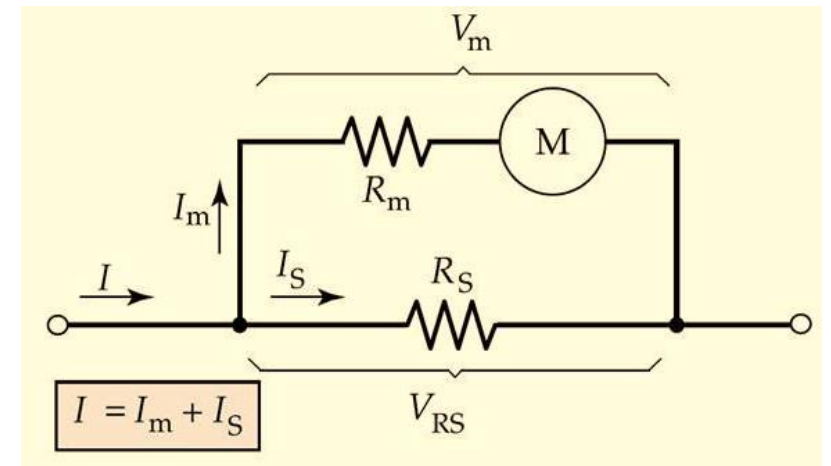- (a) FSD      (b) 0.5 FSD      (c) 0.25 FSD



# Solution

(a) At FSD:

$$\begin{aligned} \text{meter voltage } V_m &= I_m R_m \\ &= 0.1 \text{ mA} \times 99 \Omega \\ &= 9.9 \text{ mV} \end{aligned}$$

and

$$\begin{aligned} I_s R_s &= V_m \\ I_s &= \frac{V_m}{R_s} = \frac{9.9 \text{ mV}}{1 \Omega} = 9.9 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{total current } I &= I_s + I_m = 9.9 \text{ mA} + 0.1 \text{ mA} \\ &= 10 \text{ mA} \end{aligned}$$

(b) At 0.5 FSD:

$$\begin{aligned} I_m &= 0.5 \times 0.1 \text{ mA} = 0.05 \text{ mA} \\ V_m &= I_m R_m = 0.05 \text{ mA} \times 99 \Omega = 4.95 \text{ mV} \end{aligned}$$

$$I_s = \frac{V_m}{R_s} = \frac{4.95 \text{ mV}}{1 \Omega} = 4.95 \text{ mA}$$

$$\begin{aligned} \text{total current } I &= I_s + I_m = 4.95 \text{ mA} + 0.05 \text{ mA} \\ &= 5 \text{ mA} \end{aligned}$$

(c) At 0.25 FSD:

$$I_m = 0.25 \times 0.1 \text{ mA} = 0.025 \text{ mA}$$

$$\begin{aligned} V_m &= I_m R_m = 0.025 \text{ mA} \times 99 \Omega \\ &= 2.475 \text{ mV} \end{aligned}$$

$$I_s = \frac{V_m}{R_s} = \frac{2.475 \text{ mV}}{1 \Omega} = 2.475 \text{ mA}$$

$$\begin{aligned} \text{total current } I &= I_s + I_m = 2.475 \text{ mA} + 0.025 \text{ mA} \\ &= 2.5 \text{ mA} \end{aligned}$$

### 3. DC Ammeter (Cont.)

**Example 3.4:** A PMMC instrument has FSD of  $100\ \mu\text{A}$  and a coil resistance of  $1\ \text{k}\Omega$ . Calculate the required shunt resistance value to convert the instrument into an ammeter with (a) FSD =  $100\ \text{mA}$  and (b) FSD =  $1\ \text{A}$ .

**Solution**

(a) FSD =  $100\ \text{mA}$ :

$$V_m = I_m R_m = 100\ \mu\text{A} \times 1\ \text{k}\Omega = 100\ \text{mV}$$

$$I = I_s + I_m$$

$$I_s = I - I_m = 100\ \text{mA} - 100\ \mu\text{A} = 99.9\ \text{mA}$$


$$R_s = \frac{V_m}{I_s} = \frac{100\ \text{mV}}{99.9\ \text{mA}} = 1.001\ \Omega$$

(b) FSD =  $1\ \text{A}$ :

$$V_m = I_m R_m = 100\ \text{mV}$$

$$I_s = I - I_m = 1\ \text{A} - 100\ \mu\text{A} = 999.9\ \text{mA}$$

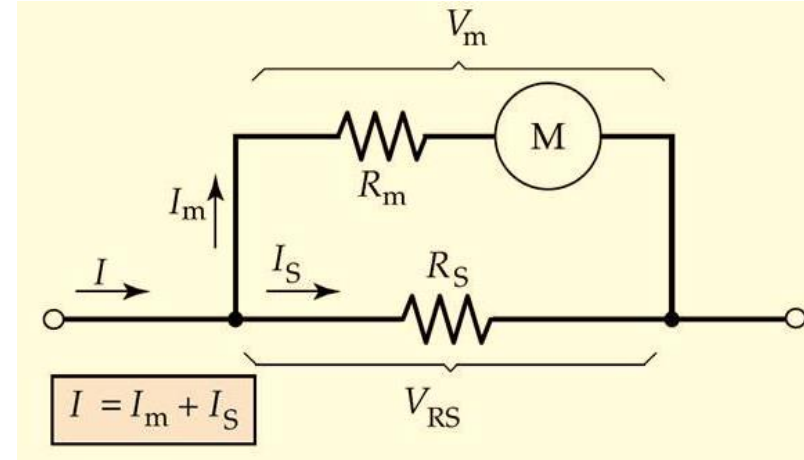
$$R_s = \frac{V_m}{I_s} = \frac{100\ \text{mV}}{999.9\ \text{mA}} = 0.10001\ \Omega$$



## 3.3 DC Ammeters: Swamping Resistance:

7


- ▶ The **moving coil** in a PMMC instrument is wound with thin **copper wire**, and its resistance can change with the **temperature**.
- ▶ Any such change in coil resistance will introduce an **error** in ammeter current measurements.
- ▶ To minimize the effect of temperature change on the PMMC resistance, a **swamping resistance** is connected in series with PMMC.
- ▶ The swamping resistance is made from constantan that have zero temperature coefficients.
- ▶ If the swamping resistance is nine times the coil resistance, a 1 % change in coil resistance would result in a total resistance change of 0.1 %.

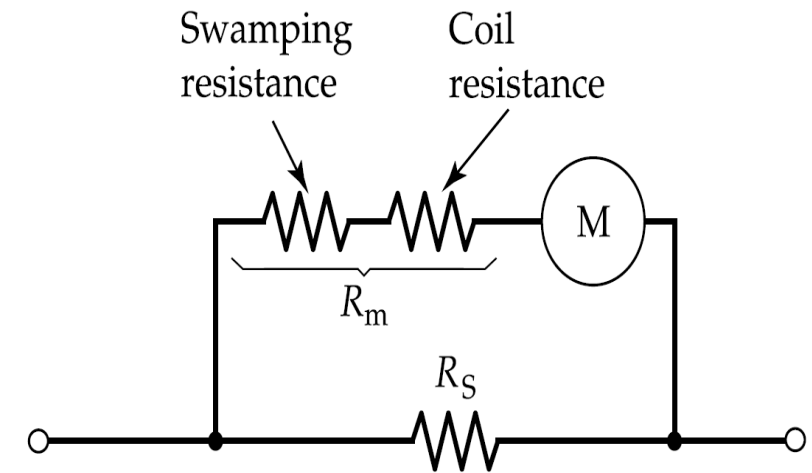


**Figure 4-2** A swamping resistance made of a material with a near-zero temperature coefficient can be connected in series with the coil of a PMMC instrument to minimize temperature errors.
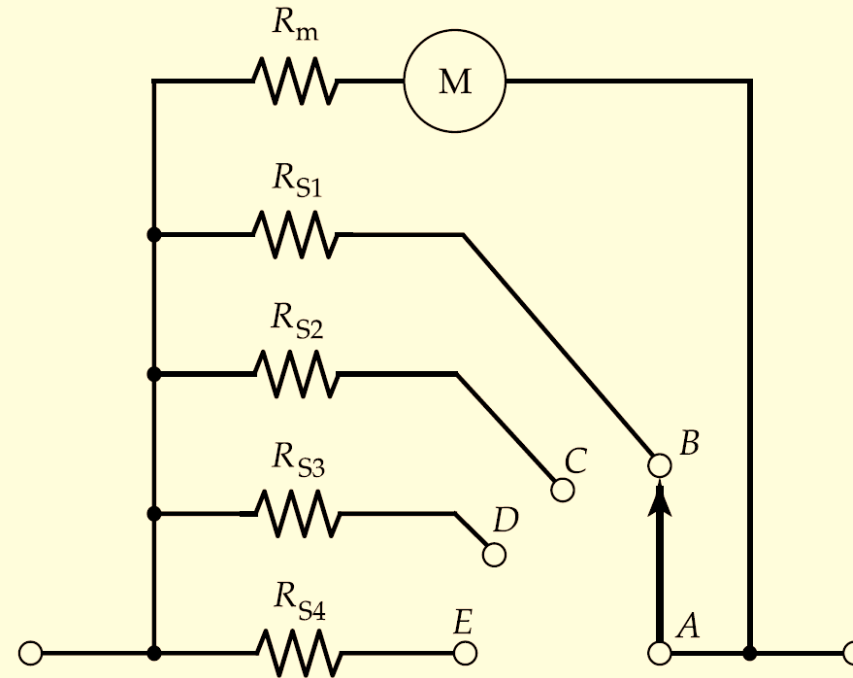
## 3.3 DC Ammeters: Multirange Ammeter:

- ▶ A rotary switch is employed to select anyone of several shunt resistances with different values.
- ▶ A **make-before-break** switch must be used **so that the instrument is not left without a shunt in parallel with it** even for a brief instant.
- ▶ A make before-break switch makes contact with the next terminal before it breaks contact with the previous terminal.



(a) Multirange ammeter circuit

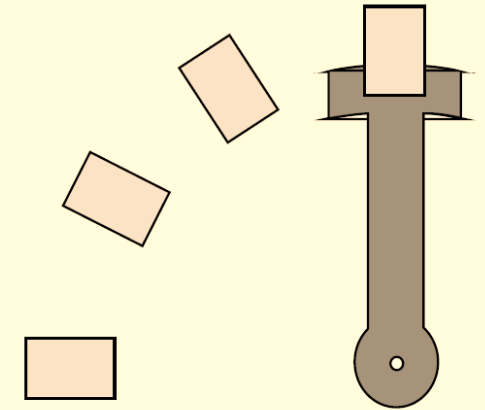


(b) Make-before-break switch

**Figure 4-3** A multirange ammeter consists of a PMMC instrument, several shunts, and a switch that makes contact with the next shunt before losing contact with the previous one when range switching.



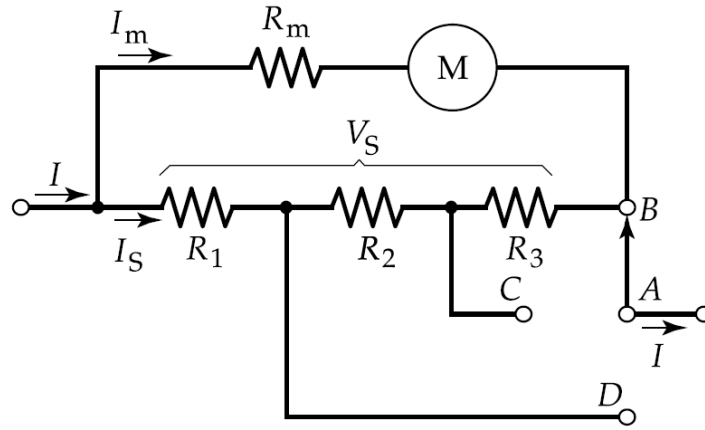
### 3.3 DC Ammeters: Multirange Ammeter (Cont.):



(a) Ayrton shunt and meter

$$(R_1 + R_2 + R_3) \parallel R_m$$

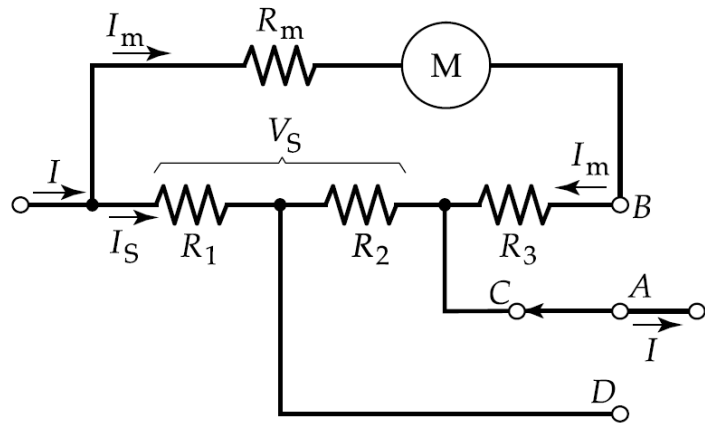

(b) Switch at terminal C

$$(R_1 + R_2) \parallel (R_m + R_3)$$

- Figures show **another method of protecting the deflection instrument** from excessive current during switching

**Figure 4-4** An Ayrton shunt used with an ammeter consists of several series-connected resistors all connected in parallel with the PMMC instrument. Range change is effected by switching between the resistor junctions.


## 3.3 DC Ammeters: Multirange Ammeter (Cont.):

10

Example 3.5:

A PMMC instrument has a three-resistor Ayrton shunt connected across it to make an ammeter, as in Figure 3-13. The resistance values are  $R_1 = 0.05 \Omega$ ,  $R_2 = 0.45 \Omega$ , and  $R_3 = 4.5 \Omega$ . The meter has  $R_m = 1 \text{ k}\Omega$  and  $\text{FSD} = 50 \mu\text{A}$ . Calculate the three ranges of the ammeter.

Solution

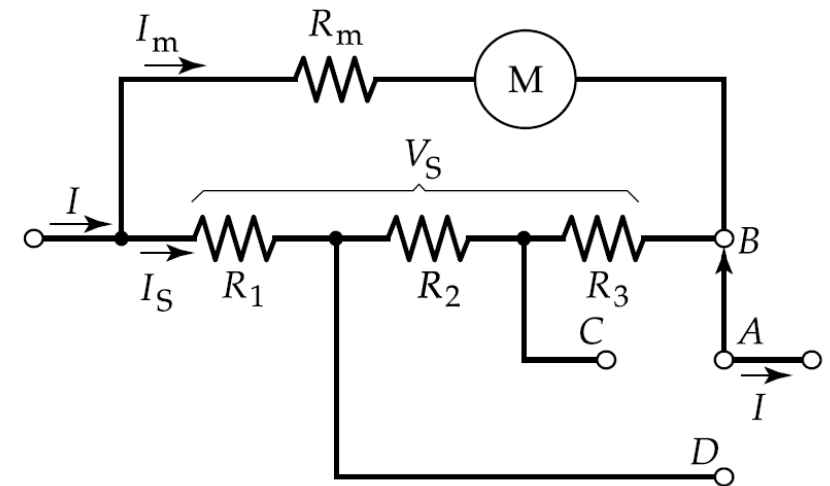

(a) Ayrton shunt and meter

# Solution

1. Switch at contact B:

$$V_s = I_m R_m = 50 \mu\text{A} \times 1 \text{ k}\Omega = 50 \text{ mV}$$

$$I_s = \frac{V_s}{R_1 + R_2 + R_3}$$
$$= \frac{50 \text{ mV}}{0.05 \Omega + 0.45 \Omega + 4.5 \Omega} = 10 \text{ mA}$$

$$I = I_m + I_s = 50 \mu\text{A} + 10 \text{ mA}$$
$$= 10.05 \text{ mA}$$

Ammeter range  $\approx 10 \text{ mA}$ .

3. Switch at contact D:

$$V_s = I_m(R_m + R_3 + R_2)$$
$$= 50 \mu\text{A}(1 \text{ k}\Omega + 4.5 \Omega + 0.45 \Omega)$$
$$\approx 50 \text{ mV}$$

$$I_s = \frac{V_s}{R_1} = \frac{50 \text{ mV}}{0.05 \Omega}$$
$$= 1 \text{ A}$$

$$I = 50 \mu\text{A} + 1 \text{ A}$$
$$= 1.00005 \text{ A}$$

Ammeter range  $\approx 1 \text{ A}$ .

2. Switch at contact C:

$$V_s = I_m(R_m + R_3)$$
$$= 50 \mu\text{A}(1 \text{ k}\Omega + 4.5 \Omega)$$
$$\approx 50 \text{ mV}$$

$$I_s = \frac{V_s}{R_1 + R_2}$$
$$= \frac{50 \text{ mV}}{0.05 \Omega + 0.45 \Omega}$$
$$= 100 \text{ mA}$$

$$I = 50 \mu\text{A} + 100 \text{ mA}$$
$$= 100.05 \text{ mA}$$


Ammeter range  $\approx 100 \text{ mA}$ .

# Chapter Outline:

- 1) Permanent Magnet Moving Coil (PMMC).
- 2) Galvanometer.
- 3) DC Ammeters
- 4) **DC Voltmeters**
- 5) Ohmmeters
- 6) AC Voltmeters
- 7) AC Ammeters

## 3.4 DC Voltmeter: Voltmeter Circuit

- ▶ The scale of the PMMC meter can be calibrated to **indicate voltage** since the **current through the coil is proportional to the voltage**.
- ▶ The PMMC is modified by adding a **series resistance** to measure **higher voltmeter range**.
- ▶ Because it increases the range of the voltmeter, the series resistance is termed a **multiplier resistance**.
- ▶ A multiplier resistance that is nine times the coil resistance will increase the voltmeter range by a factor of 10.

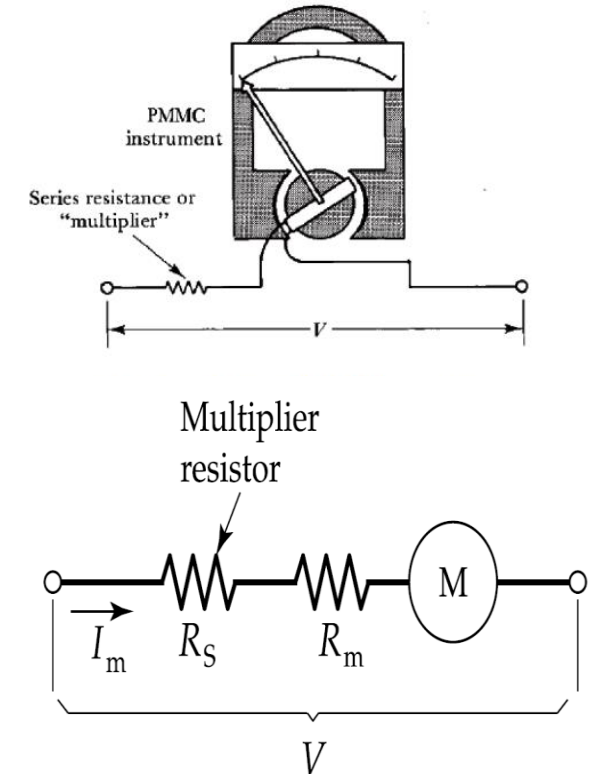


**Figure 4-5** A dc voltmeter is made up of a PMMC instrument and a series multiplier resistor. The meter current is directly proportional to the applied voltage, so that the meter scale can be calibrated to indicate the voltage.

## 3.4 DC Voltmeter (Cont.):
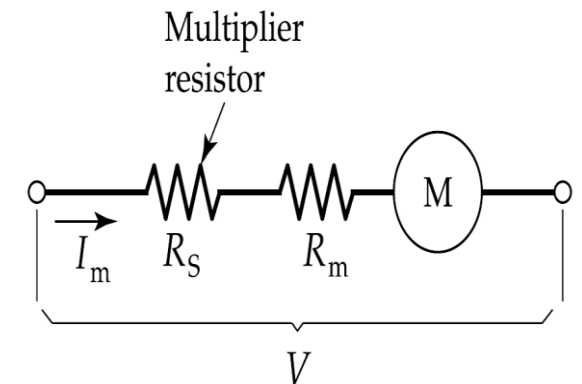
### Example 3.6:


- ▶ A PMMC instrument with FSD of  $100\ \mu\text{A}$  and a coil resistance of  $1\ \text{k}\Omega$  is to be converted into a voltmeter. **Determine** the required multiplier resistance if the voltmeter is to measure  $50\ \text{V}$  at full scale.

Also **calculate** the applied voltage when the instrument indicates  $0.8$ ,  $0.5$ , and  $0.2$  of FSD.



# Solution

15

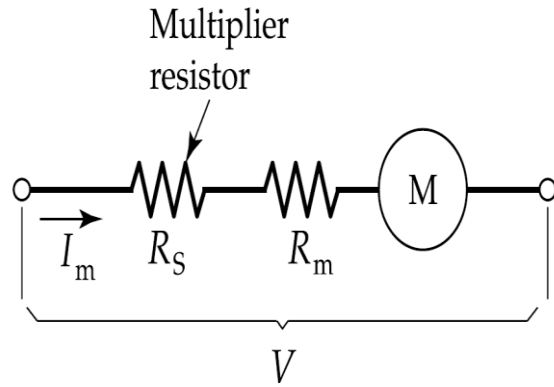

$$V = I_m(R_s + R_m)$$

$$R_s + R_m = \frac{V}{I_m}$$

$$R_s = \frac{V}{I_m} - R_m$$

For  $V = 50 \text{ V FSD}$ ,

$$I_m = 100 \mu\text{A}$$

$$R_s = \frac{50 \text{ V}}{100 \mu\text{A}} - 1 \text{ k}\Omega$$

$$= 499 \text{ k}\Omega$$

At 0.8 FSD:

$$I_m = 0.8 \times 100 \mu\text{A}$$

$$= 80 \mu\text{A}$$

$$V = I_m(R_s + R_m)$$

$$= 80 \mu\text{A}(499 \text{ k}\Omega + 1 \text{ k}\Omega)$$

$$= 40 \text{ V}$$

At 0.5 FSD:

$$I_m = 50 \mu\text{A}$$

$$V = 50 \mu\text{A}(499 \text{ k}\Omega + 1 \text{ k}\Omega)$$

$$= 25 \text{ V}$$

At 0.2 FSD:

$$I_m = 20 \mu\text{A}$$

$$V = 20 \mu\text{A}(499 \text{ k}\Omega + 1 \text{ k}\Omega)$$


$$= 10 \text{ V}$$

## 3.4 DC Voltmeter: Voltmeter Sensitivity:

The sensitivity of a voltmeter is equal to the resistance per volt:

$$S_v = \frac{R_m + R_s}{FSD} \quad \Omega/V$$

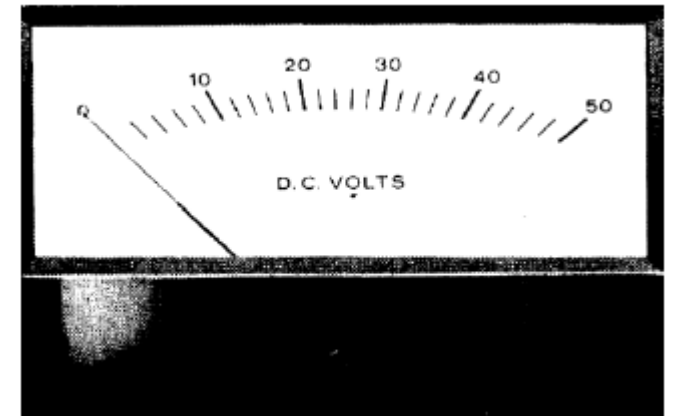- ❑ The voltmeter sensitivity is always specified by the manufacturer.
- ❑ If the sensitivity is known, the total voltmeter resistance is easily calculated as (sensitivity x range).
- ❑ Ideally, a voltmeter should have an extremely high resistance.
- ❑ If the voltmeter resistance is **too low**, it can alter the circuit voltage. This is known as **voltmeter loading effect**.







## 3.4 DC Voltmeter: Multirange Voltmeter

- ▶ It consists of a deflection instrument, several multiplier resistors, and a selector switch.
- ▶ Two possible circuits are proposed.
- ▶ Only one of the three multiplier resistors is connected in series with the meter at any time.
- ▶ The range of this voltmeter is

$$V = I_m(R_m + R)$$

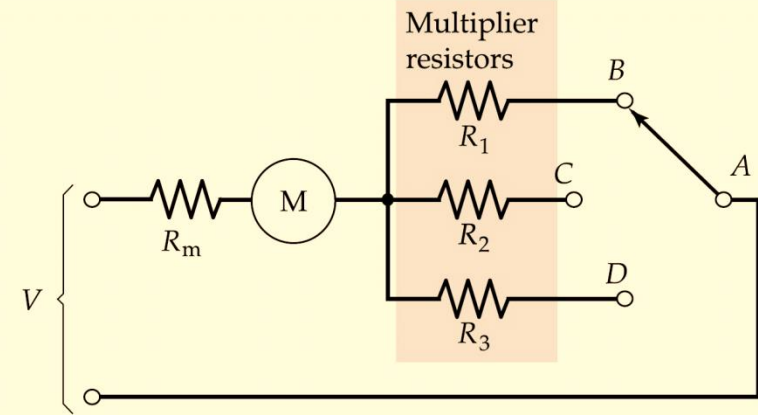

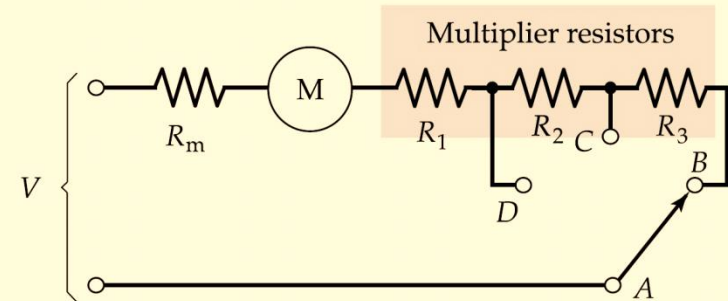(a) Multirange voltmeter circuit using switched multiplier resistors




(b) Multirange voltmeter circuit using series connected multiplier resistors

**Figure 4-6** A multirange voltmeter consists of a PMMC instrument, several multiplier resistors, and a switch for range selection. Individual or series-connected resistors may be used.


## Example 3.7:

A PMMC instrument with FSD =  $50 \mu\text{A}$  and  $R_m = 1700 \Omega$  is to be employed as a voltmeter with ranges of 10 V, 50 V, and 100 V. **Calculate** the required values of multiplier resistors for the two circuits

## Solution:

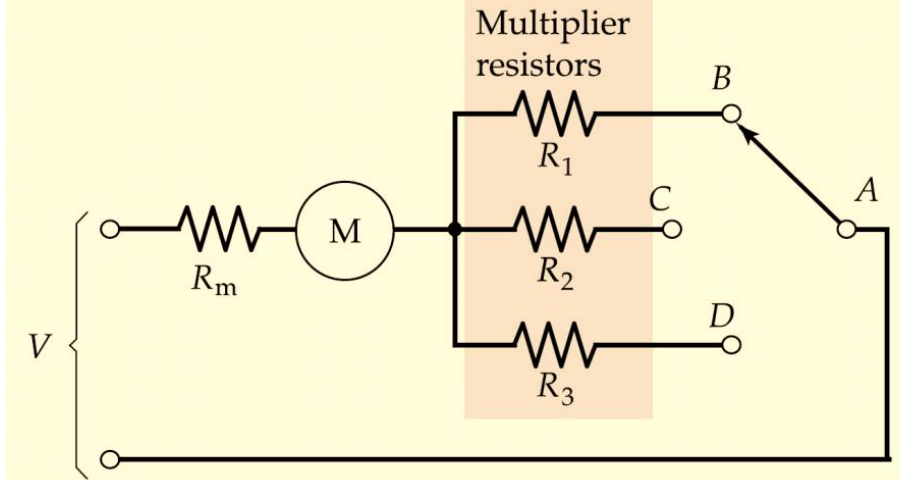

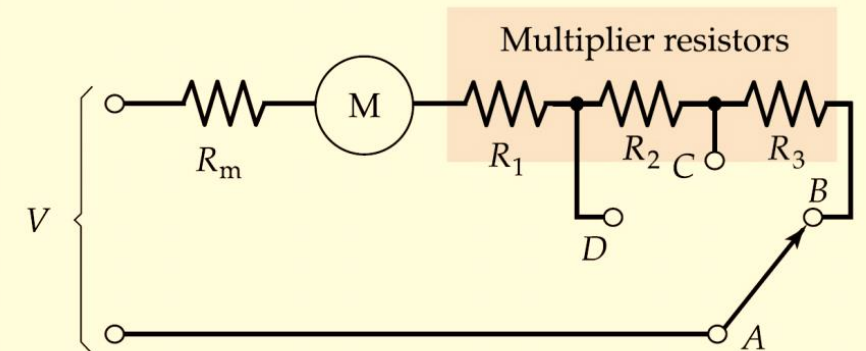(a) Multirange voltmeter circuit using switched multiplier resistors



(b) Multirange voltmeter circuit using series connected multiplier resistors

# Solution (Cont.)

$$R_m + R_1 = \frac{V}{I_m}$$

$$R_1 = \frac{V}{I_m} - R_m$$

$$= \frac{10 \text{ V}}{50 \mu\text{A}} - 1700 \Omega$$


$$= 198.3 \text{ k}\Omega$$

$$R_2 = \frac{50 \text{ V}}{50 \mu\text{A}} - 1700 \Omega$$

$$= 998.3 \text{ k}\Omega$$

$$R_3 = \frac{100 \text{ V}}{50 \mu\text{A}} - 1700 \Omega$$

$$= 1.9983 \text{ M}\Omega$$

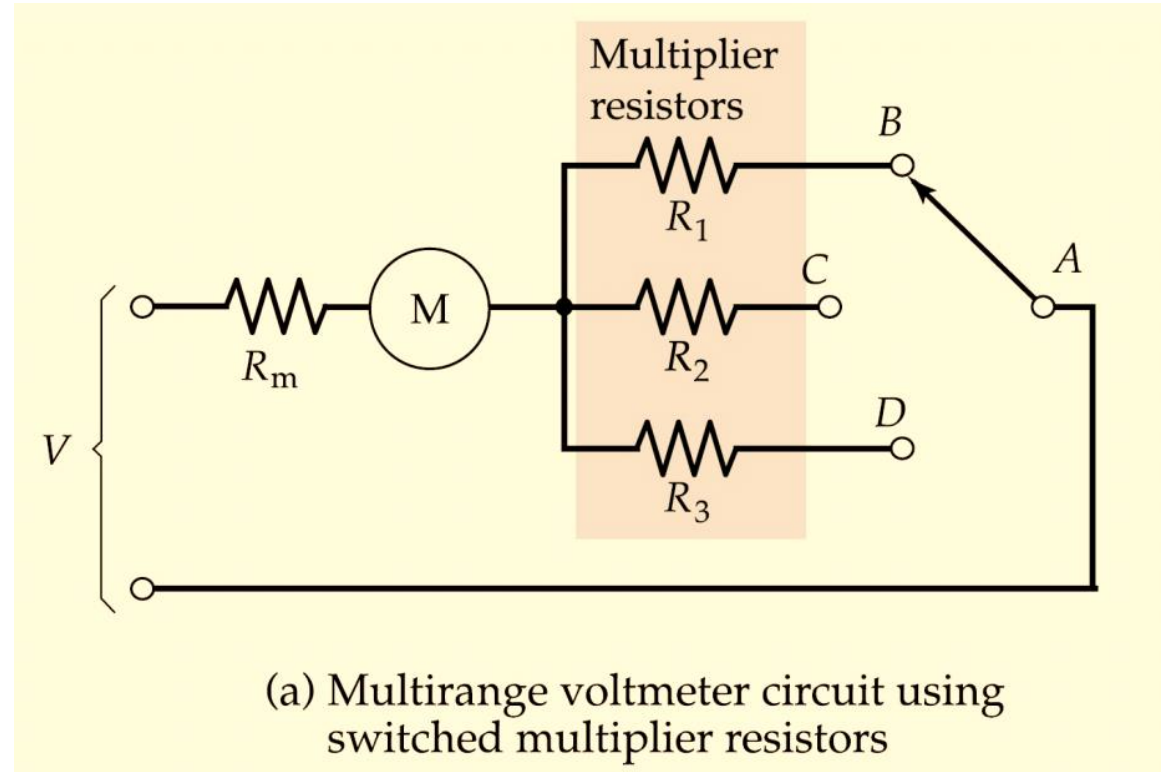

# Solution (Cont.)

20

$$R_m + R_1 = \frac{V_1}{I_m}$$

$$R_1 = \frac{V_1}{I_m} - R_m$$

$$= \frac{10 \text{ V}}{50 \mu\text{A}} - 1700 \Omega$$

$$= 198.3 \text{ k}\Omega$$

$$R_m + R_1 + R_2 = \frac{V_2}{I_m}$$

$$R_2 = \frac{V_2}{I_m} - R_1 - R_m$$

$$= \frac{50 \text{ V}}{50 \mu\text{A}} - 198.3 \text{ k}\Omega - 1700 \Omega$$


$$= 800 \text{ k}\Omega$$

$$R_m + R_1 + R_2 + R_3 = \frac{V_3}{I_m}$$

$$R_3 = \frac{V_3}{I_m} - R_2 - R_1 - R_m$$

$$= \frac{100 \text{ V}}{50 \mu\text{A}} - 800 \text{ k}\Omega - 198.3 \text{ k}\Omega - 1700 \Omega$$

$$= 1 \text{ M}\Omega$$

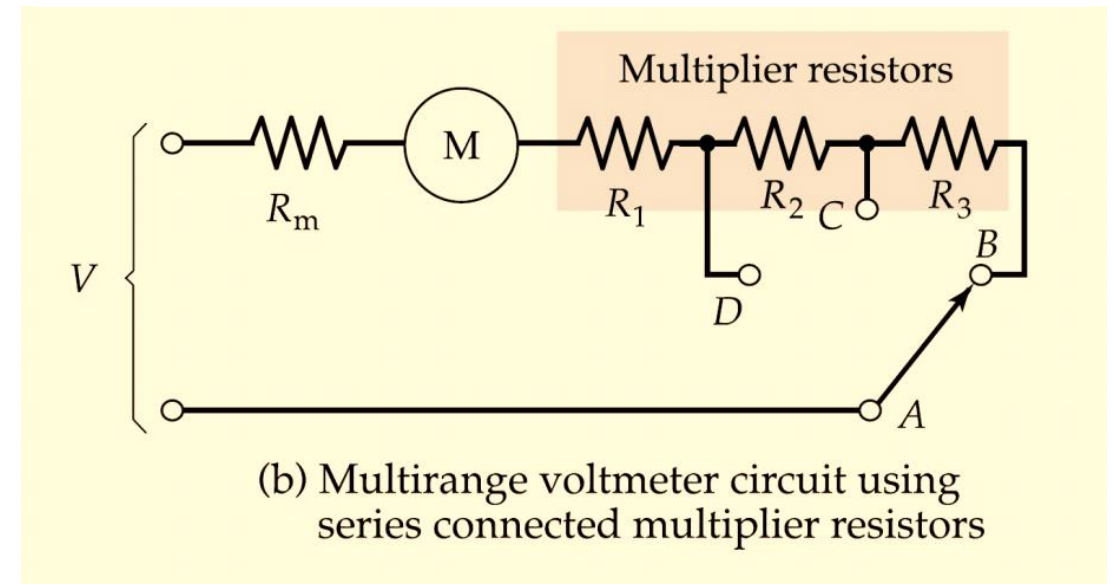


# Chapter Outline:

- 1) Permanent Magnet Moving Coil (PMMC).
- 2) Galvanometer.
- 3) DC Ammeters
- 4) DC Voltmeters
- 5) **Ohmmeters**
- 6) AC Voltmeters
- 7) AC Ammeters

## 3.5 Ohmmeter: Basic Circuit: Series Ohmmeter:

- ▶ The series ohmmeter consists of a PMMC with a battery voltage  $E_b$  connected in series.
- ▶ The unknown resistance is connected between terminals, A and B.
- ▶ A standard (known) resistance  $R_1$  is connected to protect the device from high current when low resistance is connected.

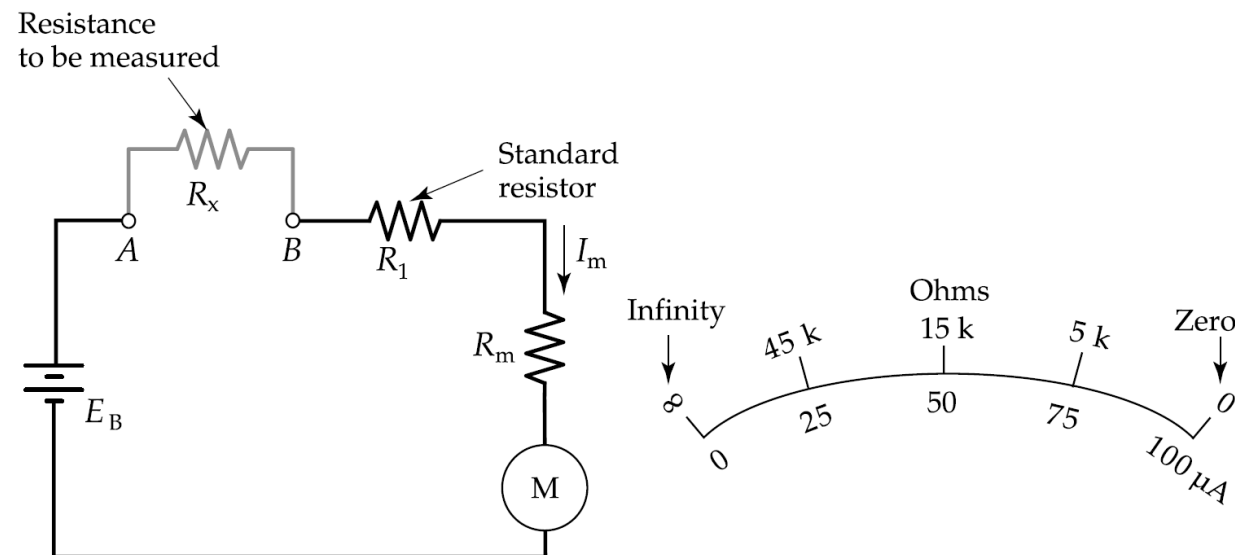

**Figure 4-11** Basic series ohmmeter circuit consisting of a PMMC instrument and a series-connected standard resistor ( $R_1$ ). When the ohmmeter terminals are shorted ( $R_x = 0$ ) meter FSD occurs. At half-scale deflection  $R_x = R_1$ , and at zero deflection the terminals are open-circuited.

$$I_m = \frac{E_b}{R_1 + R_x + R_m}$$

If  $R_x = 0$ ,  $I_m = FSD$  and if  $R_x = \infty$ ,  $I_m = 0$ .


If  $0 < R_x < \infty$ ,  $FSD < I_m < 0$

## Example 3.8:

Series ohmmeter shown in the figure is made up of a 1.5 V battery and  $(R_1 + R_m) = 15 \text{ k}\Omega$ .

(a) Determine the instrument indication when  $R_x = 0$ .

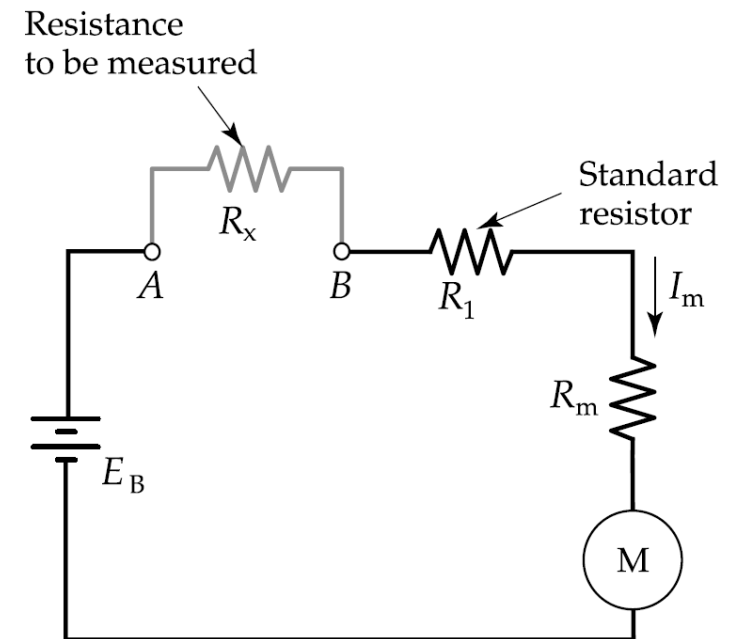(b) Determine how the resistance scale should be marked at 0.5 FSD, 0.25 FSD, and 0.75 FSD.



# Solution

24

$$(a) I_m = \frac{E_b}{R_x + R_l + R_m} = \frac{1.5 \text{ V}}{0 + 15 \text{ k}\Omega}$$
$$= 100 \mu\text{A (FSD)}$$

(b) At 0.5 FSD:

$$I_m = \frac{100 \mu\text{A}}{2} = 50 \mu\text{A}$$

$$R_x + R_l + R_m = \frac{E_b}{I}$$

$$R_x = \frac{E_b}{I_m} - (R_l + R_m)$$

$$= \frac{1.5 \text{ V}}{50 \mu\text{A}} - 15 \text{ k}\Omega$$


$$= 15 \text{ k}\Omega$$

$$(c) \text{ At 0.25 FSD: } I_m = \frac{100 \mu\text{A}}{4} = 25 \mu\text{A}$$

$$R_x = \frac{1.5 \text{ V}}{25 \mu\text{A}} - 15 \text{ k}\Omega$$
$$= 45 \text{ k}\Omega$$

$$(d) \text{ At 0.75 FSD: } I_m = 0.75 \times 100 \mu\text{A} = 75 \mu\text{A}$$

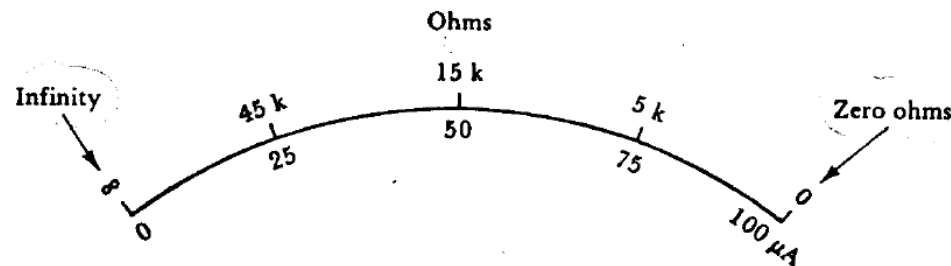
$$R_x = \frac{1.5 \text{ V}}{75 \mu\text{A}} - 15 \text{ k}\Omega$$
$$= 5 \text{ k}\Omega$$





## 3.5 Ohmmeter: Ohmmeter with Zero Control:

- ▶ In the series ohmmeter, if the battery voltage drops, the instrument scale no longer gives correct reading.
- ▶ An adjustable resistor  $R_2$  is connected in parallel with the meter to adjust the falling battery voltage.
- ▶ Ohmmeter is calibrated by making  $R_x = 0$  and adjusting  $R_2$  to give FSD (0 )

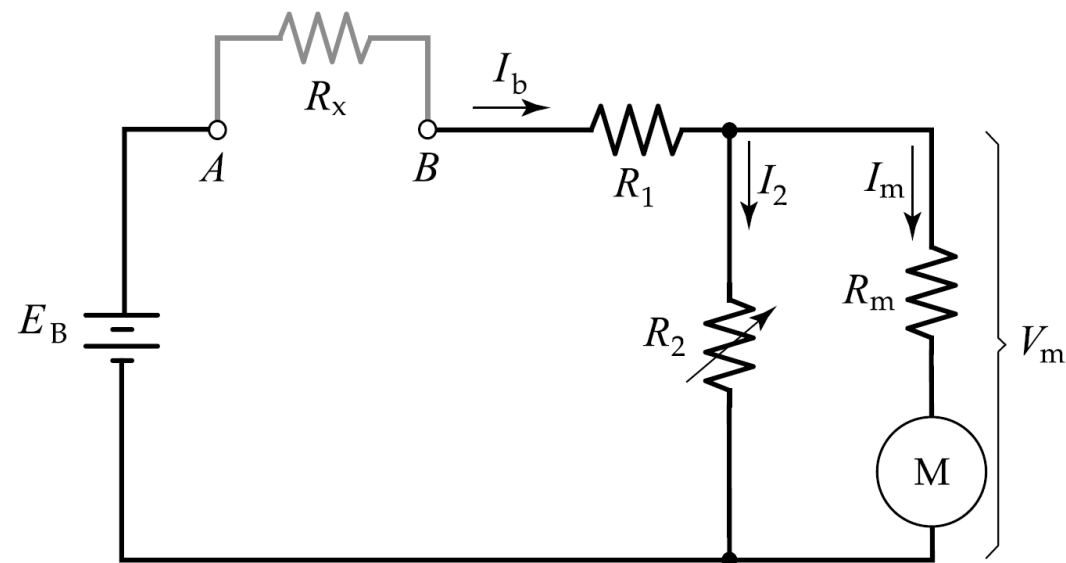


**Figure 4-12** An adjustable resistor ( $R_2$ ) connected in parallel with the meter provides an ohmmeter zero control. The ohmmeter terminals are initially short-circuited and the zero control is adjusted to give a zero-ohm reading. This eliminates errors due to variations in the battery voltage.

$$I_m = V_m / R_m, \quad V_m = I_b \cdot (R_2 // R_m)$$

$$I_m = I_b \cdot \frac{R_2 // R_m}{R_m}$$

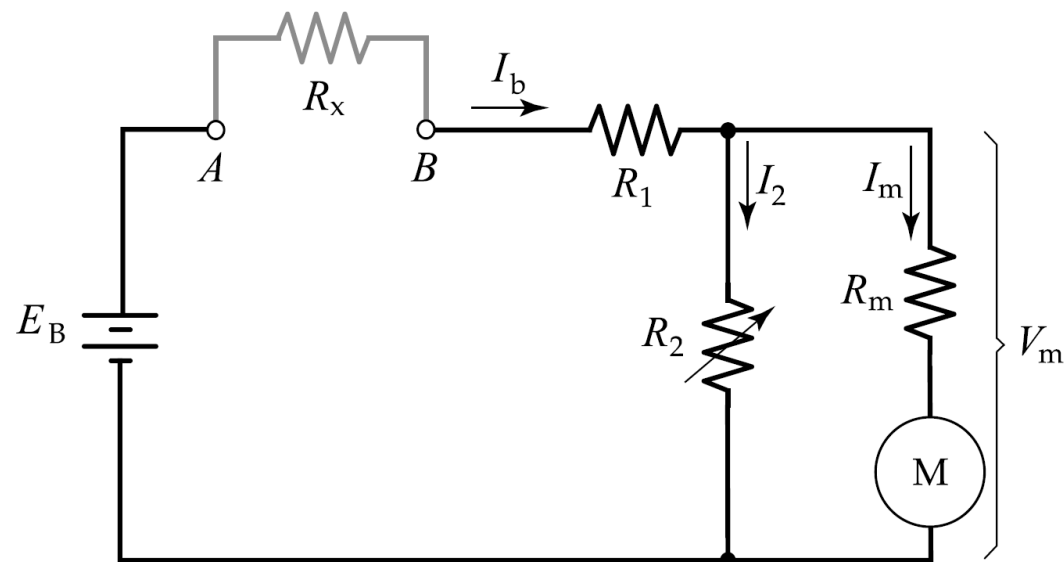
## Example 3.8:

The ohmmeter circuit in the figure has  $E_b = 1.5$  V,  $R_1 = 15$  k $\Omega$ ,  $R_m = R_2 = 50$   $\Omega$ , and meter FSD = 50  $\mu$ A. **Determine** the ohmmeter scale reading at 0.5 FSD, and **determine** the new resistance value that  $R_2$  must be adjusted to when  $E_b$  falls to 1.3 V. Also, recalculate the value of  $R_x$  at 0.5 FSD when  $E_b = 1.3$  V.



# Solution

27

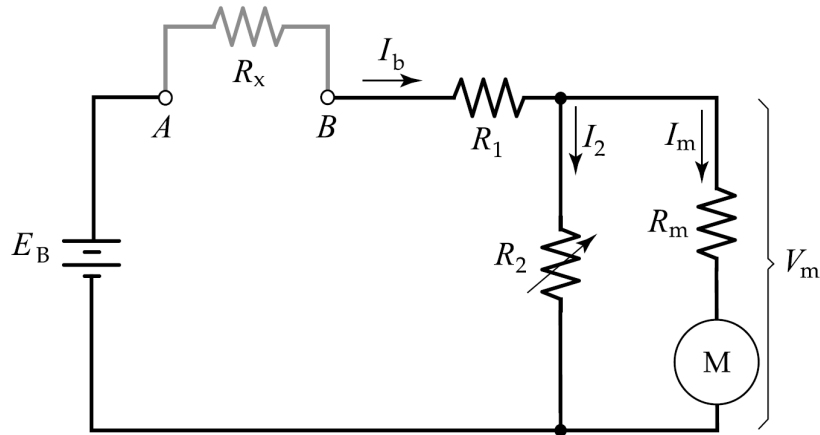

At 0.5 FSD, with  $E_b = 1.5 \text{ V}$ ,

$$V_m = I_m \times R_m = 25 \mu\text{A} \times 50 \Omega \\ = 1.25 \text{ mV}$$

$$I_2 = \frac{V_m}{R_2} = \frac{1.25 \text{ mV}}{50 \Omega} \\ = 25 \mu\text{A}$$

$$I_b = I_2 + I_m = 25 \mu\text{A} + 25 \mu\text{A} \\ = 50 \mu\text{A}$$

$$R_x + R_1 \approx \frac{E_b}{I_b} = \frac{1.5 \text{ V}}{50 \mu\text{A}}$$

$$= 30 \text{ k}\Omega$$

$$R_x = 30 \text{ k}\Omega - R_1 = 30 \text{ k}\Omega - 15 \text{ k}\Omega$$

$$= 15 \text{ k}\Omega$$

With  $R_x = 0$  and  $E_b = 1.3 \text{ V}$ ,

$$I_b \approx \frac{E_b}{R_x + R_1} = \frac{1.3 \text{ V}}{0 + 15 \text{ k}\Omega} \\ = 86.67 \mu\text{A}$$

$$I_2 = I_b - I_{m(\text{FSD})} = 86.67 \mu\text{A} - 50 \mu\text{A} \\ = 36.67 \mu\text{A}$$

$$V_m = I_m R_m = 50 \mu\text{A} \times 50 \Omega \\ = 2.5 \text{ mV}$$

$$R_2 = \frac{V_m}{I_2} = \frac{2.5 \text{ mV}}{36.67 \mu\text{A}} \\ = 68.18 \Omega$$

# Solution (Cont.)

At 0.5 FSD, with  $E_b = 1.3 \text{ V}$ ,

$$\begin{aligned}V_m &= I_m \times R_m = 25 \mu\text{A} \times 50 \Omega \\ &= 1.25 \text{ mV}\end{aligned}$$

$$\begin{aligned}I_2 &= \frac{V_m}{R_2} = \frac{1.25 \text{ mV}}{68.18 \Omega} \\ &= 18.33 \mu\text{A}\end{aligned}$$

$$\begin{aligned}I_b &= I_2 + I_m = 18.33 \mu\text{A} + 25 \mu\text{A} \\ &= 43.33 \mu\text{A}\end{aligned}$$

$$\begin{aligned}R_x + R_1 &= \frac{E_b}{I_b} = \frac{1.3 \text{ V}}{43.33 \mu\text{A}} \\ &= 30 \text{ k}\Omega\end{aligned}$$

$$\begin{aligned}R_x &= 30 \text{ k}\Omega - R_1 = 30 \text{ k}\Omega - 15 \text{ k}\Omega \\ &= 15 \text{ k}\Omega\end{aligned}$$



**END OF LECTURE**

**BEST WISHES**