



POWER ELECTRONICS I

AC-DC Converters

Three-Phase Rectifiers

Dr. Islam Mohamed


Electrical Engineering Department
Shoubra Faculty of Engineering, Benha University

Islam.ahmed@fen.bu.edu.eg

Questions Lecture two

- Q₁) what are the rating values of the Thyristors in the converter?
- Q₂) Draw the waveforms of the Thyristor voltage and current
- Q₃) What is the control range of α in the pervious case studies?
- Q₄) Write an expression of the instantaneous load current for all pervious case studies
- Q₅) what are the rating values of the freewheeling diode in the three-phase half-wave control rectifier with highly inductive loads?

Three-phase rectifier Plan

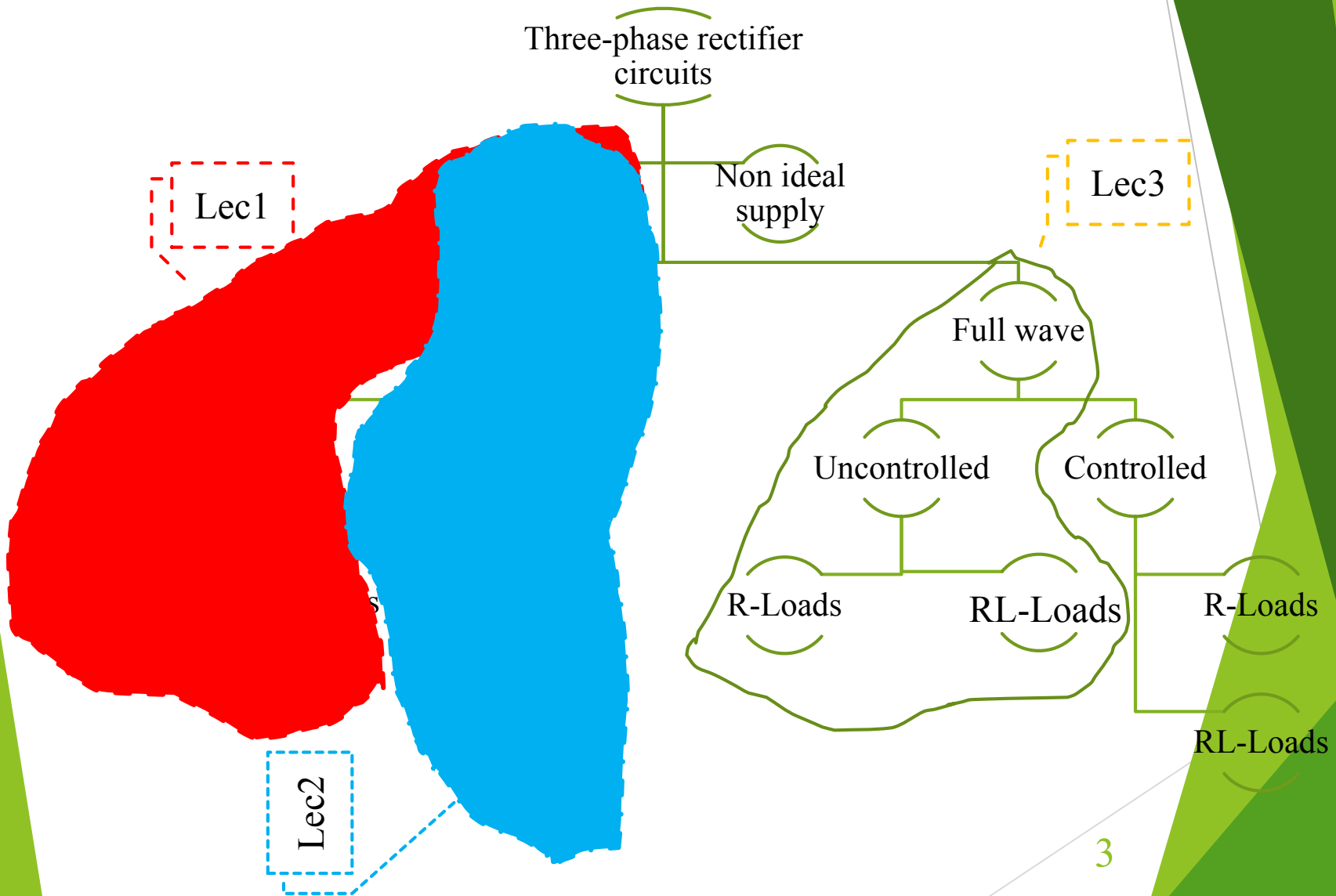

Lecture Four: Three-phase Full wave uncontrolled rectifiers circuits

Construction

- Circuit diagram
- Components

Operation

- Output waveforms
- R-load and Highly inductive load

Analysis

- Analysis of the circuit with R-load
- Analysis of the circuit with highly inductive load

End

- Summery
- Questions

General


Why three-phase Full-wave rectifiers ?

- Three-phase full wave rectifiers provide higher average output voltage compared to the all pervious rectifier circuits.
- The harmonics frequency of output voltage ripples in a three-phase full wave rectifier circuits is higher compared to the pervious rectifier. Thus, the three-phase rectifier requires a smaller filter with a lower cost.
- Three-phase full wave rectifier circuits don't produce dc current component in the source. so the transformer is not saturated.
- The rectification efficiency is the highest

High
efficiency


Large DC
output

Less
output
ripples

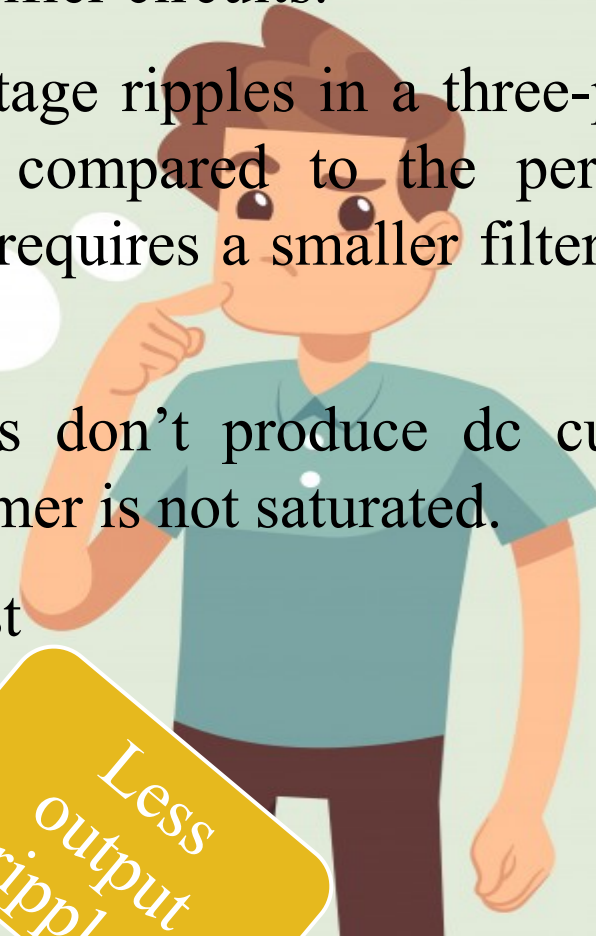

Disadvantages:

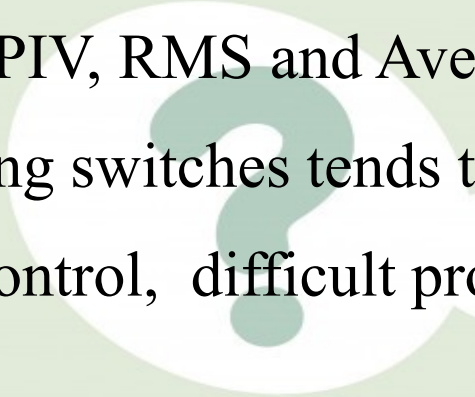- Three-phase rectifiers require **higher rating** of the power electronics switches (Diodes and Thyristors)
 - ✓ PIV, RMS and Average Current,....
- Higher rating switches tends to high cost and large size.
- Complex control, difficult protection, and large heatsink,




High Cost

High Switch
Rating

Complex
Control

Construction

Power circuit and its components

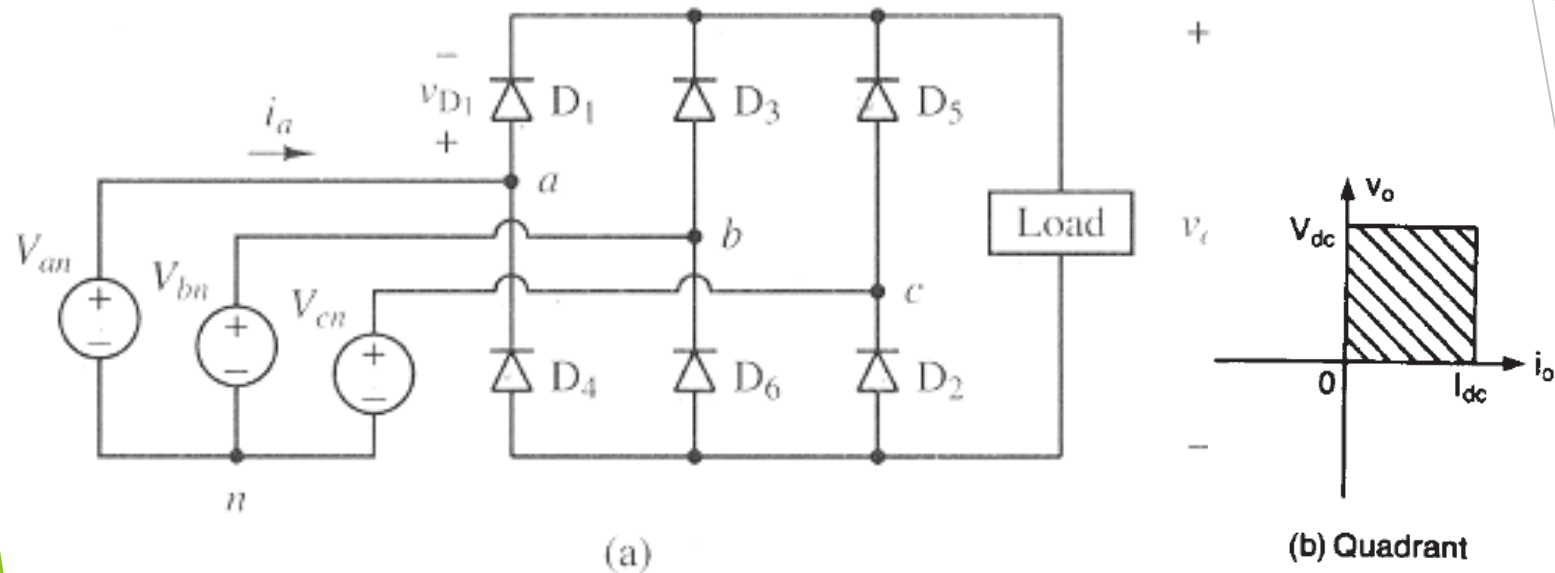


- 1- Two diodes must be forward at any instant (D_1, D_3, D_5) with (D_2, D_4, D_6).
- 2- Line voltage will be applied to the load at any instant.
- 3- A transition of the highest line-to-line voltage must take place every $360^\circ / 6 = 60^\circ$

Operation

Output Voltage waveforms

R-Loads



Highly inductive Loads

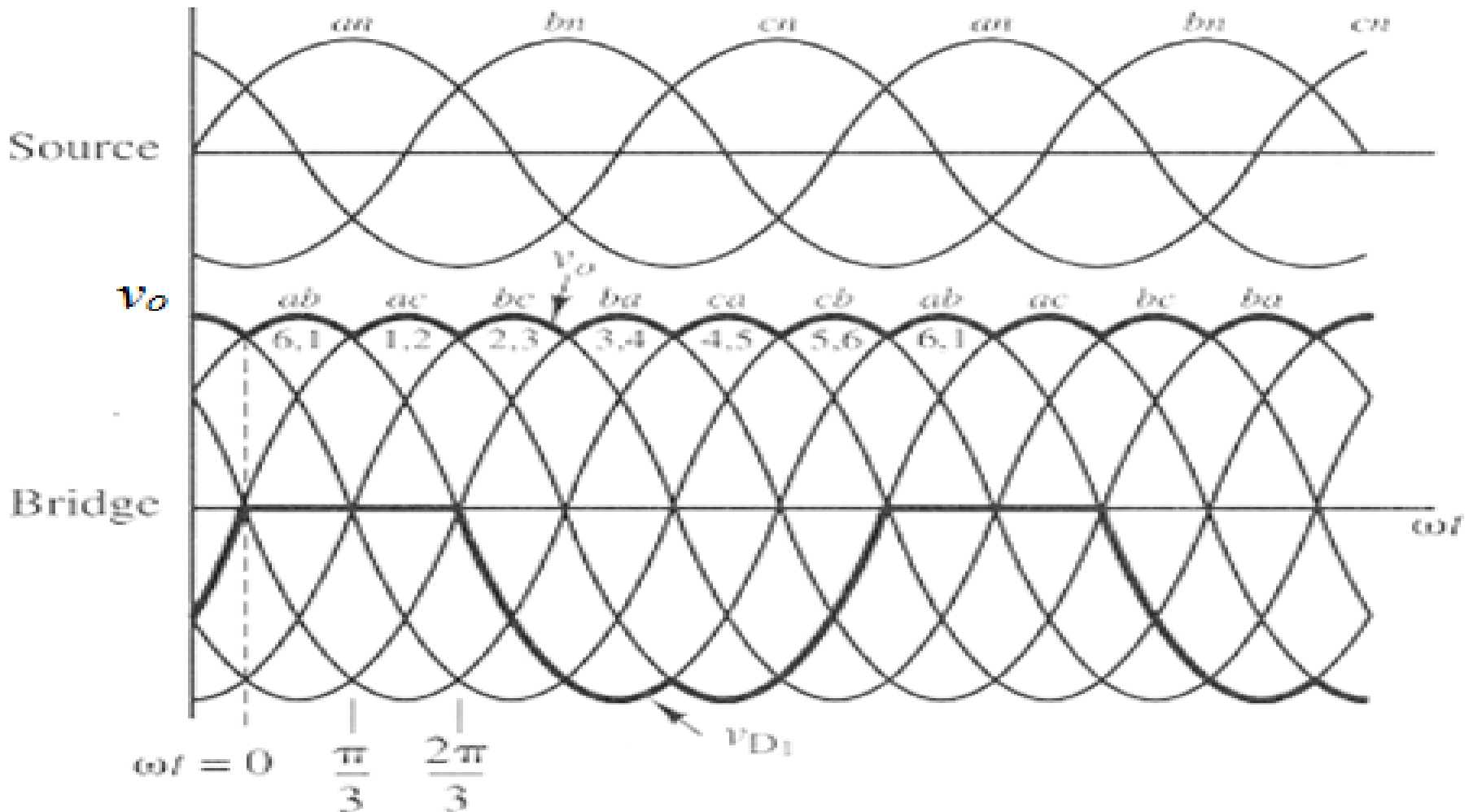



Operation

Currents waveforms

R-Loads

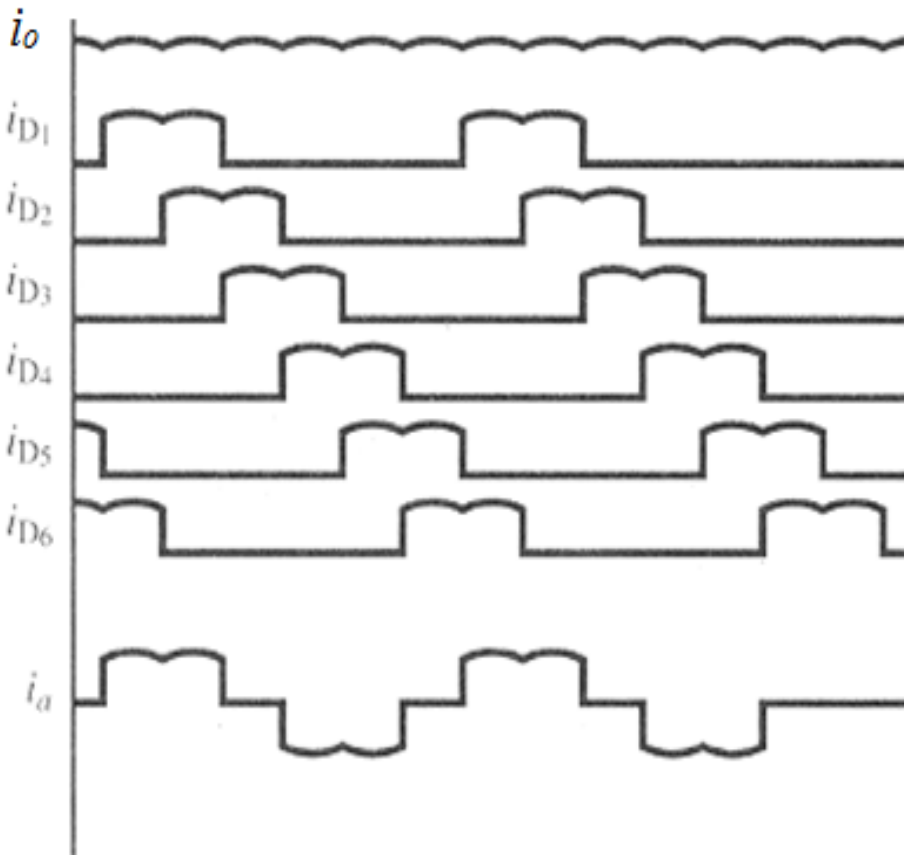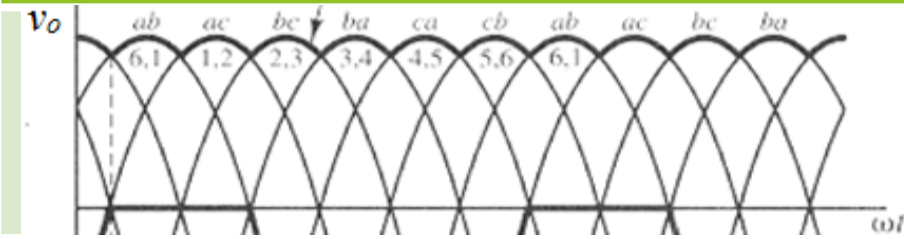

Highly inductive Loads

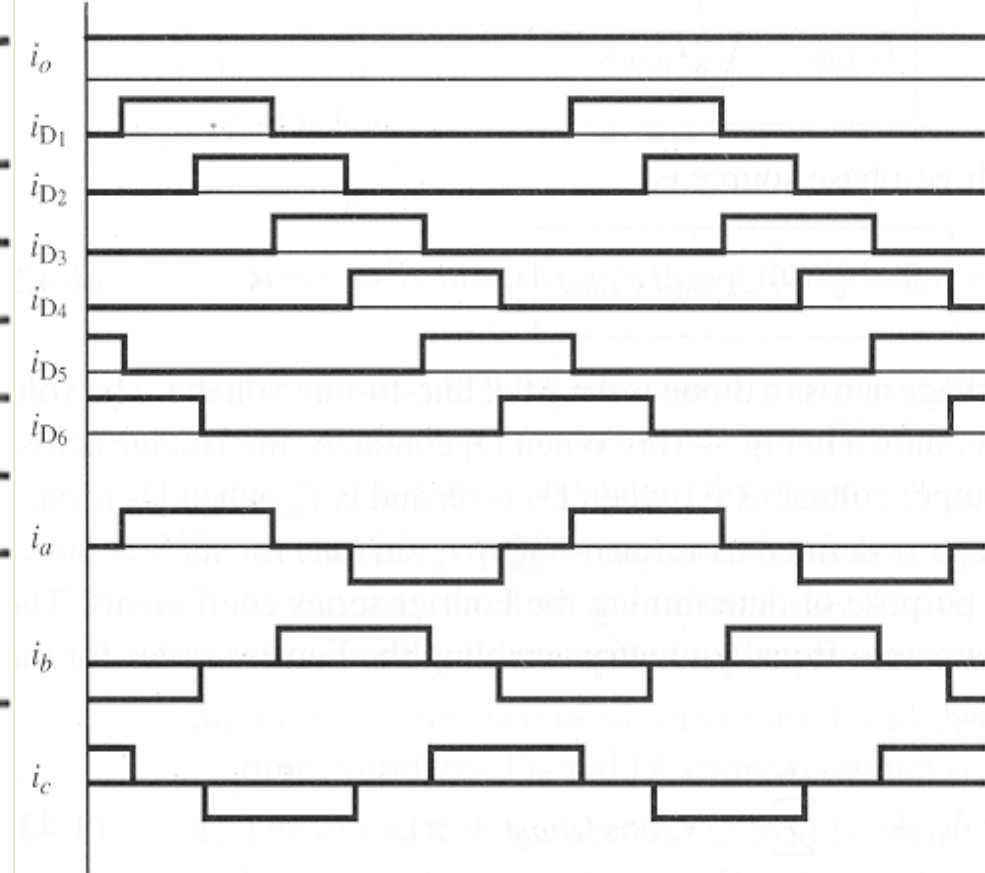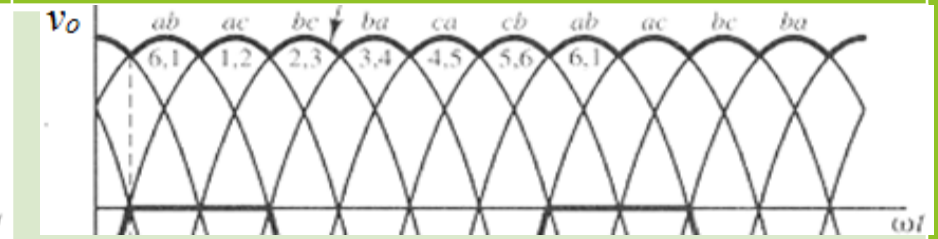


Analysis:

1- Supply voltages:

$$V_{ab}(\omega t) = V_{m1} \sin(\omega t + \pi/6), \quad V_{bc}(\omega t) = V_{m1} \sin(\omega t - \pi/2), \quad V_{ca}(\omega t) = V_{m1} \sin(\omega t - 7\pi/6)$$

2- Output average voltage:

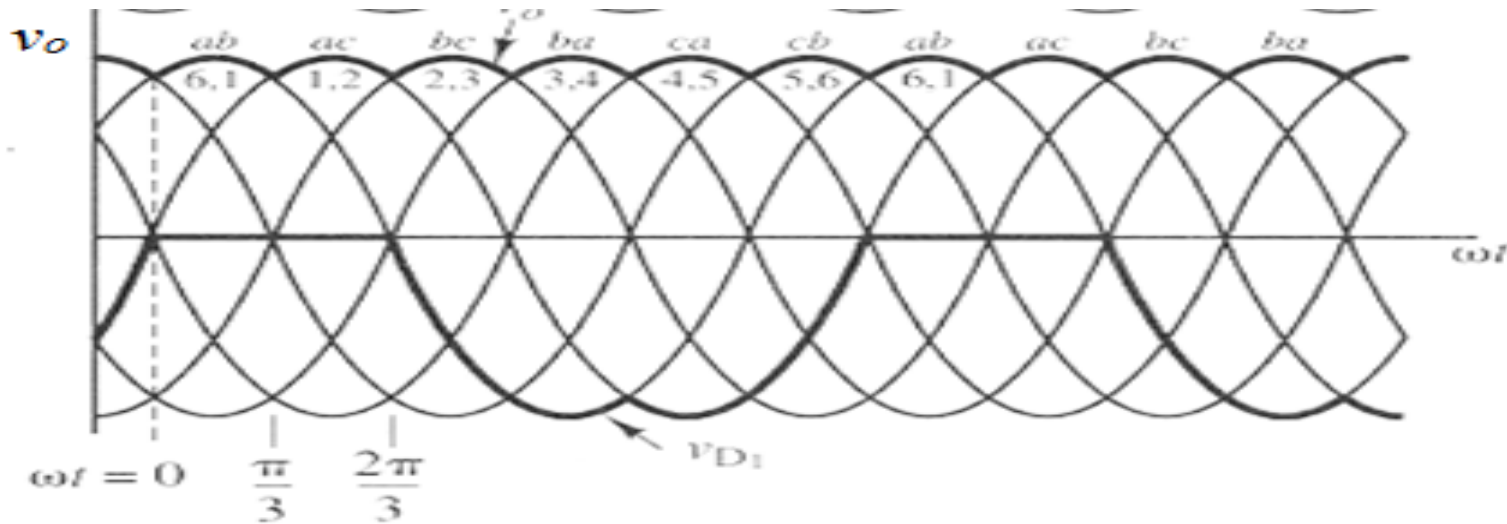

$$V_{o.avg} = \frac{1}{\pi/3} \int_{\pi/6}^{\pi/2} v_{ab} d\omega t = \frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{m,L-L} \sin \omega t d(\omega t) = \frac{3V_{m,L-L}}{\pi}$$
$$= 0.95V_{m,L-L}$$

Analysis:

3- RMS Load voltage

- Since the output voltage is periodic with period $1/6$ of the ac supply voltage, the harmonics in the output are of order $6k\omega$, $k=1,2,3,\dots$
- Advantage : output is inherently like a dc voltage, and the high-frequency low-amplitude harmonics enable filters to be effective.

$$v_o(t) = V_{o,avg} + \sum_{n=6,12,18,\dots}^{\infty} V_n \cos(n\omega_0 t + \pi)$$

$$V_n = \frac{6 V_{m,L-L}}{\pi(n^2 - 1)}, \quad n = 6, 12, 18, \dots$$

$$V_{o,rms} = \sqrt{V_{o,avg}^2 + \left(\frac{V_6}{\sqrt{2}}\right)^2 + \left(\frac{V_{12}}{\sqrt{2}}\right)^2}$$

Analysis:

4- Average load current For R & RL-Loads

For both cases:

$$I_{o, avg} = \frac{V_{o, avg}}{R}$$


5- RMS Load current

For Resistive load:

$$I_{o, rms} = V_{o, rms} / R$$

For Highly inductive load:

$$I_{o, rms} = V_{o, rms} / Z$$

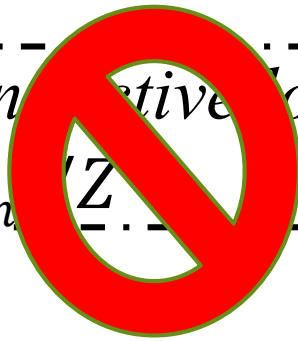

For Highly inductive load:

$$I_{o, rms} = I_{o, avg}$$



Analysis:

6- Diode currents

- Each diode conducts one-third of the time, resulting in

$$I_{D,avg} = \frac{1}{3} I_{o,avg}$$
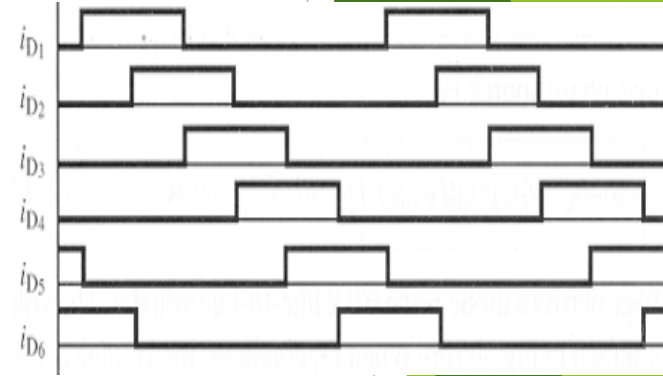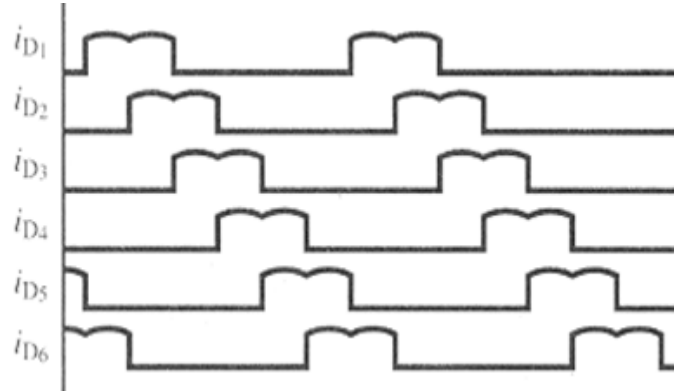
$$I_{D,rms} = \frac{1}{\sqrt{3}} I_{o,rms}$$




7- RMS supply current

$$i_a = i_{D1} - i_{D4}$$

$$i_b = i_{D3} - i_{D6}$$

$$i_c = i_{D5} - i_{D2}$$

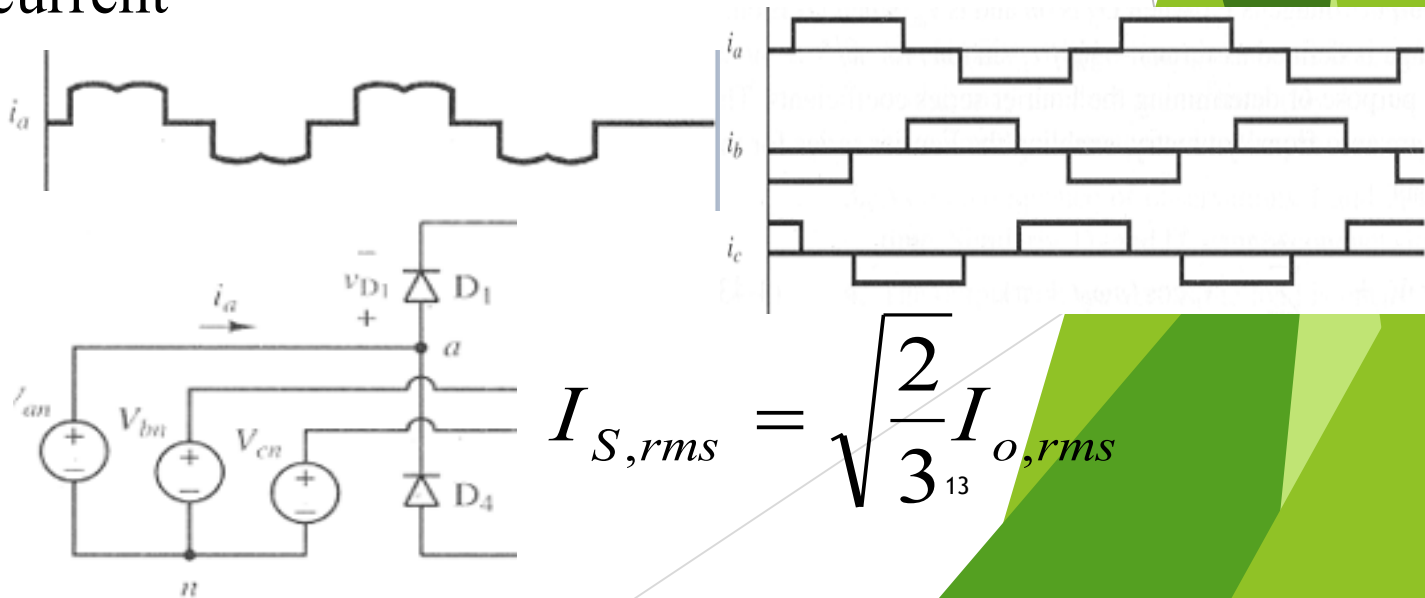

$$I_{S,rms} = \sqrt{\frac{2}{3}} I_{o,rms}$$

Analysis:


8- The harmonics in the supply currents

- Supply current waveform is: odd, $f(x)=-f(x+180)$, so using Fourier


The fundamental frequency of the ac system and harmonics of order:

$$6k \pm 1 \quad \text{where } k=1,2,3,\dots$$
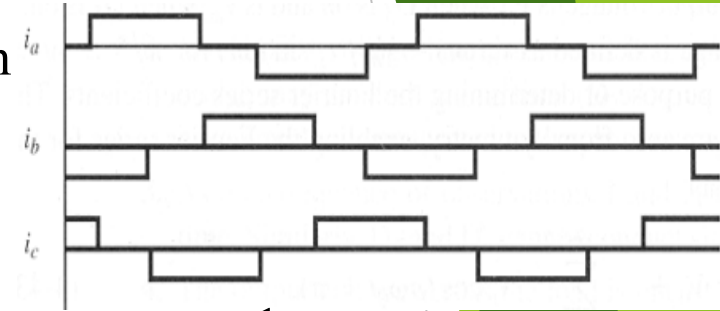
$$i_a = \frac{2\sqrt{3}}{\pi} I_o \left(\cos \omega_o t - \frac{1}{5} \cos 5\omega_o t + \frac{1}{7} \cos 7\omega_o t - \frac{1}{11} \cos 11\omega_o t + \frac{1}{13} \cos 13\omega_o t + \dots \right)$$



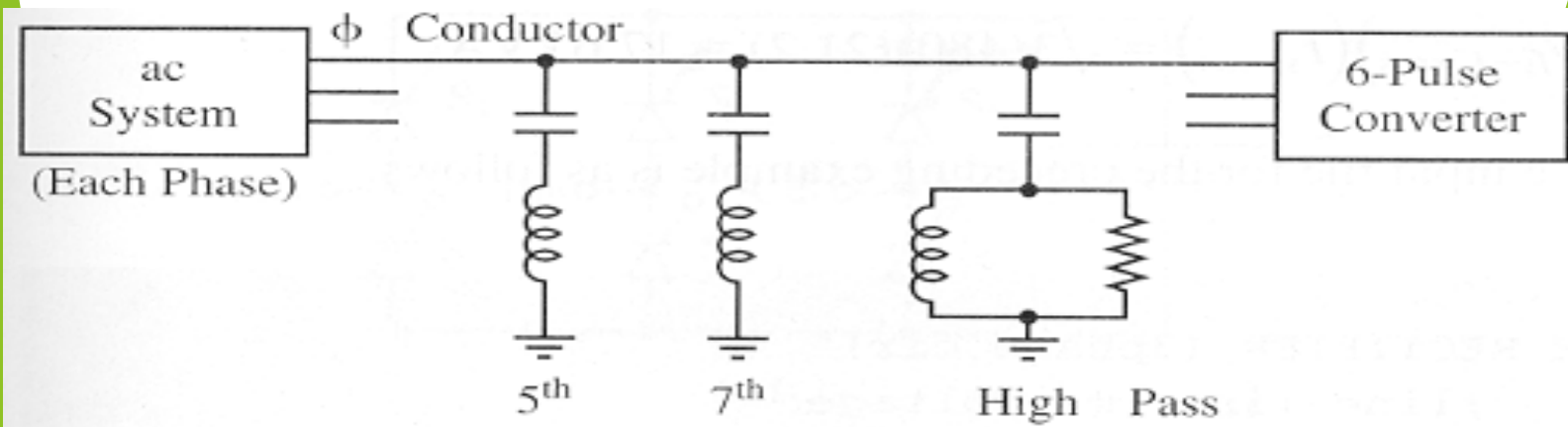- To prevent harmonic currents to enter the ac system.
 - ✓ Resonant filters for 5th and 7th harmonics.
 - ✓ High-pass filters for higher order harmonics.



Analysis:

9- Output power

$$P_S = P_O = I_{o,rms}^2 R$$

For R & RL Loads??



10- Input power factor

$$pf = \frac{P_o}{S} = \frac{I_{o,rms}^2 R}{3V_s I_{s,rms}}$$



Remember $I_{s,rms} = \sqrt{2/3} I_{o,rms}$

11- Converter efficiency

$$\eta = \frac{P_{dc}}{P_{o,rms}} = \frac{V_{o,avg} I_{o,avg}}{V_{o,rms} I_{o,rms}}$$

Questions

- Q₁) what are the rating values of the Diodes in the converter?
- Q₂) Calculate the rectification efficiency for R and highly inductive loads.
- Q₃) what happen to the load voltage and current waveforms if a freewheeling diode is connected incase RL-loads?
- Q₄) what happen to the load voltage and current waveforms if a freewheeling diode is connected incase RL-loads?