



POWER ELECTRONICS I

AC-DC Converters

Three-Phase Rectifiers

Dr. Islam Mohamed


Electrical Engineering Department
Shoubra Faculty of Engineering, Benha University

Islam.ahmed@fen.bu.edu.eg

Questions Lecture 3

- Q₁) what are the rating values of the Diodes in the converter?
- Q₂) Calculate the rectification efficiency for R and highly inductive loads.
- Q₃) what happen to the load voltage and current waveforms if a freewheeling diode is connected incase RL-loads?
- Q₄) what happen to the load voltage and current waveforms if a freewheeling diode is connected incase RL-loads?

Three-phase rectifier Plan

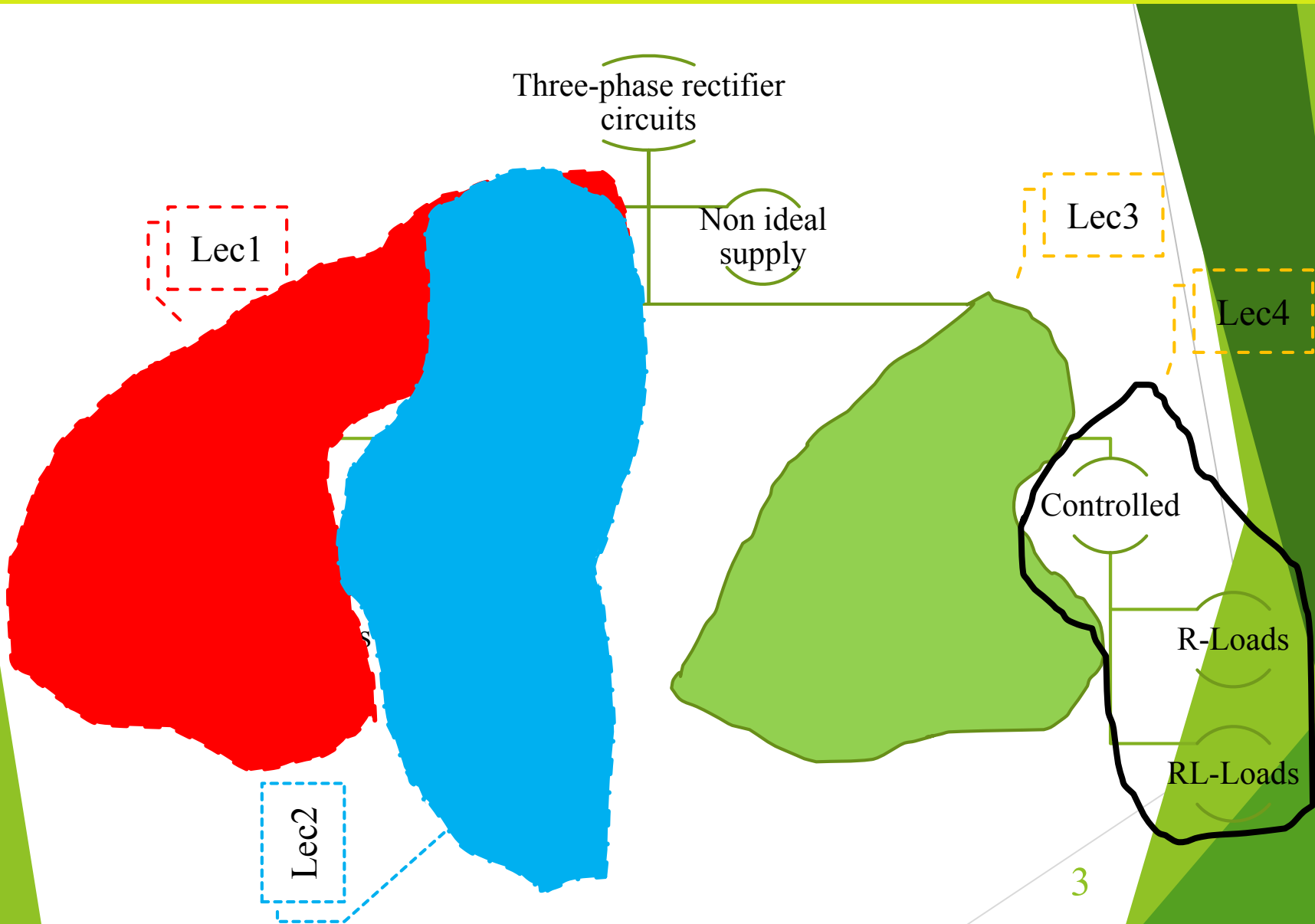

Lecture Four: Three-phase Full wave Controlled rectifiers circuits

Construction

- Circuit diagram
- Components

Operation

- Output waveforms
- R-load and Highly inductive load

Analysis


- Analysis of the circuit with R-load
- Analysis of the circuit with highly inductive load

End


- Summery
- Questions

Construction

Power circuit and its components

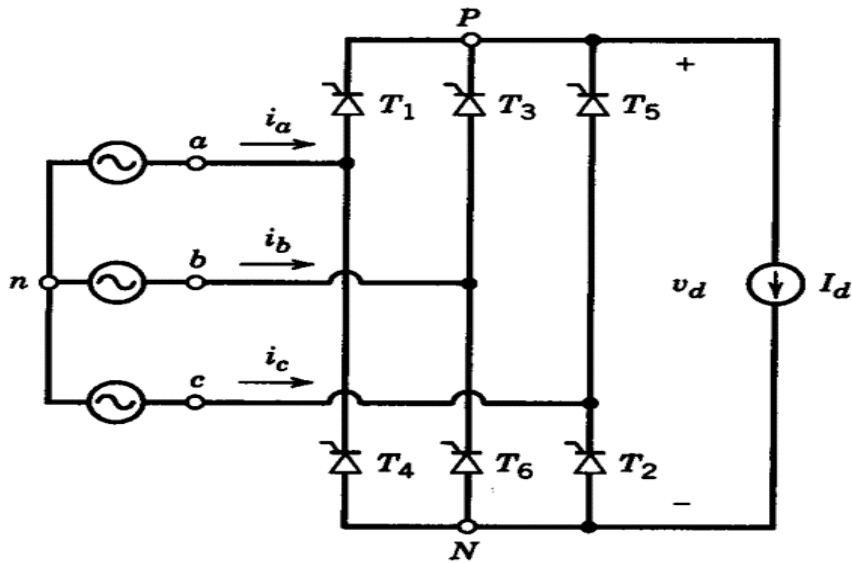

(a)

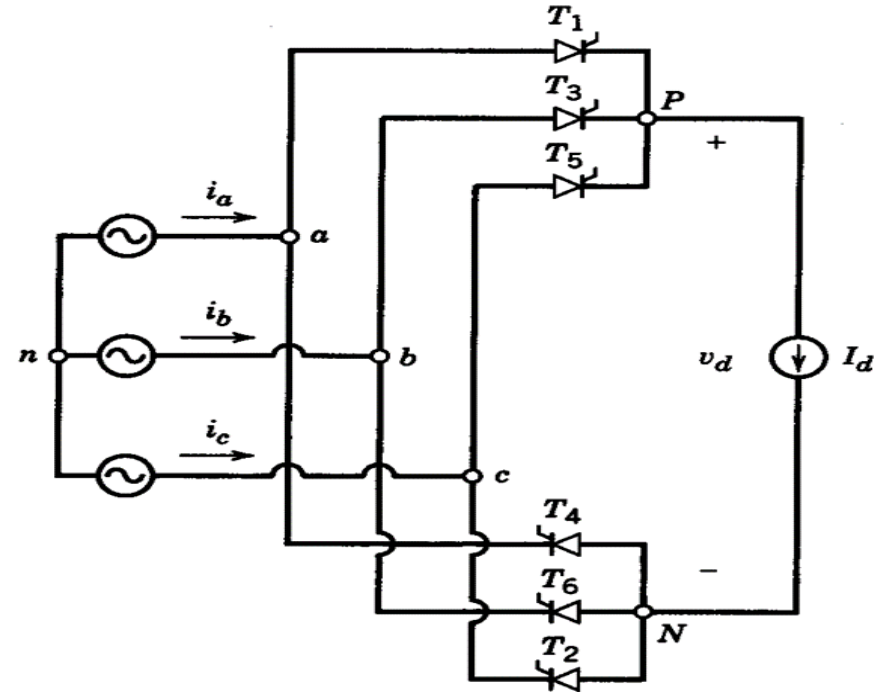


(b)

- 1- Two Thyristors must be forward at any instant (T_1, T_3, T_5) with (T_2, T_4, T_6)
- 2- Line voltage will be applied to the load at any instant.
- 3- A transition of the highest line-to-line voltage must take place every $360^\circ / 6 = 60^\circ$

Construction


Power circuit and its components

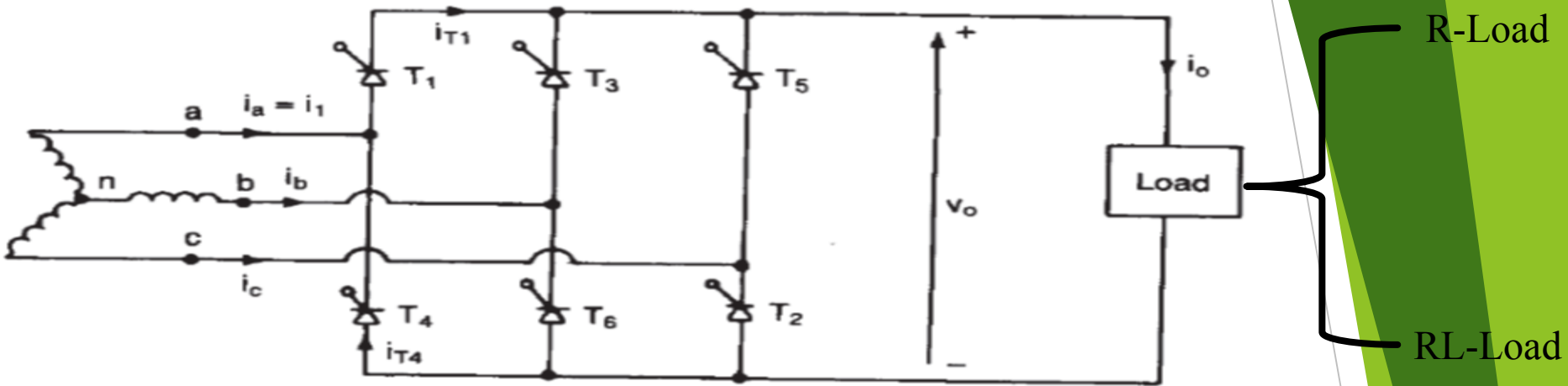

- The three thyristors (T_1, T_3 and T_5) will not work together at the same time or two of them also will not work together at the same time.
- The three thyristors (T_2, T_4 and T_6) will not work together at the same time or two of them also will not work together at the same time.
- (T_1 and T_4), (T_3 and T_6) or (T_5 and T_2) will not work together at the same time.
- Each thyristor is triggered at an interval of $2\pi/3$.
- Each thyristors pair ($(T_6 \& T_1)$, ($T_1 \& T_2$), ($T_2 \& T_3$), ($T_3 \& T_4$), ($T_4 \& T_5$), ($T_5 \& T_6$)) is triggered at an interval of $\pi/3$.
- The frequency of output ripple voltage is $6f_s$.

Construction

Firing schemes

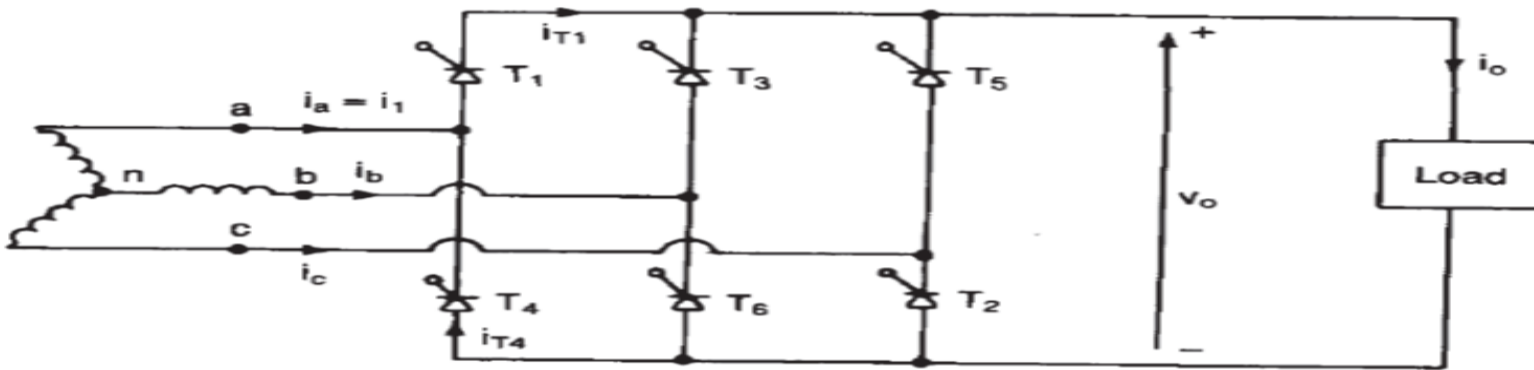

Firing Angle	T ₁	T ₂	T ₃	T ₄	T ₅	T ₆
0°	30°	90	150°	210	270°	330
30°	60°	120°	180°	240°	300°	360°
60°	90°	150°	210°	270°	330°	390°
90°	120°	180°	240°	300°	360°	420°

- Thyristors are numbered in the order in which they are triggered.
- The thyristor triggering sequence is 12, 23, 34, 45, 56, 61, 12, 23, 34,


Operation

- T_1 is triggered at $\omega t = (30 + \alpha)$, T_6 is already conducting when T_1 is turned ON.
- During the interval $(30 + \alpha)$ to $(90 + \alpha)$, T_1 and T_6 conduct together & the output load voltage is equal to $v_o = v_{ab} = (v_{an} - v_{bn})$.
- T_2 is triggered at $\omega t = (90 + \alpha)$, T_6 turns off naturally as it is reverse biased as soon as T_2 is triggered. During the interval $(90 + \alpha)$ to $(150 + \alpha)$, T_1 and T_2 conduct together & the output load voltage $v_o = v_{ac} = (v_{an} - v_{cn})$.
- T_3 is triggered at $\omega t = (150 + \alpha)$, T_1 turns off naturally as it is reverse biased as soon as T_3 is triggered. During the interval $(150 + \alpha)$ to $(210 + \alpha)$, T_2 and T_3 conduct together & the output load voltage $v_o = v_{bc} = (v_{bn} - v_{cn})$.
- T_4 is triggered at $\omega t = (210 + \alpha)$, T_2 turns off naturally as it is reverse biased as soon as T_4 is triggered. During the interval $(210 + \alpha)$ to $(270 + \alpha)$, T_3 and T_4 conduct together & the output load voltage $v_o = v_{ba} = (v_{bn} - v_{an})$.
- T_5 is triggered at $\omega t = (270 + \alpha)$, T_3 turns off naturally as it is reverse biased as soon as T_5 is triggered. During the interval $(270 + \alpha)$ to $(330 + \alpha)$, T_4 and T_5 conduct together & the output load voltage $v_o = v_{ca} = (v_{cn} - v_{an})$.
- T_6 is triggered at $\omega t = (330 + \alpha)$, T_4 turns off naturally as it is reverse biased as soon as T_6 is triggered. During the interval $(330 + \alpha)$ to $(390 + \alpha)$, T_5 and T_6 conduct together & the output load voltage $v_o = v_{cb} = (v_{cn} - v_{bn})$.

Operation

Output Voltage waveforms for R& RL loads


When $\alpha=0$

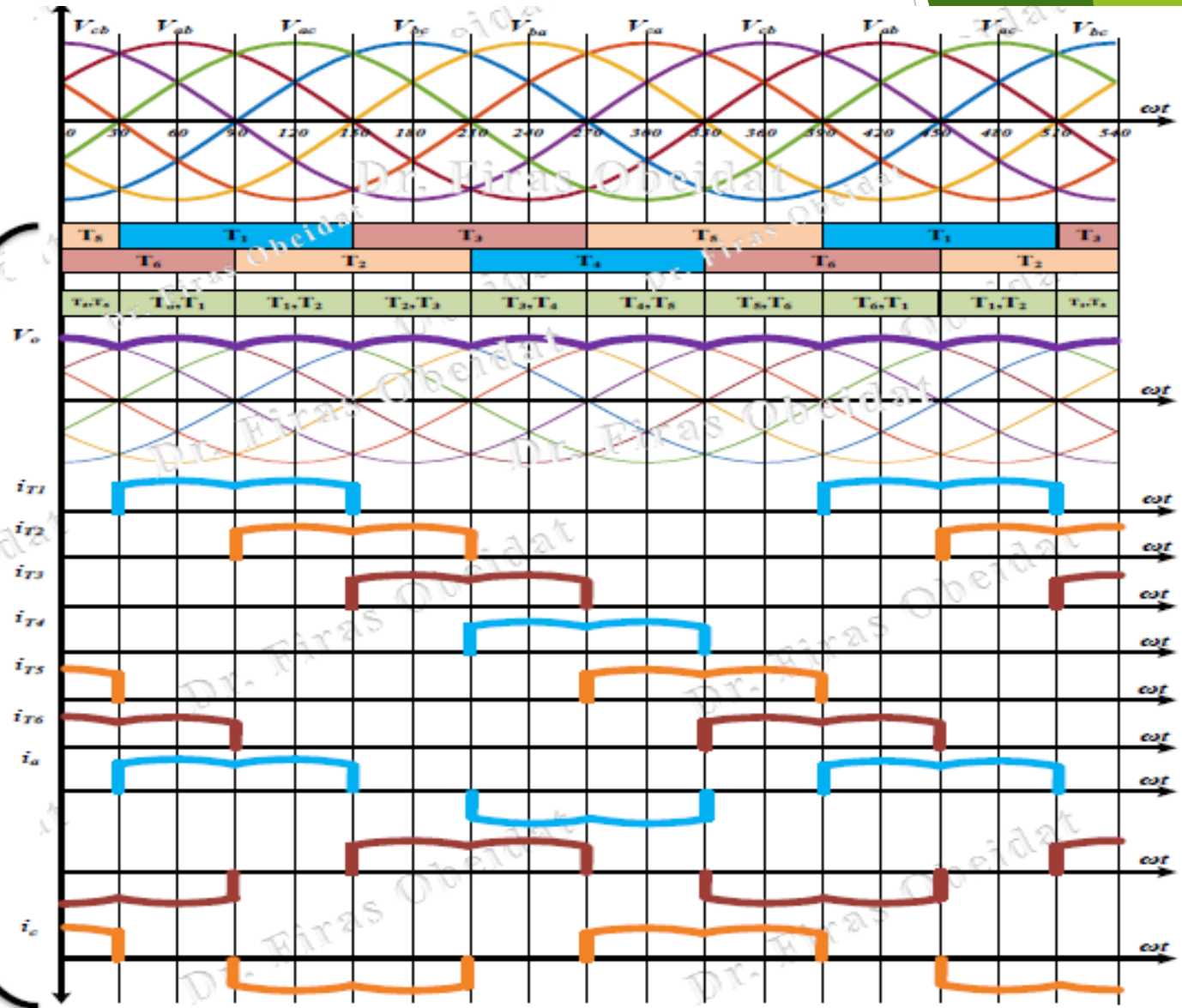


Operation

Output Voltage waveforms for R& RL loads

When $\alpha=30$

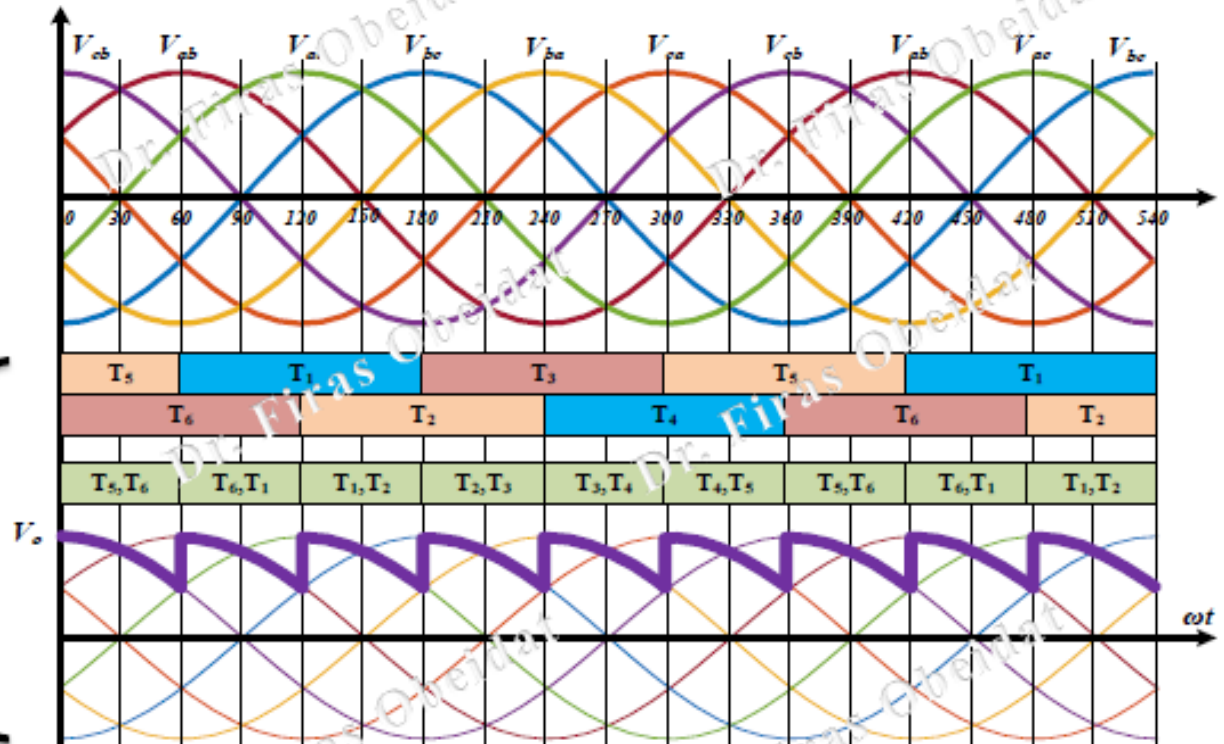


When $\alpha=60$

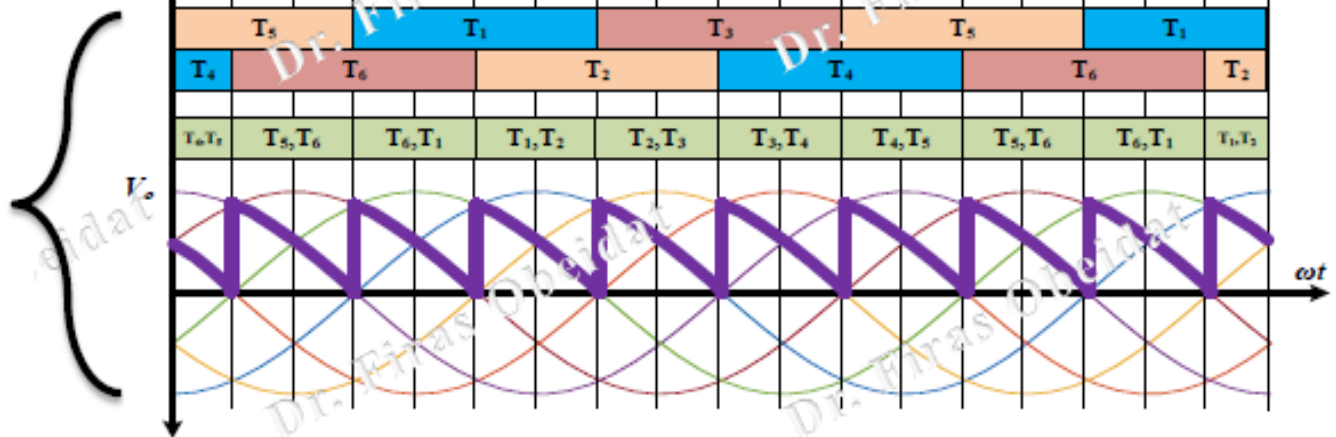


Operation

Output Voltage waveforms

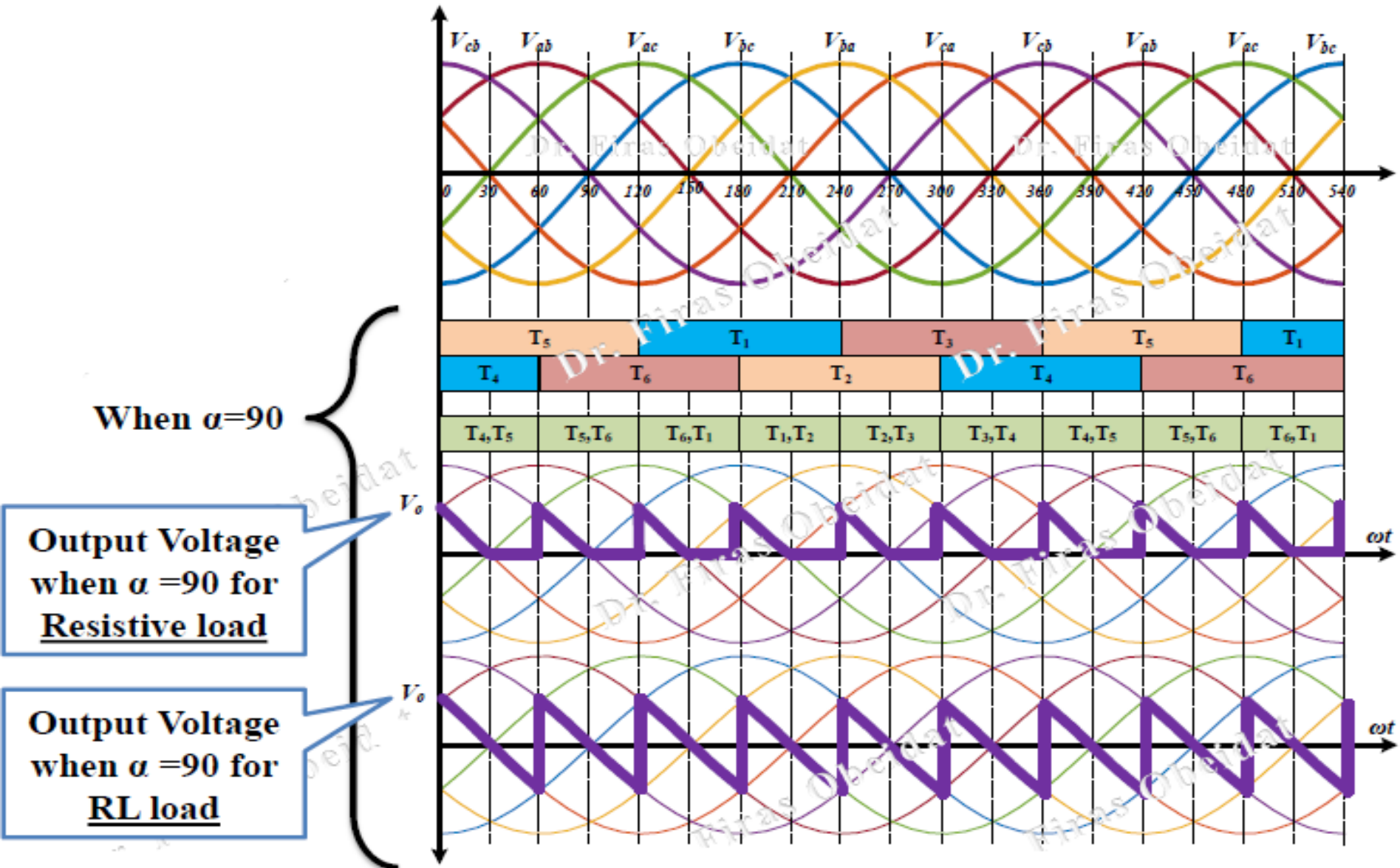

Operation

Output Voltage waveforms for RL-loads

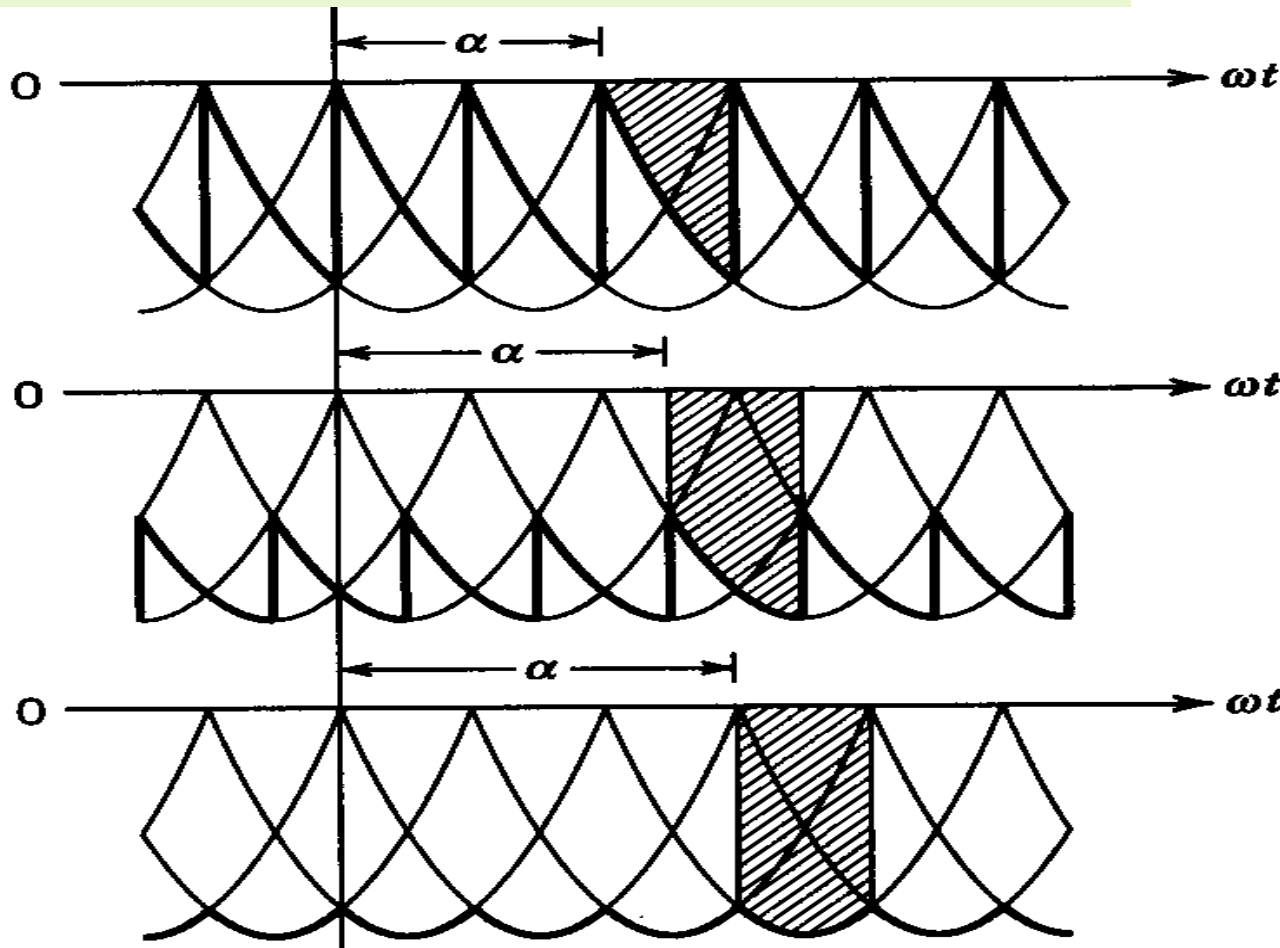



What about output Voltage waveforms for R-loads after $\alpha > 120$

What about output currents waveforms for R-loads and RL-loads?



Operation

Currents waveforms

R-Loads

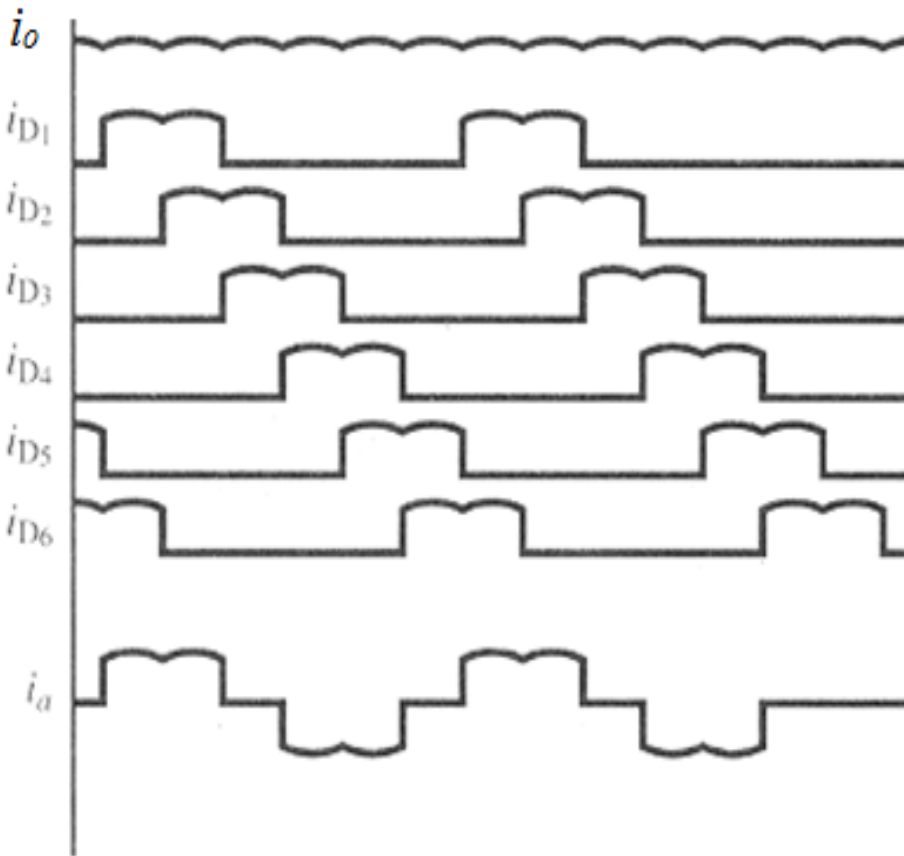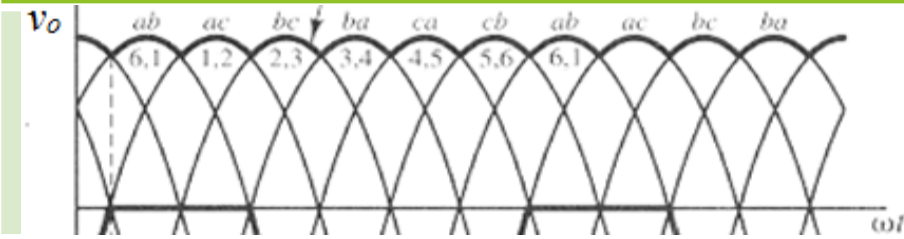

Highly inductive Loads

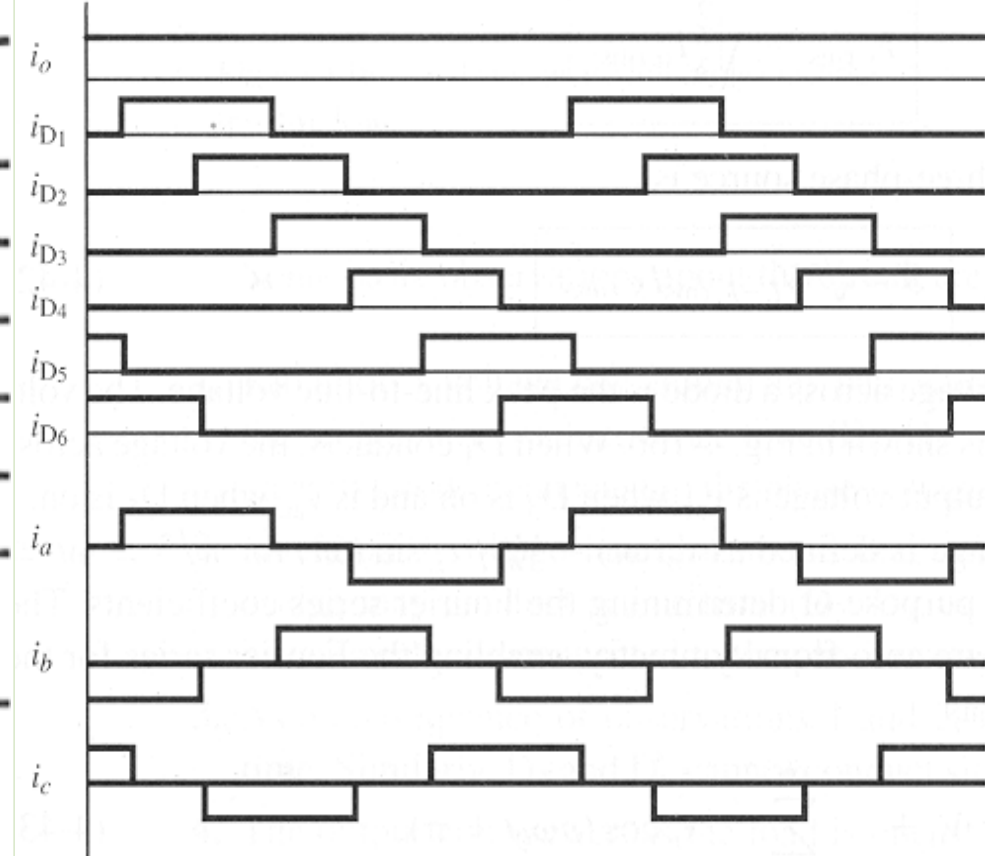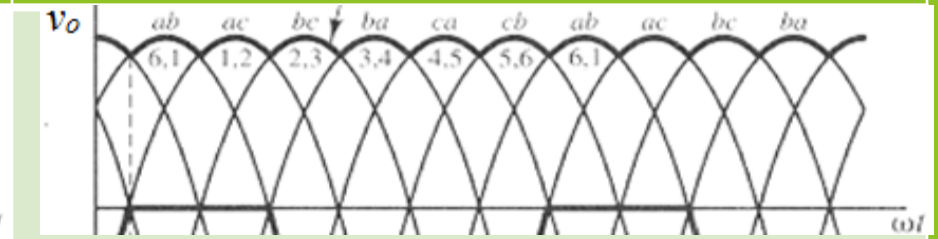

Analysis:


1- Supply voltages:

$$V_{ab}(\omega t) = V_{ml} \sin(\omega t + \pi/6), \quad V_{bc}(\omega t) = V_{ml} \sin(\omega t - \pi/2), \quad V_{ca}(\omega t) = V_{ml} \sin(\omega t - 7\pi/6)$$

$\alpha \leq 60$ for R & RL loads:

2- Output average voltage
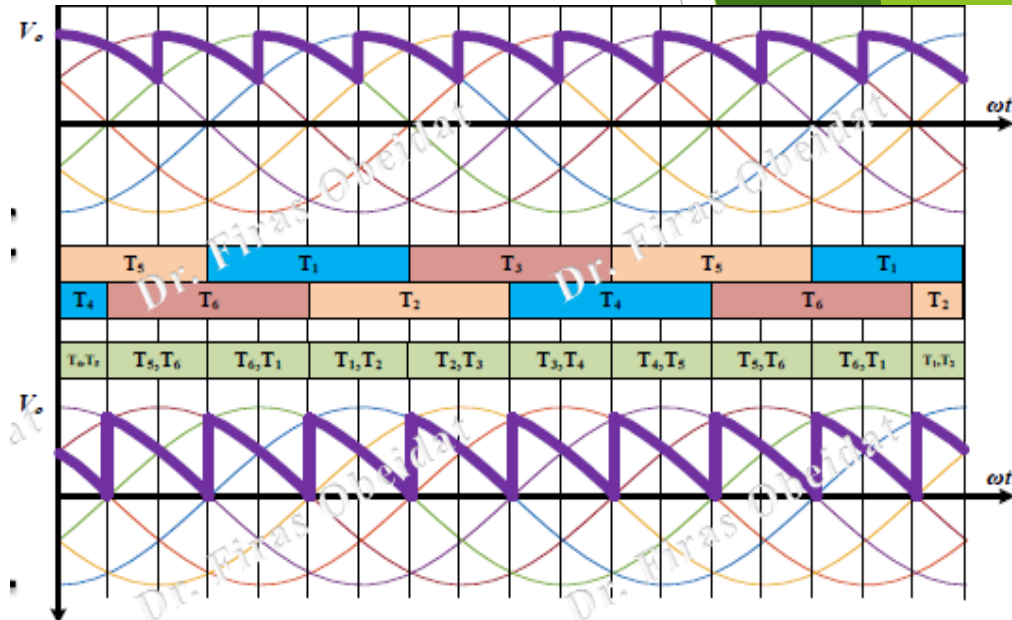
$$V_{o,avg} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) d\omega t = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$



3- Output rms voltage for R & RL loads:

$$V_{o,rms} = \sqrt{\frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} (\sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}))^2 d\omega t} = \sqrt{3} V_m \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

Analysis:

4- Average load current For R & RL-Loads

For both cases:

$$I_{o, avg} = \frac{V_{o, avg}}{R}$$

5- RMS Load current

For Resistive load:

$$I_{o, rms} = V_{o, rms} / R$$

~~For RL load: $I_{o, rms} = V_{o, rms} / Z$~~

For Highly inductive load:


$$I_{o, rms} = I_{o, avg}$$

Analysis:

$$60 < \alpha$$

for R-loads:

$$60 < \alpha < 120$$

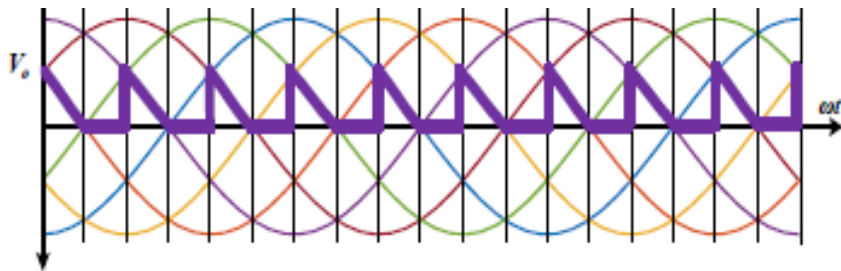


$$V_{o,avg} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right) d\omega t = \frac{3\sqrt{3}V_m}{\pi} \cos\left(\frac{\pi}{3} + \alpha\right)$$

$$V_{o,rms} = \sqrt{\frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6}} \left(\sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right)\right)^2 d\omega t}$$

for RL-loads:

$$60 < \alpha < 180$$

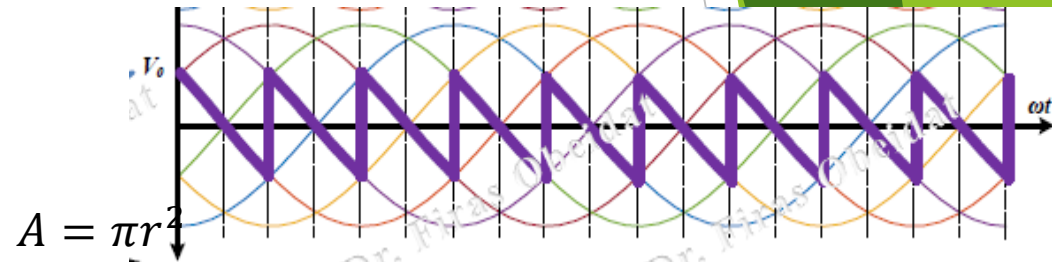

$$A = \pi r^2$$

$$V_{o,avg} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right) d\omega t = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$

$$V_{o,rms} = \sqrt{\frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \left(\sqrt{3}V_m \sin\left(\omega t + \frac{\pi}{6}\right)\right)^2 d\omega t} = \sqrt{3}V_m \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

Analysis:

$$60 < \alpha$$

For both cases:

$$I_{o, avg} = \frac{V_{o, avg}}{R}$$


5- RMS Load current

For Resistive load:

$$I_{o, rms} = V_{o, rms} / R$$

~~*For Resistive load:*~~

$$I_{o, rms} = V_{o, rms} / R$$

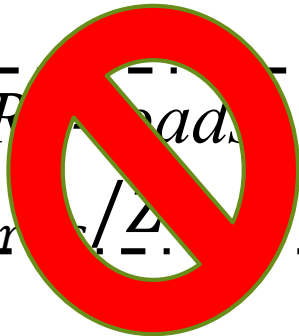

For Highly inductive load:

$$I_{o, rms} = I_{o, avg}$$



Analysis:

6- Thyristor currents

- Each thyristor conducts one-third of the time, resulting in

$$I_{T,avg} = \frac{1}{3} I_{o,avg}$$
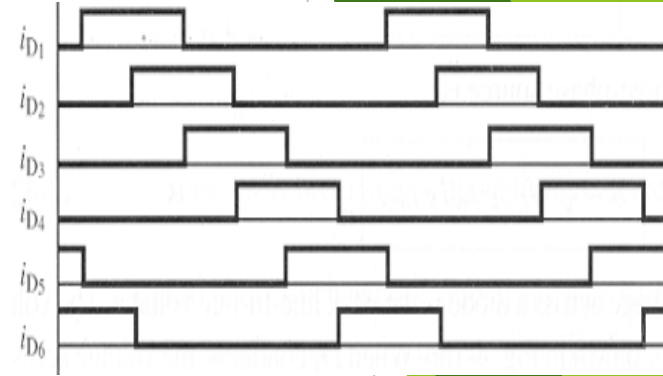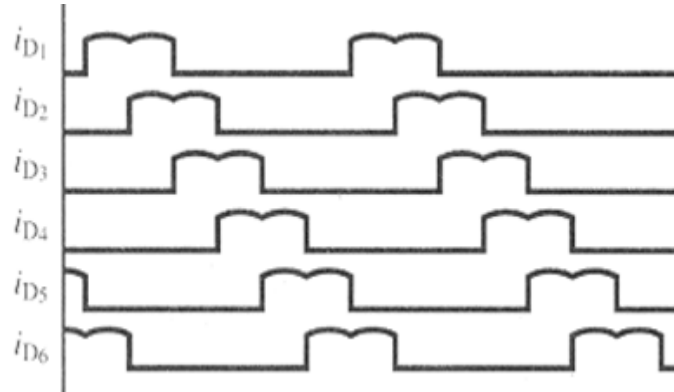
$$I_{T,rms} = \frac{1}{\sqrt{3}} I_{o,rms}$$





7- RMS supply current

$$i_a = i_{T1} - i_{T4}$$

$$i_b = i_{T3} - i_{T6}$$

$$i_c = i_{T5} - i_{T2}$$

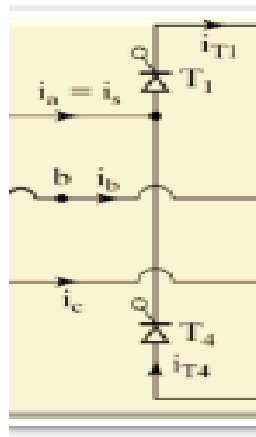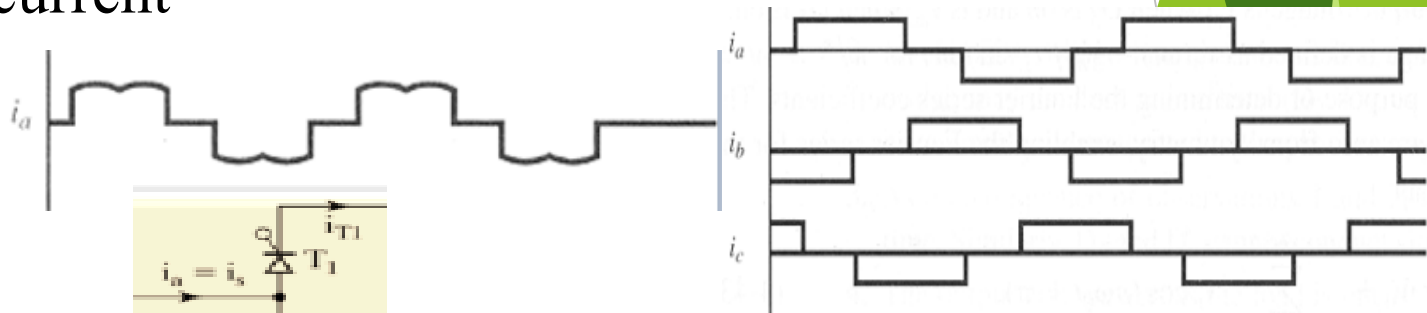

$$I_{S,rms} = \sqrt{\frac{2}{3}} I_{o,rms}$$

Analysis:

8- Output power

$$P_S = P_O = I_{o,rms}^2 R$$

For R & RL Loads??



9- Input power factor

$$pf = \frac{P_o}{S} = \frac{I_{o,rms}^2 R}{3V_s I_{s,rms}}$$



Remember $I_{s,rms} = \sqrt{2/3} I_{o,rms}$

10- Converter efficiency

$$\eta = \frac{P_{dc}}{P_{o,rms}} = \frac{V_{o,avg} I_{o,avg}}{V_{o,rms} I_{o,rms}}$$

Questions

- Q₁) what are the rating values of the Thyristors in the converter?
- Q₂) Draw a relation between the rectification efficiency and firing angles for R-load and highly inductive loads.
- Q₃) Draw a relation between the average output voltage and firing angles for R-load and highly inductive loads.
- Q₄) Draw the load voltage and current waveforms if a freewheeling diode is connected in case RL-loads.
- Q₅) Draw the load voltage and current waveforms at for RL-loads if T₂, T₄, T₆ are replaced with diodes At $\alpha = 30, 60, 90$