



1. A three-phase, uncontrolled bridge rectifier is supplied from a 480 V (rms, line-to-line), 50 Hz 3-phase AC source, feeding a highly inductive load with $R=50 \Omega$.
 - (a) Plot the waveforms of the output voltage, diode currents, diode voltage and supply current.
 - (b) Determine:
 - i. the mean values of the load voltage and current,
 - ii. the average and rms values of the diode currents,
 - iii. PIV of the diodes,
 - iv. the rms value of the supply current,
 - v. the rectification ratio and converter efficiency.

2. A three-phase, uncontrolled bridge rectifier is connected to a 220 V (rms, line-to-line), 50 Hz 3-phase AC supply. The rectifier is supplying an inductive load of $R=25\Omega$ and $L=100\text{mH}$. Determine using **Fourier series**:
 - (a) the average values of the rectifier output voltage and current,
 - (b) the amplitude of the most dominant harmonic of the load voltage and current,
 - (c) the rms value of the supply current,
 - (d) the %THD of the supply current
 - (e) The supply apparent power and power factor.

3. A three-phase, fully controlled bridge rectifier is connected to a 220 V (rms, line-to-line) 50 Hz 3-phase AC supply. The rectifier is supplying a pure resistive load of $R=25\Omega$. Determine:
 - (a) the required firing angle if the average output voltage is 50% of the maximum output voltage,
 - (b) the average and rms values of the load current,
 - (c) the average and rms values of the thyristor current,
 - (d) the rectification ratio and converter efficiency,
 - (e) the input power factor.



4. A three-phase, fully controlled bridge rectifier is connected to a 660 V (rms, line-to-line) 3-phase AC supply. The rectifier is supplying a DC load current ($R=25\ \Omega$) and a thyristor voltage drop of 1.2 V.
- (a) Determine the mean values of the load voltage at firing delay angles (α) of: 0° , 30° , 45° , 60° and 90° .
 - (b) Plot the waveforms of the load voltage and thyristor voltages at $\alpha=75^\circ$.
 - (c) Calculate the average and rms values of the thyristor current (i_{T1}).
 - (d) Calculate the average power loss in each thyristor.