


Chapter 1

(Part 3)

Single phase AC voltage controllers

By


Dr. Ayman Yousef

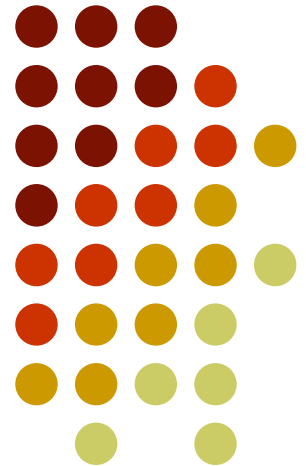



Single-phase full-wave AC voltage controllers with R-L load

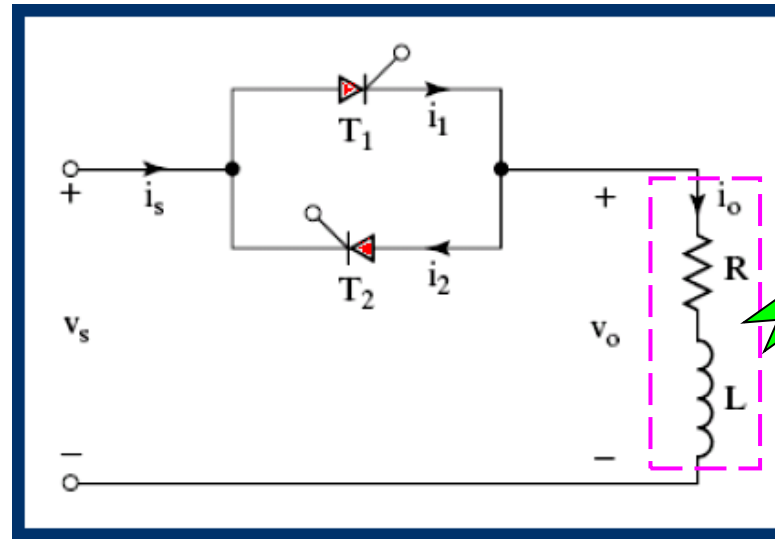Single-phase full-wave AC voltage controllers with R-L load




R-L load

- The thyristor T_1 is forward biased during the **positive half cycle** of input supply and conduct when suitable pulse applied on its gate $\omega t = \alpha$.
- The thyristor T_2 is forward biased during the **negative half cycle** of input supply and conduct when suitable pulse applied on its gate $\omega t = \pi + \alpha$.



Single-phase full-wave AC voltage controllers with R-L load



- Due to the **inductance** in the load, the load current i_o flowing through T_1 would **not fall to zero** at $\omega t = \pi$, when the input supply voltage starts to become **negative**.
- The thyristor T_1 will **continue to conduct** the load current until all the **inductive energy** stored in the load inductor L is completely utilized and the load current through T_1 falls to zero at $\omega t = \beta =$ **extinction angle**.
- The thyristor T_1 conducts from $\omega t = \alpha$ to β . The conduction angle of T_1 is $\delta = (\beta - \alpha)$, which depends on the **delay angle α** and the **load impedance angle ϕ** .

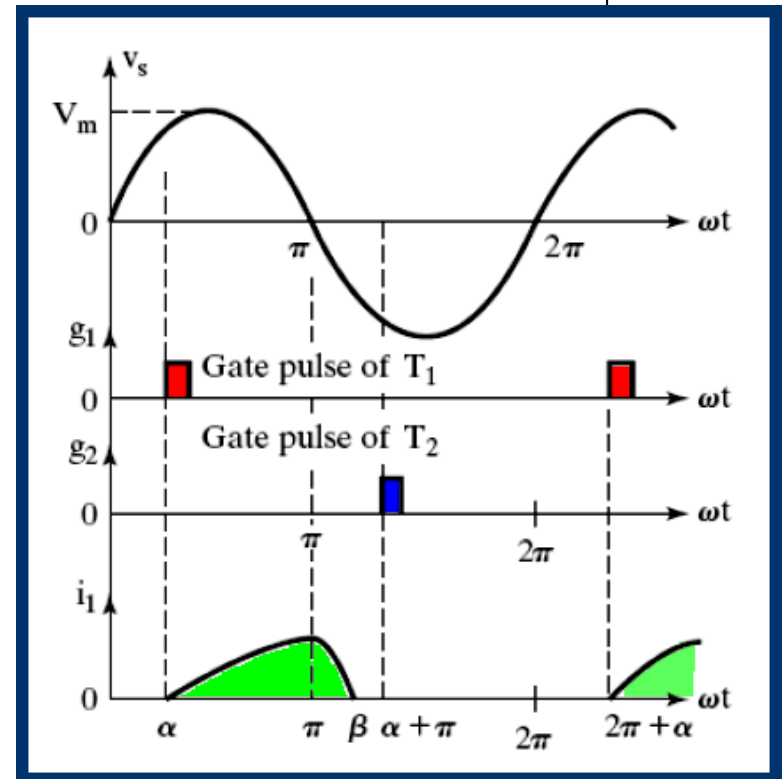

Single-phase full-wave AC voltage controllers with R-L load

In case of $\beta > \pi + \alpha$

- The **problem**, when (T_2) is fired at $\omega t = \pi + \alpha$, while (T_1) is **still conducting** due to load inductance, (T_2) cannot be turned on. This will result in **asymmetric output voltage and current waveforms**.
- The **solution** of this problem, **continuous gating signals** with a duration of $(\pi - \alpha)$ should be used.
- Another problem, when the current in (T_1) falls to zero, (T_2) would be turned on. But, a **continuous gating signal results in high switching losses** of thyristors and **requires a larger isolating transformer in the gating circuit**.
- In practice, **a train of pulses with short durations**, are normally used to overcome these problems.

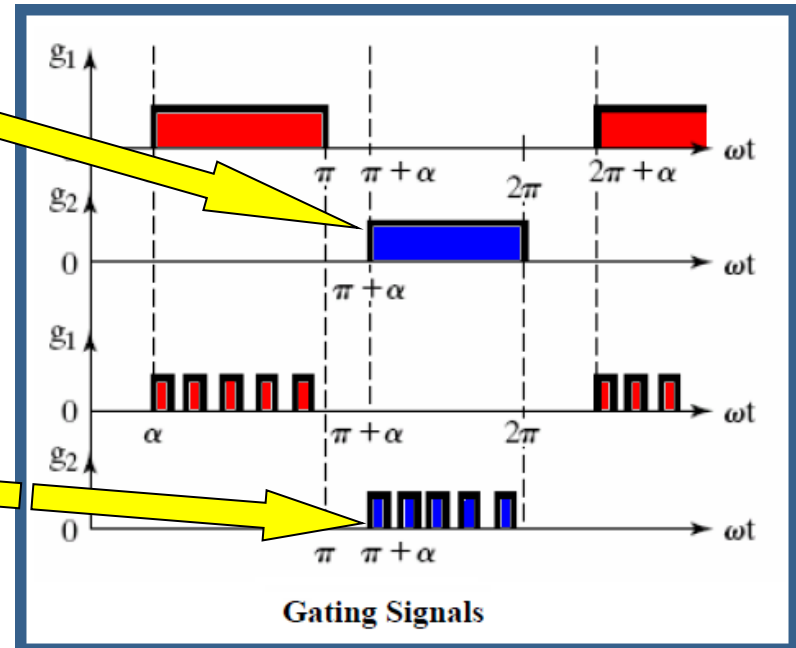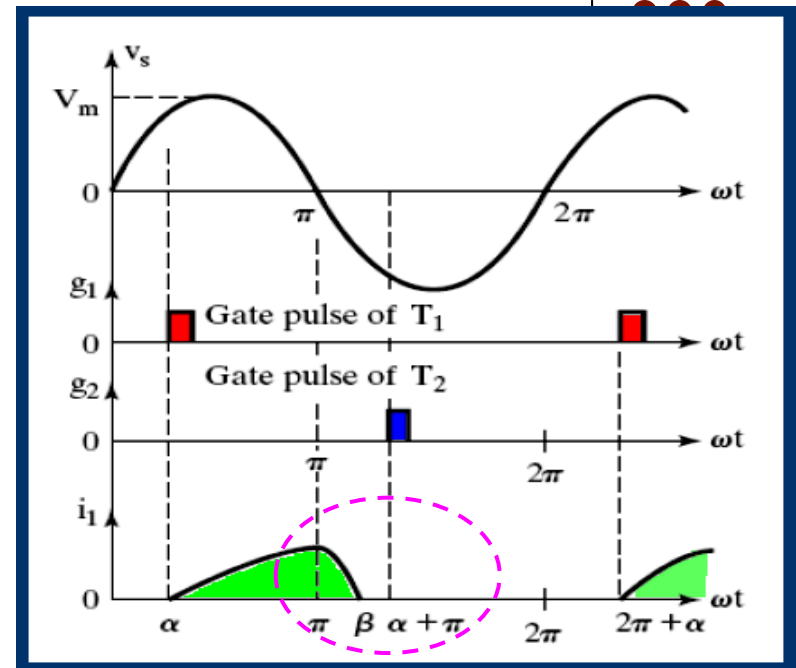



Waveforms of single phase full wave ac voltage controller with RL load



In case of ($\alpha < \varphi$)

- The load voltage and current can be **sinusoidal** if the firing delay angle (α) is less than the load angle (φ).

In case of ($\alpha > \varphi$)

- If (α) is greater than (φ), which is usually the case, the load current would be **discontinuous** and **non-sinusoidal**.
- In discontinuous load current operation occurs for $\alpha > \varphi$ and $\beta < (\pi + \alpha)$ i.e., $(\beta - \alpha) < \pi$, conduction angle $< \pi$.

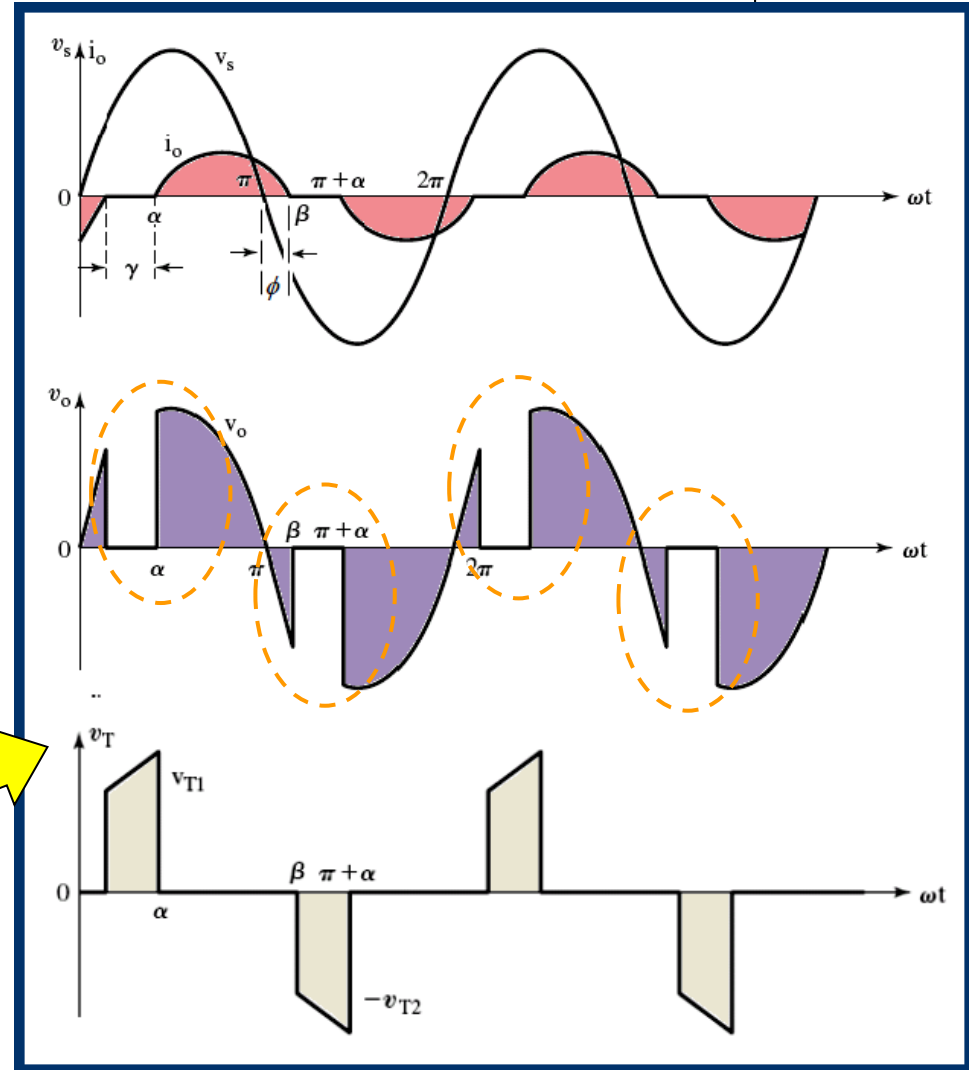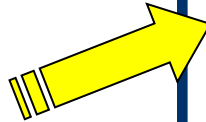
Waveforms of single phase full wave ac voltage controller with RL load for $\alpha > \varphi$.



Analysis of Single phase full wave AC voltage controller with inductive load



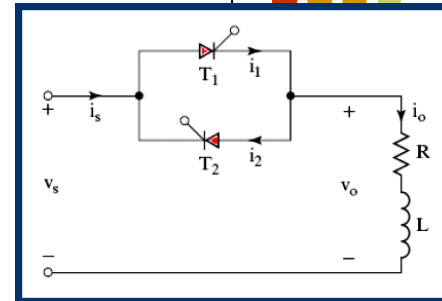The load current i_o (thyristor current i_{T1})



$$v_s = V_m \sin \omega t \quad \Rightarrow \quad \text{instantaneous value of the input supply voltage}$$

- Assuming that thyristor (T_1) is triggered at $\omega t = \alpha$, The load current which flows through the thyristor T_1 during $\omega t = \alpha$ to β can be found from the equation:

$$L \left(\frac{di_1}{dt} \right) + Ri_1 = V_m \sin \omega t$$

- The solution of the above differential equation gives the general expression for the thyristor (load) current, during this period, is in the form:

$$i_o = i_{T1} = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}} \quad \text{Where } V_m = \sqrt{2}V_s = \text{maximum or peak value of input supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.} \quad \phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \text{Load impedance angle (power factor angle of load).}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

Analysis of Single phase full wave AC voltage controller with inductive load



- The value of the constant A_1 can be determined from the initial condition. i.e. initial value of load current $i_o = 0$, at $\omega t = \alpha$. Hence from the equation for I_o equating i_o to zero and substituting $\omega t = \alpha$

$$i_o = i_{T1} = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L}t}$$

Therefore $A_1 e^{\frac{-R}{L}t} = \frac{-V_m}{Z} \sin(\alpha - \phi) \implies A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[\frac{-V_m}{Z} \sin(\alpha - \phi) \right]$

- Substituting the value of constant A_1 from the above equation into the expression for i_o , we obtain

$$i_o = i_{T1} = \frac{V_m}{Z} \sin(\omega t - \phi) - e^{\frac{R}{L}(\alpha/\omega - t)} \left[\frac{V_m}{Z} \sin(\alpha - \phi) \right] \implies \text{Where } \alpha \leq \omega t \leq \beta$$

$$i_o = i_{T1} = \frac{\sqrt{2}V_s}{Z} \left\{ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{R}{L}(\alpha/\omega - t)} \right\}$$



Analysis of Single phase full wave AC voltage controller with inductive load

Calculation of the extinction angle β

- The extinction angle β , depends upon the load inductance and is defined as the value of ωt at which the load current i_o falls to zero and T_1 is turned off, and it can be estimated by using the condition that $i_o = 0$, at $\omega t = \beta$

$$i_o = 0 = \frac{V_m}{Z} \left[\sin(\beta - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)} \right] \implies \text{As } \frac{V_m}{Z} \neq 0 \text{ we can write}$$

$$\left[\sin(\beta - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)} \right] = 0 \implies \sin(\beta - \phi) = \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)}$$

- The extinction angle β can be determined from this equation by using the iterative method of solution (trial and error method).
- In the exponential term the value of α and β should be substituted in radians.
- After β is calculated, we can determine the thyristor conduction angle δ .

Analysis of Single phase full wave AC voltage controller with inductive load



Conduction Angle δ

- After β is calculated, we can determine the thyristor conduction angle δ .

$$\delta = (\beta - \alpha)$$

- Conduction angle δ increases as α is decreased for a known value of β .
- Maximum thyristor conduction angle $\delta = (\beta - \alpha) = \pi$ radians = 180° for $\alpha \leq \varphi$.
- In case of $\alpha > \varphi$, the type of operation will be **discontinuous load current**, and we get $\beta < (\pi + \alpha)$, and greater than π radian or 180° . Then, the range of extinction angle β

$$\pi < \beta < (\pi + \alpha)$$


Analysis of Single phase full wave AC voltage controller with inductive load



RMS Output Voltage

$$V_o = \sqrt{\frac{2}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d(\omega t)}$$

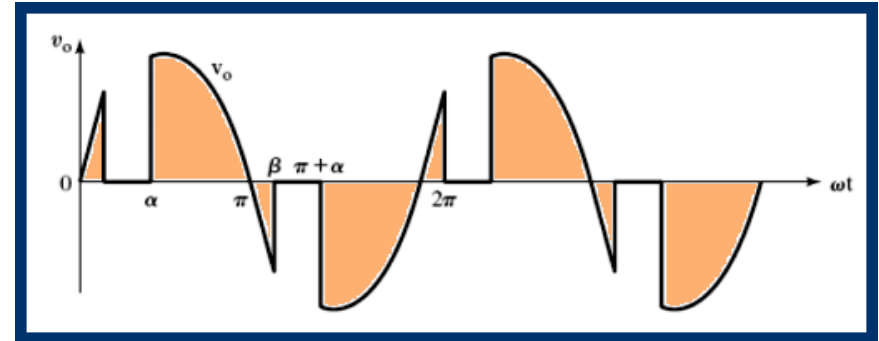
$$V_o = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[(\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right]}$$



The Average Thyristor Current

$$I_{T(Avg)} = \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} i_{T_1} d(\omega t) \right]$$
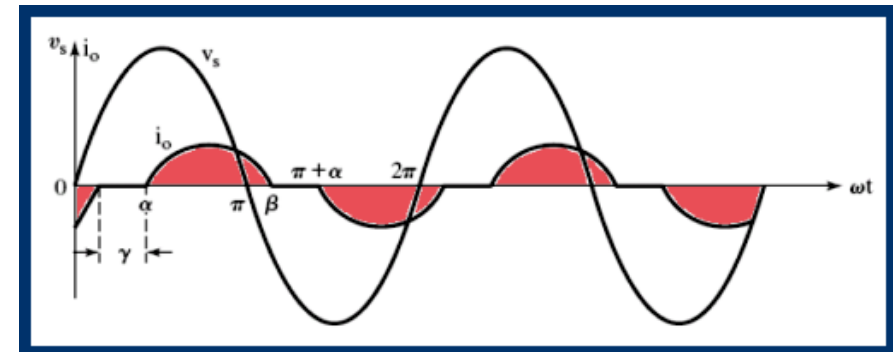
$$I_{T(Avg)} = \frac{V_m}{2\pi Z} \int_{\alpha}^{\beta} \left[\sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{-\frac{R}{L}(\alpha/\omega - t)} \right] d(\omega t)$$



Analysis of Single phase full wave AC voltage controller with inductive load



RMS Thyristor Current $I_{T(RMS)}$

$$I_{T(RMS)} = \sqrt{\left[\frac{1}{2\pi} \int_{\alpha}^{\beta} i_{T1}^2 d(\omega t) \right]}$$


$$i_o = i_{T1} = \frac{\sqrt{2}V_s}{Z} \left\{ \sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{R}{L}(\alpha/\omega - t)} \right\}$$

$$I_{T(RMS)} = \sqrt{\left[\frac{1}{2\pi} \int_{\alpha}^{\beta} \left[\frac{\sqrt{2}V_s}{Z} \left\{ \sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{R}{L}(\alpha/\omega - t)} \right\} \right]^2 d(\omega t) \right]}$$

$$I_{T(RMS)} = \frac{V_s}{Z} \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} \left\{ \sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{R}{L}(\alpha/\omega - t)} \right\}^2 d(\omega t)}$$

RMS Output Current
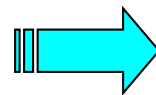
$$I_o = \sqrt{I_{T(rms)}^2 + I_{T(rms)}^2}$$



$$I_o = \sqrt{2} I_{T(rms)}$$

Ex .3: A single-phase full-wave AC voltage controller supplies an RL load. The supply rms voltage is 120 V, 60 Hz. The load has $R=2.5\Omega$ and $L=6.5$ mH, the firing delay angles of thyristors are equal: $\alpha_1 = \alpha_2 = \pi/2$.



Determine:

- the conduction angle of the thyristor T_1
- the rms output voltage
- the rms thyristor current
- the average thyristor current
- the rms output current
- the input power.

Solution

$$V_s = 120 \text{ V} \quad f = 60 \text{ Hz} \quad R = 2.5 \Omega \quad L = 6.5 \text{ mH} \quad \alpha_1 = \alpha_2 = 90^\circ$$

$$\phi = \tan^{-1} (\omega L/R) = \tan^{-1} (2\pi \times 60 \times 6.5 \times 10^{-3} / 2.5) = 44.4^\circ$$

A conduction angle of the thyristor T_1

$$\delta = (\beta - \alpha)$$

- In order to determine the conduction angle δ , firstly, we must find the extinction angle β from the given equation

$$\sin(\beta - \phi) = \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)}$$



$$\sin(\beta - \phi) = \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\beta - \alpha)}$$

- By solving this equation numerically using trial and error method, and because $\alpha > \phi$, the extinction angle (β) can be determined with the given range

$$\pi < \beta < (\pi + \alpha) \implies \beta \cong 220^\circ$$

$$\text{Then, } \delta = \beta - \alpha = 220^\circ - 90^\circ = 130^\circ$$

B rms output voltage

$$V_o = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[(\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right]}$$

$$V_o = V_s \left[\frac{1}{\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{\frac{1}{2}}$$

$$V_o = 120 \left[\frac{1}{\pi} \left\{ (220 - 90) + \frac{\sin 2 \times 90}{2} - \frac{\sin 2 \times 220}{2} \right\} \right]^{\frac{1}{2}} = 90.25 \text{v}$$



C rms thyristor current

$$I_{T(RMS)} = \frac{V_s}{Z} \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} \left\{ \sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{R}{L}(\alpha/\omega - t)} \right\}^2 d(\omega t)}$$

D average thyristor current

$$I_{T(Avg)} = \frac{V_m}{2\pi Z} \int_{\alpha}^{\beta} \left[\sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{R}{L}(\alpha/\omega - t)} \right] d(\omega t)$$

E rms output current

$$I_o = \sqrt{2} I_{T(rms)}$$

F input power factor

$$PF = \frac{P_o}{VA}$$

$$P_o = I_o^2 \times R \quad VA = V_s \times I_s$$

Harmonic analysis of output voltage and current with RL load



rms output voltage

$$V_o = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{\pi} \left[(\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right]}$$

rms thyristor current

$$I_{T(RMS)} = \frac{V_s}{Z} \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} \left\{ \sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{-\frac{R}{L}(\omega t - \alpha)} \right\}^2 d(\omega t)}$$

rms output current

$$I_o = \sqrt{2} I_{T(rms)}$$

Harmonic analysis of output voltage and current with RL load



The fundamental component of load voltage

$$a_1 = \frac{V_m}{2\pi} [\cos 2\alpha - \cos 2\beta]$$

$$\vartheta_1 = \tan^{-1} \frac{a_1}{b_1}$$

$$b_1 = \frac{V_m}{2\pi} [2(\beta - \alpha) + \sin 2\alpha - \sin 2\beta]$$

The n th component of load voltage

$$a_n = \frac{V_m}{\pi} \left\{ \frac{\cos(1+n)\alpha - \cos(1+n)\beta}{(1+n)} + \frac{\cos(1-n)\alpha - \cos(1-n)\beta}{(1-n)} \right\}$$

$$\vartheta_n = \tan^{-1} \frac{a_n}{b_n}$$


$$b_n = \frac{V_m}{\pi} \left\{ \frac{\sin(1-n)\beta - \sin(1-n)\alpha}{(1-n)} - \frac{\sin(1+n)\beta - \sin(1+n)\alpha}{(1+n)} \right\}$$

$n = 3, 5, 7, \dots$

Harmonic analysis of output voltage and current with RL load



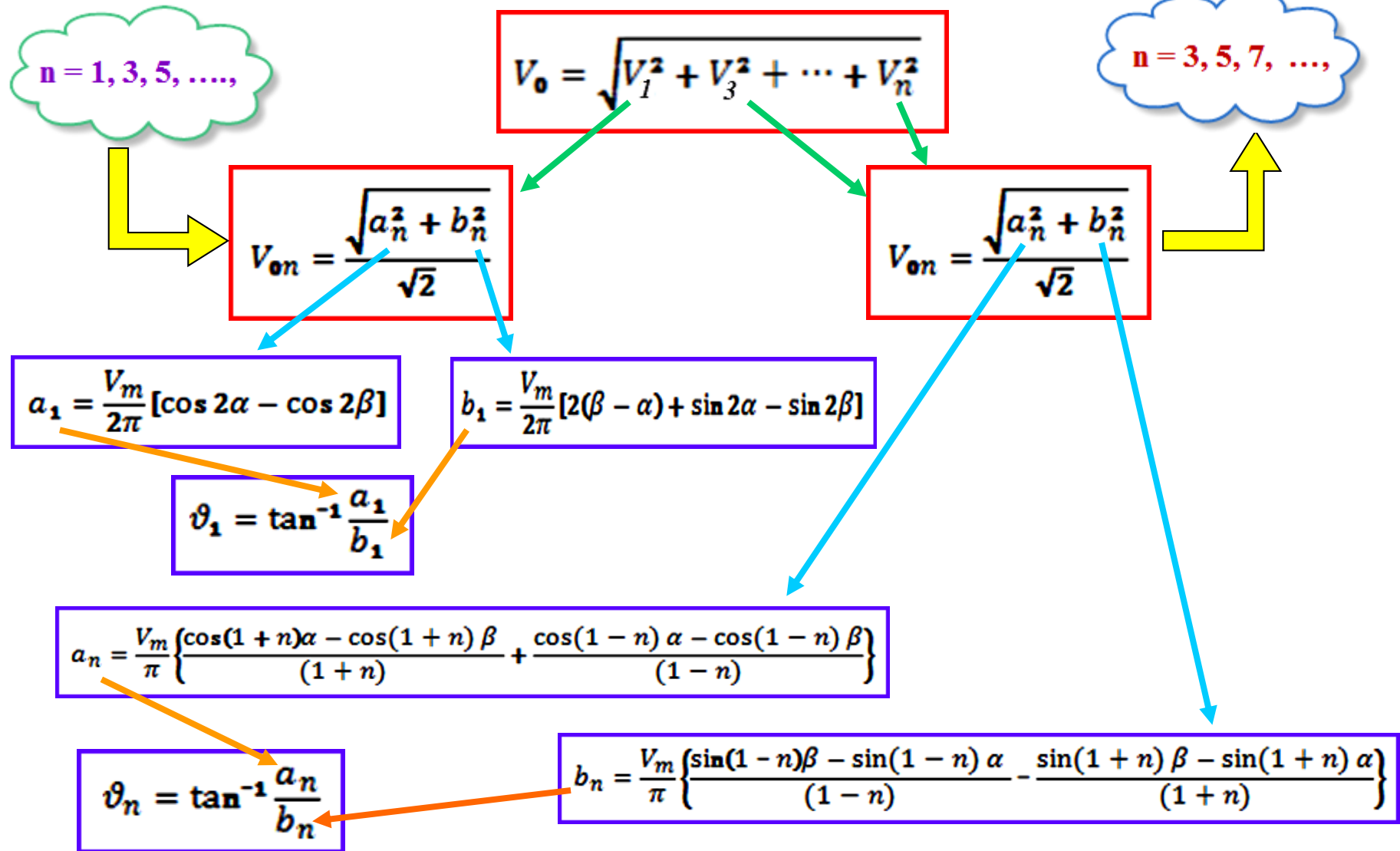
The RMS of load voltage from Fourier series



Harmonic analysis of output voltage and current with RL load



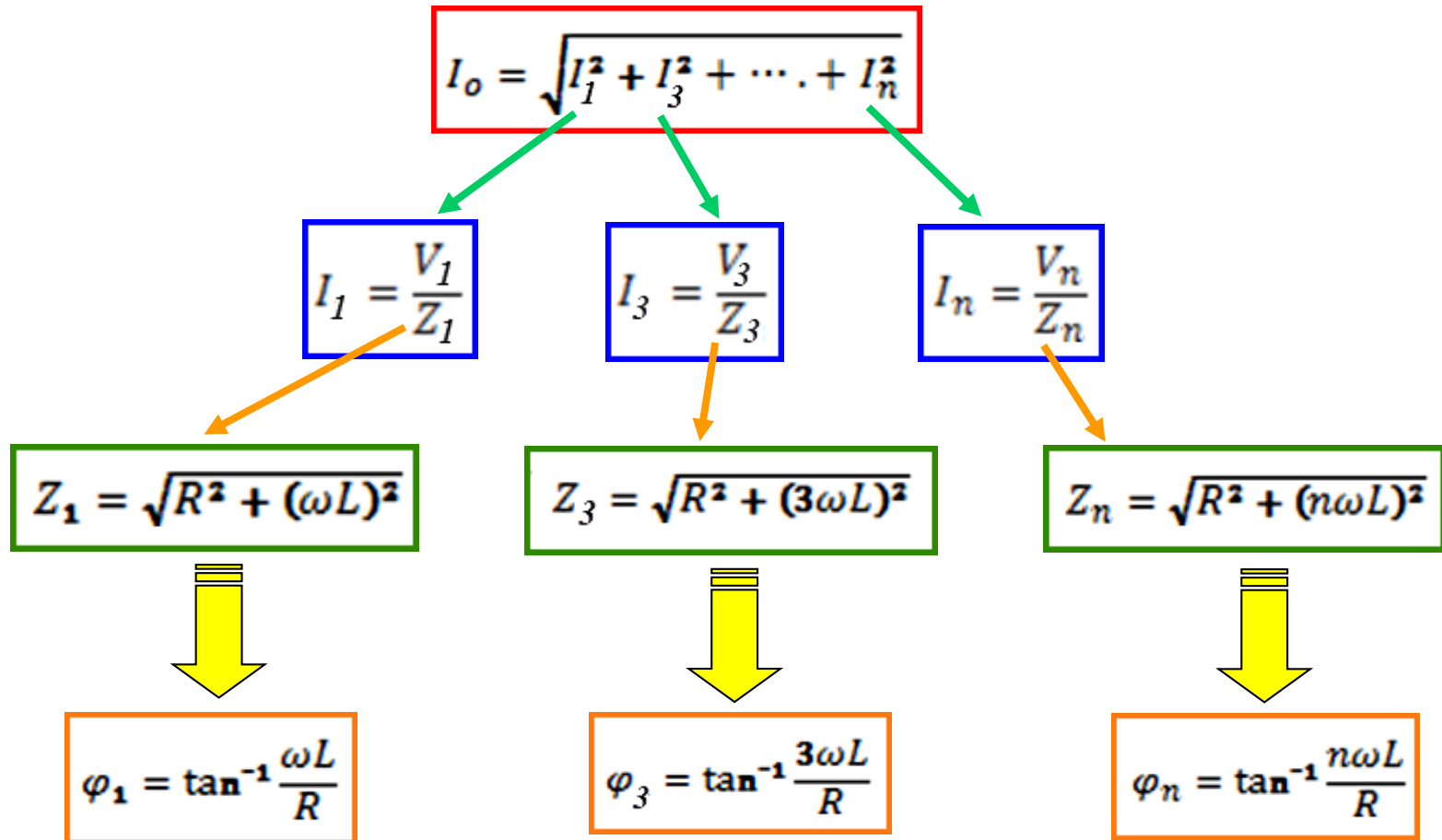The RMS of the load current obtained from Fourier series



Harmonic analysis of output voltage and current with RL load



Active power

$$P = V_1 I_1 \cos(\vartheta_1 - \varphi_1) + V_2 I_2 \cos(\vartheta_2 - \varphi_2) + \dots + V_n I_n \cos(\vartheta_n - \varphi_n)$$

$$P = I_0^2 R$$

$$P = (I_1^2 + I_2^2 + \dots + I_n^2) R$$

Reactive power

$$Q_1 = V_1 I_1 \sin(\vartheta_1 - \varphi_1)$$