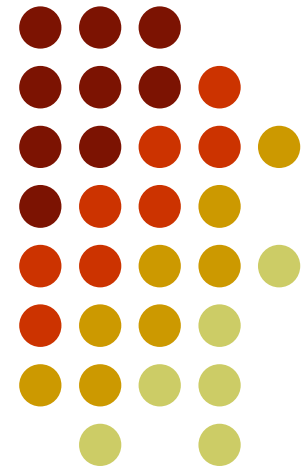



Chapter 3

Three-phase half-wave AC voltage controllers (Part 2)

By


Dr. Ayman Yousef



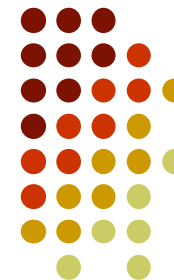

Analysis of three-phase half-wave AC voltage controller

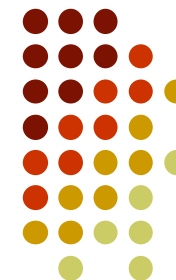Analysis of three-phase half-wave AC voltage controller with resistive load



Expressions for the instantaneous output phase voltage:

For $\alpha = 45^\circ$, the waveform of output phase voltage (v_{an})

instantaneous input voltage per phase

$$v_{AN} = \sqrt{2}V_s \sin \omega t$$

$$v_{BN} = \sqrt{2}V_s \sin\left(\omega t - \frac{2\pi}{3}\right)$$


$$v_{CN} = \sqrt{2}V_s \sin\left(\omega t + \frac{2\pi}{3}\right)$$

instantaneous input line voltages

$$v_{AB} = \sqrt{6}V_s \sin\left(\omega t + \frac{\pi}{6}\right)$$

$$v_{BC} = \sqrt{6}V_s \sin\left(\omega t - \frac{\pi}{2}\right)$$
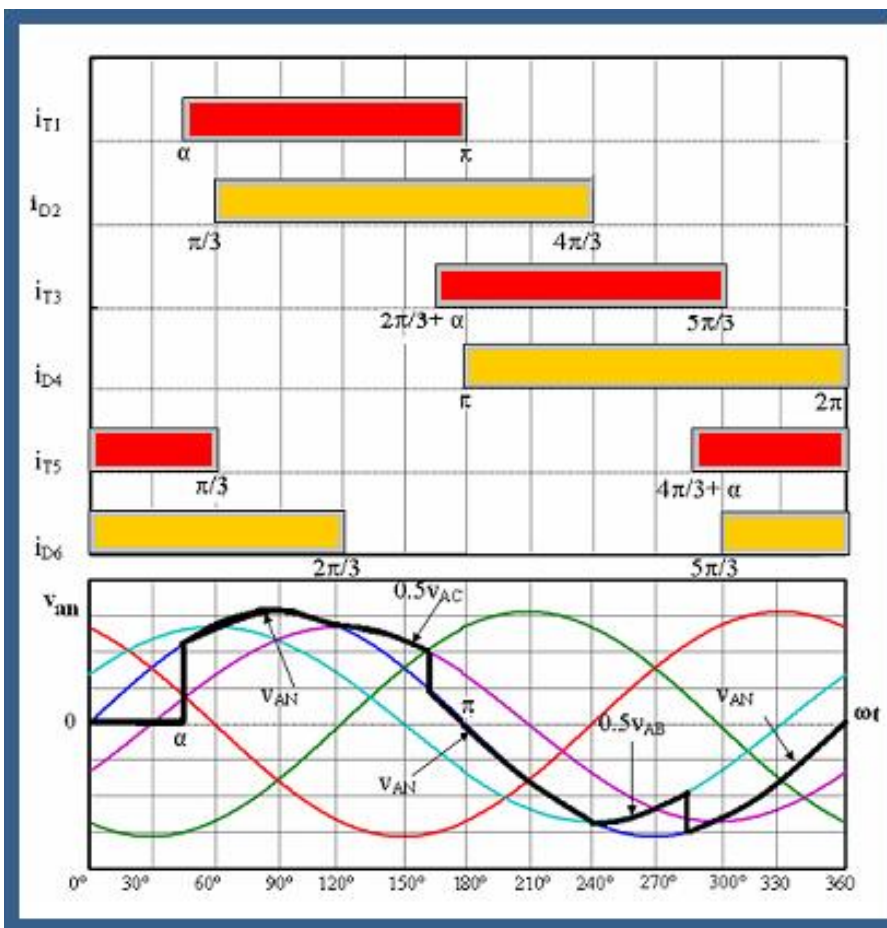
$$v_{CA} = \sqrt{6}V_s \sin\left(\omega t - \frac{7\pi}{6}\right)$$




Analysis of three-phase half-wave AC voltage controller with resistive load



For $\alpha = 45^\circ$, the expressions for instantaneous output phase voltage (v_{an}) is given by:

$0 \leq \omega t < \alpha$	➔	$v_{an} = 0$
$\alpha \leq \omega t < 2\pi/3$	➔	$v_{an} = V_{AN}$
$2\pi/3 \leq \omega t < \alpha + 2\pi/3$	➔	$v_{an} = 0.5 V_{AC}$
$\alpha + 2\pi/3 \leq \omega t < \pi$	➔	$v_{an} = V_{AN}$
$\pi \leq \omega t < 4\pi/3$	➔	$v_{an} = V_{AN}$
$4\pi/3 \leq \omega t < 4\pi/3 + \alpha$	➔	$v_{an} = 0.5 V_{AB}$
$\alpha + 4\pi/3 \leq \omega t < 2\pi$	➔	$v_{an} = V_{AN}$

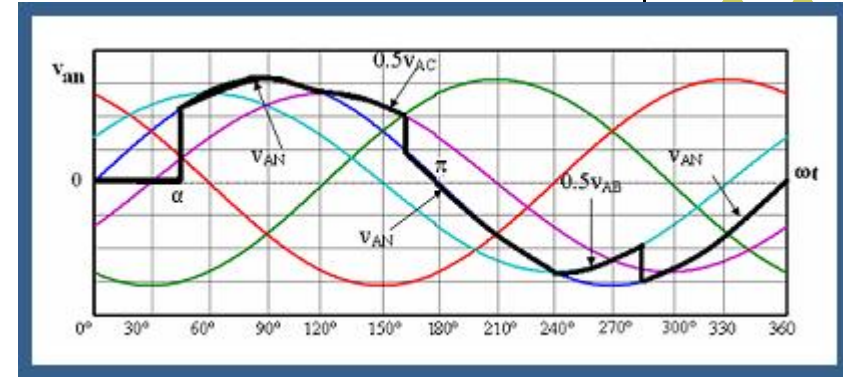

$$v_{CA} = \sqrt{6} V_s \sin(\omega t - 7\pi/6)$$

$$v_{AC} = -v_{CA} = \sqrt{6} V_s \sin(\omega t - (7\pi/6 - \pi))$$

$$v_{AC} = \sqrt{6} V_s \sin(\omega t - \pi/6)$$


Analysis of three-phase half-wave AC voltage controller with resistive load



The rms value of the output phase voltage

$V_{an(rms)}$
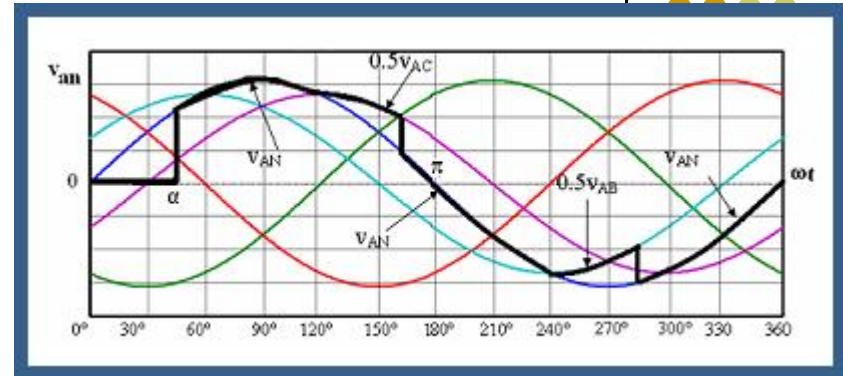
$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$



$$v_{an} = \left\{ \frac{1}{2\pi} \left[\int_{\alpha}^{2\pi/3} v_{AN}^2 d\omega t + \int_{2\pi/3}^{2\pi/3+\alpha} (0.5v_{AC})^2 d\omega t + \int_{2\pi/3+\alpha}^{\pi} v_{AN}^2 d\omega t + \int_{\pi}^{4\pi/3} v_{AN}^2 d\omega t + \int_{4\pi/3}^{4\pi/3+\alpha} (0.5v_{AB})^2 d\omega t + \int_{4\pi/3+\alpha}^{2\pi} v_{AN}^2 d\omega t \right] \right\}^{0.5}$$

$\alpha = 45^\circ$

$$v_{AN} = \sqrt{2} V_s \sin \omega t$$

$$v_{AB} = \sqrt{6} V_s \sin(\omega t + \pi/6)$$


$$v_{AC} = \sqrt{6} V_s \sin(\omega t - \pi/6)$$

$$v_{an} = \sqrt{6} V_s \left[\frac{1}{2\pi} \left\{ \int_{\alpha}^{2\pi/3} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{2\pi/3}^{2\pi/3+\alpha} \left(\frac{1}{4}\right) \sin^2 \omega t d(\omega t) + \int_{2\pi/3+\alpha}^{\pi} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{\pi}^{4\pi/3} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{4\pi/3}^{4\pi/3+\alpha} \left(\frac{1}{4}\right) \sin^2 \omega t d(\omega t) + \int_{4\pi/3+\alpha}^{2\pi} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) \right\} \right]^{0.5}$$

$$V_0 = \sqrt{3} V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right)}$$



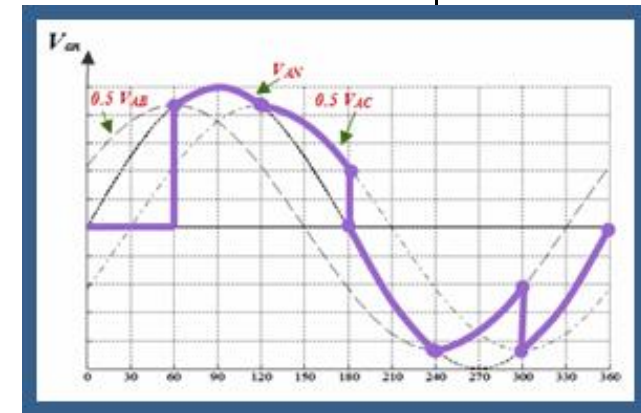Analysis of three-phase half-wave AC voltage controller with resistive load



RMS value of the output voltage

Firing angle range

$0 \leq \alpha < 60^\circ$

Two thyristors and one diode conduct.
 One thyristor and one diode conduct.
 One thyristor and two diodes conduct.

$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$

$60^\circ \leq \alpha < 120^\circ$

One Thyristor and one Diode conduct
 One Thyristor and two Diodes conduct


$60^\circ \leq \alpha < 90^\circ$

$90^\circ \leq \alpha < 120^\circ$

$120^\circ \leq \alpha < 210^\circ$

One Thyristor and one Diode conduct

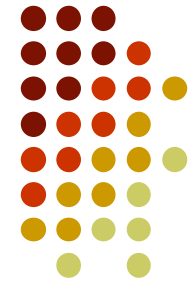Analysis of three-phase half-wave AC voltage controller with resistive load



RMS value of the output voltage

- The expressions of the rms value of the output voltage per phase for balanced star-connected resistive load are :

$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$

Mode (1)

$$0^\circ \leq \alpha < 90^\circ$$



$$V_0 = \sqrt{3}V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right)}$$

Mode (2)

$$90^\circ \leq \alpha < 120^\circ$$



$$V_0 = \sqrt{3}V_s \sqrt{\frac{1}{\pi} \left(\frac{11\pi}{24} - \frac{\alpha}{2} \right)}$$

Mode (3)

$$120^\circ \leq \alpha < 210^\circ$$



$$V_0 = \sqrt{3}V_s \sqrt{\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} - \frac{\sqrt{3} \cos 2\alpha}{16} \right)}$$

Analysis of three-phase half-wave AC voltage controller with resistive load



RMS Output current

$$I_0 = \frac{V_0}{R_L}$$

Where: $I_0 = I_a$ is the Output (load) current in phase (a)

Output power

$$P_0 = 3I_0^2 R_L$$

Input VA rating

$$VA = 3V_s I_0$$

Supply power factor

$$PF = \frac{P_0}{VA}$$



Ex .1: The three-phase unidirectional controller supplies a wye-connected resistive load of $10 \Omega/\text{phase}$ and the line-to-line input voltage is 380-V , 50 Hz . The firing delay angle is 150° .

- (a) Draw the output phase voltage waveform.
- (b) Drive the output phase voltage expression.
- (b) Determine the rms output phase voltage and current.
- (b) Determine the input power factor.

Solution

$$V_L = 380\text{v} \quad f_s = 50 \text{ Hz} \quad R = 10 \text{ ohm} \quad \alpha = 150^\circ$$

(a) the rms output phase voltage

Mode (3)
Firing angle range
($120^\circ \leq \alpha < 210^\circ$)



$$V_0 = \sqrt{3}V_s \sqrt{\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right)}$$

$V_{an(rms)}$

$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$

$$V_{a(rms)} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (0.5 v_{AC})^2 d\omega + \frac{1}{2\pi} \int_0^{2\pi} (0.5 v_{AB})^2 d\omega}$$

$$v_{AB} = \sqrt{6} V_s \sin(\omega t + \pi/6)$$


$$v_{AC} = \sqrt{6} V_s \sin(\omega t - \pi/6)$$

$$V_{a(rms)} = \sqrt{6} V_s \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{1}{4} \sin^2 \omega t d\omega + \frac{1}{2\pi} \int_0^{2\pi} \frac{1}{4} \sin^2 \omega t d\omega}$$

$$V_0 = \sqrt{3} V_s \sqrt{\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right)}$$


$$V_s = 380/\sqrt{3} = 219.4v$$
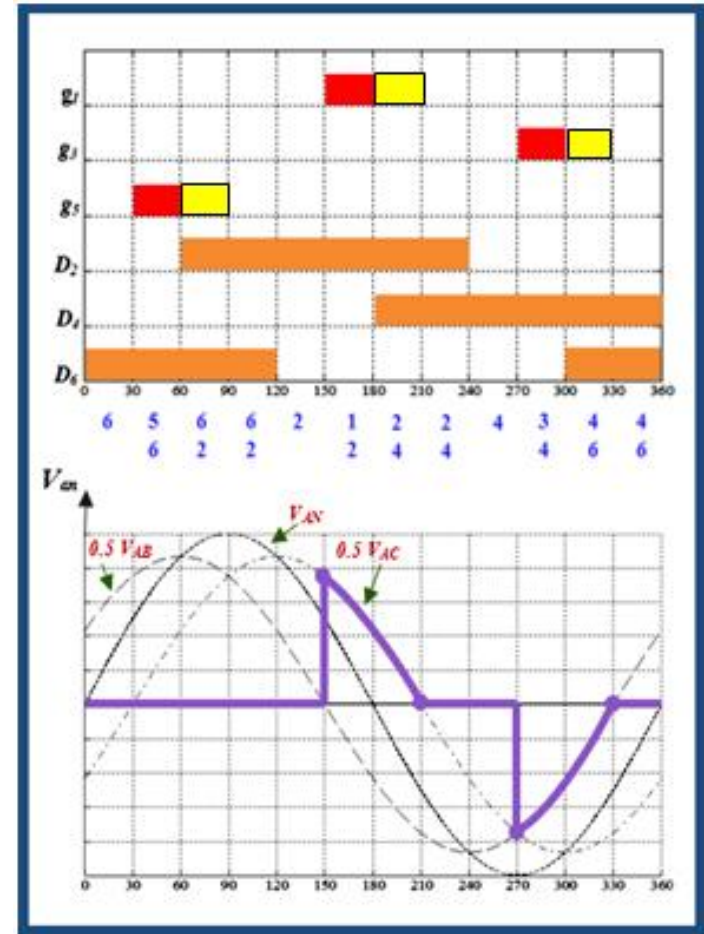
$$V_{a(rms)} = \sqrt{3} \times 219.4 \sqrt{\frac{1}{\pi} \left(\frac{7\pi}{24} - \frac{150\pi}{4 \times 180} + \frac{\sin 2 \times 150}{16} + \frac{\sqrt{3} \cos 2 \times 150}{16} \right)} = 109.8 v$$




RMS Output current

$$I_o = \frac{V_o}{R_L}$$

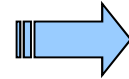

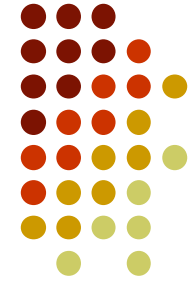
$$I_o = 109.8/10 = 10.98 \text{ A} \approx 11 \text{ A}$$



Output power


$$P_o = 3I_o^2 R_L$$

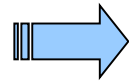

$$P_o = 3 (11)^2 \times 10 = 3630 \text{ w}$$

Input VA rating


$$VA = 3V_s I_o$$

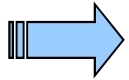

$$VA = 3 \times 219.4 \times 11 = 7240.2 \text{ VA}$$

Supply power factor

$$PF = \frac{P_o}{VA}$$

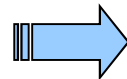

$$PF = 3630 / 7240.2 = 0.5 \text{ (lagging)}$$



Ex .2: The three-phase unidirectional AC voltage controller supplies a wye connected resistive load of 50Ω , and the line to line voltage is 208V at 60Hz . The delay is $\alpha = \pi/3$.


- (a) Draw the output phase voltage waveform.
- (b) Drive the output phase voltage expression.
- (c) Determine the rms value of output voltage and current
- (d) Determine the input power factor.
- (d) the expressions for the instantaneous output voltage of phase a.

Solution

$$V_L = 208 \text{ v} \quad f_s = 60 \text{ Hz} \quad R = 50 \text{ ohm} \quad \alpha = 60^\circ = \pi/3 \text{ radians}$$

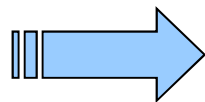(a) the rms output phase voltage

Mode (1)
Firing angle range
($0^\circ \leq \alpha < 90^\circ$)



$$V_0 = \sqrt{3} V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right)}$$

$$V_s = 208 / \sqrt{3} = 120 \text{ v}$$

$V_{an(rms)}$


$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$

$$v_{an} = \left\{ \frac{1}{2\pi} \left[\int_{\pi/3}^{2\pi/3} v_{AN}^2 d\omega t + \int_{2\pi/3}^{\pi} (0.5v_{AC})^2 d\omega t + \int_{\pi}^{4\pi/3} v_{AN}^2 d\omega t + \int_{4\pi/3}^{5\pi/3} (0.5v_{AB})^2 d\omega t + \int_{5\pi/3}^{2\pi} v_{AN}^2 d\omega t \right] \right\}^{0.5}$$

$$v_{AN} = \sqrt{2} V_s \sin \omega t$$


$$v_{AC} = \sqrt{6} V_s \sin (\omega t - \pi/6)$$
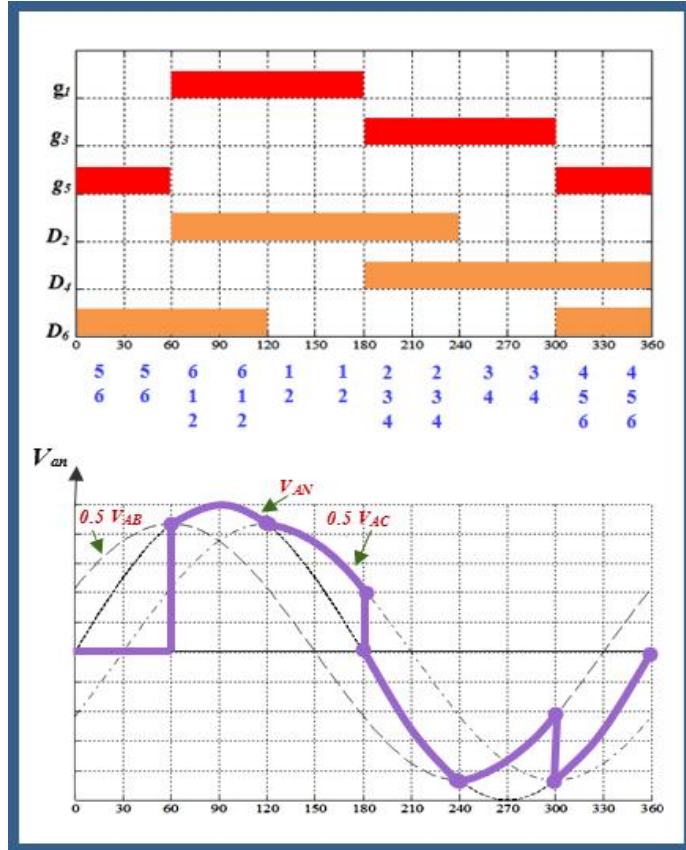
$$v_{AB} = \sqrt{6} V_s \sin (\omega t + \pi/6)$$



$$v_{an} = \sqrt{6} V_s \left\{ \frac{1}{2\pi} \left[\int_{\pi/3}^{2\pi/3} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{2\pi/3}^{\pi} \left(\frac{1}{4}\right) \sin^2 \omega t d(\omega t) + \int_{\pi}^{4\pi/3} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{4\pi/3}^{5\pi/3} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) + \int_{5\pi/3}^{2\pi} \left(\frac{1}{3}\right) \sin^2 \omega t d(\omega t) \right] \right\}^{0.5}$$

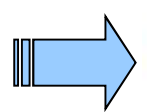
$$V_0 = \sqrt{3} V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{3} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right)}$$



$$V_{a(rms)} = \sqrt{3} \times 120 \left(\frac{1}{\pi} \left[\frac{\pi}{3} - \frac{\pi/3}{4} + \frac{\sin 2 \times 60^\circ}{8} \right] \right)^{0.5} = \mathbf{110.86 \text{ v}}$$

RMS Output current

$$I_o = \frac{V_o}{R_L}$$

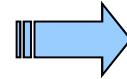


$$I_o = 110.86/50 = 2.22 \text{ A}$$



Output power


$$P_o = 3I_o^2 R_L$$

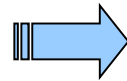

$$P_o = 3 (2.22)^2 \times 50 = 739.26 \text{ w}$$

Input VA rating


$$VA = 3V_s I_o$$

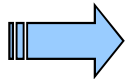

$$VA = 3 \times 120 \times 2.22 = 799.2 \text{ VA}$$


Supply power factor

$$PF = \frac{P_o}{VA}$$

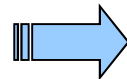

$$PF = 739.26 / 799.2 = 0.925 \text{ (lagging)}$$

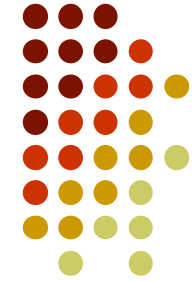
Expressions for the instantaneous output voltage of phase a.



$$V_s = 120 \text{ v}$$


$$v_{AN} = \sqrt{2} V_s \sin \omega t$$

For $0 \leq \omega t < \pi/3$

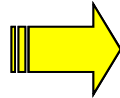

$$v_{an} = 0$$


For $\pi/3 \leq \omega t < 2\pi/3$

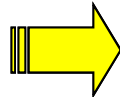

$$v_{an} = v_{AN} = 169.7 \sin \omega t$$


$$v_{AC} = \sqrt{6} V_s \sin(\omega t - \pi/6)$$

For $2\pi/3 \leq \omega t < \pi$

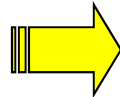


$$v_{an} = v_{AC}/2 = -v_{CA}/2 = 147.1 \sin(\omega t - \pi/6)$$

For $\pi \leq \omega t < 4\pi/3$

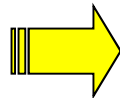


$$v_{an} = v_{AN} = 169.7 \sin \omega t$$

For $4\pi/3 \leq \omega t < 5\pi/3$

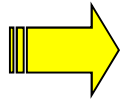

$$v_{an} = v_{AB}/2 = 147.1 \sin(\omega t + \pi/6)$$

For $5\pi/3 \leq \omega t < 2\pi$

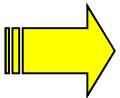

$$v_{an} = v_{AN} = 169.7 \sin \omega t$$

$$v_{AB} = \sqrt{6} V_s \sin(\omega t + \pi/6)$$