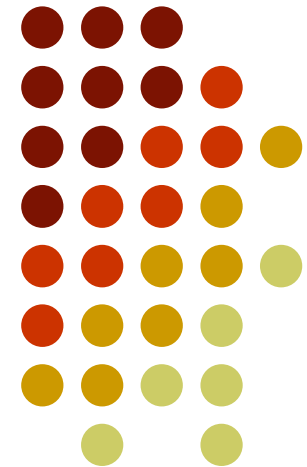


Chapter 4

Three-phase full-wave AC voltage controllers

By

Dr. Ayman Yousef






**Three-phase full-wave
AC voltage controllers
with resistive load**

Three-Phase Full-Wave AC Voltage Controller (Three-Wire, Star-Connected Load)




- | The neutral of the supply is not connected to the neutral of the load.
- | The firing sequence of thyristors is $T_1, T_2, T_3, T_4, T_5, T_6$.
- | The gate-control circuit must be capable of triggering at the same instant two thyristor, one in each of two phases.
- | These pulses are applied at intervals of 60° to various thyristors in a sequence the same as that of the supply voltage.

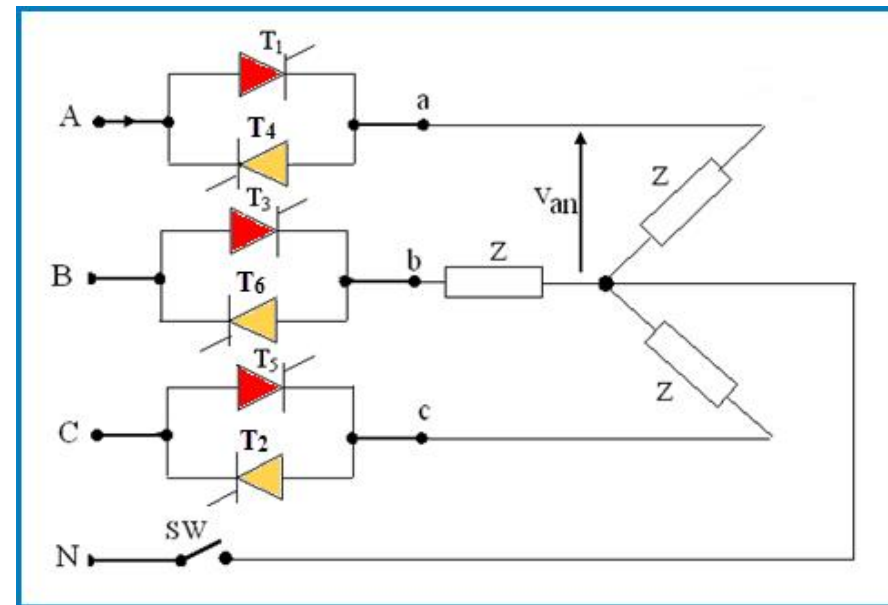

- | The current flow to the load is controlled by the thyristors T_1, T_3 and T_5 and the thyristors T_2, T_4 and T_6 provide the return current path.

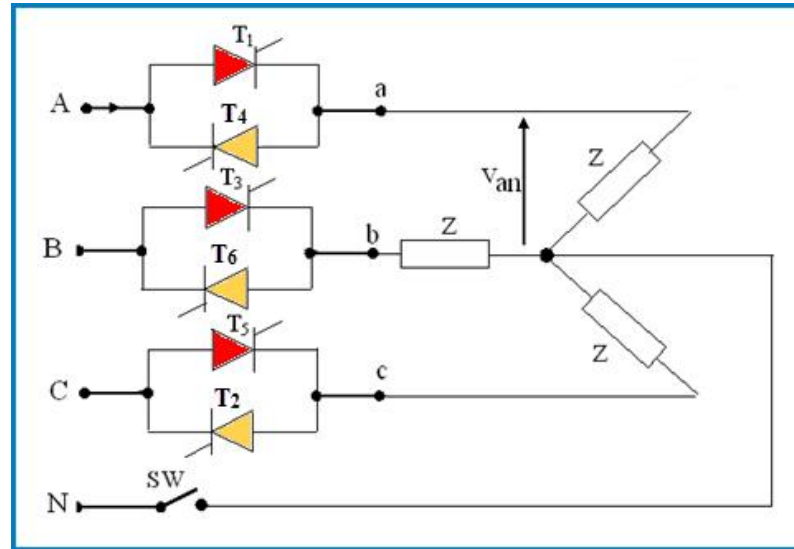Three-Phase Full-Wave AC Voltage Controller



instantaneous input voltage per phase

V_s = RMS value of input ac supply

$$v_{AN} = \sqrt{2} V_s \sin \omega t$$

$$v_{BN} = \sqrt{2} V_s \sin (\omega t - 120^\circ)$$

$$v_{CN} = \sqrt{2} V_s \sin (\omega t + 120^\circ)$$


instantaneous input line voltages

$$v_{AB} = \sqrt{6} V_s \sin (\omega t + 30^\circ)$$

$$v_{BC} = \sqrt{6} V_s \sin (\omega t - 90^\circ)$$

$$v_{CA} = \sqrt{6} V_s \sin (\omega t + 150^\circ)$$

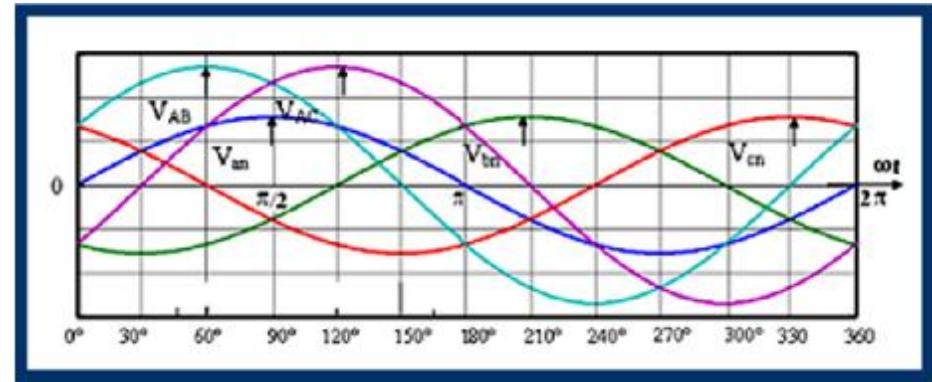Three-Phase Full-Wave AC Voltage Controller



- At any interval, either **three SCRs** or **two SCRs**, or **no SCRs** may be **ON (conduct)**
- If **three SCRs** conduct, a normal three-phase operation occurs and the output (load) phase voltage (v_{an}) is the same as the input (supply) phase voltage (v_{AN})

$$v_{an} = v_{AN} = \sqrt{2} V_s \sin \omega t$$


- If **two SCRs** conduct, the current flows only through two lines and the third line is open-circuited, and the output phase voltage (v_{an})

$$v_{an} = \frac{v_{AB}}{2} = \frac{\sqrt{3} \sqrt{2} V_s}{2} \sin \left(\omega t + \frac{\pi}{6} \right)$$

- If **no SCRs** conduct, the output phase voltage becomes zero.

$$v_{an} = 0$$

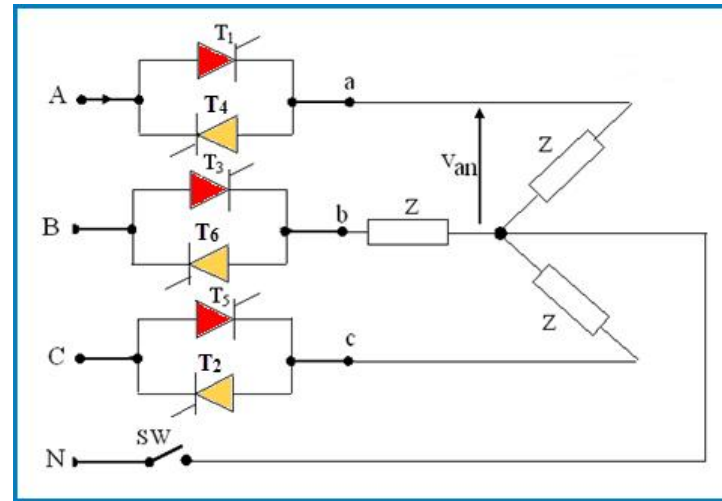Three-Phase full-Wave AC Voltage Controller




- I Mode ($0^\circ \leq \alpha < 60^\circ$) in this mode of operation, either **two** or **three thyristors** can **conduct** at the same time.
- I
- I Mode ($60^\circ \leq \alpha < 90^\circ$) in this mode of operation, at any time **two thyristors**, one in each phase, always conduct.
- I For ($90^\circ \leq \alpha < 150^\circ$) in this mode of operation, at any time **one** or **two thyristors** conduct at the same time.



3-Phase full-Wave AC Voltage Controller Mode ($0^\circ \leq \alpha < 60^\circ$)



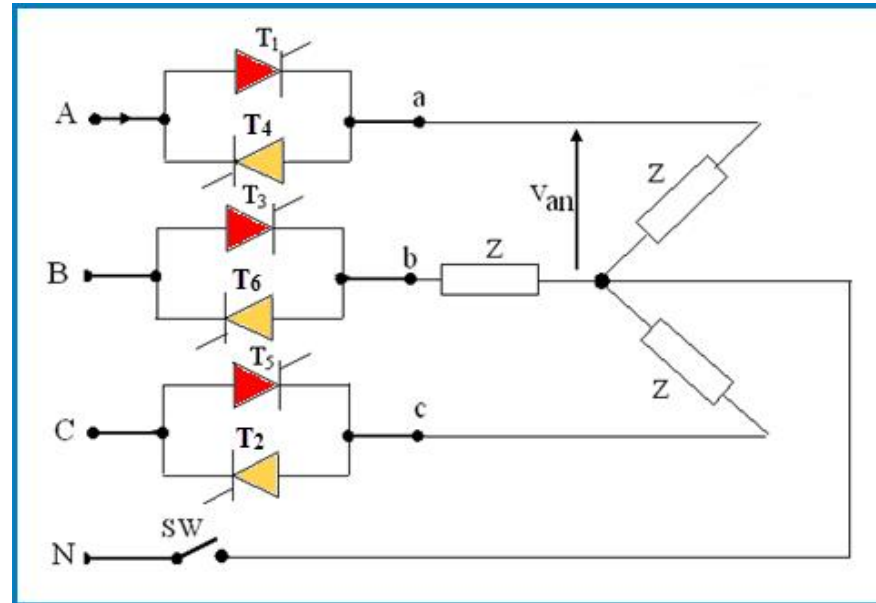
Switching Pattern of 3-Phase half-Wave AC Voltage Controller



I For ($0^\circ \leq \alpha < 60^\circ$)




In this mode of operation, either **two** or **three thyristors** can **conduct** at the same time.

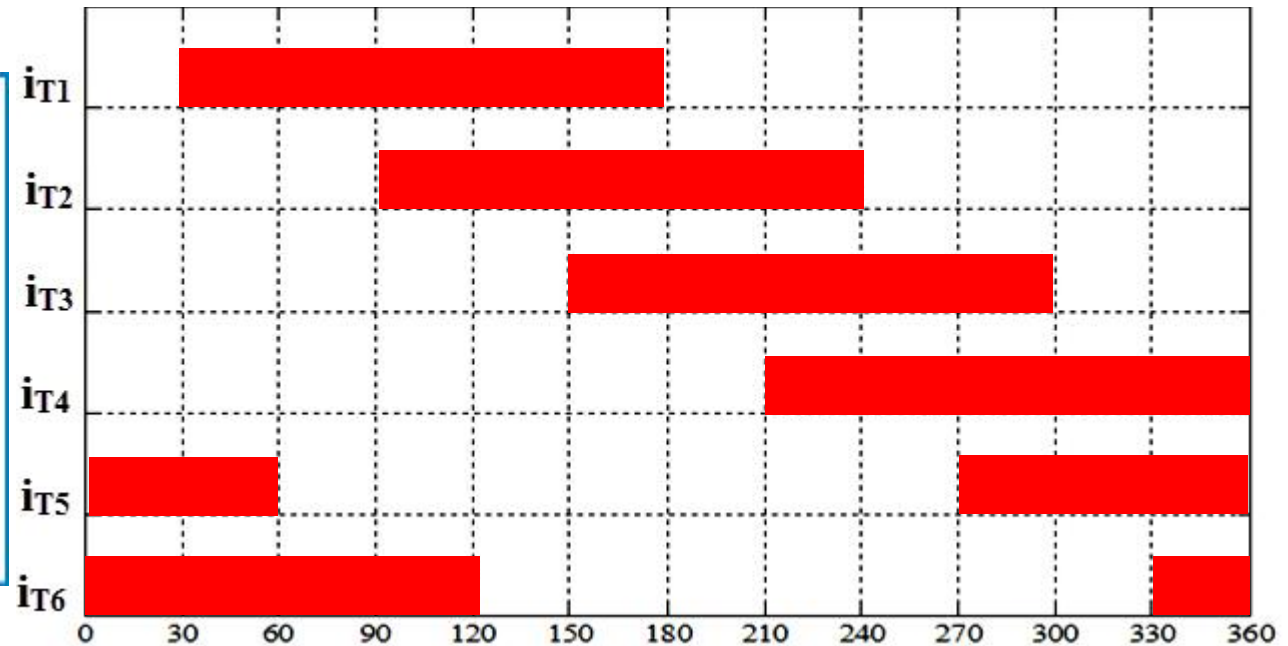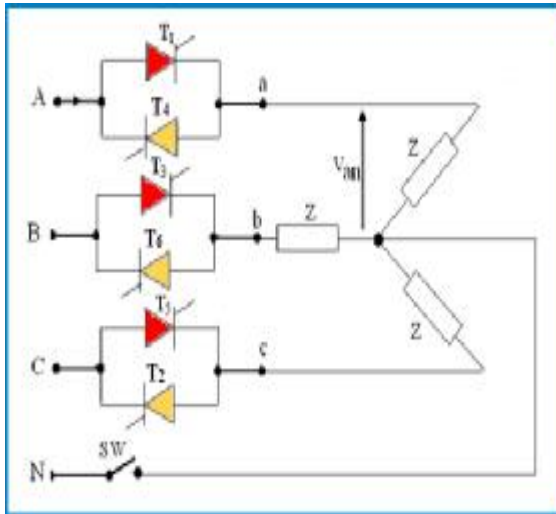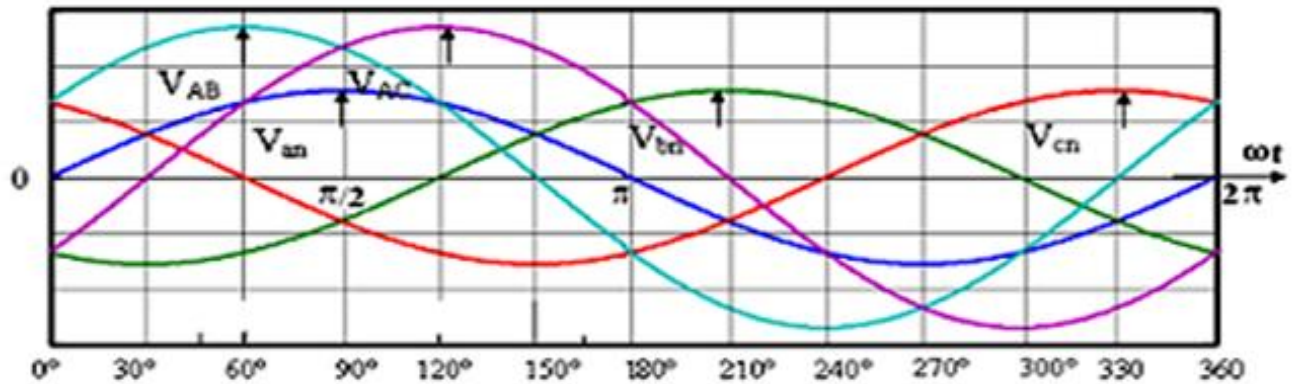Switching Pattern of 3-Phase full-Wave AC Voltage Controller at $(\alpha = 30^\circ)$




5	5	6	6	1	1	2	2	3	3	4	4
6	6	1	1	2	2	3	3	4	4	5	5
	1		2		3		4		5		6

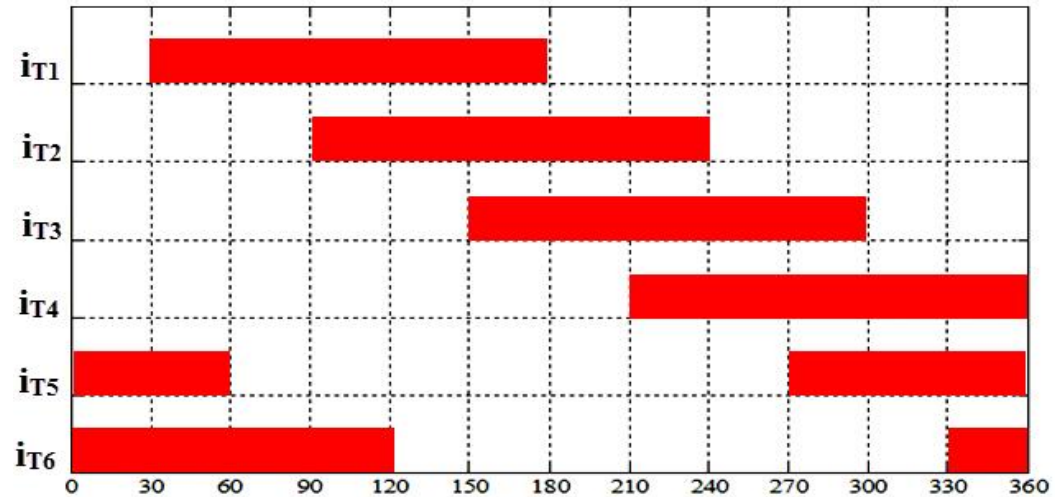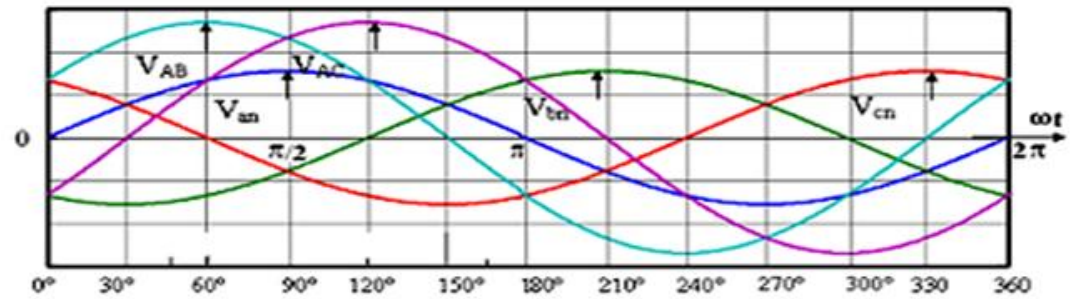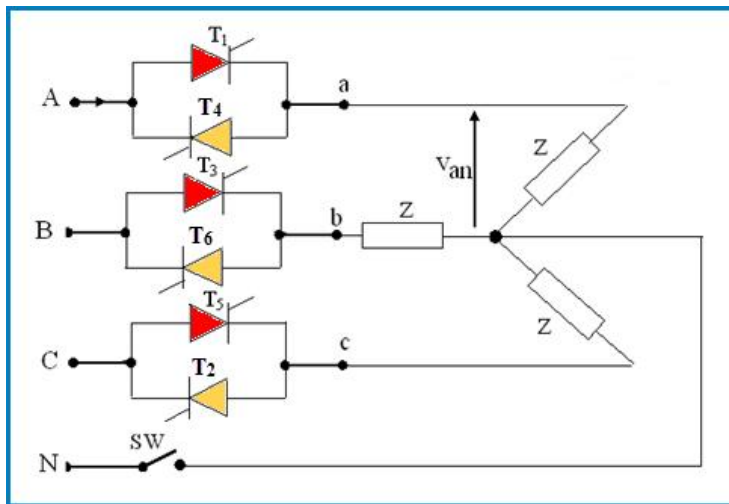Output voltage waveform for three-phase, star- connected, three-wire full- wave AC voltage controller ($\alpha=30^\circ$).




5	5	6	6	1	1	2	2	3	3	4	4
6	6	1	1	2	2	3	3	4	4	5	5
	1		2		3		4		5		6

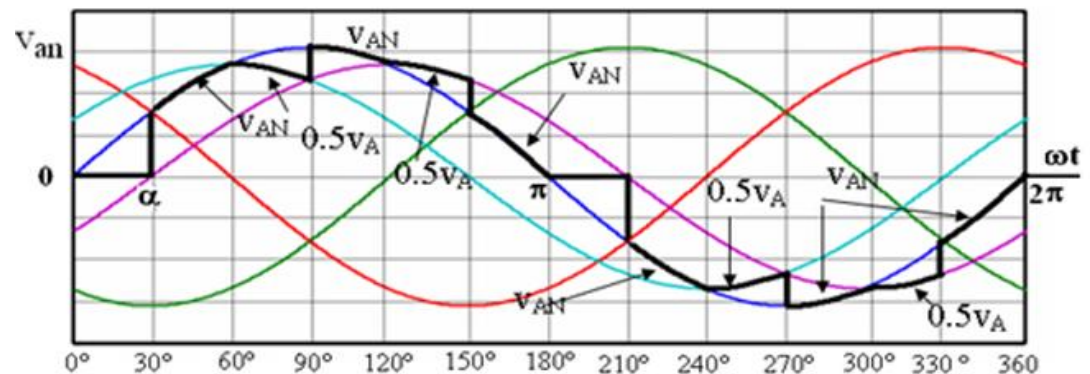



3-Phase full-Wave AC Voltage Controller Mode ($60^\circ \leq \alpha < 90^\circ$)



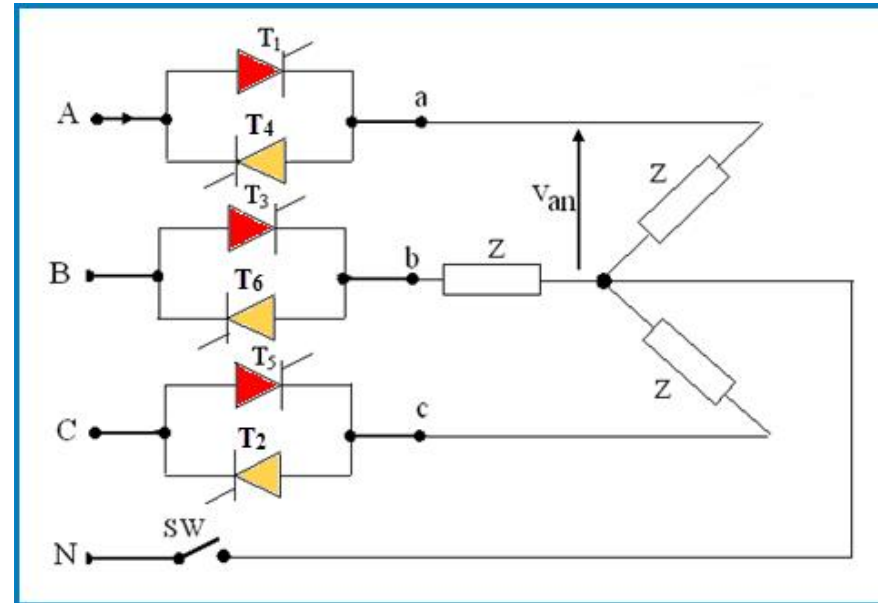
Switching Pattern of 3-Phase Half-Wave AC Voltage Controller



I Mode ($60^\circ \leq \alpha < 90^\circ$)





In this mode of operation, at any time **two thyristors**, one in each phase, always conduct.

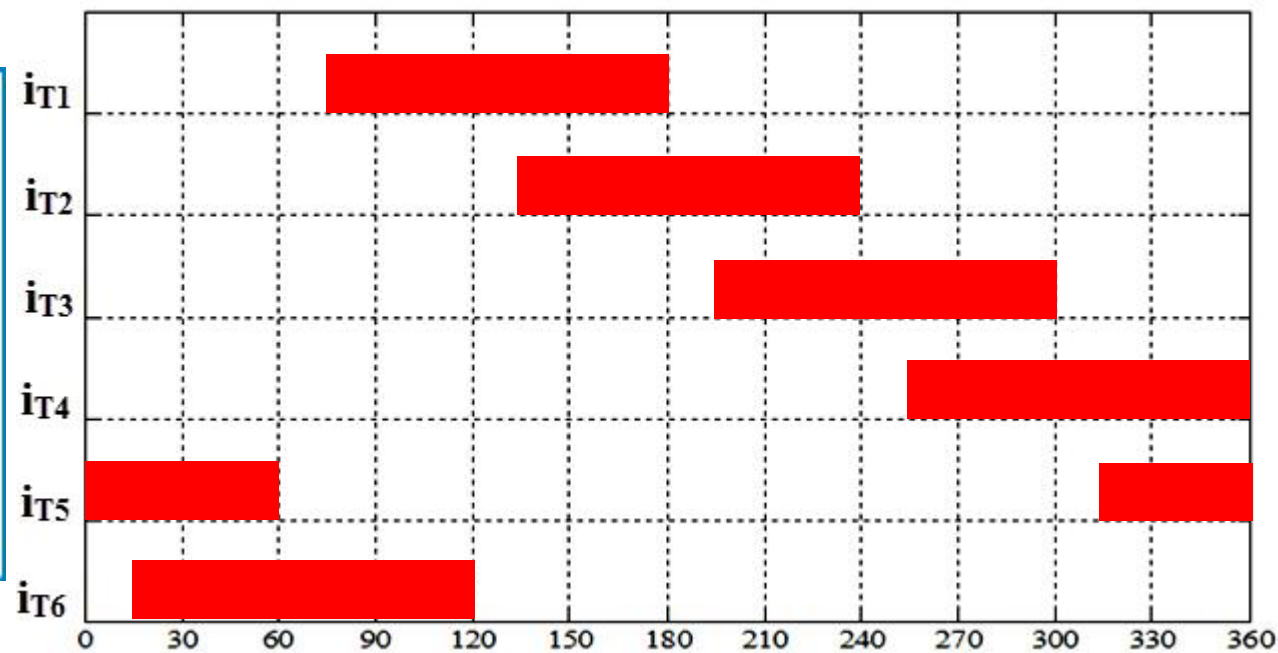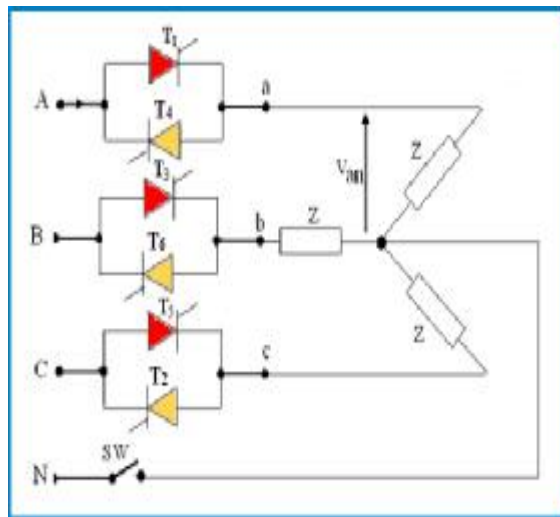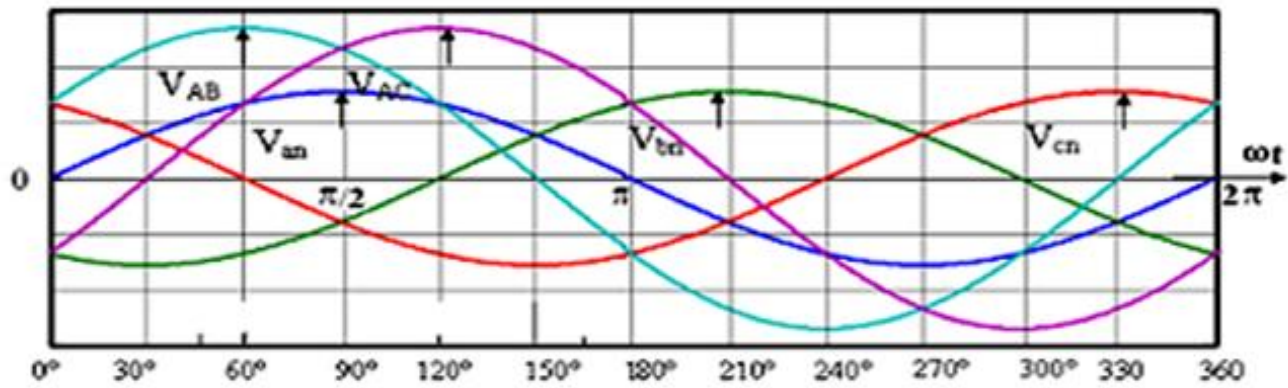Switching Pattern of 3-Phase Full-Wave AC Voltage Controller at $(\alpha = 75^\circ)$.



5	5	6	6	6	1	1	1	2	2	2	3	3	3	4	4	4
	6	1	1	2	2	3	3	4	4	5	5					

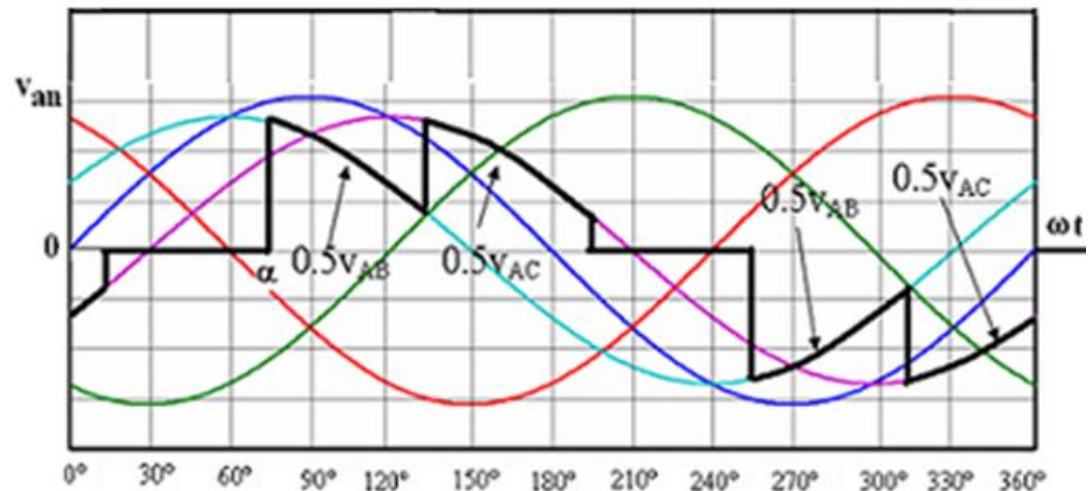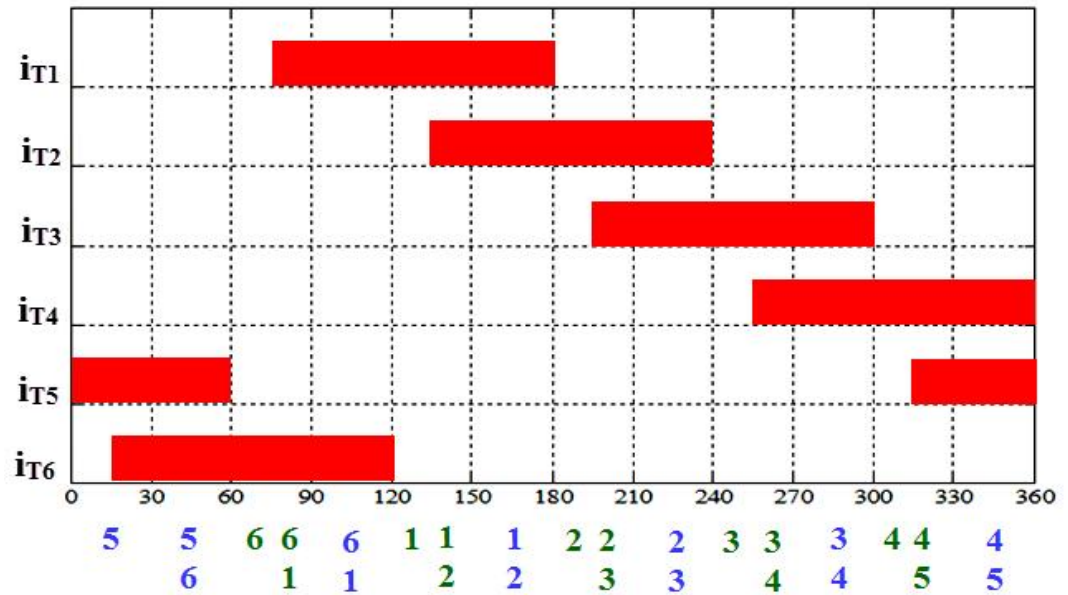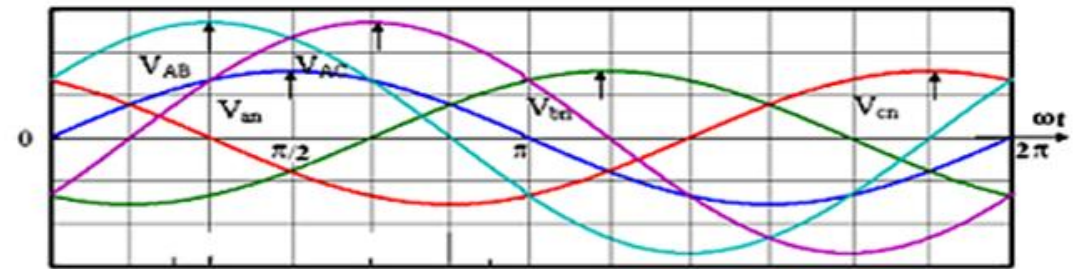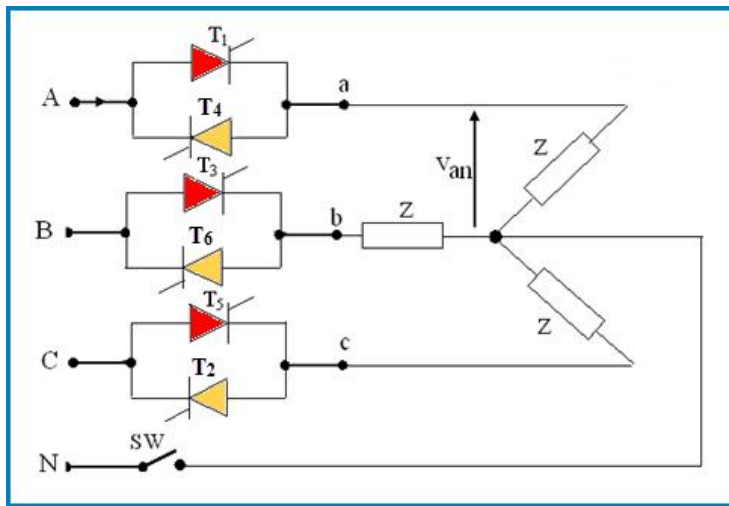
Output voltage waveform for three-phase, star- connected, three-wire full- wave AC voltage controller ($\alpha=75^\circ$).





**3-Phase full-Wave
AC Voltage Controller
Mode ($90^\circ \leq \alpha < 150^\circ$)**



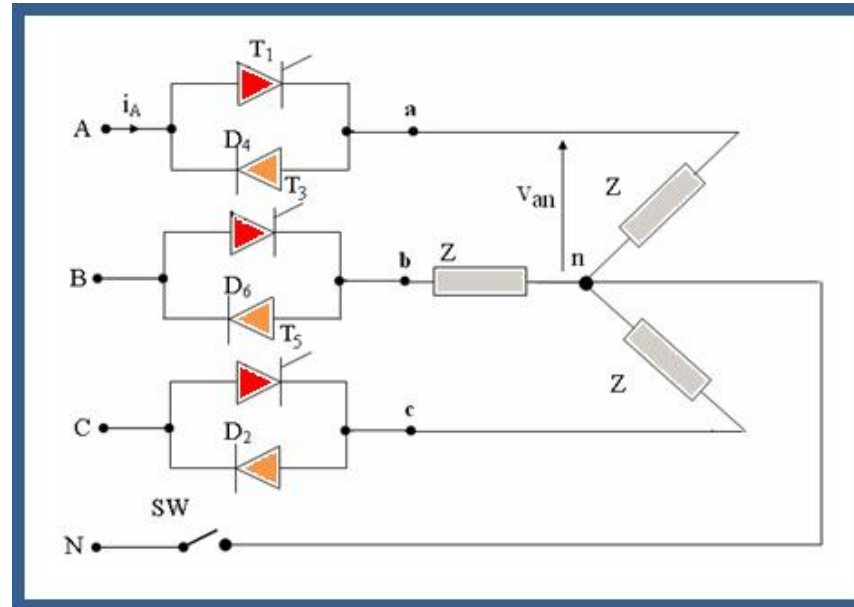
Switching Pattern of 3-Phase Half-Wave AC Voltage Controller







I Mode ($90^\circ \leq \alpha < 150^\circ$)

In this mode of operation, at any time **one** or **two thyristors** conduct at the same time.

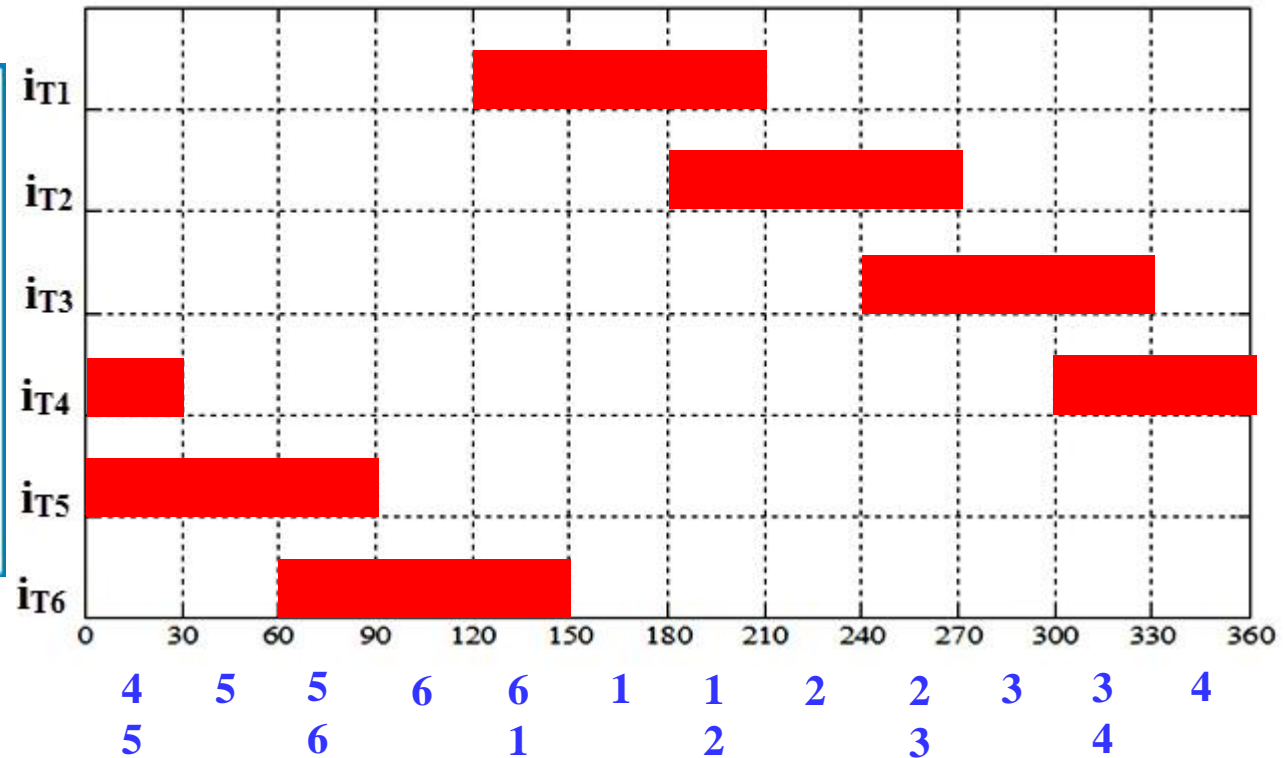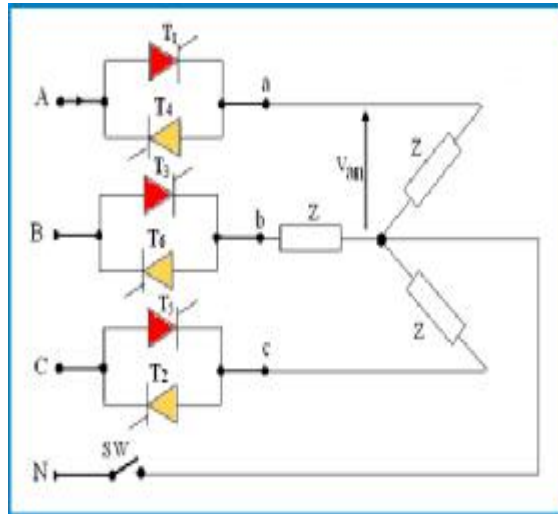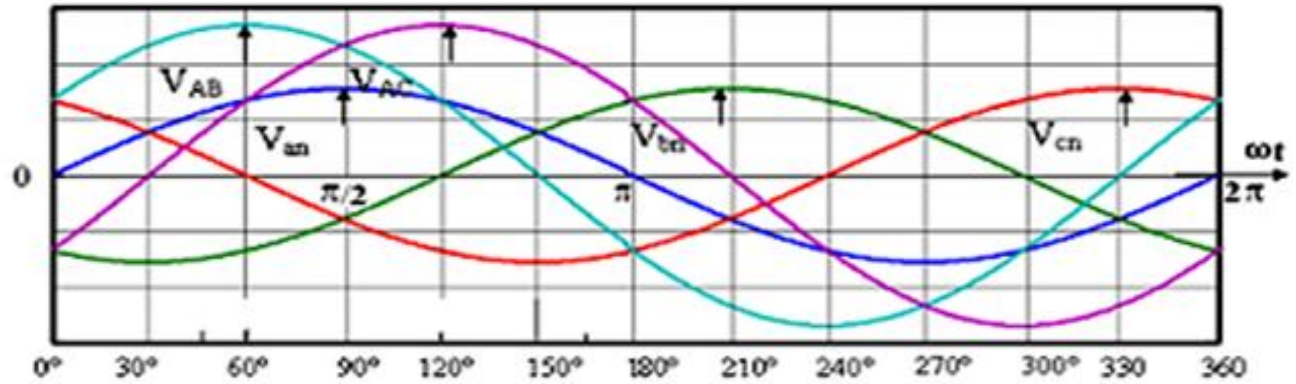Switching Pattern of 3-Phase Full-Wave AC Voltage Controller at $(\alpha = 120^\circ)$.



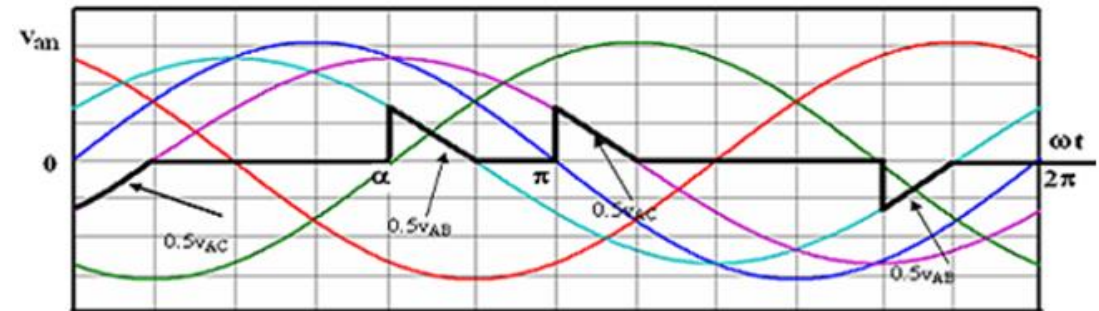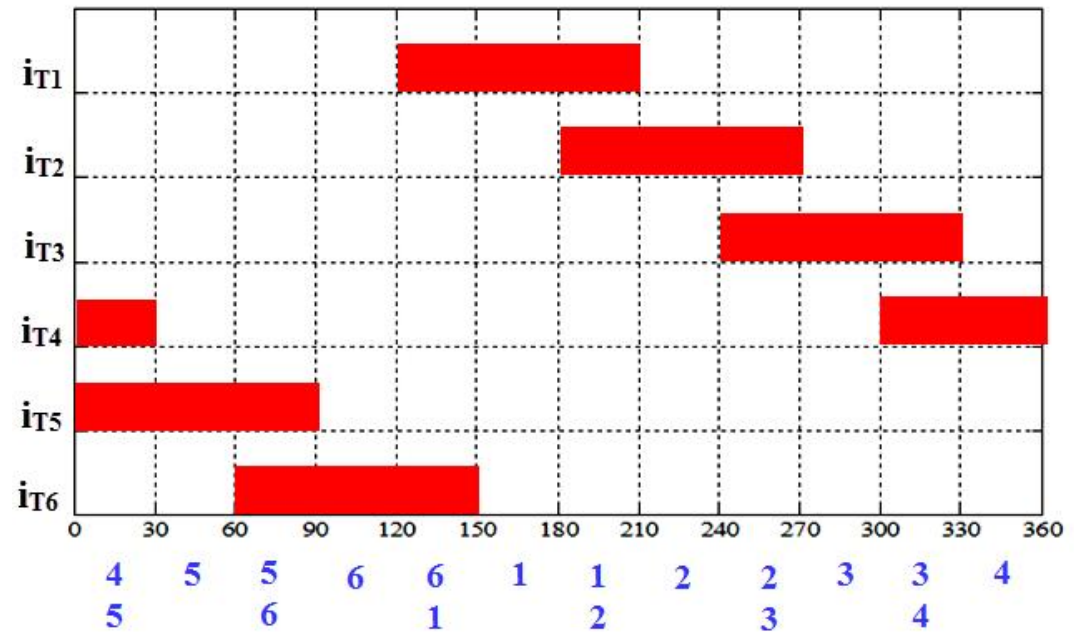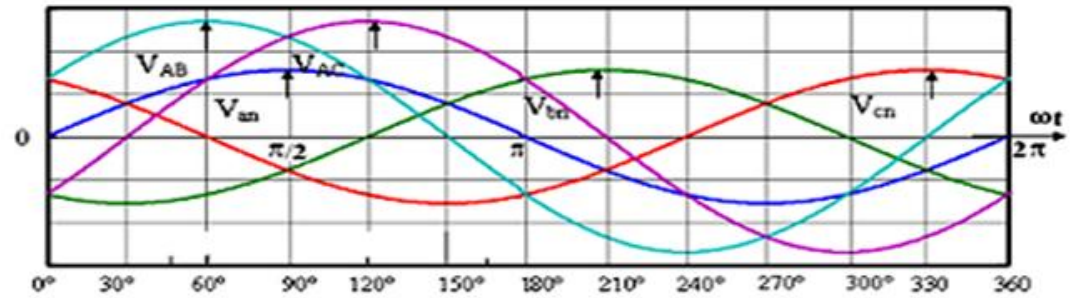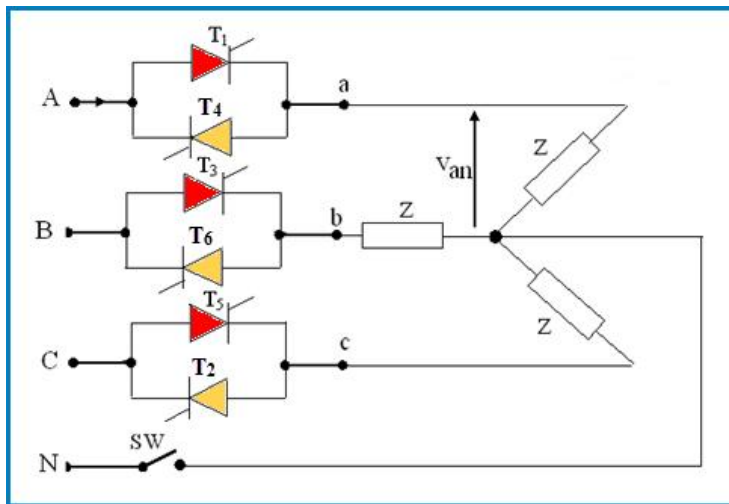Output voltage waveform for three-phase, star- connected, three-wire full- wave AC voltage controller ($\alpha=120^\circ$).




Analysis of three-phase Full-wave AC voltage controller with resistive load




RMS value of the output voltage

- I The expressions of the rms value of the output voltage per phase for balanced star-connected resistive load are as follows:
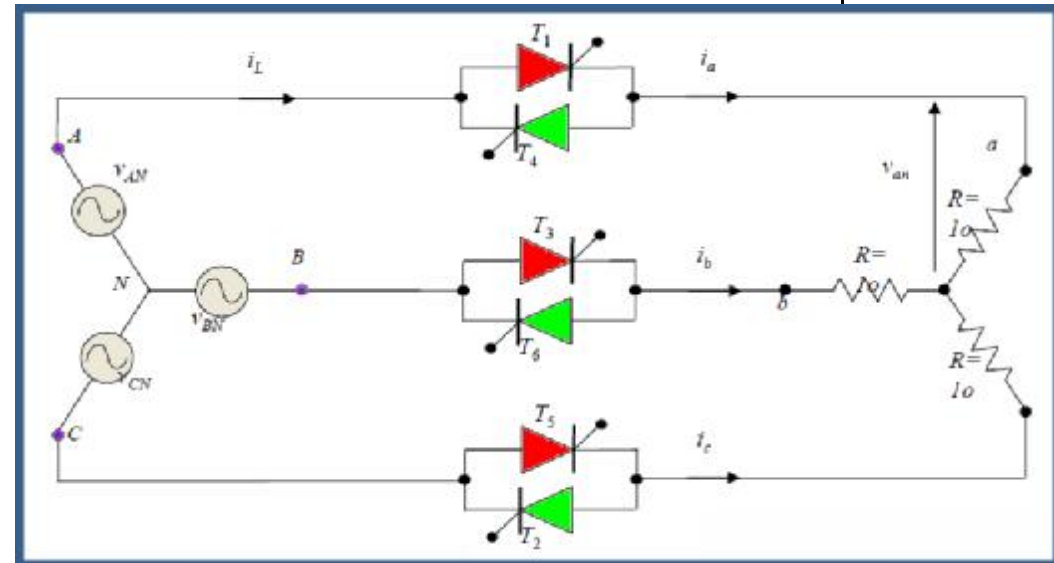
$$V_0 = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$


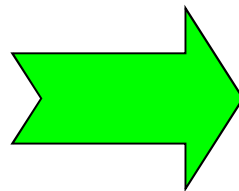
$$\begin{aligned} v_{AN} &= \sqrt{2}V_s \sin(\theta) \\ v_{BN} &= \sqrt{2}V_s \sin\left(\theta - \frac{2\pi}{3}\right) \\ v_{CN} &= \sqrt{2}V_s \sin\left(\theta + \frac{2\pi}{3}\right) \end{aligned}$$




$$\begin{aligned} v_{AB} &= \sqrt{6}V_s \sin\left(\theta + \frac{\pi}{6}\right) \\ v_{BC} &= \sqrt{6}V_s \sin\left(\theta - \frac{\pi}{2}\right) \\ v_{CA} &= \sqrt{6}V_s \sin\left(\theta - \frac{\pi}{6}\right) \end{aligned}$$

RMS output voltage at:

$$0 \leq \alpha < 60^\circ$$
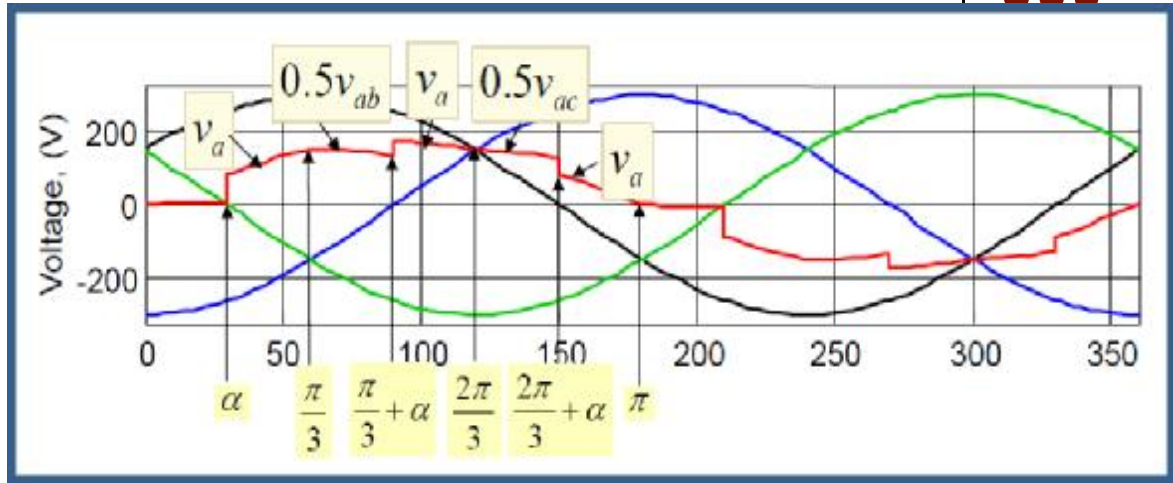
$$V_o = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$



$$V_o = \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{\pi/3} v_a^2 d(\omega t) + \int_{\pi/3}^{\pi/3+\alpha} \frac{v_{ab}^2}{4} d(\omega t) + \int_{\pi/3+\alpha}^{2\pi/3} v_a^2 d(\omega t) + \int_{2\pi/3}^{2\pi/3+\alpha} \frac{v_{ac}^2}{4} d(\omega t) + \int_{2\pi/3+\alpha}^{\pi} v_a^2 d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{\pi/3} \frac{\sin^2 \omega t}{3} d(\omega t) + \int_{\pi/3}^{\pi/3+\alpha} \frac{\sin^2(\omega t + \pi/6)}{4} d(\omega t) + \int_{\pi/3+\alpha}^{2\pi/3} \frac{\sin^2 \omega t}{3} d(\omega t) + \int_{2\pi/3}^{2\pi/3+\alpha} \frac{\sin^2(\omega t - \pi/6)}{4} d(\omega t) + \int_{2\pi/3+\alpha}^{\pi} \frac{\sin^2 \omega t}{3} d(\omega t) \right]}$$


$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{6} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{8} \right)}$$

$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{2\pi} + \frac{3}{4\pi} \sin 2\alpha \right\}}$$

RMS output voltage at:

$$60^\circ \leq \alpha < 90^\circ$$
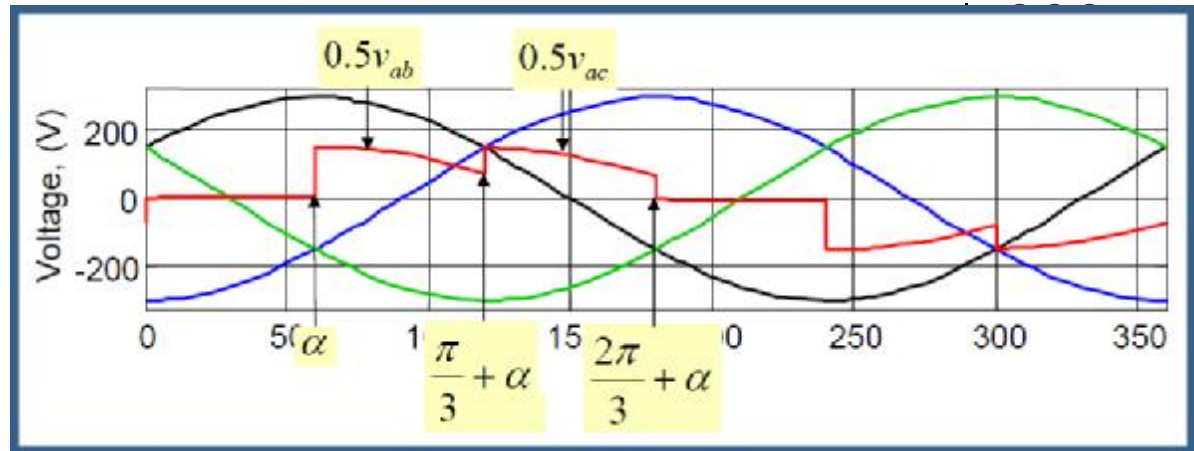
$$V_o = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$



$$V_o = \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{\pi/3+\alpha} \frac{v_{ab}^2}{4} d(\omega t) + \int_{\pi/3+\alpha}^{2\pi/3+\alpha} \frac{v_{ac}^2}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{\pi/3+\alpha} \frac{\sin^2(\omega t + \pi/6)}{4} d(\omega t) + \int_{\pi/3+\alpha}^{2\pi/3+\alpha} \frac{\sin^2(\omega t - \pi/6)}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha+\pi/6}^{\pi/3+\alpha+\pi/6} \frac{\sin^2 \omega t}{4} d(\omega t) + \int_{\pi/3+\alpha-\pi/6}^{2\pi/3+\alpha-\pi/6} \frac{\sin^2 \omega t}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha+\pi/6}^{\pi/2+\alpha} \frac{\sin^2 \omega t}{4} d(\omega t) + \int_{\pi/6+\alpha}^{\pi/2+\alpha} \frac{\sin^2 \omega t}{4} d(\omega t) \right]}$$


$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left(\frac{\pi}{12} + \frac{3 \sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right)}$$

$$V_o = V_s \sqrt{\left\{ \frac{1}{2} + \frac{9}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}}$$

RMS output voltage at:

$$90^\circ \leq \alpha < 150^\circ$$
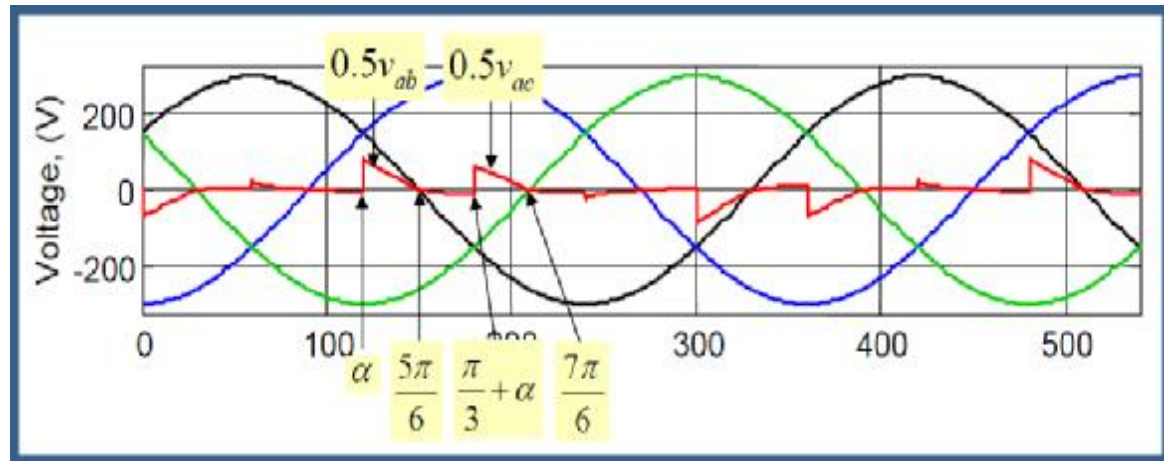
$$V_o = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$



$$V_o = \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{5\pi/6} \frac{v_{ab}^2}{4} d(\omega t) + \int_{\pi/3+\alpha}^{7\pi/6} \frac{v_{ac}^2}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{5\pi/6} \frac{\sin^2(\omega t + \pi/6)}{4} d(\omega t) + \int_{\pi/3+\alpha}^{7\pi/6} \frac{\sin^2(\omega t - \pi/6)}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\alpha+\pi/6}^{5\pi/6+\pi/6} \frac{\sin^2 \omega t}{4} d(\omega t) + \int_{\pi/3+\alpha-\pi/6}^{7\pi/6-\pi/6} \frac{\sin^2 \omega t}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left[\int_{\pi/6+\alpha}^{\pi} \frac{\sin^2 \omega t}{4} d(\omega t) + \int_{\pi/6+\alpha}^{\pi} \frac{\sin^2 \omega t}{4} d(\omega t) \right]}$$

$$V_o = \sqrt{6}V_s \sqrt{\frac{1}{\pi} \left(\frac{5\pi}{24} - \frac{\alpha}{4} + \frac{\sin 2\alpha}{16} + \frac{\sqrt{3} \cos 2\alpha}{16} \right)}$$


$$V_o = V_s \sqrt{\left\{ \frac{5}{4} - \frac{3\alpha}{2\pi} + \frac{3}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}}$$

Analysis of three-phase Full-wave AC voltage controller with resistive load




Mode I (also known as Mode 2/3): ($0^\circ \leq \alpha < 60^\circ$)
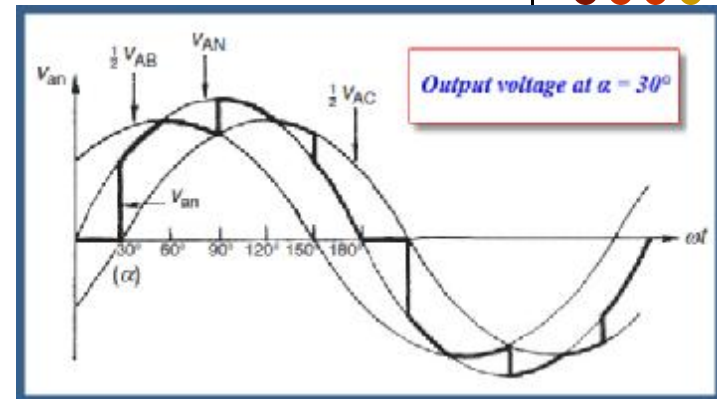
$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{2\pi} + \frac{3}{4\pi} \sin 2\alpha \right\}}$$




Mode II (also known as Mode 2/2): ($60^\circ \leq \alpha < 90^\circ$)
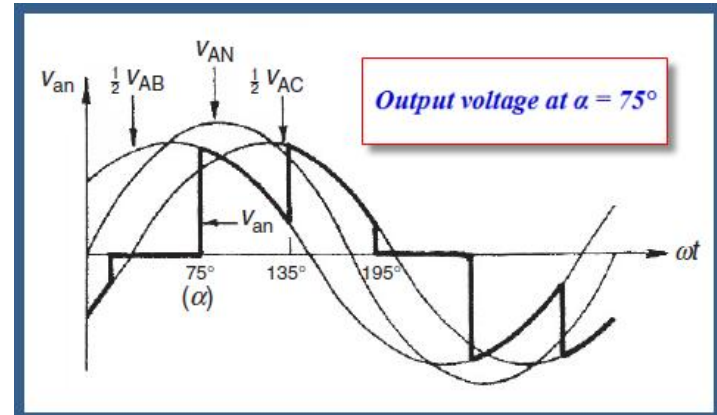
$$V_o = V_s \sqrt{\left\{ \frac{1}{2} + \frac{9}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}}$$



Mode III (also known as Mode 0/2): ($90^\circ \leq \alpha < 150^\circ$)
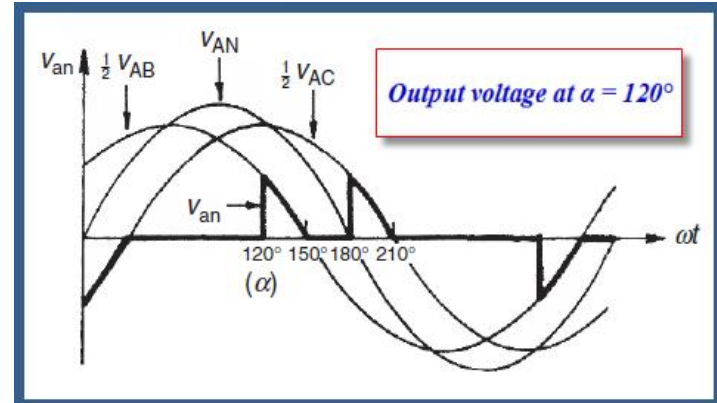
$$V_o = V_s \sqrt{\left\{ \frac{5}{4} - \frac{3\alpha}{2\pi} + \frac{3}{8\pi} \sin 2\alpha + \frac{3\sqrt{3}}{8\pi} \cos 2\alpha \right\}}$$



Analysis of three-phase Full-wave AC voltage controller with resistive load



RMS Output current

$$I_0 = \frac{V_0}{R_L}$$

Where: $I_0 = I_a$ is the Output
(load) current in phase (a)

Output power


$$P_0 = 3I_0^2 R_L$$

Input VA rating

$$VA = 3V_s I_0$$

Supply power factor

$$PF = \frac{P_0}{VA}$$

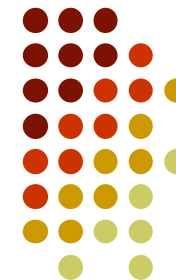

Ex .1: The three-phase bidirectional controller supplies a wye-connected resistive load of $10 \Omega/\text{phase}$ and the line-to-line input voltage is 380-V , 50 Hz . The firing delay angle is 30° .

- (a) Draw the output phase voltage waveform.
- (b) Drive the output phase voltage expression.
- (b) Determine the rms output phase voltage and current.
- (b) Determine the input power factor.

Solution

$$V_L = 380\text{v} \quad f_s = 50 \text{ Hz} \quad R = 10 \text{ ohm} \quad \alpha = 30^\circ$$

(a) the rms output phase voltage

Mode (1)
Firing angle range
($0^\circ \leq \alpha < 60^\circ$)



$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{2\pi} + \frac{3}{4\pi} \sin 2\alpha \right\}}$$

$$V_s = 380/\sqrt{3} = 219.4\text{v}$$

$$v_{AN} = \sqrt{2} V_s \sin \omega t$$

$$v_{AB} = \sqrt{6} V_s \sin(\omega t + \pi/6)$$

$$v_{AC} = \sqrt{6} V_s \sin(\omega t - \pi/6)$$

The expression for the instantaneous output phase voltage, v_{an} , the positive half-cycle is:

$$0 \leq \omega t < \pi/6 : v_{an} = 0.$$

$$\pi/6 \leq \omega t < \pi/3 : v_{an} = v_{AN} = \sqrt{2} V_s \sin(\omega t).$$

$$\pi/3 \leq \omega t < \pi/2 : v_{an} = 0.5 v_{AB} = \sqrt{6}/2 V_s \sin(\omega t + \pi/6).$$



$$\pi/2 \leq \omega t < 2\pi/3 : v_{an} = v_{AN} = \sqrt{2} V_s \sin(\omega t).$$

$$2\pi/3 \leq \omega t < 5\pi/6 : v_{an} = 0.5 v_{AC} = \sqrt{6}/2 V_s \sin(\omega t - \pi/6).$$

$$5\pi/6 \leq \omega t < \pi : v_{an} = v_{AN} = \sqrt{2} V_s \sin(\omega t).$$

The rms value of the output phase voltage (V_o) can be derived as follows:
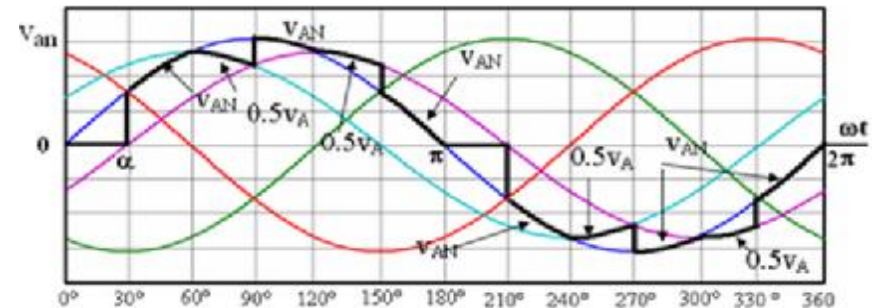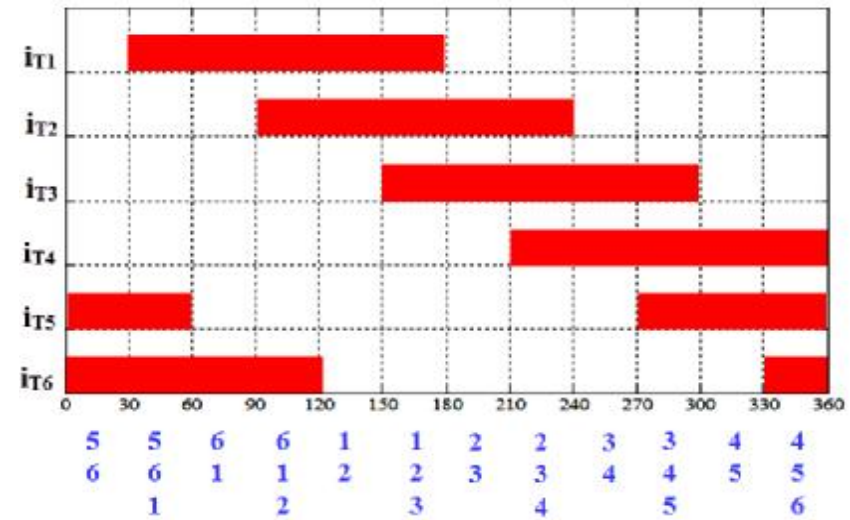
$$V_o = \left[\frac{1}{\pi} \left[\int_{\pi/6}^{\pi/3} v_{AN}^2 d\omega t + \int_{\pi/3}^{\pi/2} (0.5v_{AB})^2 d\omega t + \int_{\pi/2}^{2\pi/3} v_{AN}^2 d\omega t + \int_{2\pi/3}^{5\pi/6} (0.5v_{AC})^2 d\omega t + \int_{5\pi/6}^{\pi} v_{AN}^2 d\omega t \right] \right]^{0.5}$$



$V_{an(rms)}$

$$V_o = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_{an}^2 d(\omega t)}$$

$$V_o = \sqrt{6} V_s \left[\frac{1}{\pi} \left\{ \int_{\frac{\pi}{6}}^{\frac{\pi}{3}} \frac{1}{\pi^3} \sin^2 \omega t \cdot \omega t \cdot d\omega t + \int_{\frac{\pi}{2}}^{\frac{2\pi}{3}} \frac{1}{\pi^4} \sin^2 \omega t \cdot \omega t \cdot d\omega t + \int_{\frac{\pi}{2}}^{\frac{2\pi}{3}} \frac{1}{3} \sin^2 \omega t \cdot \omega t \cdot d\omega t + \int_{\frac{\pi}{2}}^{\frac{2\pi}{3}} \frac{1}{\pi^4} \sin^2 \omega t \cdot \omega t \cdot d\omega t + \int_{\frac{5\pi}{6}}^{\frac{\pi}{3}} \frac{1}{\pi^3} \sin^2 \omega t \cdot \omega t \cdot d\omega t \right\} \right]^{0.5}$$

$$V_s = 380/\sqrt{3} = 219.4v$$




$$V_o = V_s \sqrt{\left\{ 1 - \frac{3\alpha}{2\pi} + \frac{3}{4\pi} \sin 2\alpha \right\}}$$

$$V_o = V_s \left[1 - \frac{1}{4} + \frac{3}{4\pi} \sin\left(\frac{\pi}{3}\right) \right]^{0.5} = 215.2 \text{ V}$$

RMS Output current


$$I_o = \frac{V_o}{R_L}$$

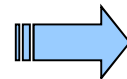

$$I_a = \frac{215.2}{10} = 21.52 \text{ A}$$

Output power

$$P_o = 3I_o^2 R_L$$

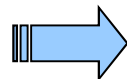

$$P_o = 3 \times (21.52)^2 \times 10 = 13.897 \text{ kW}$$

Input VA rating

$$VA = 3V_s I_o \Rightarrow VA = 3 \times 220 \times 21.52 = 14.203 \text{ kVA}$$



Supply power factor

$$PF = \frac{P_0}{VA} \Rightarrow P.F. = \frac{13.893}{14.203} = 0.978$$

Exercise:

- Repeat the previous example for $\alpha = 75^\circ$ and 120° .
- Derive two general expressions for the rms output phase voltage for mode (II) and mode (III).