

Benha University
Faculty of Engineering (Shoubra)
Electronics and Communications Engineering



ECE 211
Electrical and Electronic Measurements
(2020-2021)

Lecture 6&7: Analog Electronic Voltmeters and
Digital Voltmeters (DVM)


Dr. Islam Mansour

Electronics Voltmeter Outline:

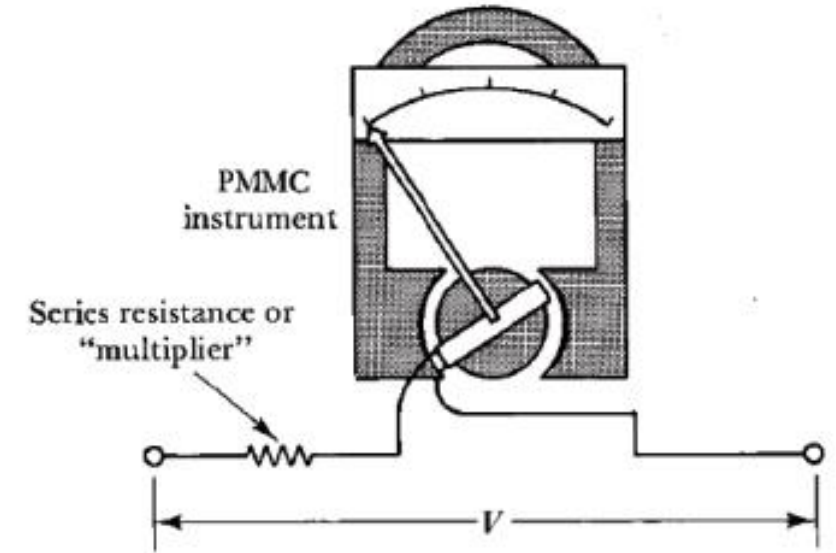1. Introduction.
2. Transistor Voltmeter Circuits.
3. Operational Amplifier Voltmeter Circuits.
4. AC Electronic Voltmeters.
5. Multimeter Probes.

Introduction:

- The electromechanical instruments have some limitations: **as having low resistance (loading effect)** and **cannot measure very low voltages**.
- The low input voltages need to be **amplified** to measurable levels and electronic circuits are required to **offer high input resistance**.
- Electronic circuits voltmeters with **transistors**, **operational amplifiers** (or op-amp) can be used to amplify small voltage and provide high input resistance .
- These analog circuits include:
 1. Emitter-Follower Voltmeter.
 2. FET-input Voltmeter.



Transistor Voltmeter Circuits.

Emitter-Follower Voltmeter:

A BJT emitter follower is used where the PMMC and R_s are connected to the Emitter.

The voltage to be measured, that is, E , is connected to the base of the transistor.

The base current, I_b is:

$$I_b = \frac{I_m}{\beta}, \quad \beta : (\text{Transistor gain})$$

The input resistance, R_i is:

$$R_{in} \approx \frac{E}{I_b}$$

which is **much larger** than $R_s + R_m$ since I_b is small.

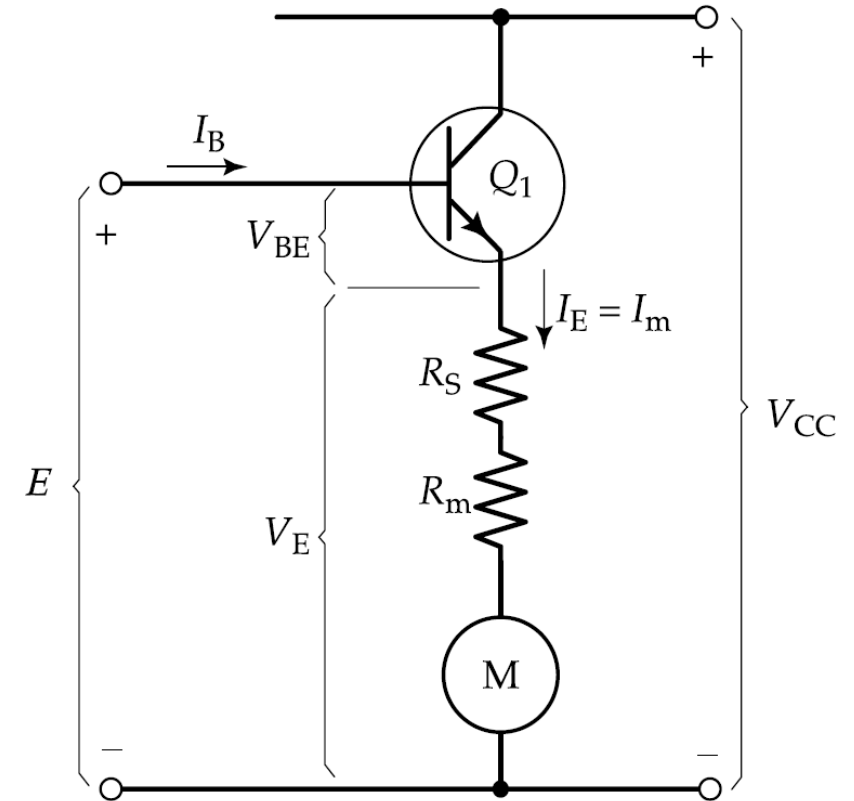


Figure 5-1 Emitter-follower voltmeter. The emitter follower offers a high input resistance to a measured voltage, and a low output resistance to a deflection meter. The base-emitter voltage drop (V_{BE}) introduces an error in the measurement.

Emitter-Follower Voltmeter (Cont.):

Example 1:

A simple emitter-follower voltmeter with: $V_{CC} = 12\text{ V}$, $R_m = 2\text{ k}\Omega$, 1 mA FSD meter current, and current gain = 50.

Determine :


- (a) Appropriate multiplier resistance that can give FSD 5 V.
- (b) Input resistance

Solu:

(a)

$$R_s = \frac{V_E}{I_m} - R_m = \frac{E - V_{BE}}{I_m} - R_m = \frac{5 - 0.7}{1\text{ mA}} - 2 = 2.3\text{ k}\Omega$$

(b) $R_{in} = \frac{E}{I_b} = \beta \cdot \frac{E}{I_m} = 50 \cdot \frac{5}{1\text{ mA}} = 250\text{ k}\Omega$

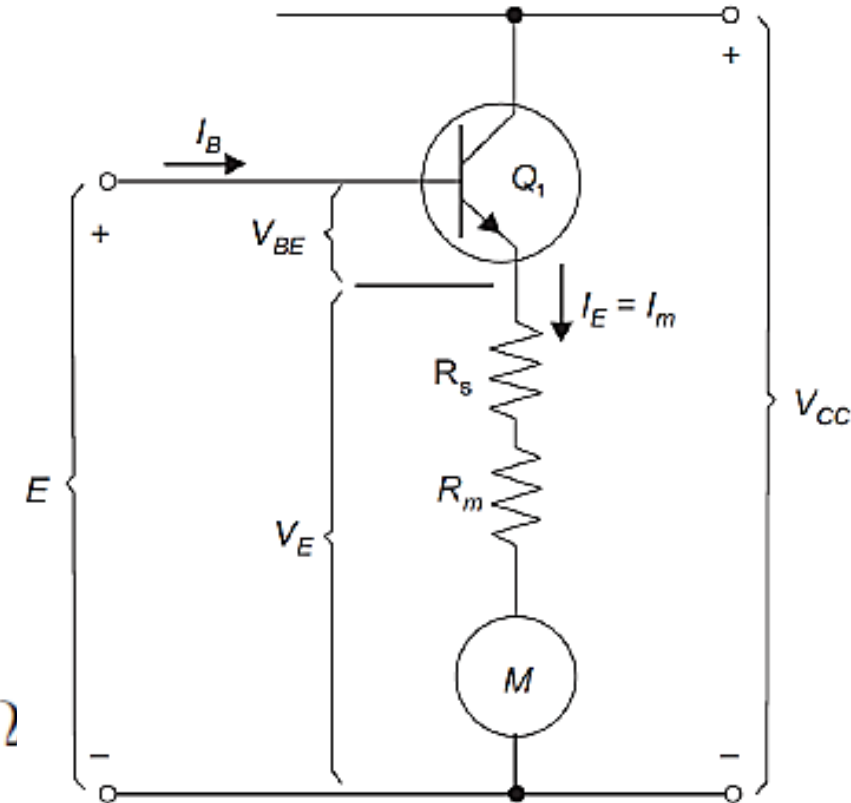

Example 2:

The simple emitter-follower voltmeter circuit in Figure 4-1 has $V_{CC} = 20\text{ V}$, $R_s + R_m = 9.3\text{ k}\Omega$, $I_m = 1\text{ mA}$ at full scale, and transistor $h_{FE} = 100$.

- (a) Calculate the meter current when $E = 10\text{ V}$,
(b) Determine the voltmeter input resistance with and without the transistor.

Solution

(a)
$$V_E = E - V_{BE} = 10\text{ V} - 0.7\text{ V}$$
$$= 9.3\text{ V}$$

$$I_m = \frac{V_E}{R_s + R_m} \approx \frac{9.3\text{ V}}{9.3\text{ k}\Omega}$$
$$= 1\text{ mA}$$


(b) With the transistor,

$$I_B \approx \frac{I_m}{h_{FE}} \approx \frac{1\text{ mA}}{100}$$
$$= 10\text{ }\mu\text{A}$$

$$R_i \approx \frac{E}{I_B} \approx \frac{10\text{ V}}{10\text{ }\mu\text{A}}$$
$$= 1\text{ M}\Omega$$

Without the transistor,

$$R_i = R_s + R_m = 9.3\text{ k}\Omega$$

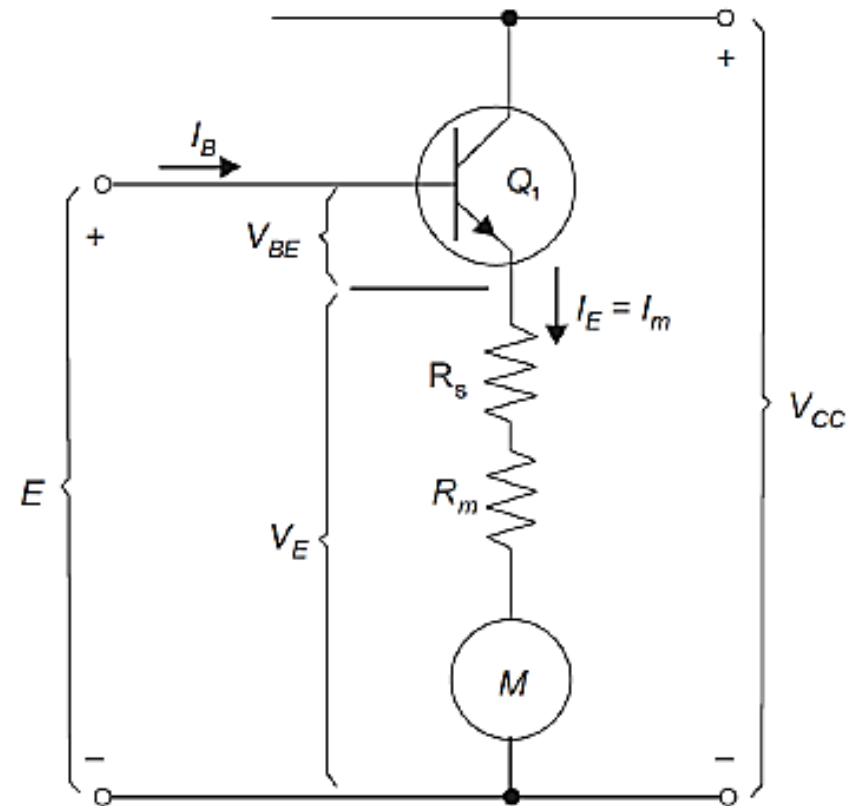

Emitter-Follower Voltmeter (Cont.) :

- To reduce the drop V_{BE} , a one more emitter-follower and a voltage divider are used with a ± 12 V dual polarity supply is connected.
- When $E = 0$, the resistance R_5 is adjusted to make $V_{E2} = 0.7$ and $V_m = 0$.
- When E is exist, the PMMC voltage is:

$$V_m = E - 0.7 - (-0.7) = E$$

- So, the voltage drop is removed.

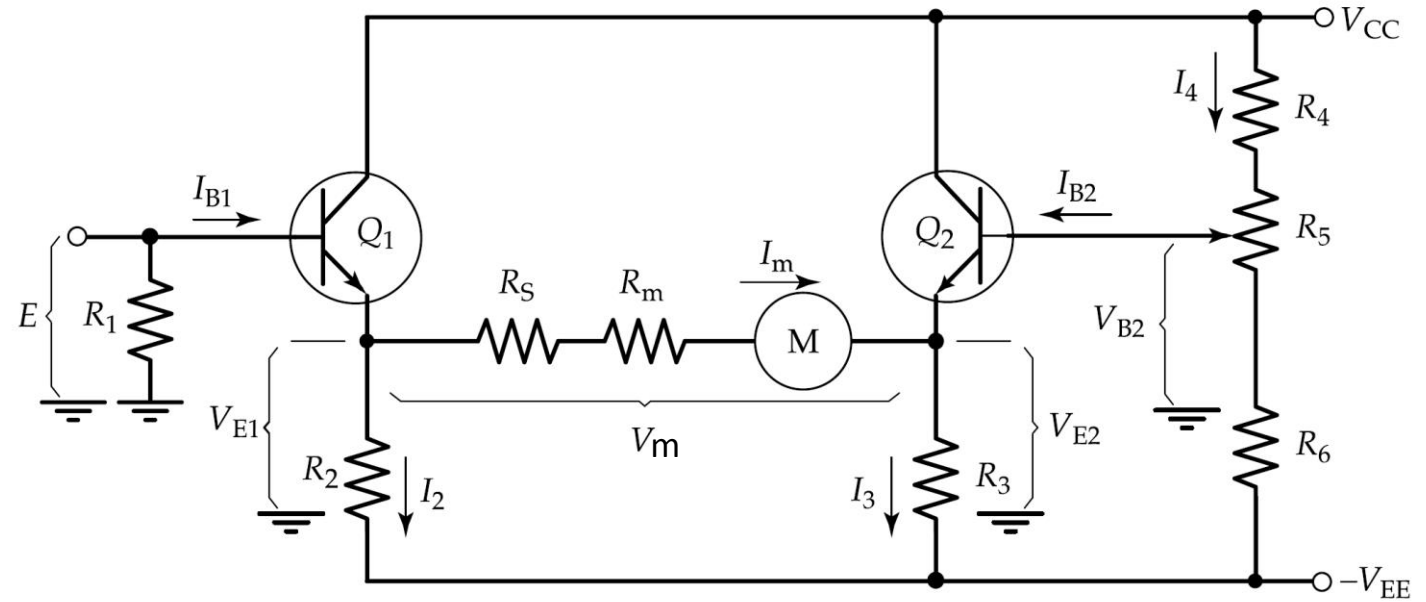


Figure 5-2 Practical emitter-follower voltmeter circuit using a second transistor (Q_2) and a voltage divider (R_4 , R_5 , and R_6) to eliminate the V_{BE} error introduced by Q_1 .

Example 3:

An emitter-follower voltmeter circuit such as that in Figure 4-2 has $R_2 = R_3 = 3.9 \text{ k}\Omega$ and $V_{CC} = \pm 12 \text{ V}$.


(a) Determine I_2 and I_3 when $E = 0 \text{ V}$.

(b) Calculate the meter circuit voltage when $E = 1 \text{ V}$ and when $E = 0.5 \text{ V}$.

Solution

(a)
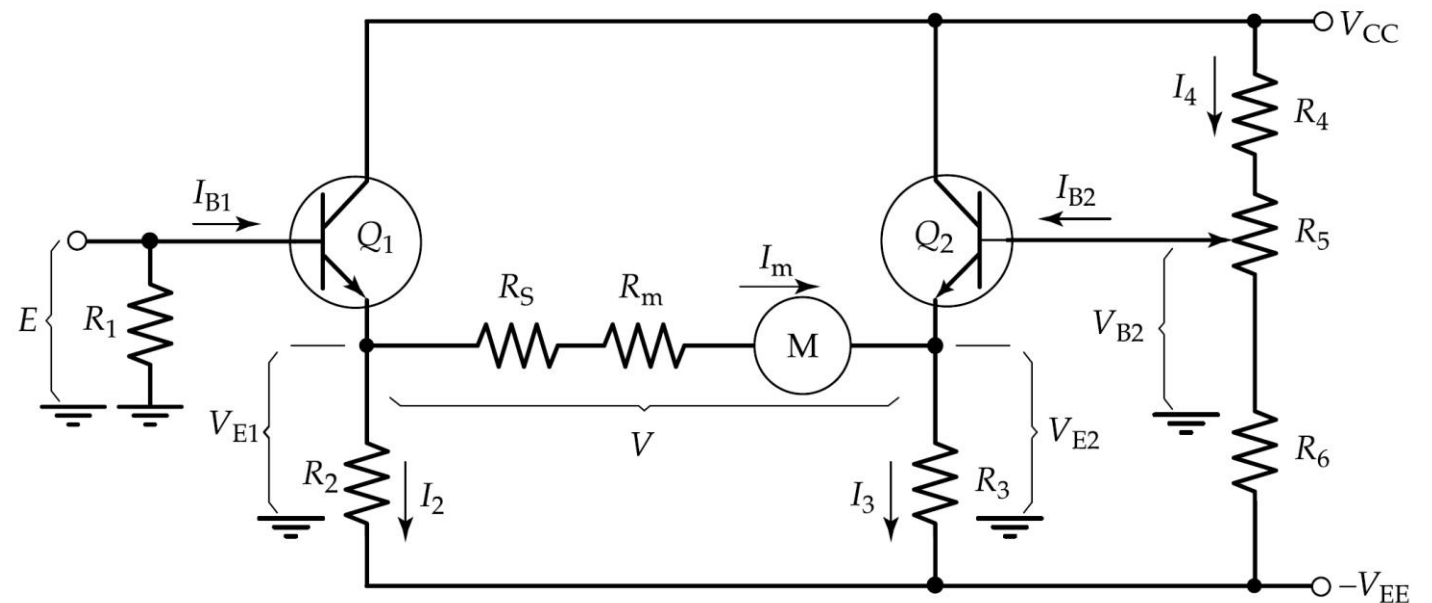
$$\begin{aligned} V_{R2} = V_{R3} &= 0 \text{ V} - V_{BE} - V_{EE} \\ &= 0 \text{ V} - 0.7 \text{ V} - (-12 \text{ V}) \\ &= 11.3 \text{ V} \\ I_2 = I_3 &= \frac{V_{R2}}{R_2} = \frac{11.3 \text{ V}}{3.9 \text{ k}\Omega} \\ &\approx 2.9 \text{ mA} \end{aligned}$$



(b) When $E = 1 \text{ V}$,

$$\begin{aligned}V_{E1} &= E - V_{BE} = 1 \text{ V} - 0.7 \text{ V} \\ &= 0.3 \text{ V}\end{aligned}$$

$$\begin{aligned}V_{E2} &= V_{B2} - V_{BE} = 0 \text{ V} - 0.7 \text{ V} \\ &= -0.7 \text{ V}\end{aligned}$$

$$\begin{aligned}V &= V_{E1} - V_{E2} = 0.3 \text{ V} - (-0.7 \text{ V}) \\ &= 1 \text{ V}\end{aligned}$$

When $E = 0.5 \text{ V}$,

$$\begin{aligned}V_{E1} &= E - V_{BE} = 0.5 \text{ V} - 0.7 \text{ V} \\ &= -0.2 \text{ V}\end{aligned}$$

$$\begin{aligned}V_{E2} &= V_{B2} - V_{BE} = 0 \text{ V} - 0.7 \text{ V} \\ &= -0.7 \text{ V}\end{aligned}$$

$$\begin{aligned}V &= V_{E1} - V_{E2} = -0.2 \text{ V} - (-0.7 \text{ V}) \\ &= 0.5 \text{ V}\end{aligned}$$

FET-input Voltmeter:

Advantage:

The Field Effect Transistor (FET) provide extremely high input resistance.

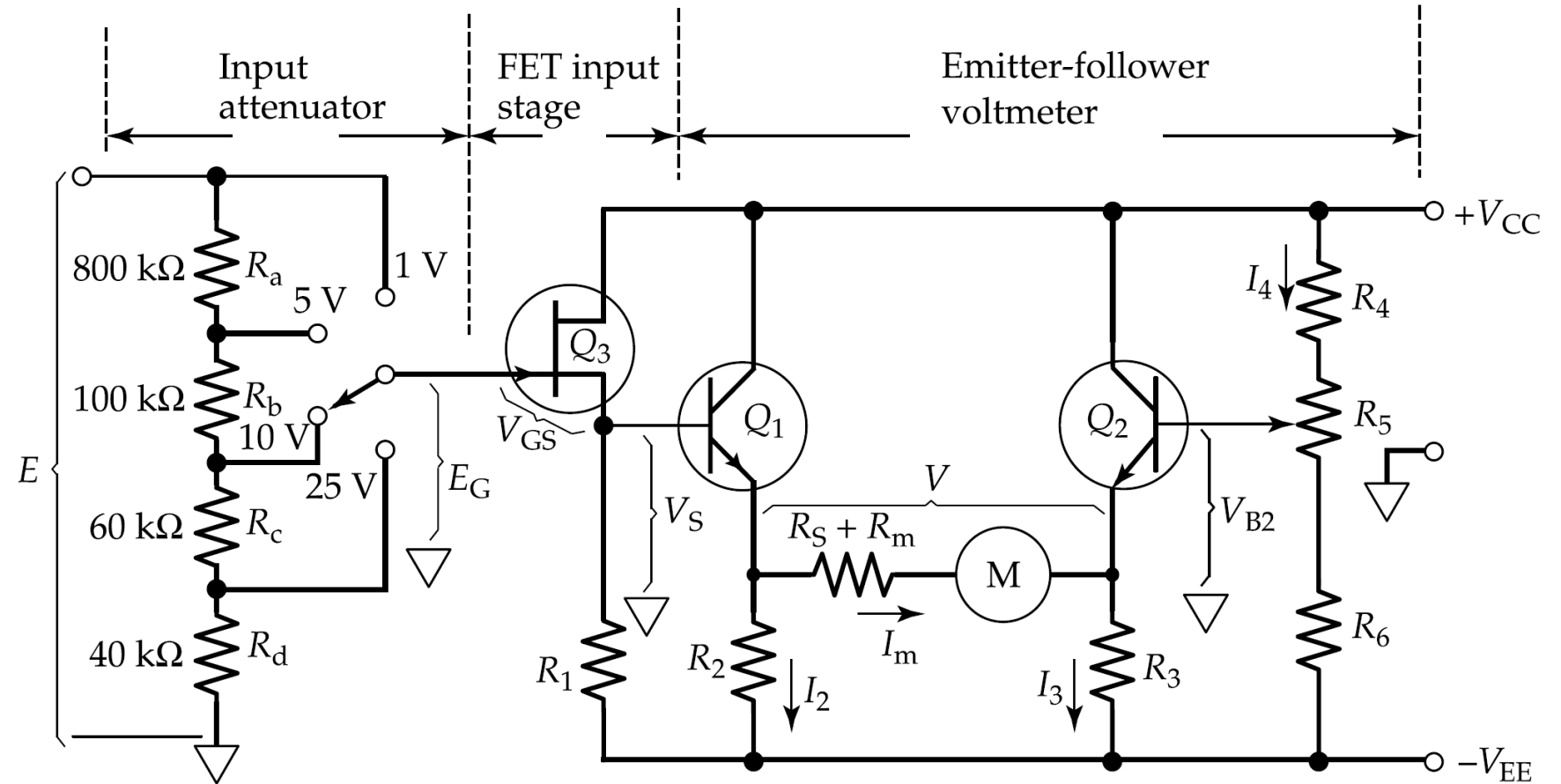


Figure 5-4 A voltmeter input attenuator is simply a voltage divider that accurately divides the voltage to be measured. The FET input stage (Q_3) gives the emitter follower a very high input resistance.

Example 4:

Determine the meter reading for the circuit in Figure 4-4 when $E = 7.5\text{ V}$ and the meter is set to its 10 V range. The FET gate-source voltage is -5 V , $V_p = +5\text{ V}$, $R_s + R_m = 1\text{ k}\Omega$, and $I_m = 1\text{ mA}$ at full scale.

Solution

On the 10 V range:

$$E_G = E \frac{R_c + R_d}{R_a + R_b + R_c + R_d}$$
$$= 7.5\text{ V} \times \frac{60\text{ k}\Omega + 40\text{ k}\Omega}{800\text{ k}\Omega + 100\text{ k}\Omega + 60\text{ k}\Omega + 40\text{ k}\Omega}$$

$$= 0.75\text{ V}$$

$$V_S = E_G - V_{GS} = 0.75\text{ V} - (-5\text{ V})$$

$$= 5.75\text{ V}$$

$$V_{E1} = V_S - V_{BE} = 5.75\text{ V} - 0.7\text{ V} = 5.05\text{ V}$$

$$V_{E2} = V_P - V_{BE} = 5\text{ V} - 0.7\text{ V}$$


$$= 4.3\text{ V}$$

$$V = V_{E1} - V_{E2} = 5.05\text{ V} - 4.3\text{ V}$$

$$= 0.75\text{ V} = E_G$$

$$I_m = \frac{V}{R_s + R_m} = \frac{0.75\text{ V}}{1\text{ k}\Omega}$$

$$= 0.75\text{ mA (75% of full scale)}$$

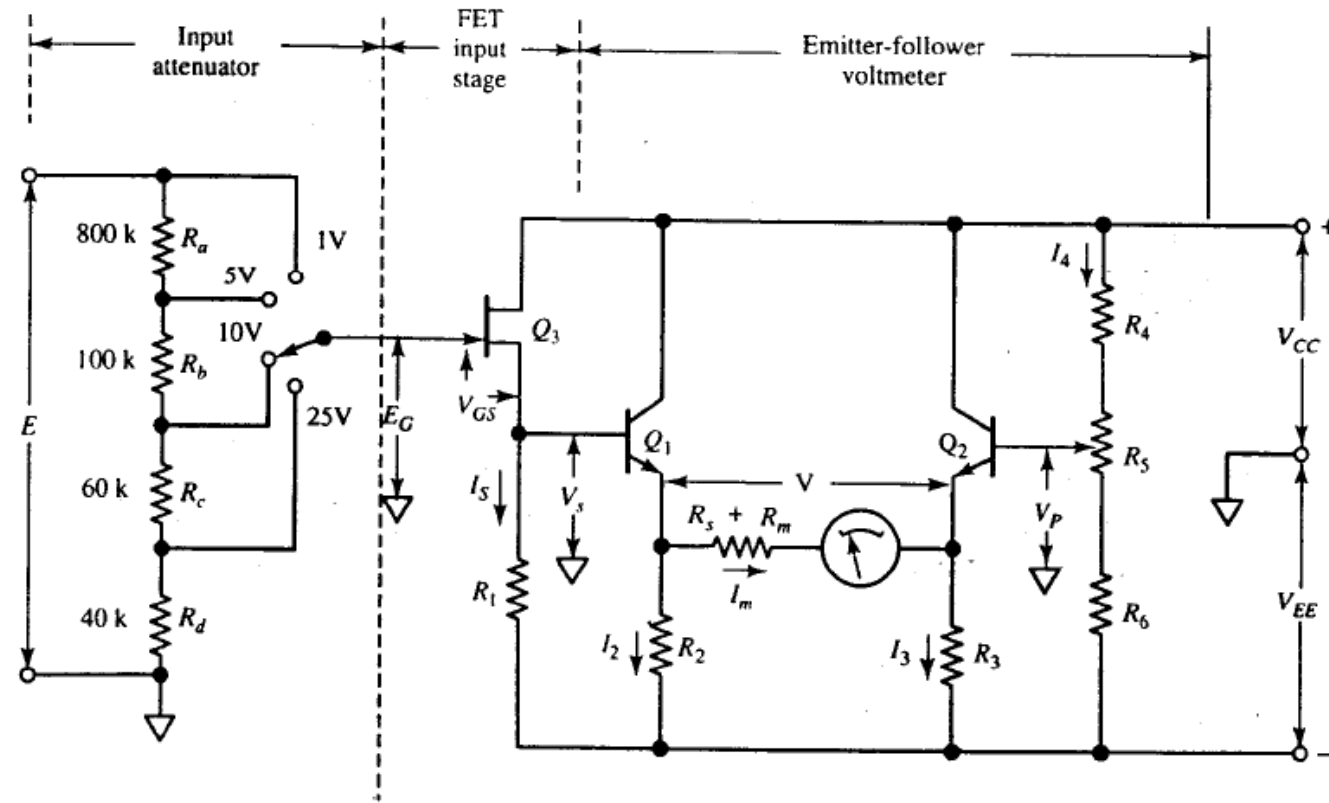

On the 10 V range, full scale represents 10 V, and 75% of full scale would be read as 7.5 V.

Operational Amplifier Voltmeter Circuits.

Operational Amplifier

The Op. Amp IC is a perfect choice to be used in the electronic voltmeters


- **Ideal Op. Amp** has the fo

- $R_{in} = \infty$

- $R_o = 0$


- $A_v = \infty$

A_v is the open loop voltage gain

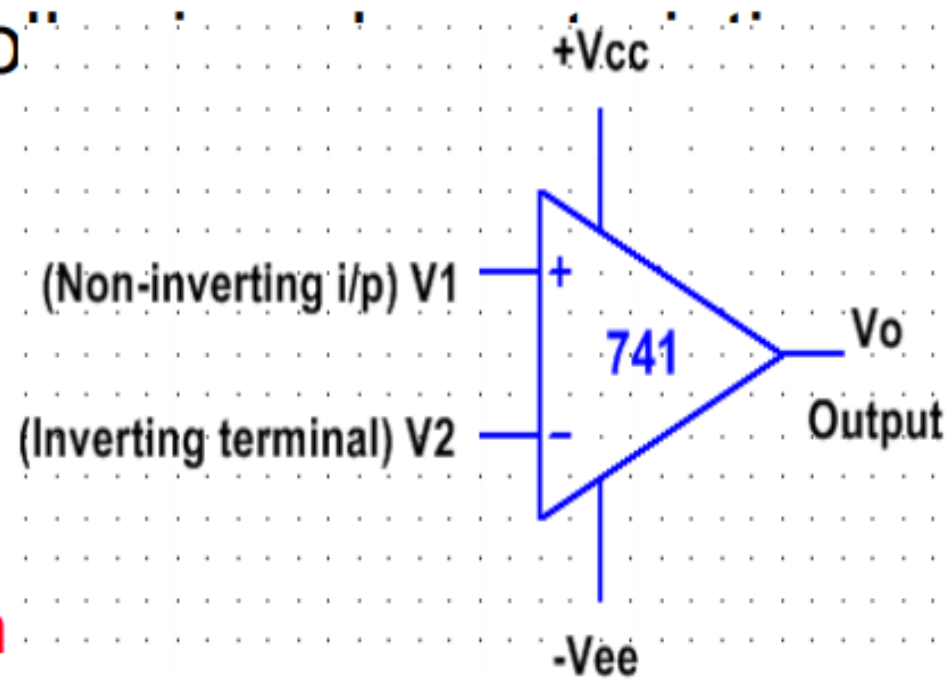


Operational Amplifier Voltmeter

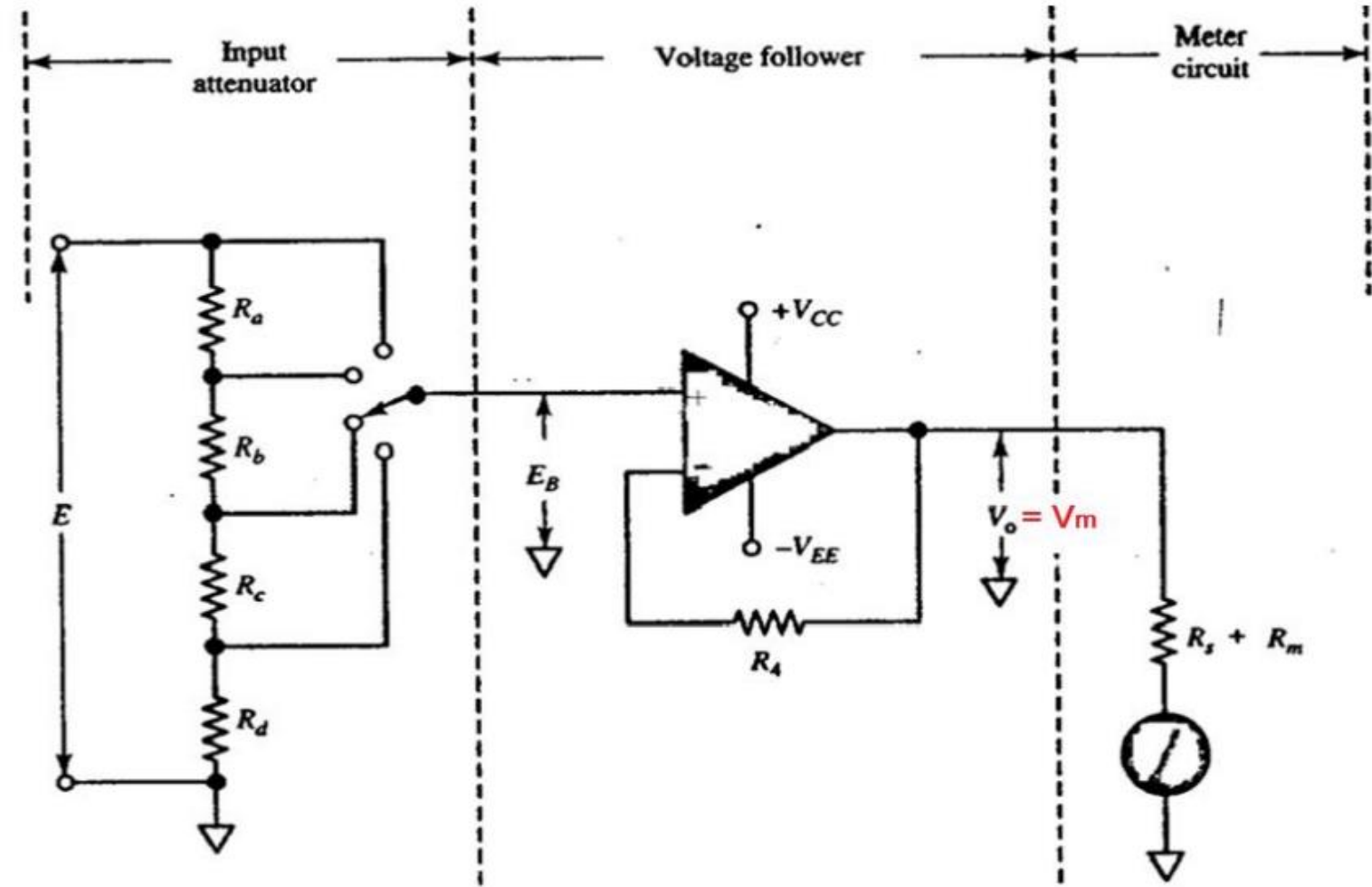- The voltage follower has a much **higher input resistance** and **lower output resistance** than the emitter follower.
- The input voltage is applied to the op-amp noninverting input terminal, and the feedback from the output goes to the inverting input.
- The attenuator selects the voltmeter range.



IC Operational Amplifier


Inverting Amplifier

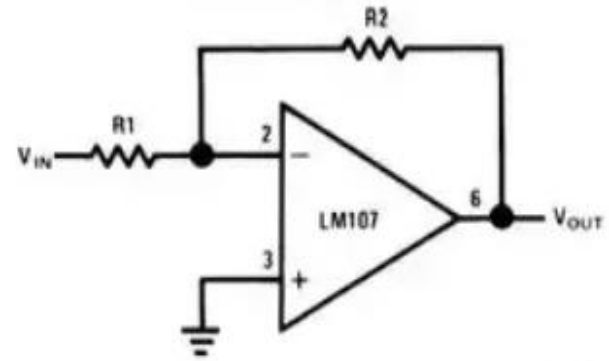

00705701


$$V_{OUT} = -\frac{R_2}{R_1} V_{IN}$$

Non-Inverting Amplifier

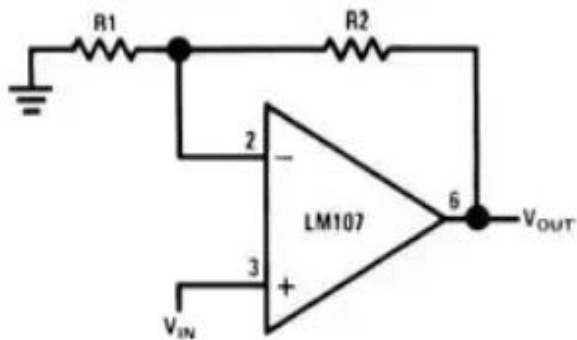

00705702
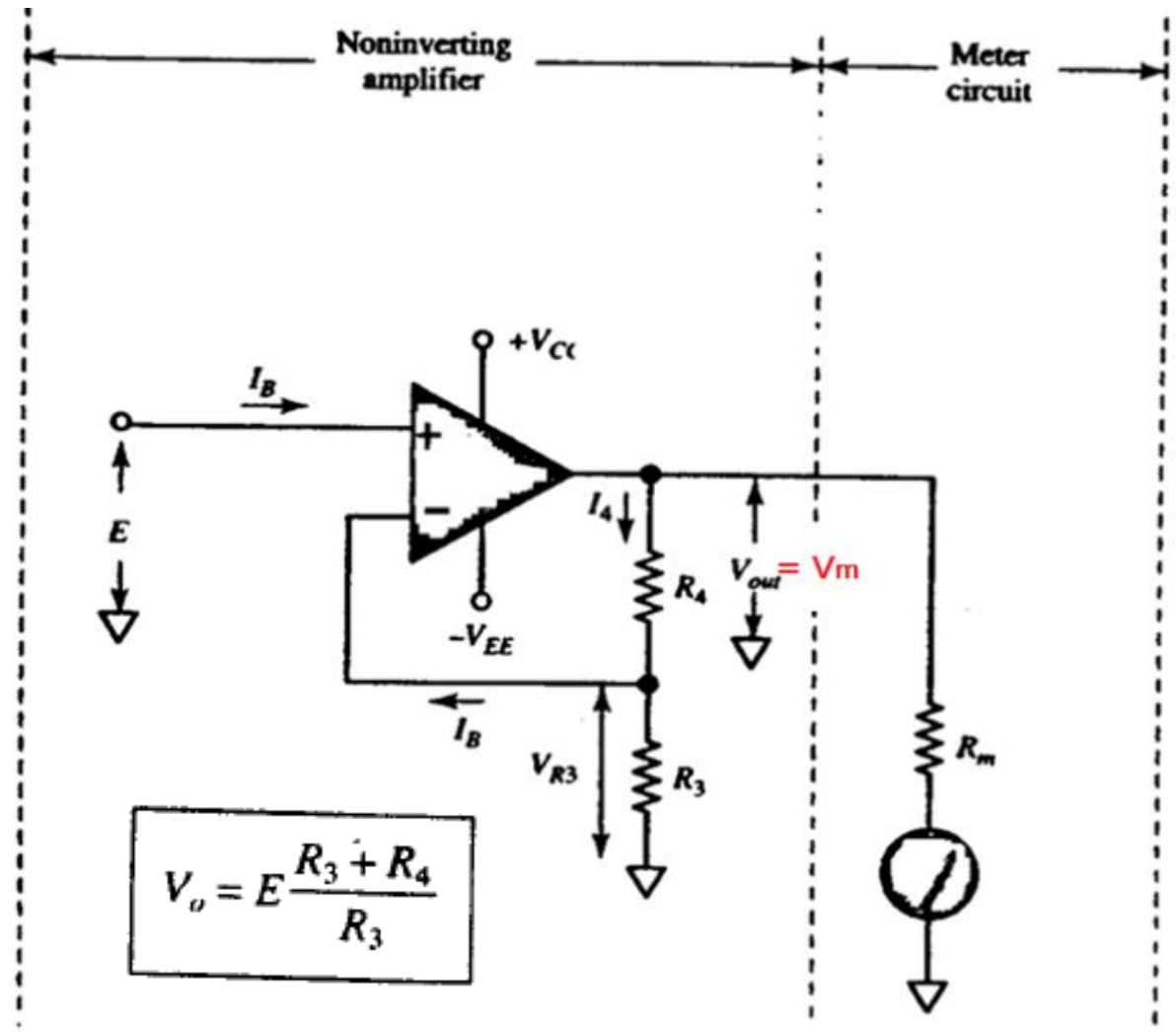
$$V_{OUT} = \frac{R_1 + R_2}{R_1} V_{IN}$$



$$V_o = E \frac{R_3 + R_4}{R_3}$$

An op-amp noninverting amplifier voltmeter is very easily designed. Current I_4 through R_3 and R_4 is first selected very much larger than the op-amp input bias current (I_B). Then the resistors are calculated as

$$R_3 = \frac{E}{I_4} \quad \text{and} \quad R_4 = \frac{V_o - E}{I_4}$$

Example 5:

An op-amp voltmeter circuit as in Figure 4-7 is required to measure a maximum input of 20 mV. The op-amp input current is $0.2 \mu\text{A}$, and the meter circuit has $I_m = 100 \mu\text{A}$ FSD and $R_m = 10 \text{ k}\Omega$. Determine suitable resistance values for R_3 and R_4 .

Solution

Select

$$I_4 \gg I_B$$

$$I_4 = 1000 \times I_B = 1000 \times 0.2 \mu\text{A} \\ = 0.2 \text{ mA}$$

At full scale,


$$I_m = 100 \mu\text{A}$$

and

$$V_{out} = I_m \times R_m = 100 \mu\text{A} \times 10 \text{ k}\Omega \\ = 1 \text{ V}$$

$$R_3 = \frac{E}{I_4} = \frac{20 \text{ mV}}{0.2 \text{ mA}} \\ = 100 \Omega$$
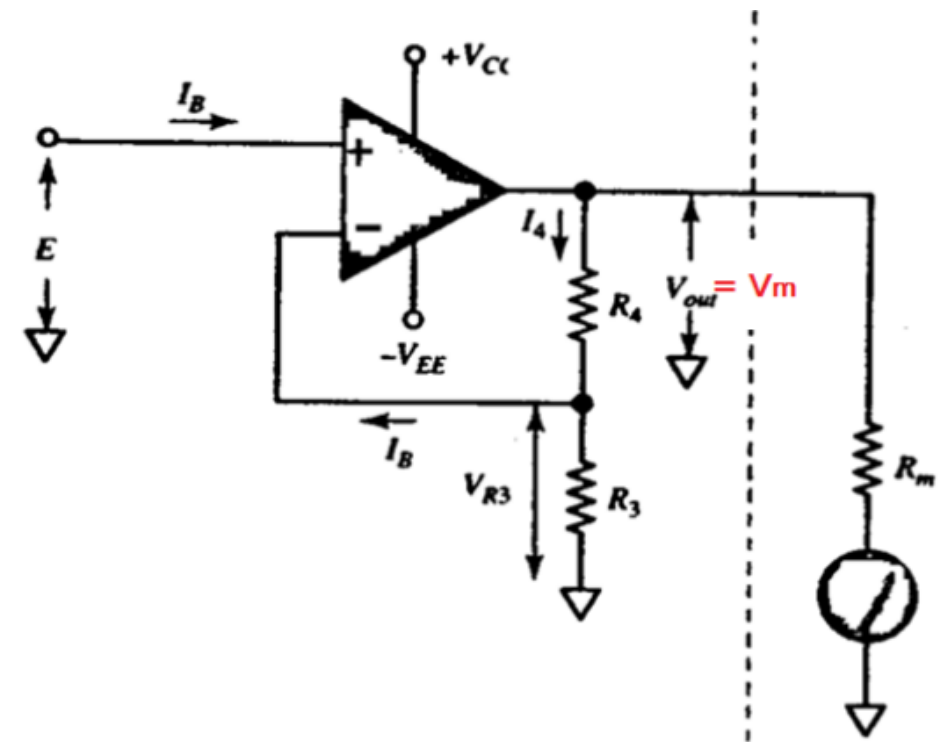
$$R_4 = \frac{V_o - E}{I_4} = \frac{1 \text{ V} - 20 \text{ mV}}{0.2 \text{ mA}} \\ = 4.9 \text{ k}\Omega$$



Voltage-to-current converter Voltmeter

$$I_m = I_{R3} = \frac{E}{R_3}$$


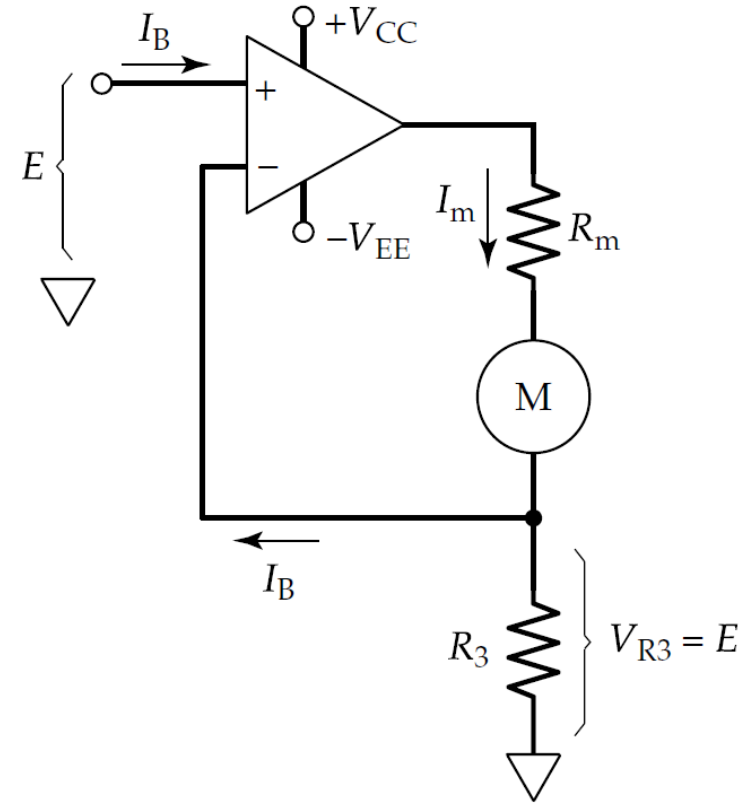


Figure 5-8 Voltmeter circuit using an op-amp voltage-to-current converter. The meter current is E/R_3 .

AC Electronic Voltmeters


AC Electronic Voltmeters

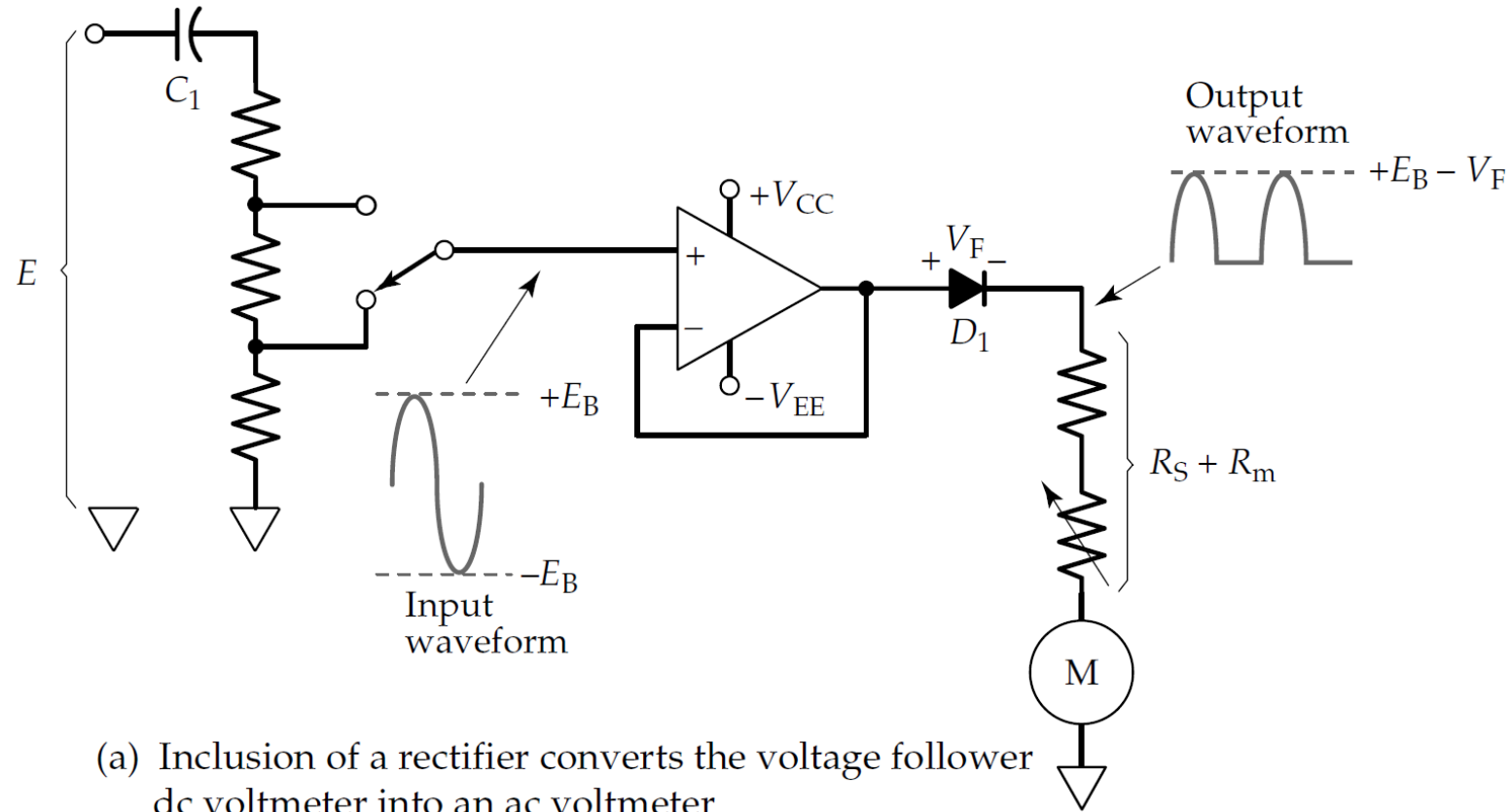- D1 is half-wave rectifier
- The coupling capacitor C1 to block unwanted dc voltage.
- The voltage drop (V_F) across the rectifier is a source of error in the circuit.
- Also, the rectifier voltage drop is not always exactly 0.7 V, as usually assumed for a silicon diode and it varies with temperature change.



AC Electronic Voltmeters (Cont.)

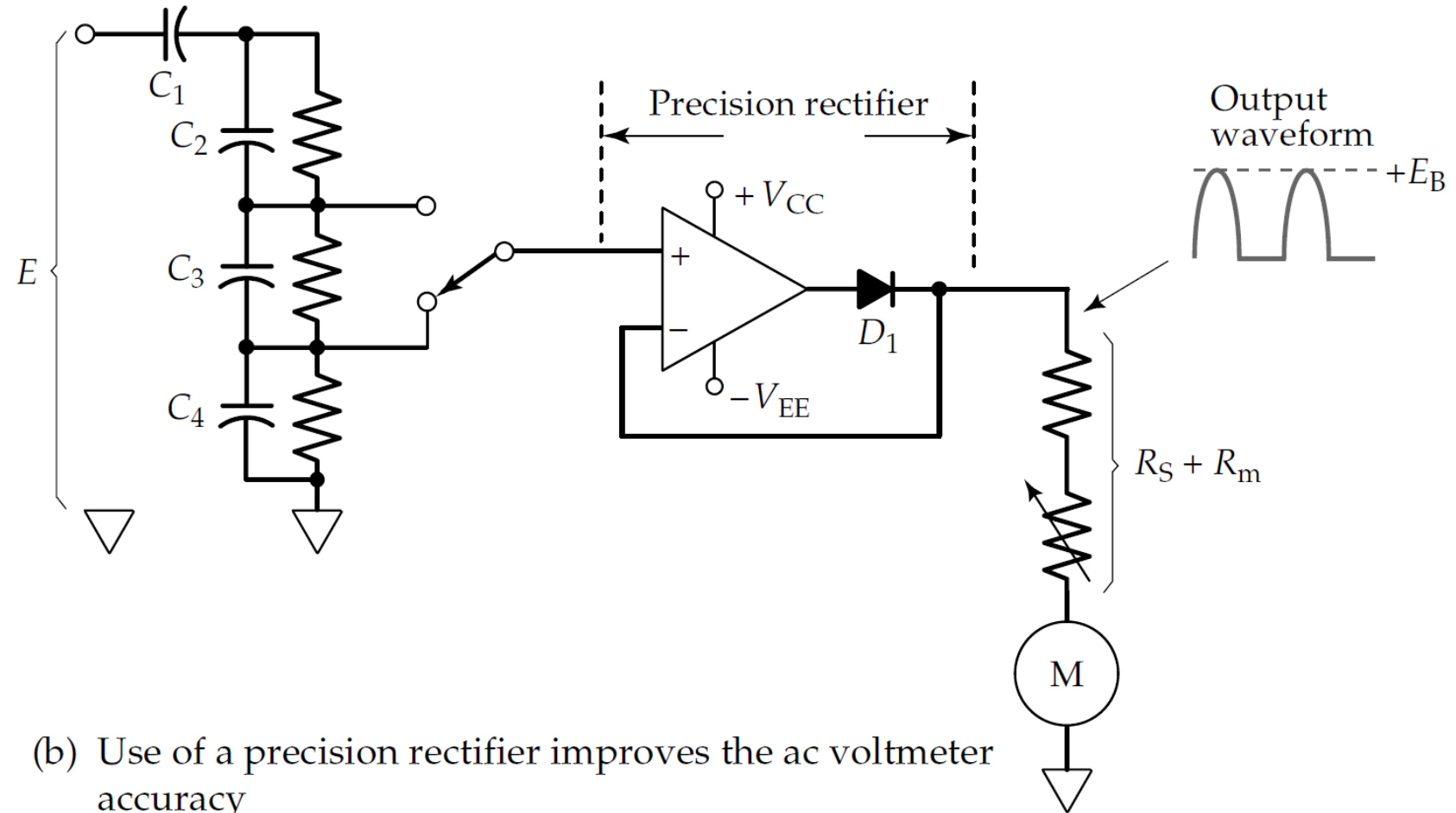- To avoid these errors, the voltage follower feedback connection to the inverting terminal is taken from the cathode of rectifier D_1 instead of from the amplifier output.



AC Electronic Voltmeters (Cont.)

- The input is amplified by factor

$$A_v = (R_2 + R_3)/R_3.$$



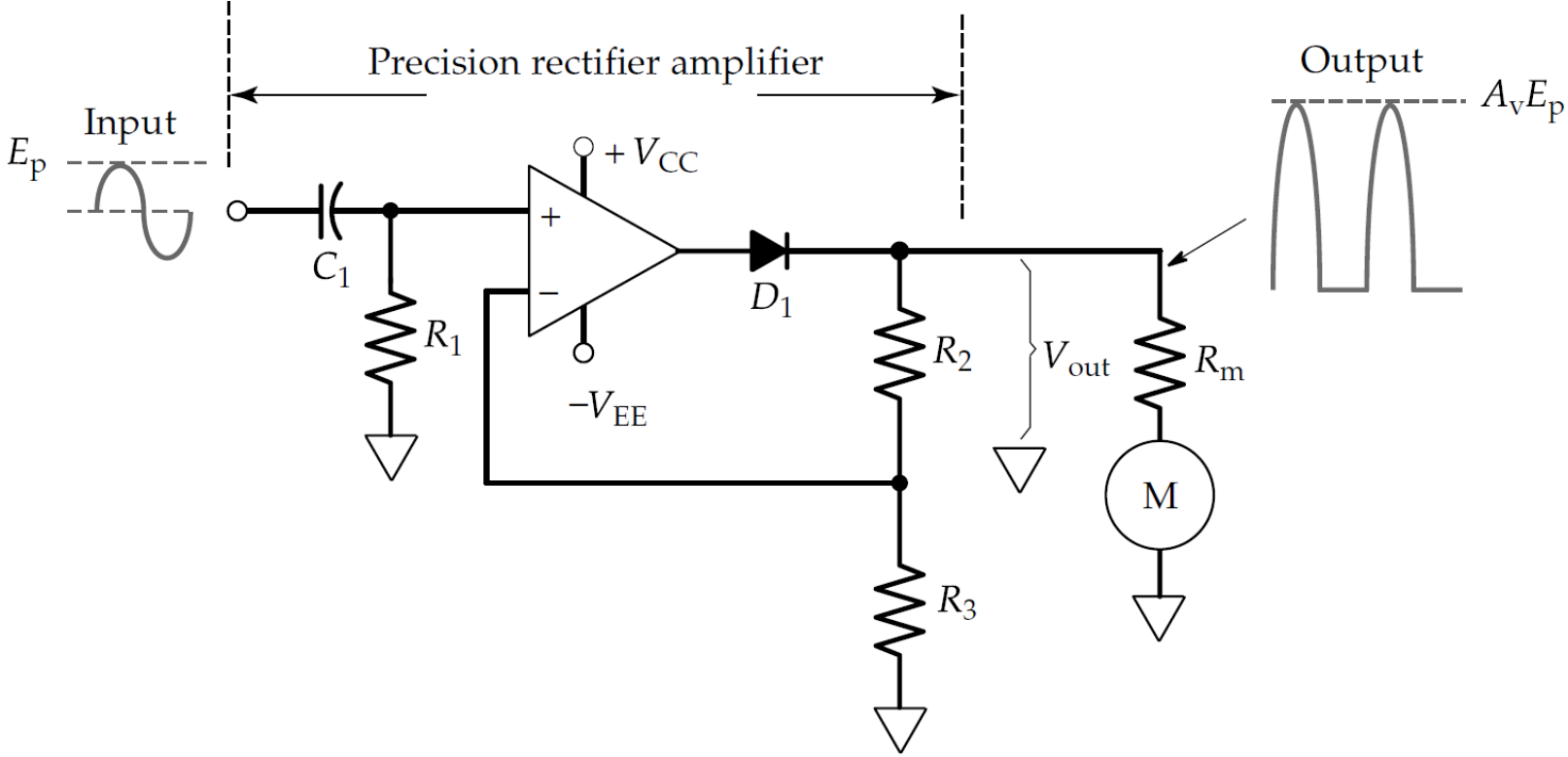


Figure 5-13 Ac voltmeter circuits using an op-amp noninverting amplifier together with precision half-wave rectification. Low-level voltages are amplified before measurement.

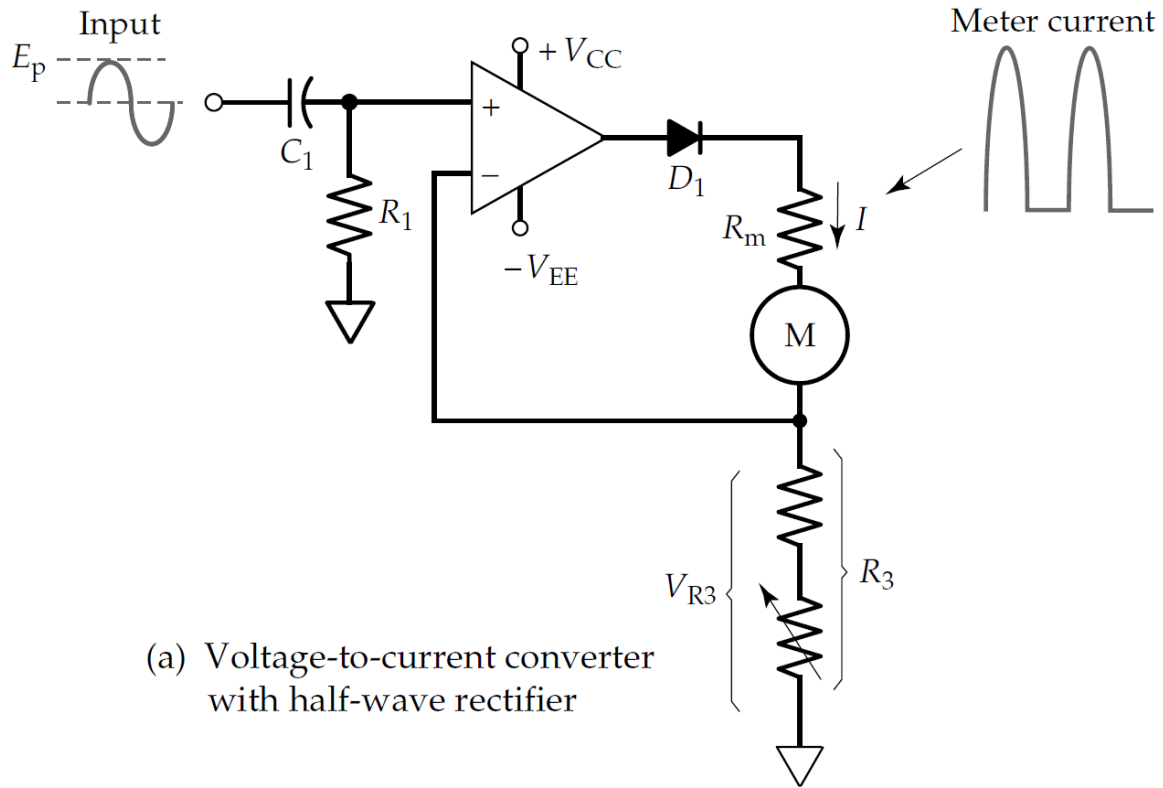

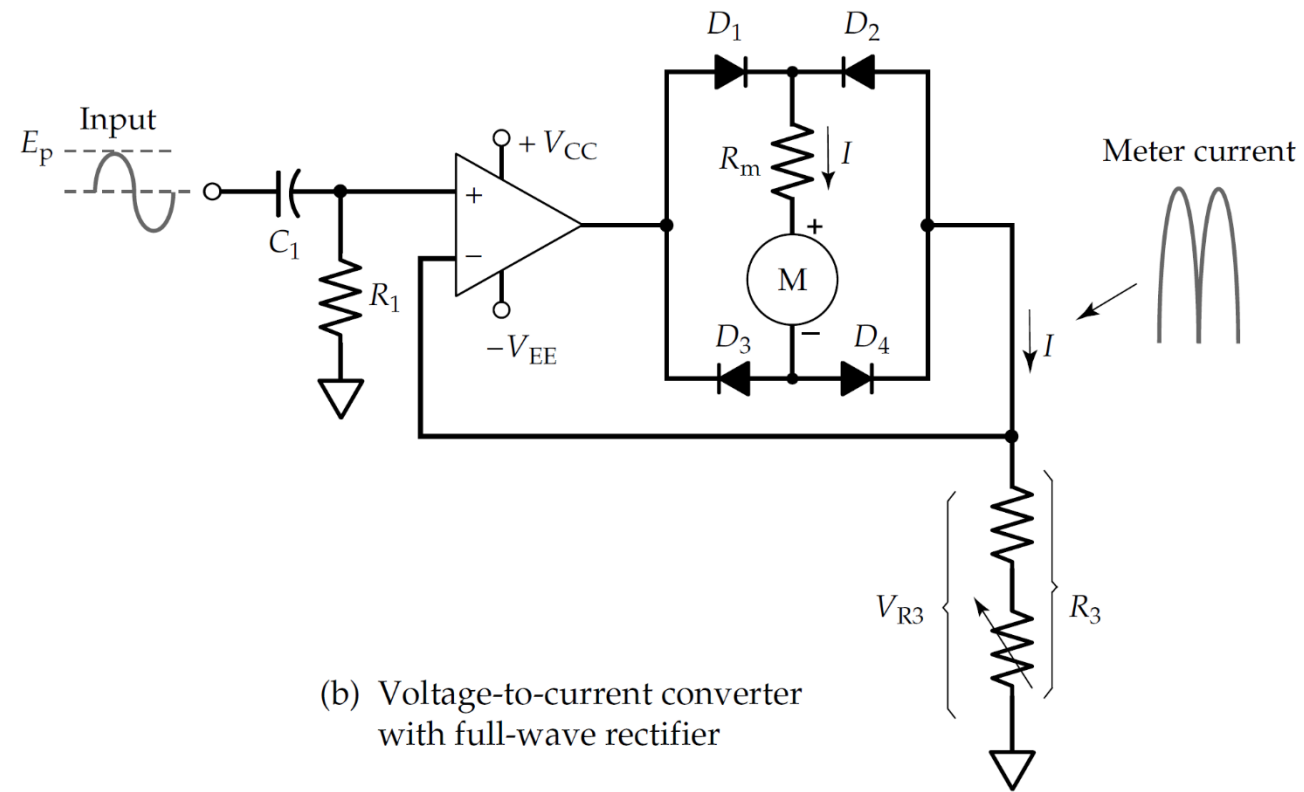(a) Voltage-to-current converter with half-wave rectifier



(b) Voltage-to-current converter with full-wave rectifier

Op-amp Half-bridge Rectifier Voltmeter

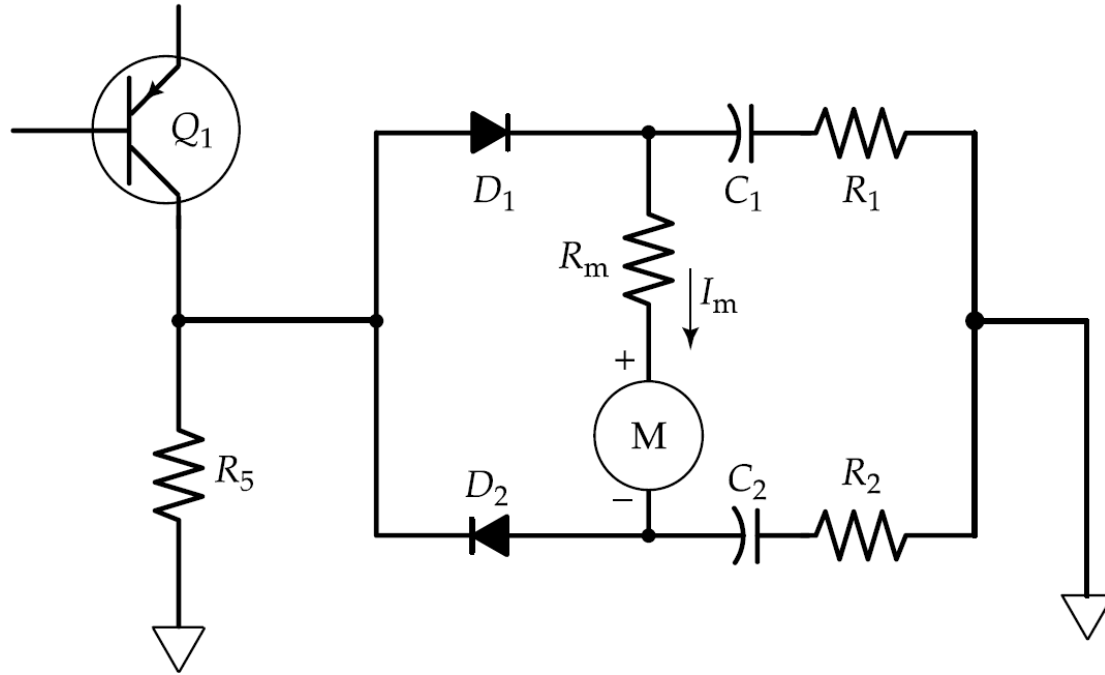


Figure 5-15 Ac electronic voltmeter using half-bridge full-wave rectification.

Voltmeter & Shunt


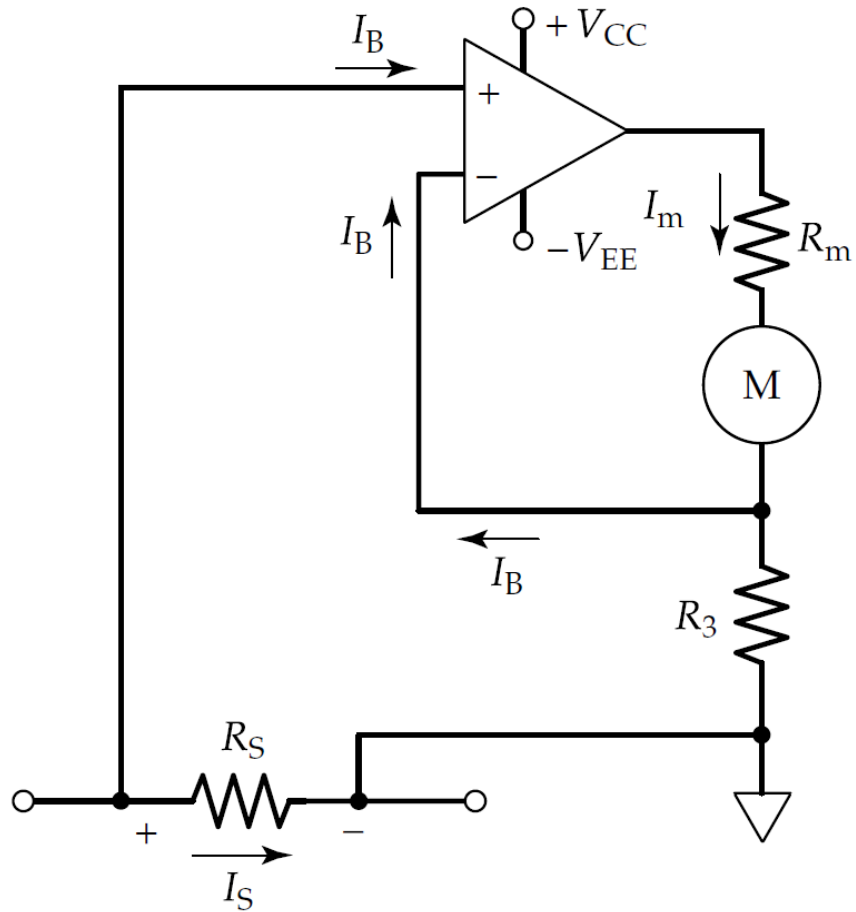
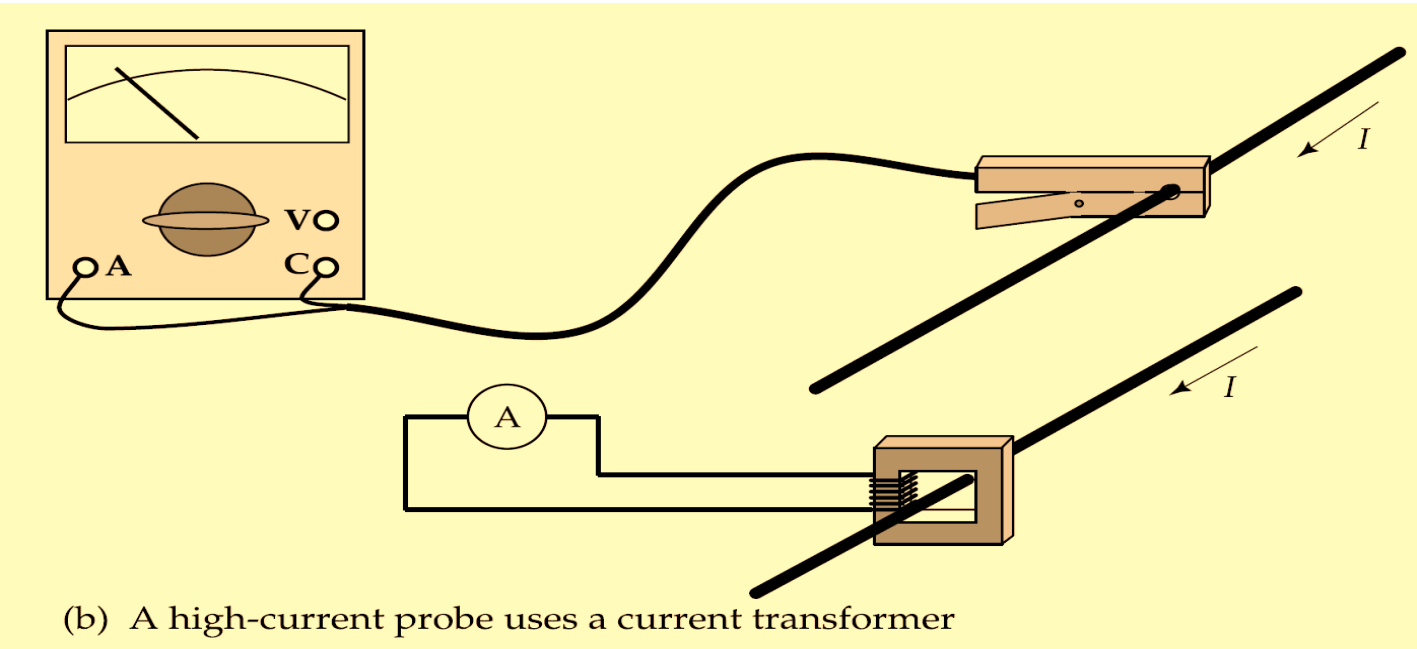



Figure 5-16 An electronic voltmeter can be used for current measurement by measuring the voltage drop across a shunt (R_S). The instrument scale is calibrated to indicate current.

Multimeter Probes

Multimeter Probes

- There are many probes and adapters available to extend multimeter ranges.
 1. High-Voltage Probe
 2. High-Current Probes
 3. RF probe allows the meter to measure the voltage level of a waveform with a frequency upper its cutoff frequency.

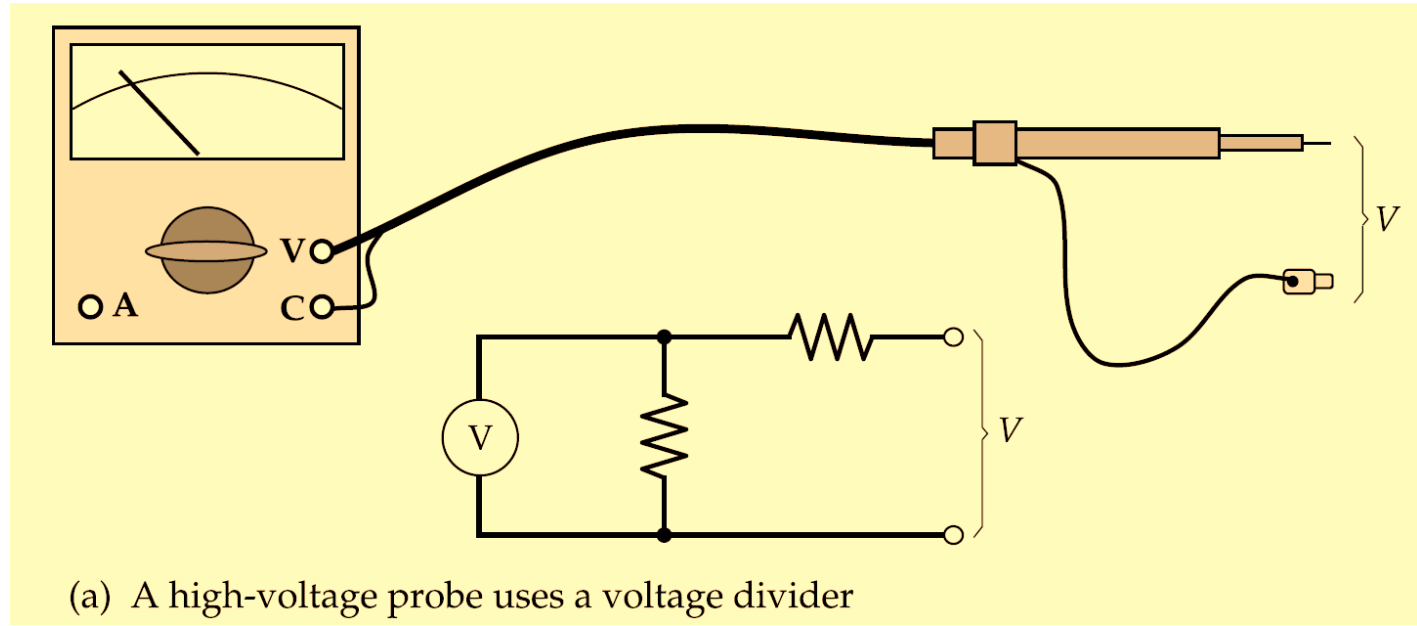

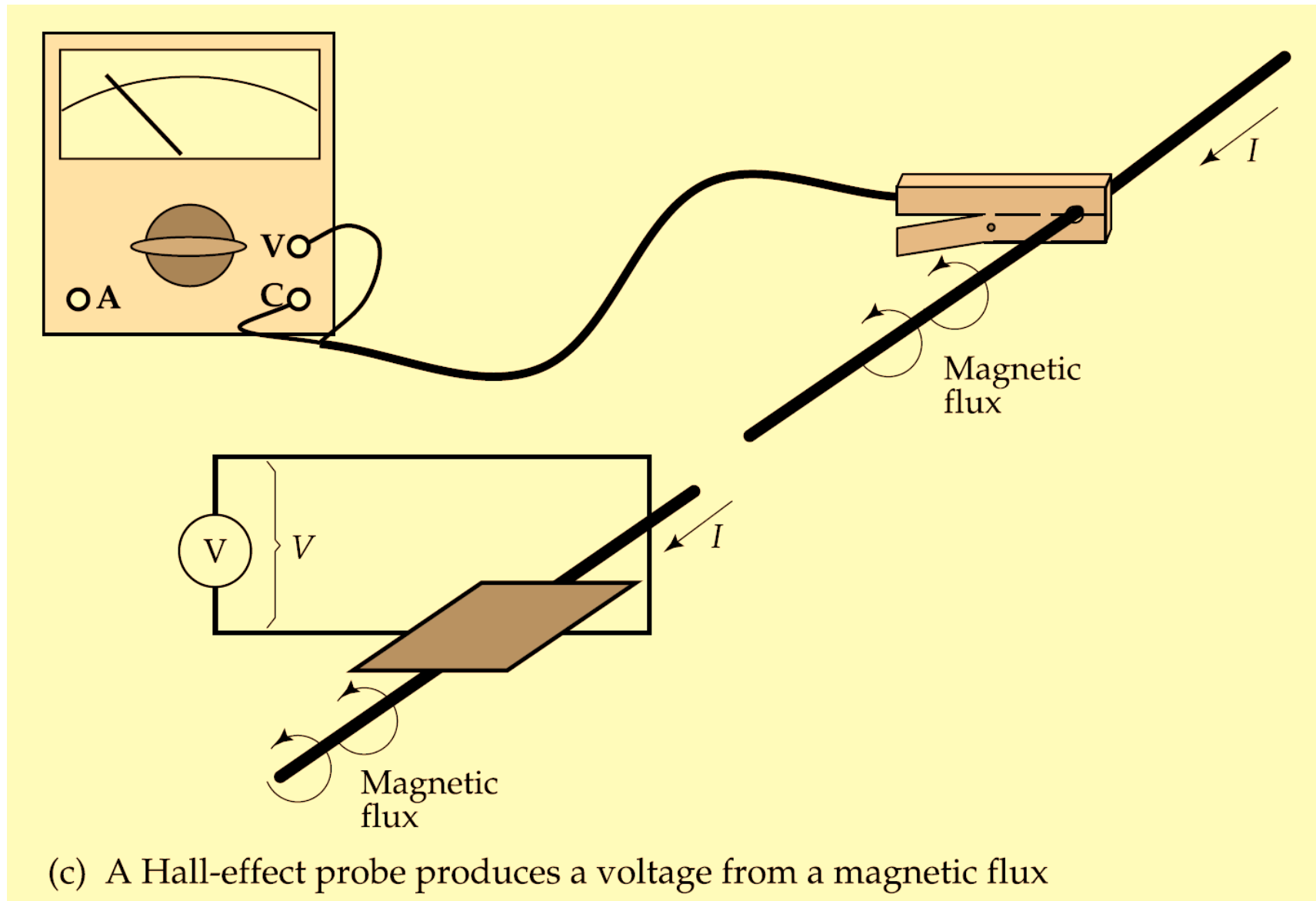

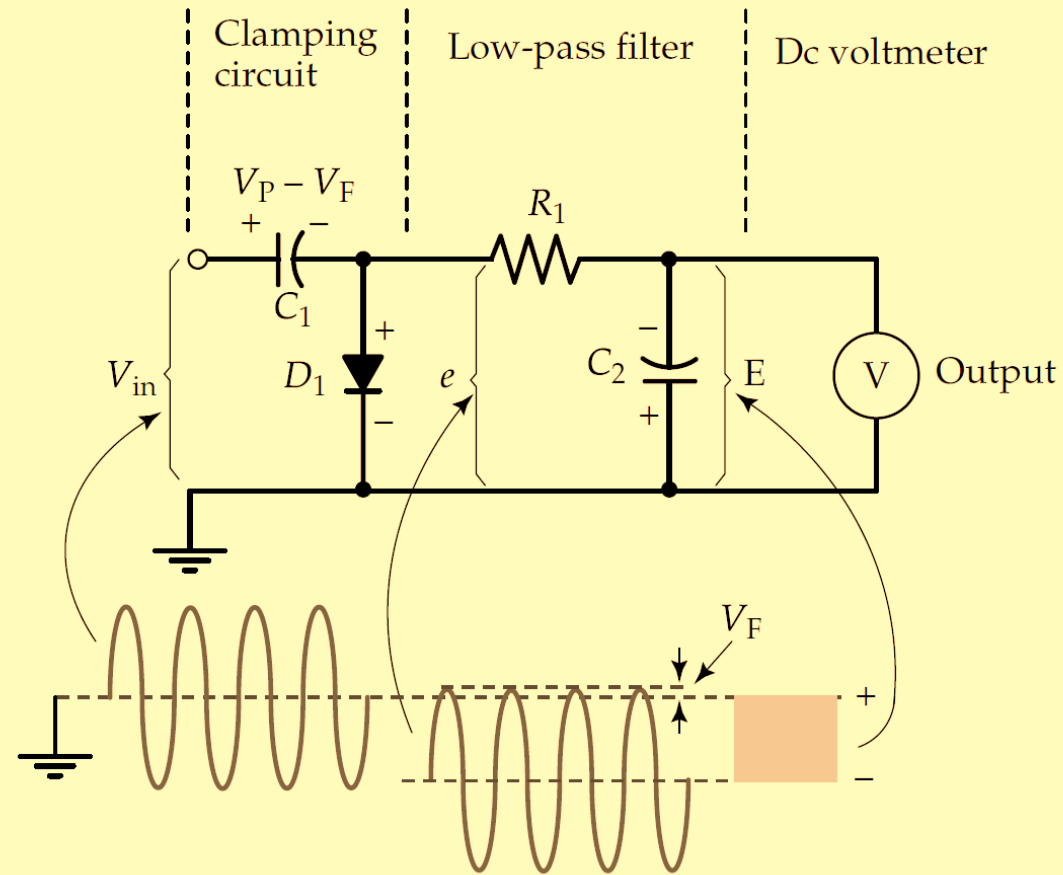



Figure 5-20 Peak detector circuit consisting of a clamper circuit and a low-pass filter. The peak voltage of a high-frequency waveform is converted to a dc quantity that can be measured on a dc voltmeter.

DVM Outline:

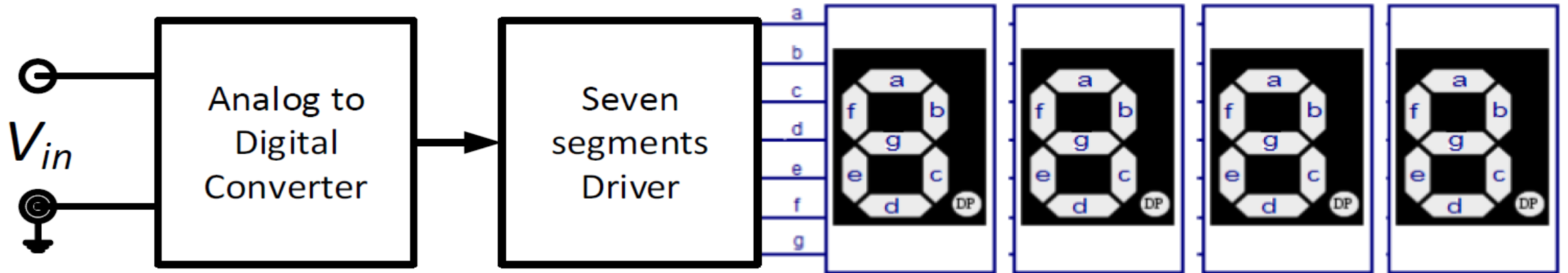1. Introduction.
2. Ramp Type Digital Voltmeters.
3. Dual Slope Digital Voltmeters.
4. DVM Range Changing.
5. Digital Voltmeter Accuracy.
6. Types of Digital Multi-meters.

Introduction:


- Two types will be covered: **Ramp-type** and **Dual slope Integrator DVMs**.
- Digital voltmeters (DVM) are essentially **analog-to-digital converters** with **digital displays** to indicate the measured voltage.




Digital Voltmeter Basic Block Diagram

Seven-Segment LED Display

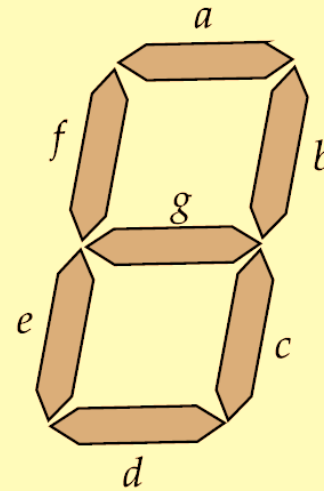
- There are two types:
1. Common Anode
 2. Common Cathode



(a) Seven-segment LED display

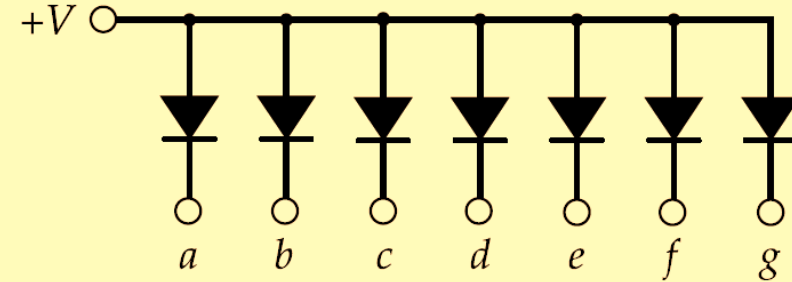

(b) Common-anode connections

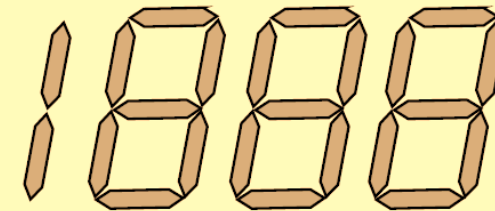

(c) Three-and-a-half digit display

Figure 6-10 Light-emitting diodes arranged in a *seven-segment* format can display any numeral from 0 to 9.

2. Ramp Type Digital Voltmeters

Ramp Type Digital Voltmeters:


- A ramp signal is generated.
- The comparator compares the input V_i with the ramp V_R .

$$V_1 = \begin{cases} 1, & \text{if } V_i \geq V_r \\ 0, & \text{if } V_i < V_r \end{cases}$$



- If the comparator output V_1 is high, the counting circuit will count the pulses from clock generator.
- If the output V_1 is low, the counting will stop.

- $N_{pulses} \propto V_i$.

- The value of V_i will be displayed

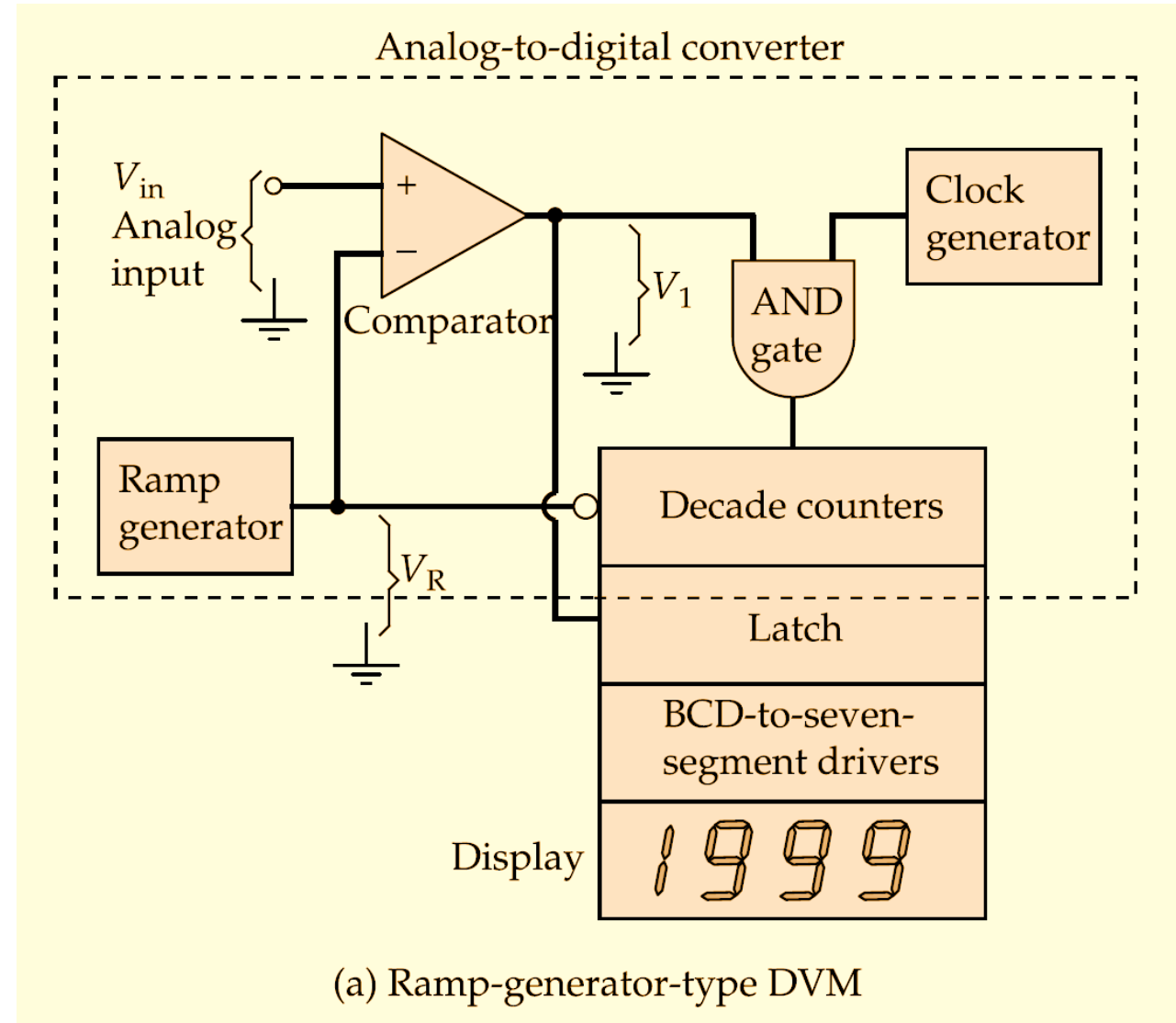


Ramp Type Digital Voltmeters (Cont.):

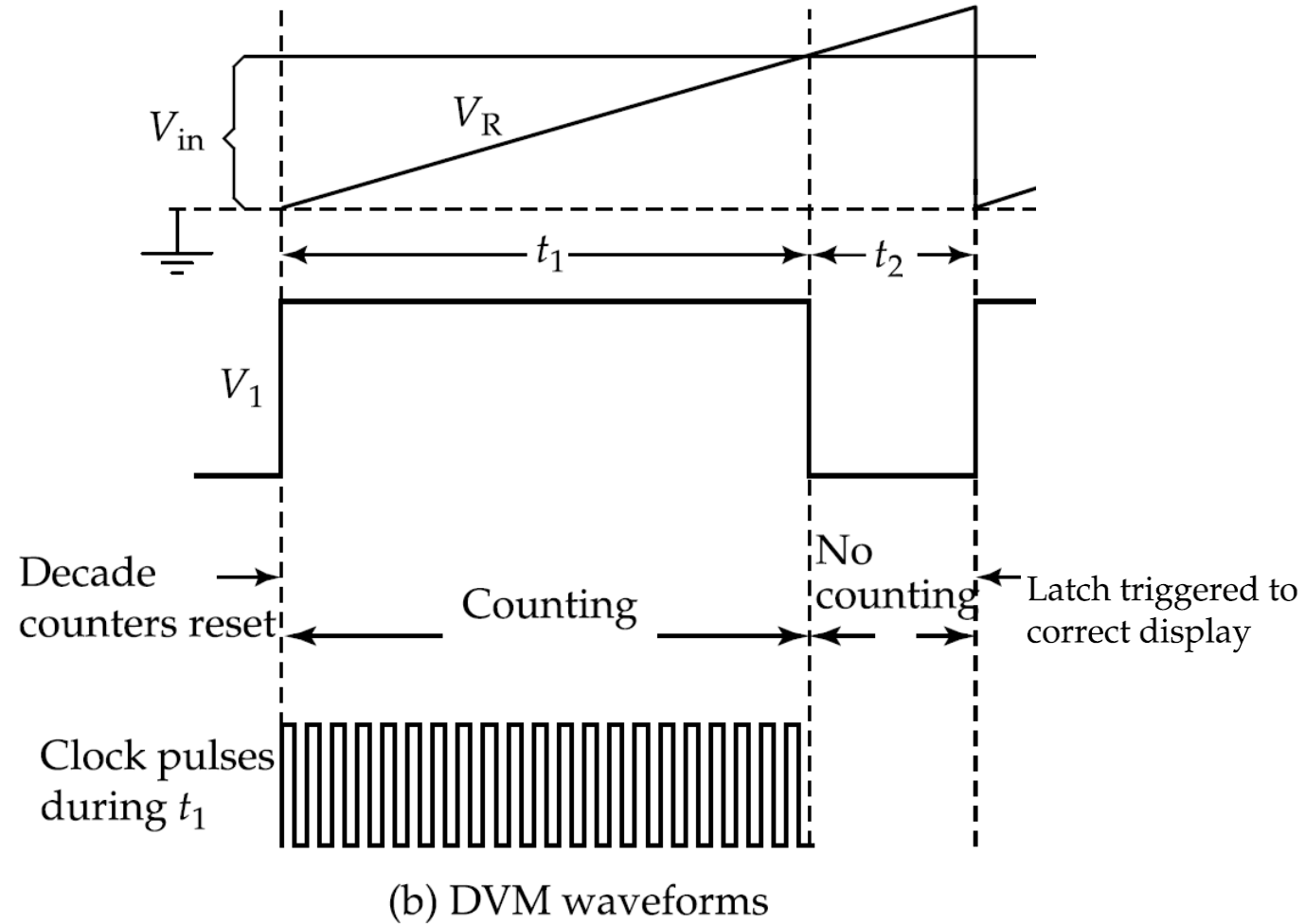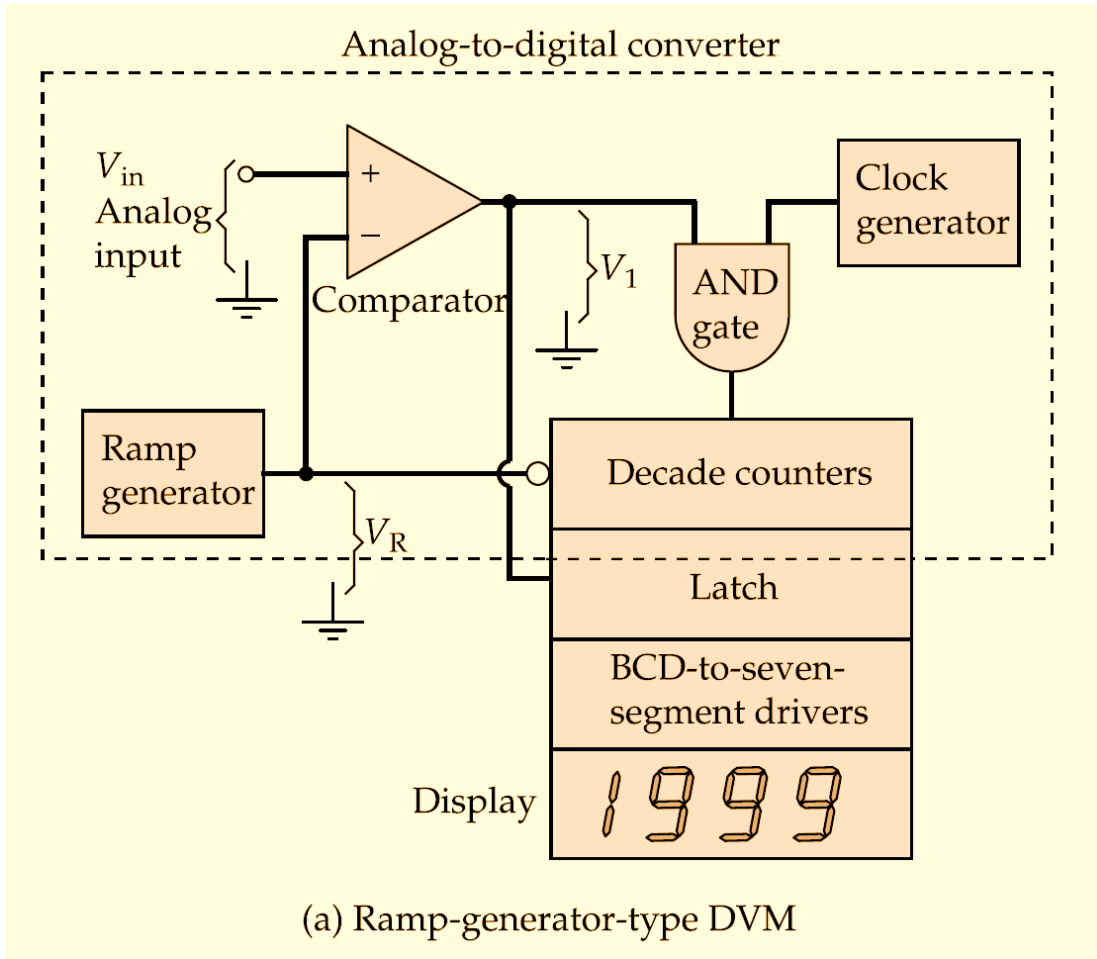


Ramp Type Digital Voltmeters (Cont.):

The use of the Latch:

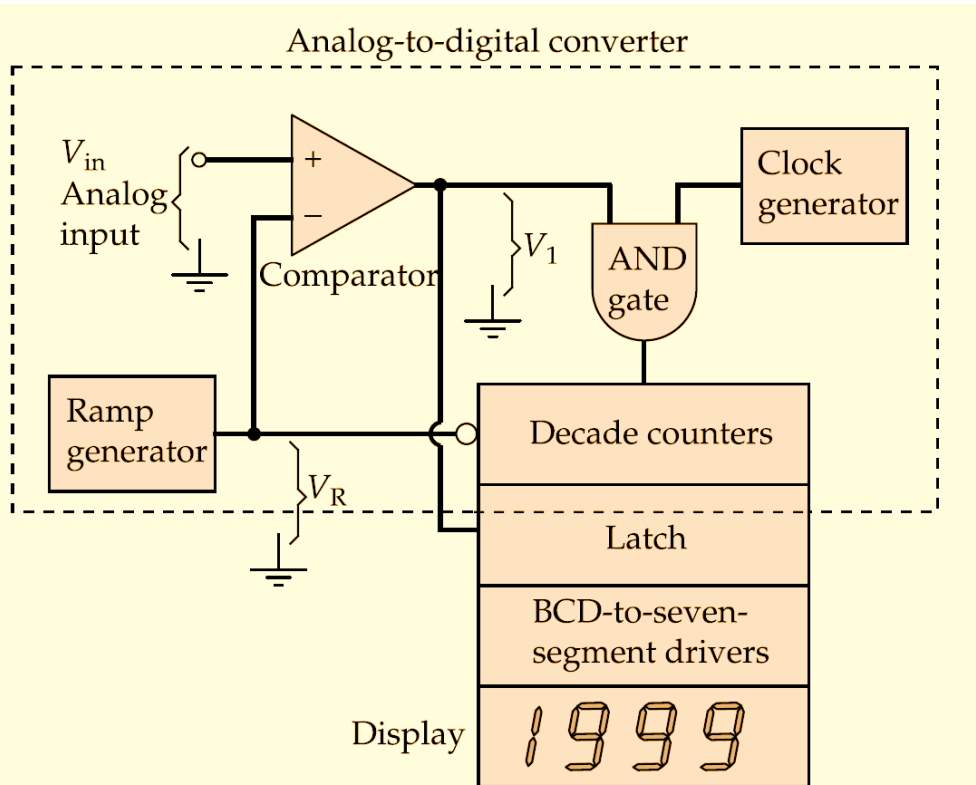1. The latch isolates the display from the counting circuit during the t_1 .
2. It will connect the display to the counting circuit at the rising edge of the comparator output.



(a) Ramp-generator-type DVM

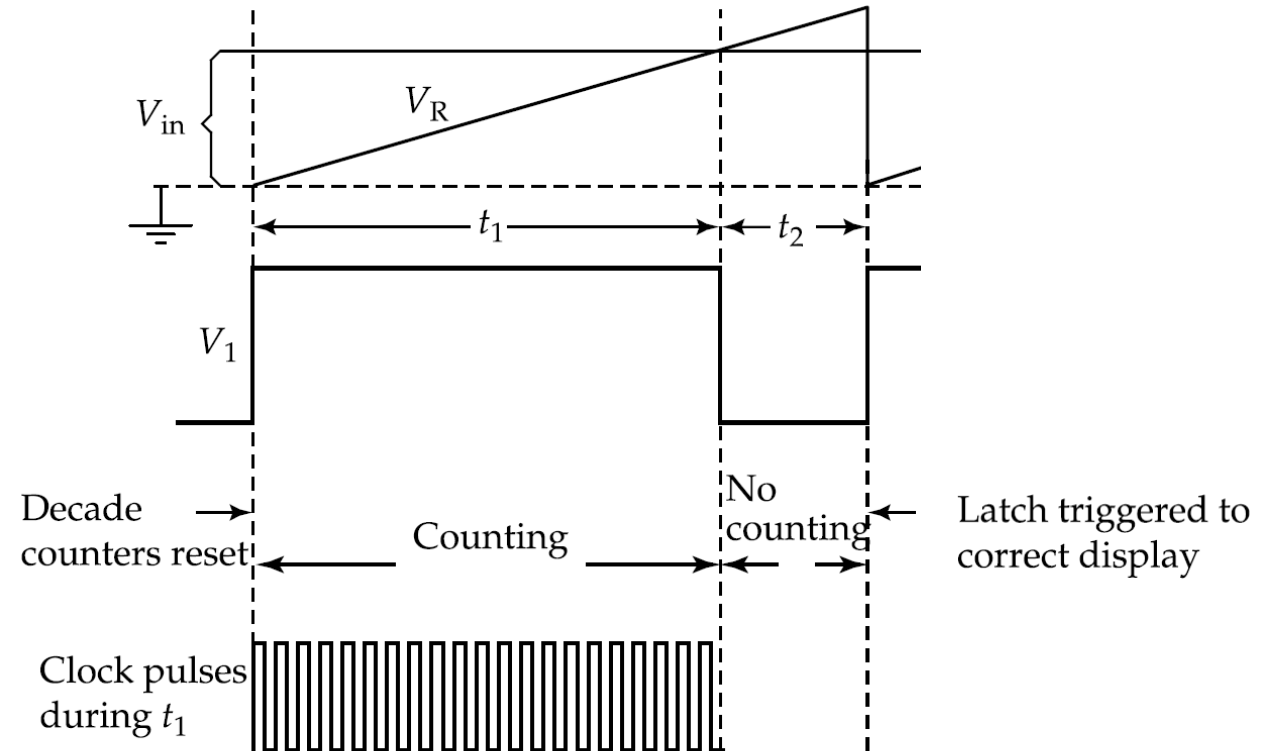

(b) DVM waveforms

End of Lecture

Best Wishes