



1. A certain transistor has a β_{DC} of 200. When the base current is $50 \mu\text{A}$, determine the collector current.
2. A BJT has $\alpha_{DC} = 0.99$; $I_B = 25 \mu\text{A}$, and $I_{CBO} = 200 \text{ nA}$. Find (a) the dc collector current, (b) the dc emitter current, and (c) the percentage error in emitter current when leakage current is neglected.

3. Determine I_B , I_C , I_E , V_{CE} , and V_{CB} in Figure 1 for the following values: $R_B = 22 \text{ k}\Omega$, $R_C = 220 \Omega$, $V_{BB} = 6 \text{ V}$, $V_{CC} = 9 \text{ V}$, and $\beta_{DC} = 90$.

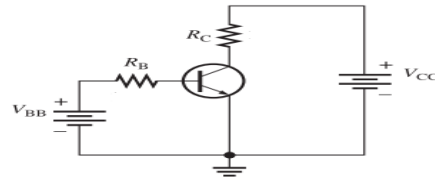


Figure 1

4. Determine whether or not the transistor in Figure 1 is saturated for the following values: $\beta_{DC} = 125$, $V_{BB} = 1.5 \text{ V}$, $R_B = 6.8 \text{ k}\Omega$, $R_C = 180 \Omega$, and $V_{CC} = 12 \text{ V}$. Assume $V_{CE(\text{sat})} = 0.2 \text{ V}$.
5. If $P_{D(\text{max})} = 1 \text{ W}$, how much voltage is allowed from collector to emitter if the transistor is operating with $I_C = 100 \text{ mA}$?

6. The transistor in Figure 2 has the following maximum ratings: $P_{D(\text{max})} = 500 \text{ mW}$, $V_{CE(\text{max})} = 25 \text{ V}$, and $I_{C(\text{max})} = 200 \text{ mA}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?

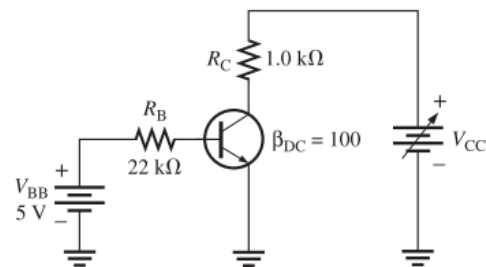


Figure 2

7. A transistor has a $P_{D(\text{max})} = 5 \text{ W}$ at 25°C . The derating factor is $10 \text{ mW}/^\circ\text{C}$. What is the $P_{D(\text{max})}$ at 70°C ?
8. A transistor connected as in Figure 3 has an $r'_e = 20 \Omega$. If R_C is 1200Ω , what is the voltage gain?

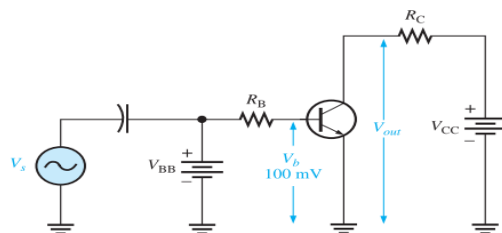


Figure 3



9. Determine the minimum value of I_B required to saturate the transistor in Figure 4 if β_{DC} is 125 and $V_{CE(sat)}$ is 0.2 V.

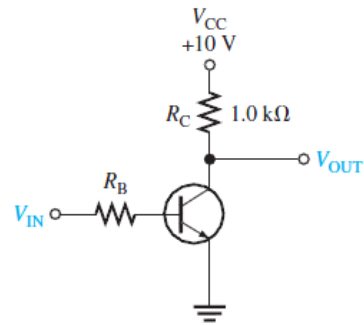


Figure 4

Design Problems

10. The transistor in the circuit of figure 5 has $\beta = 100$ and exhibits a V_{BE} of 0.7 V at $I_C = 1$ mA. Design the circuit so that a current of 2 mA flows through the collector and a voltage of +5 V appears at the collector.

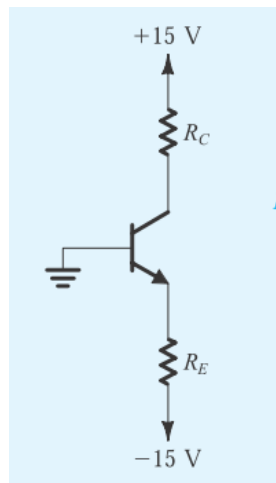


Figure 5