

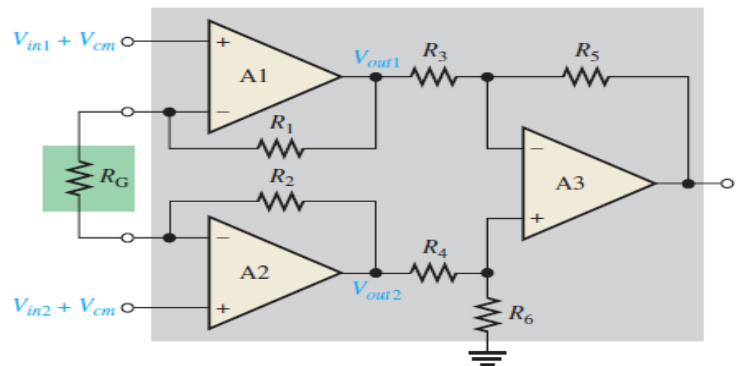


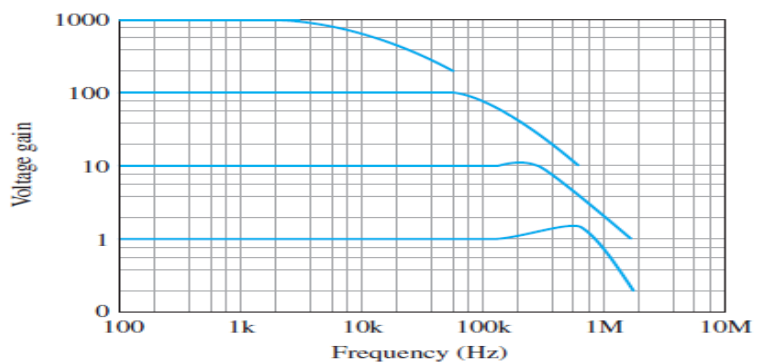

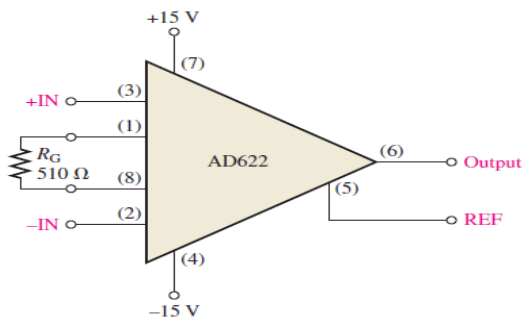
1. Determine the value of the external gain-setting resistor  $R_G$  for a certain IC instrumentation amplifier with  $R_1 = R_2 = 25K\Omega$ . The closed-loop voltage gain is to be 500.



2. Calculate the voltage gain and determine the bandwidth using the graph in Figure. Modify the circuit for a gain of approximately 45.




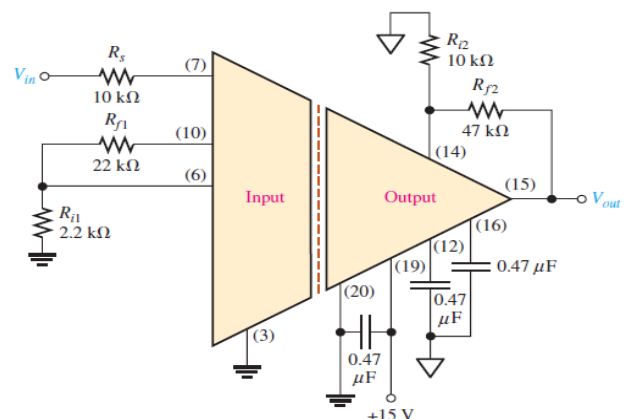3. Determine the total voltage gain of the 3656KG isolation amplifier in Figure




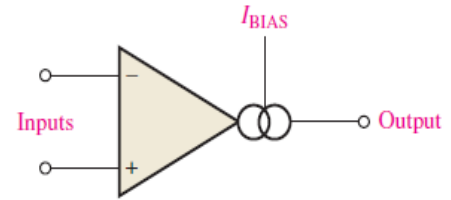4. If an OTA has a  $g_m = 1000 \text{ mS}$  what is the output current when the input voltage is  $25 \text{ mV}$ ?


Based on  $K \approx 16 \text{ mS/mA}$  calculate the approximate bias current required to produce  $g_m = 1000 \text{ mS}$ .



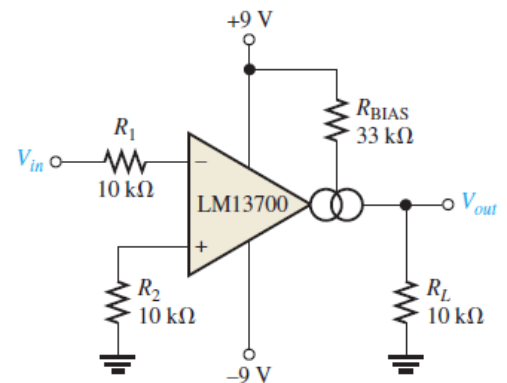
5. The OTA in Figure is connected as an inverting fixed-gain amplifier where  $+V_{BIAS} = +V$ . Determine the approximate voltage gain.  $K \approx 16 \text{ mS/mA}$



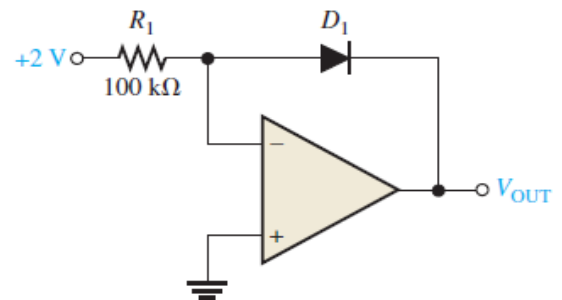
6. Determine the output voltage for the log amplifier in Figure. Assume  $I_R = 50 \text{ nA}$ .



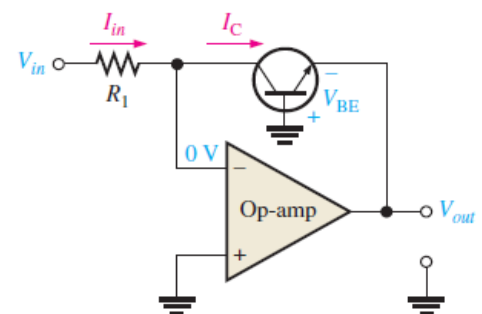7. What is  $V_{out}$  for a transistor log amplifier with  $V_{in} = 3 \text{ V}$  and  $R_1 = 68 \text{ k}\Omega$ ? Assume  $I_{EBO} = 40 \text{ nA}$ .



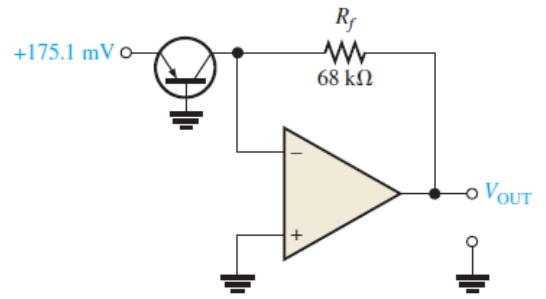8. For the antilog amplifier in Figure, find the output voltage. Assume  $I_{EBO} = 40 \text{ nA}$ .



9. Determine the load current in each circuit of Figure

