




1. When the ac input voltage of a certain power supply changes, the input to the voltage regulator decreases by 5 V as a result, and the output of the regulator decreases by 0.25 V. The nominal output is 15 V. Determine the line regulation in %/V.


2. A certain voltage regulator has a 12 V output when there is no load ($I_L = 0$) When there is a full-load current of 10 mA, the output voltage is 11.9 V. Express the voltage regulation as a percentage change from no-load to full-load and also as a percentage change for each mA change in load current.

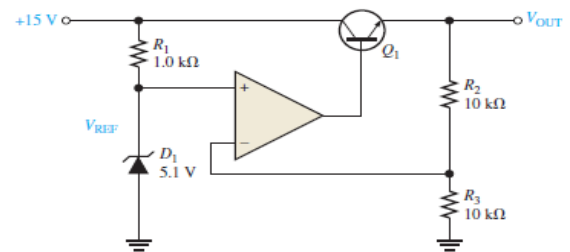3. Determine the output voltage for the regulator in Figure


A 3.3 V zener replaces the 5.1 V zener, $R_1 = 1.8 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, and $R_3 = 18 \text{ k}\Omega$. What is the output voltage?



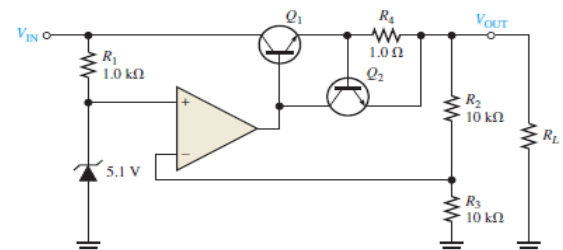4. Determine the maximum current that the regulator in Figure can provide to a load.



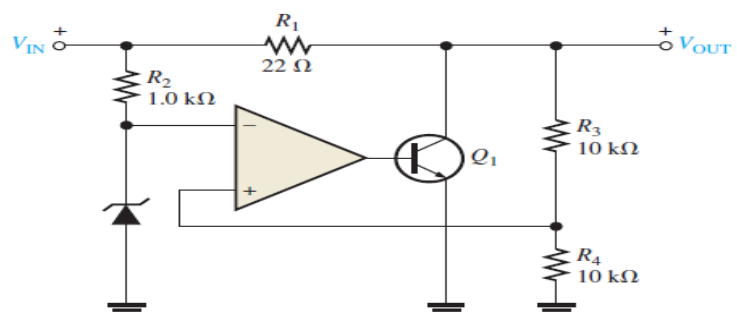
5. What power rating must R_1 have if the maximum input voltage is 12.5 V?



6. For the circuit shown in Fig, $R_1 = 10\text{ K}\Omega$ and $C_1 = 220\text{ pF}$, Find:

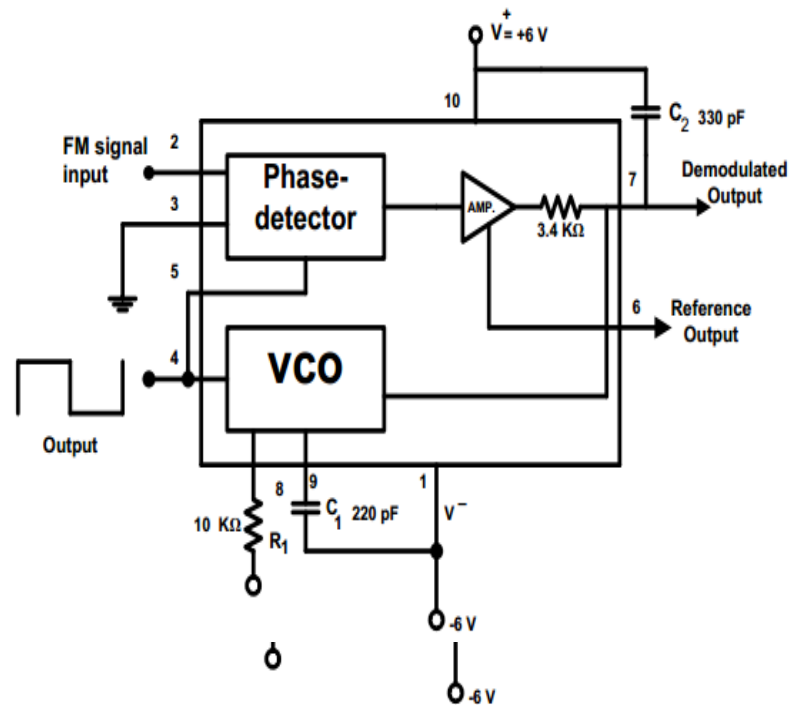- a) The free running-frequency f_0 .
- b) The lock range f_L .
- c) The capture range f_c .

What value of capacitor, C_1 , to obtain a center frequency of 100 KHz.



7. For the circuit shown in Fig, Find: f_0, f_L, f_c .

