
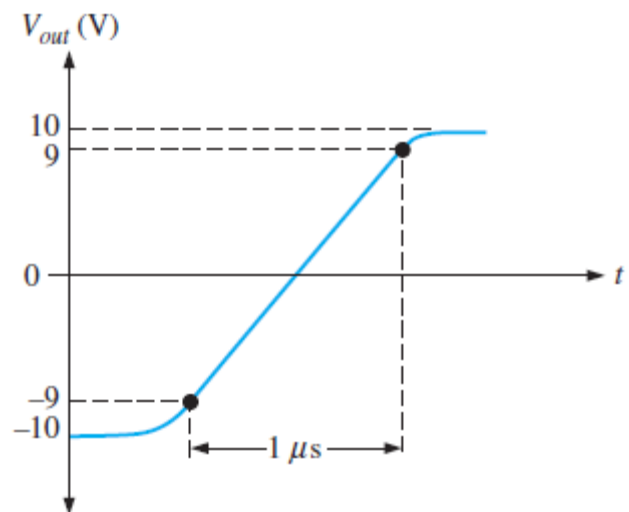


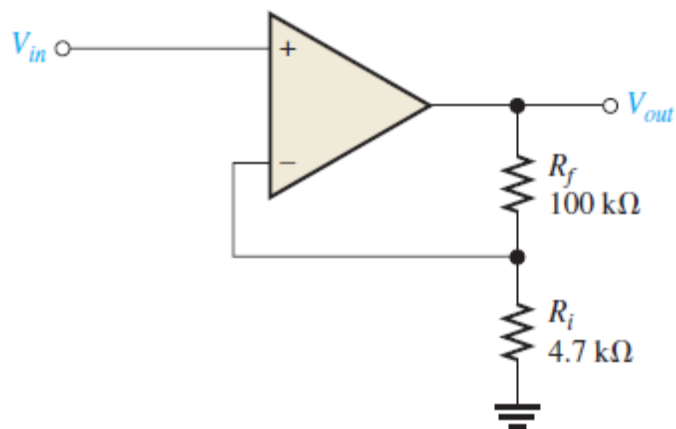


1. A certain op-amp has an open-loop differential voltage gain of 100,000 and a common-mode gain of 0.2. Determine the CMRR and express it in decibels.
2. The output voltage of a certain op-amp appears as shown in Figure in response to a step input. Determine the slew rate.



3. Determine the closed-loop voltage gain of the amplifier in Figure




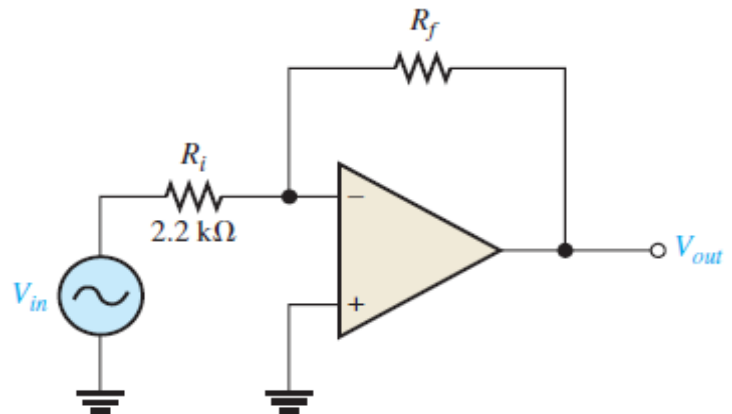4. Given the op-amp configuration in Figure, determine the value of  $R_f$  required to produce a closed-loop voltage gain of  $-100$ .




5. Design an operational amplifier circuit with gain equals:  
 a) 12      b) -12

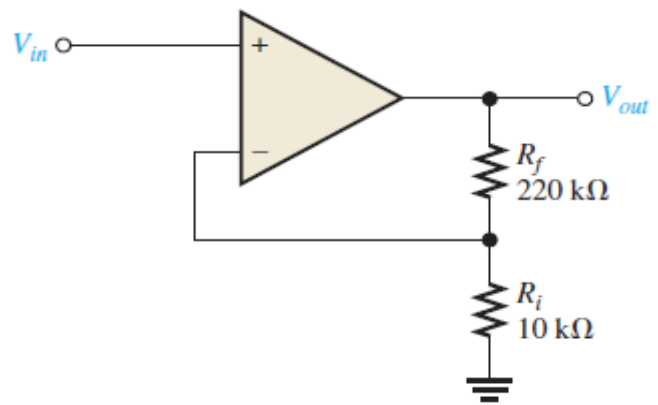6. Determine the input and output impedances of the amplifier in Figure. The op-amp datasheet gives  $Z_{in} = 2\text{M}\Omega$ ,  $Z_{out} = 75\Omega$ , and  $A_{ol} = 200,000$ . and then Find the closed-loop voltage gain.



7. The op-amp in problem 6 is used in a voltage-follower configuration. Determine the input and output impedances.

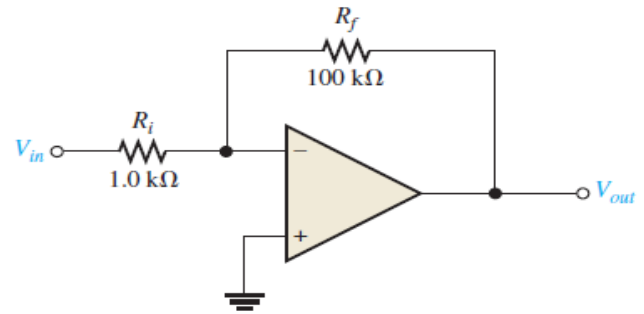8. Find the values of the input and output impedances in Figure. Also, determine the closed-loop voltage gain. The op-amp has the following parameters:  $A_{ol} = 50,000$ ;  $Z_{in} = 4\text{M}\Omega$ ; and  $Z_{out} = 50\Omega$ .



9. Design an operational amplifier circuit with the following specifications:

(Two stages, Total gain = 30 dB,  $Z_i = 100\text{K}\Omega$ ,  $Z_o = 1\Omega$ )

The op-amp has the following parameters:  $A_{ol} = 50,000$  and  $Z_{out} = 5\text{K}\Omega$ .

10. A certain op-amp has three internal amplifier stages with the following gains and critical frequencies:

Stage 1:  $A_{v1} = 40\text{ dB}$ ,  $f_{c1} = 2\text{ kHz}$


Stage 2:  $A_{v2} = 32\text{ dB}$ ,  $f_{c2} = 40\text{ kHz}$

Stage 3:  $A_{v3} = 20\text{ dB}$ ,  $f_{c3} = 150\text{ kHz}$


Determine the open-loop midrange gain in decibels and the total phase lag when  $f = f_{c1}$ .

11. A certain amplifier has an open-loop midrange gain of 150,000 and an open-loop 3 dB bandwidth of 200 Hz. The attenuation (B) of the feedback loop is 0.002. What is the closed-loop bandwidth?

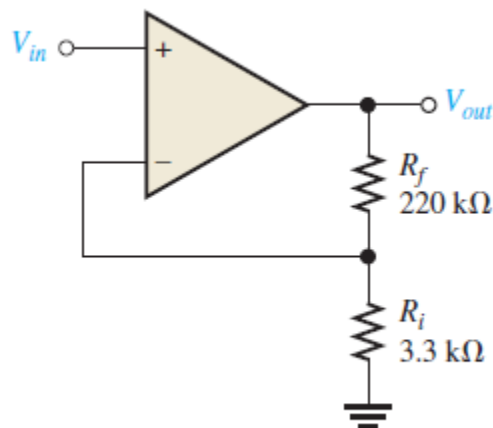12. Determine the bandwidth of each of the amplifiers in Figure. Both op-amps have an open-loop gain of 100 dB and a unity-gain bandwidth ( $f_T$ ) of 3 MHz.



(a)

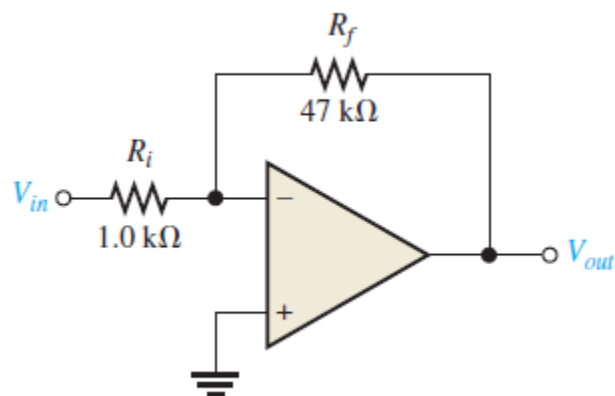

(b)