



1. A single-pole high-pass filter has a frequency-selective circuit with  $R = 2.2\text{k}\Omega$  and  $C = 0.0015\ \mu\text{F}$ .

What is the critical frequency? What is the roll-off rate of the filter?

2. What is the bandwidth of a band-pass filter whose critical frequencies are 3.2 kHz and 3.9 kHz? What is the  $Q$  of this filter?

3. A certain band-pass filter has a center frequency of 15 kHz and a bandwidth of 1 kHz. Determine  $Q$  and classify the filter as narrow-band or wide-band.

4. What is the center frequency of a filter with a  $Q$  of 12 and a bandwidth of 1 kHz?

5. If resistor  $R_2$  in the feedback circuit of an active single-pole filter of the type in Figure 1 is  $10\ \text{k}\Omega$ , the damping factor must be 1.414, what value must  $R_1$  be to obtain a maximally flat Butterworth response?

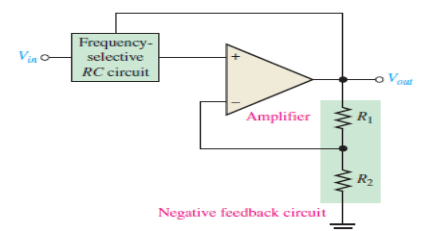


Figure 1

6. Determine the critical frequency of the Sallen-Key low-pass filter in Figure 2, and set the value of  $R_1$  for an approximate Butterworth response.

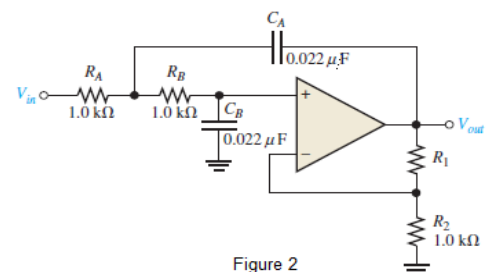


Figure 2

7. For the four-pole filter in Figure 3, determine the capacitance values required to produce a critical frequency of 2680 Hz if all the resistors in the  $RC$  low-pass circuits are  $1.8\ \text{k}\Omega$ , Also select values for the feedback resistors to get a Butterworth response.

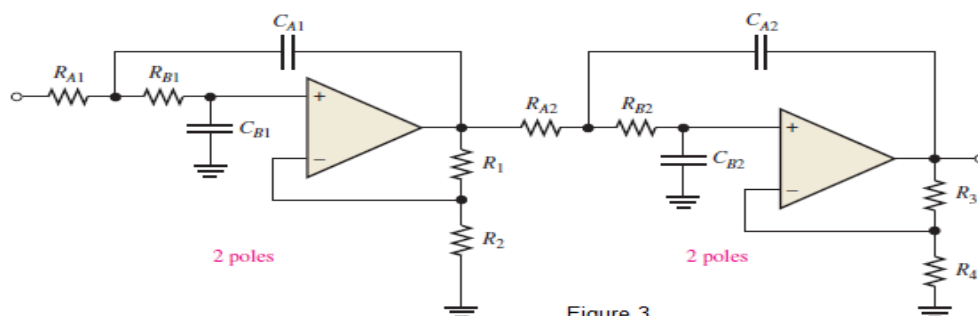


Figure 3

8. Using a block diagram format, show how to implement the following roll-off rates using single-pole and 2-pole LPF with Butterworth responses:

- a) -40 dB/decade.
- b) -20 dB/decade.
- c) -60 dB/decade.
- d) -100 dB/decade.
- e) -120 dB/decade.

9. Choose values for the Sallen-Key high-pass filter in Figure 4 to implement an equal-value second-order Butterworth response with a critical frequency of approximately 10 kHz.

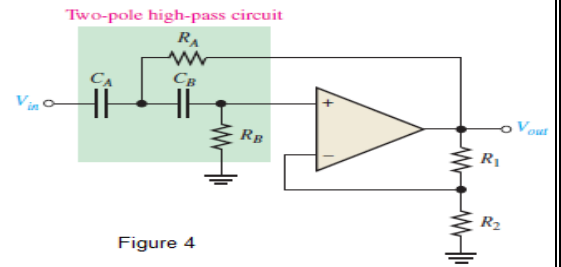


Figure 4

10. Determine the center frequency, maximum gain, and bandwidth for the filter in Figure 5.



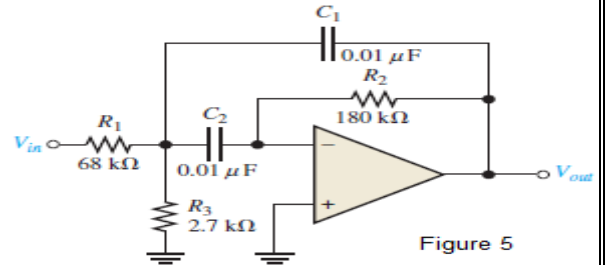


Figure 5

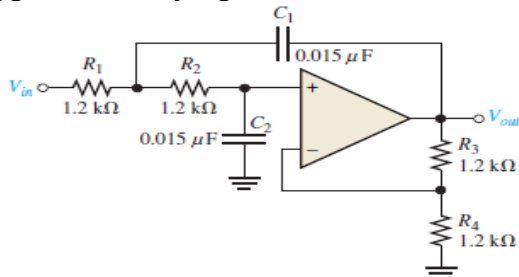
11. What is the damping factor in each active filter shown in Figure, Which filters are approximately optimized for a Butterworth response characteristic?



(a)

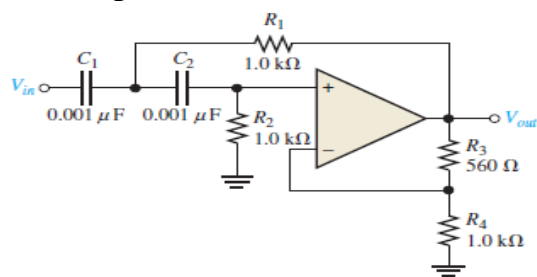

(b)

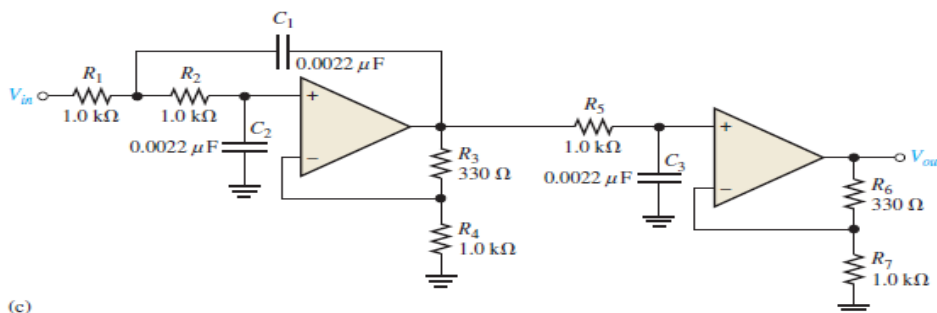

(c)

12. Determine the center frequency,  $Q$ , and  $BW$  for the passband of the state-variable filter in Figure 6.

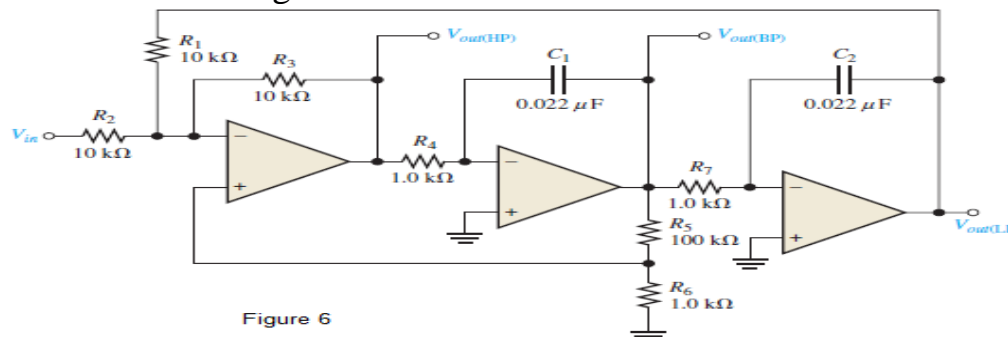


Figure 6

13. Verify that the band-stop filter in Figure 7 has a center frequency of 60 Hz, and optimize the filter for a  $Q$  of 10.



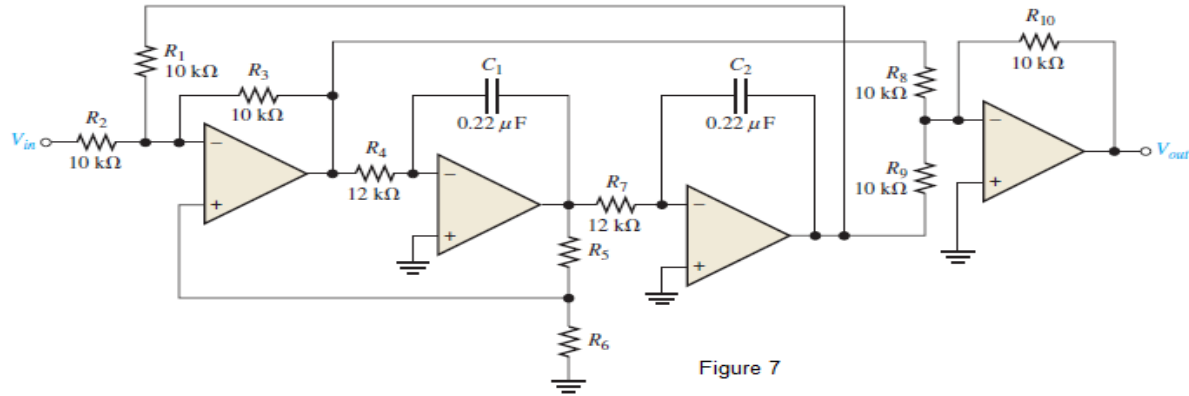


Figure 7

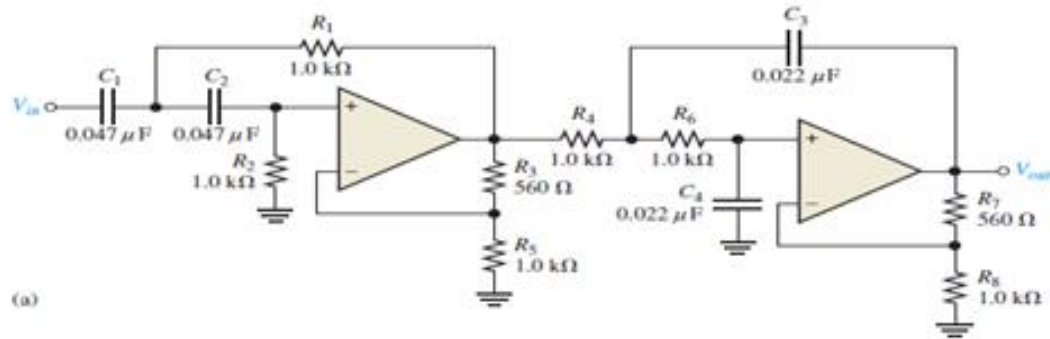
14. Determine the center frequency and bandwidth for each filter in Figure



(a)

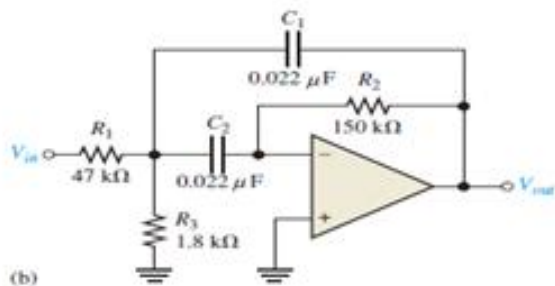

(b)

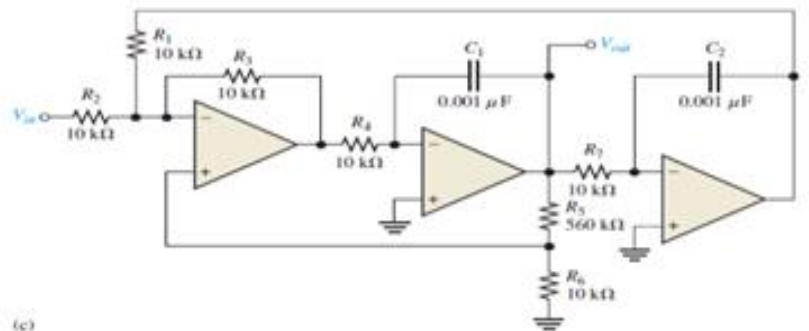

(c)

ORDER	ROLL-OFF DB/DECADE	1ST STAGE			2ND STAGE			3RD STAGE		
		POLES	DF	$R_1/R_2$	POLES	DF	$R_3/R_4$	POLES	DF	$R_5/R_6$
1	-20	1	Optional							
2	-40	2	1.414	0.586						
3	-60	2	1.00	1	1	1.00	1			
4	-80	2	1.848	0.152	2	0.765	1.235			
5	-100	2	1.00	1	2	1.618	0.382	1	0.618	1.382
6	-120	2	1.932	0.068	2	1.414	0.586	2	0.518	1.482