




Faculty of Engineering–Shoubra
Electrical Engineering Department
2nd year communication
Sheet (4)

Review Questions


- 1 Sketch the circuit of a simple BJT emitter-follower voltmeter circuit and compare it to a non-electronic voltmeter.
- 2 Sketch the circuit of an emitter-follower voltmeter using two transistors. Carefully explain the circuit operation.
- 3 Draw a circuit diagram for an FET-input voltmeter with an input attenuator. Explain the circuit operation.

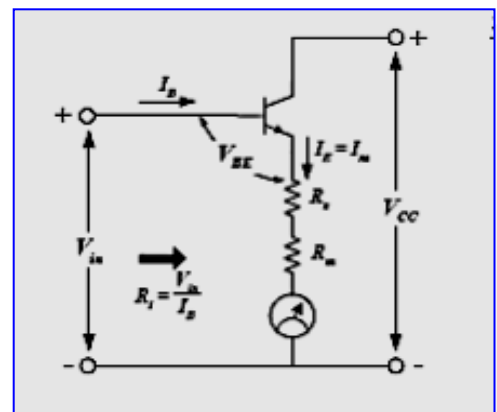Problems

1 A simple emitter-follower voltmeter circuit as shown in Fig1. has $V_{cc} = 12\text{ V}$, $R_m = 1\text{ k}\Omega$, a 2 mA meter, and a transistor with $h_{FE} = 80$. Calculate a suitable resistance for R_s to give FSD when $V_{in} = 5\text{ V}$. Also, determine the voltmeter input resistance.




2 A Practical emitter-follower voltmeter circuit, as in Fig. 2, has the following components: $R_1=12\text{ k}\Omega$, $R_2=R_3=2.7\text{ k}\Omega$, $R_4=R_6=3.3\text{ k}\Omega$, $R_5 = 500\ \Omega$, and $R_s + R_m = 10\text{ k}\Omega$. A $100\ \mu\text{A}$ meter is used, the supply voltage is $\pm 9\text{ V}$, and the transistors have $h_{FE} = 75$. Determine V_p , I_2 , I_3 , I_{B1} , I_{B2} , and I_4 when $V_{in} = 0$.

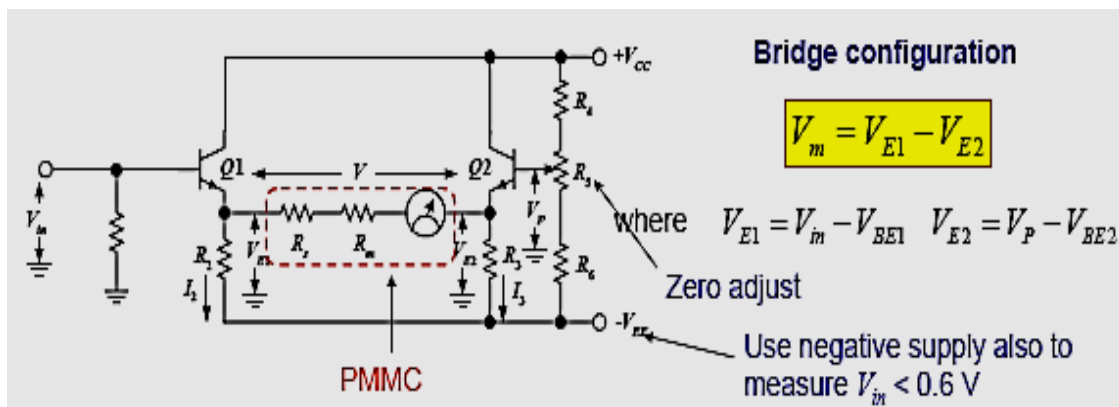

3 Calculate the meter deflections (I_m) for the circuit in Problem 5-2 when the input voltage levels are 0.6 V, 0.75 V, and 1 V.

4 The FET-input voltmeter circuit fig. 3 with an input attenuator has $V_{GS} = -3$ V, $V_{B2} = +3$ V, $(R_s + R_m) = 10$ k Ω , and $I_m = 100$ μ A at full scale. Determine the meter current when $E = 3.5$ V and the input attenuator is set to 5 V range?

Fig.3

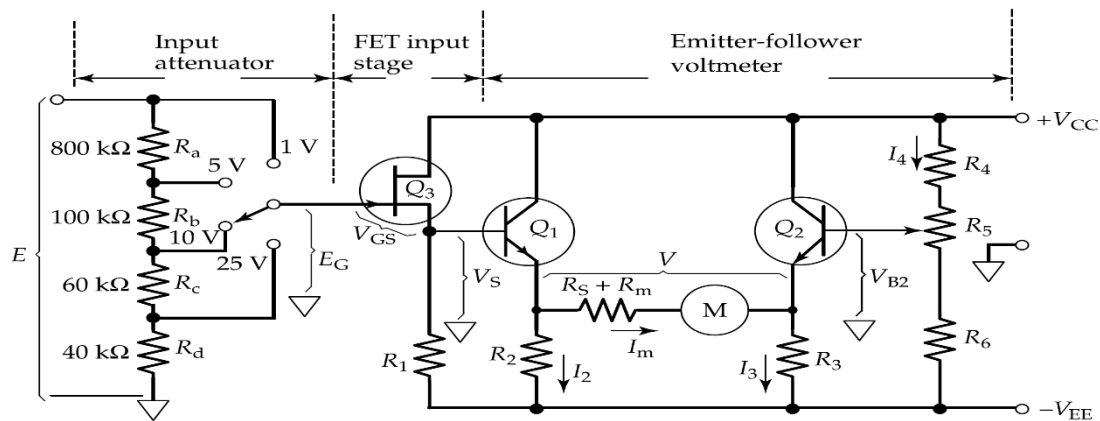

5 The FET input voltmeter circuit in Fig. 3 has the following components:

$R_1 = 6.8$ k Ω , $R_2 = R_3 = 4.7$ k Ω , $R_4 = 1.5$ k Ω , $R_5 = 500$ Ω , $R_6 = 3.3$ k Ω , $R_s + R_m = 20$ k Ω . The meter full-scale current is 50 μ A, the supply voltage is ± 10 V, the BJTs have $h_{FE} = 80$, and the FET gate-source voltage is $V_{GS} = -3$ V. Determine V_{B2} , I_s , I_2 , I_3 , and I_4 when $E = 0$. Also, calculate the range of adjustment for V_{B2}

