

Faculty of Engineering–Shoubra
Electrical Engineering Department
2nd year communication
Sheet (3)




(1) A PMMC inst. With a 750Ω coil resistance gives FSD with a $500 \mu\text{A}$ coil current. Determine the required shunt resistance to convert the instrument into a **DC ammeter with FSD**:

- (a) 50 mA (b) 30 mA

(2) A **DC ammeter** is constructed of 133.3Ω resistance in parallel with a PMMC inst. If the inst. has $1.2 \text{ K}\Omega$ coil resistance and $30 \mu\text{A}$ FSD, Determine the measured current at:

- (a) FSD (b) 0.5 FSD (c) 0.33 FSD

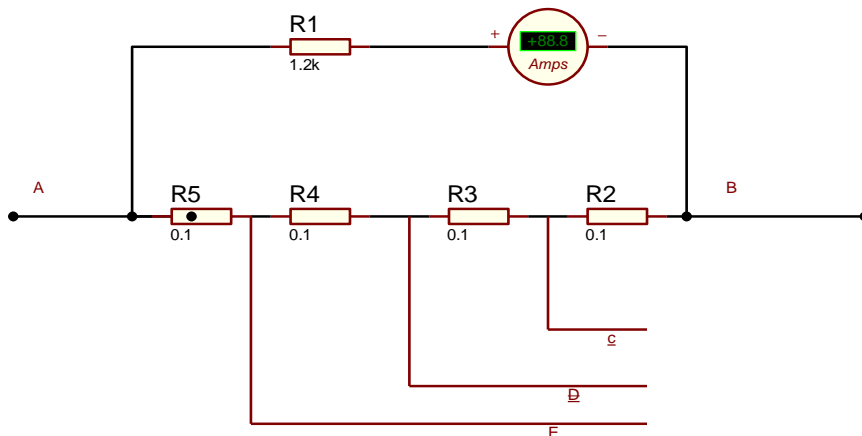(3) A DC ammeter consists of an **Ayrton shunt** in parallel with a PMMC inst. that has a $1.2 \text{ k}\Omega$ coil resistance and $100 \mu\text{A}$ FSD. The **Ayrton shunt** is made up of four 0.1Ω series connected resistors. Calculate the ammeter range at each setting of the shunt.



(4) A 12 V source supplies 25 A to a load. Calculate the load current that would be measured, and the ammeter loading effect when using **an ammeter with resistance of**:

- (a) 0.52Ω (b) 0.12Ω (c) 0.002Ω

(5) A PMMC inst. with a 900Ω coil resistance and an FSD $75 \mu\text{A}$ coil is to be **used as a DC voltmeter**. Calculate the individual multiplier resistance to give a FSD of


- (a) 5V (b) 30V (c) 100V.

Also determined the voltmeter sensitivity in each case?

(6) A PMMC inst. With a $900\ \Omega$ coil resistance and an FSD $75\ \mu\text{A}$ coil is to be used as a DC voltmeter. Calculate the multiplier resistance values when series connected multipliers are used to have the ranges:

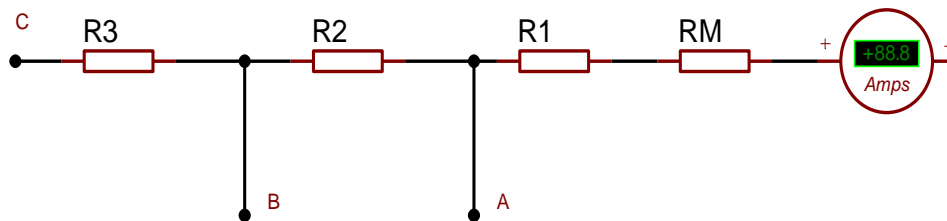- (a) 5V (b) 30V (c) 100V.

Also determined its sensitivity in each case?



(7) A PMMC inst. with $R_m = 1.3\ \text{k}\Omega$ and $\text{FSD} = 500\ \mu\text{A}$ is used in a multi range DC voltmeter. The series connected multiplier resistors are $R_1 = 38.7\ \text{k}\Omega$, $R_2 = 40\ \text{k}\Omega$, and $R_3 = 40\ \text{k}\Omega$. Calculate the three voltage ranges and determine the voltmeter sensitivity for each range setting.

(8) Two resistors $R_1 = 47\ \text{k}\Omega$, $R_2 = 82\ \text{k}\Omega$, are connected in series across a 15V supply. A voltmeter on 10 V range is connected to measure across R_2 . The voltmeter sensitivity is $10\ \text{k}\Omega/\text{V}$. Calculate V_{R_2} , and the voltmeter loading effect when the voltmeter is:

- (a) Disconnected
(b) Connected

(9) A $100\ \text{k}\Omega$ potentiometer and $33\ \text{k}\Omega$ resistor are connected in series across a 9 V supply. Calculate the max. voltage that can be measured across the potentiometer, and the voltmeter loading effect using a voltmeter with:

- (a) $20\ \text{k}\Omega/\text{V}$ sensitivity and a 15V range.
(b) $100\ \text{k}\Omega/\text{V}$ sensitivity and a 10V range.

(10) Two resistors $R_1 = 70\ \text{k}\Omega$, $R_2 = 50\ \text{k}\Omega$, are connected in series across a 12V supply. A voltmeter on 5 V range is connected to measure the voltage across R_2 . Calculate V_{R_2} , and the voltmeter loading effect when the voltmeter:

- (a) Disconnected
(b) Has a sensitivity of $20\ \text{k}\Omega/\text{V}$
(c) Has a sensitivity of $200\ \text{k}\Omega/\text{V}$

(11) An AC voltmeter uses a bridge rectifier with silicon diodes and a PMMC instrument with $FSD = 75 \mu A$. If the meter coil resistance is 900Ω and the multiplier resistor is $708 k\Omega$, calculate the applied rms voltage when the voltmeter indicates FSD and find the voltmeter sensitivity.

(12) Determine the new multiplier resistance required for the voltmeter in problem (11) to extend its range to $300V$ FSD. Then determine the pointer position of the voltmeter when the applied RMS voltage is:


- (a) $150 V$,
- (b) $75 V$

(13) A rectifier AC ammeter is to indicate full scale for a $1 A$ rms current (I_{prms}). The PMMC instrument used has 1200Ω coil resistance and $500\mu A$ of FSD (I_{mav}), and the current transformer has $N_s = 7000$ and $N_p = 10$. Silicon diodes are used and the meter series resistance is $R_s = 150 k\Omega$. Determine the required secondary shunt resistance value (R_L). $I_L R_L = I_m (R_s + R_m) + 2V_f$


(14) A rectifier AC ammeter has the following components: PMMC instrument with FSD of $200 \mu A$ (I_{mav}), and $R_m = 900 \Omega$, current transformer with $N_s = 600$ and $N_p = 50$, diodes with $V_f = 0.7V$, meter series resistance $R_s = 270 k\Omega$, transformer secondary shunt resistance $R_L = 98.7 k\Omega$. Calculate the level of transformer primary current for instrument FSD.

(15) A basic series ohmmeter is made up of a $3V$ battery, PMMC meter and a resistance R_1 which made ($R_1 + R_m = 20 k\Omega$). Draw the circuit diagram then determine:

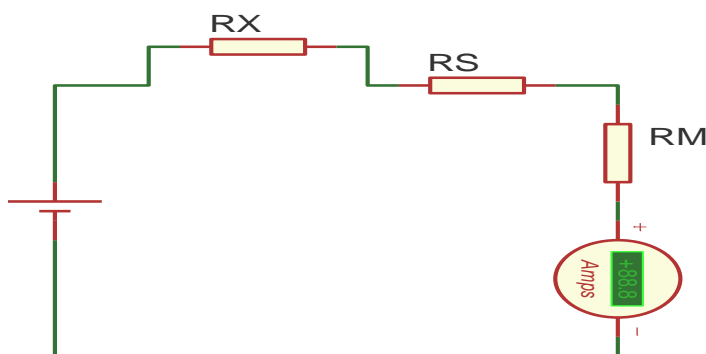- a) The instrument indication (I_{mFSD}) when $R_X = 0 \Omega$.
- b) How the resistance scale should be marked at $0.5FSD$, $0.25FSD$ and $0.75FSD$.



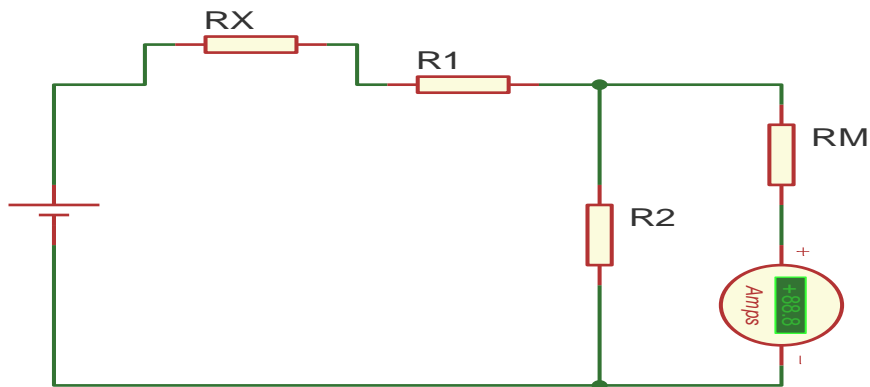(16) A series ohmmeter is made up of a supply voltage $V_B=3V$ series resistor $R_1=30k\Omega$, meter shunt resistance $R_2=50\Omega$, meter FSD= $50\mu A$ and a meter resistance $R_m=50\Omega$. Determine the resistance measured at 0, 0.5, 0.25, and 0.75 of FSD.



(17) For the series ohmmeter circuit in problem (16) “ $V_B = 3V$ series resistor $R_1=30k\Omega$, meter shunt resistance $R_2=50\Omega$, meter FSD= $50\mu A$ and a meter resistance $R_m=50\Omega$ ”. Determine the new resistance to which R_2 must be adjusted when V_B falls to $2.5V$; also determine the new resistance measured at 0.5, 0.75 of FSD.

(18) Using a $3 V$ battery together with a meter that has $1mA$ FSD and a coil resistance of 50Ω , design a series ohmmeter to have measured resistance = $2k\Omega$ at half scale deflection.

