

# Electrical and Electronic Measurements

## Lecture 6: Digital Voltmeters

**Dr. Haitham El-Hussieny**

Electronics and Communications Engineering  
**Faculty of Engineering (Shoubra)**  
**Benha University**



October 2018

# Lecture Outline:


- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.
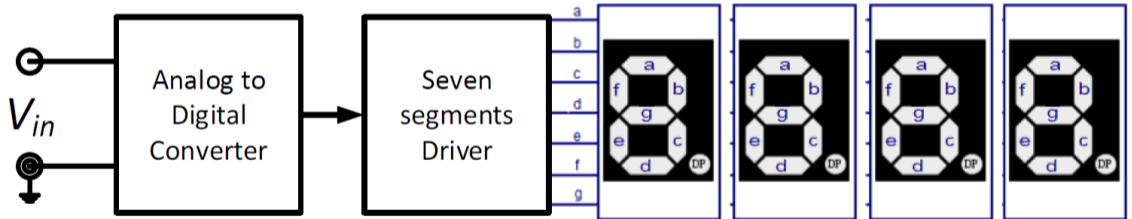
## Introduction:

- Two types will be covered: **Ramp-type** and **Dual slope Integrator DVMs**.
- Digital voltmeters (DVM) are essentially **analog-to-digital converters** with **digital displays** to indicate the measured voltage.



**Digital Voltmeter Basic Block Diagram**

# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.**
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

## Ramp Type Digital Voltmeters:


- A ramp signal is generated.
- the comparator compares the input  $V_i$  with the ramp  $V_r$ .

$$V_1 = \left\{ \begin{array}{ll} 1, & \text{if } V_i \geq V_r \\ 0, & \text{if } V_i < V_r \end{array} \right\}$$

- If the comparator output  $V_1$  is high, the counting circuit will count the pulses from clock generator.
- If the output  $V_1$  is low, the counting will stop.


- $N_{pulses} \propto V_i$ .

- The value of  $V_i$  will be displayed

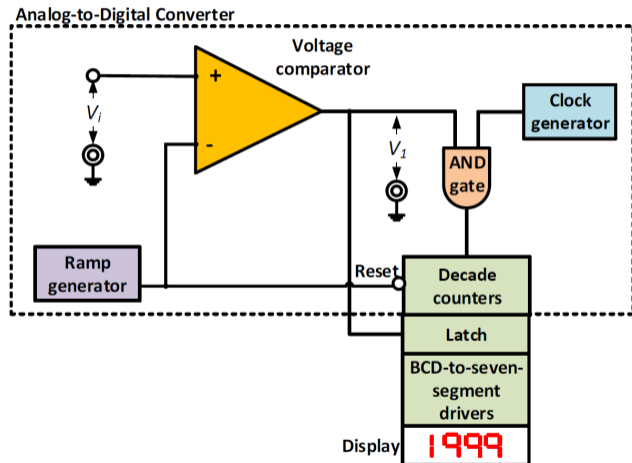


Ramp type DVM block

# Ramp Type Digital Voltmeters:

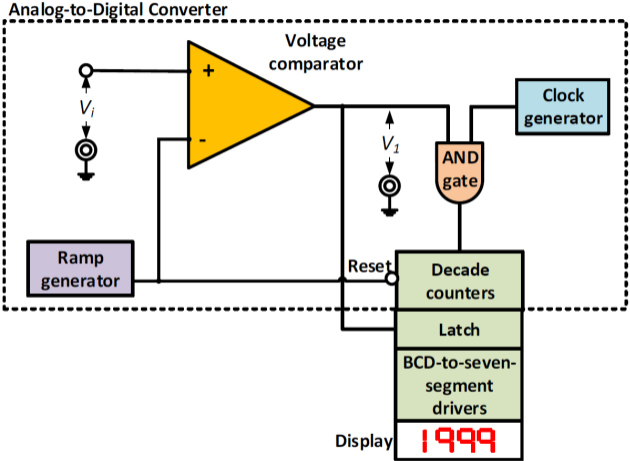

Ramp type DVM block

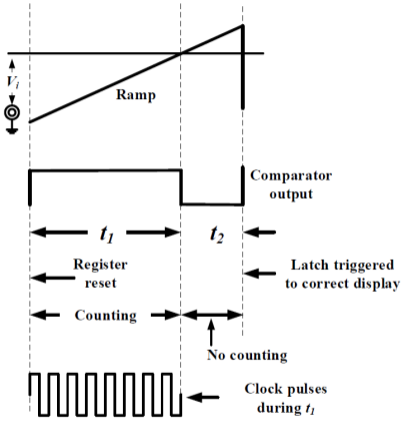


DVM waveform


# Ramp Type Digital Voltmeters:
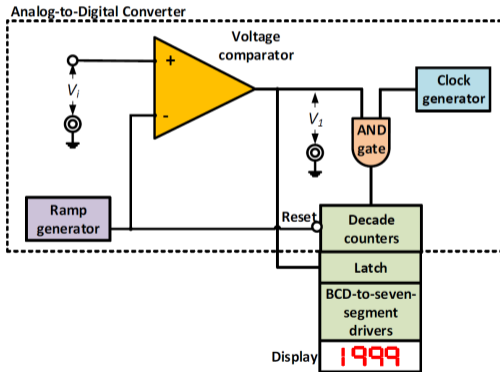
## The use of the Latch:

- The latch isolates the display from the counting circuit during the  $t_1$ .
- It will connect the display to the counting circuit at the rising edge of the comparator output.



Ramp type DVM block

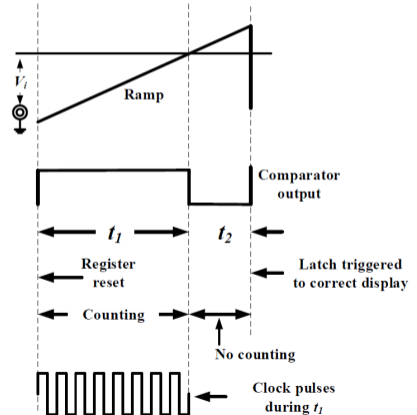




# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.**
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.

# Dual Slope Digital Voltmeters:

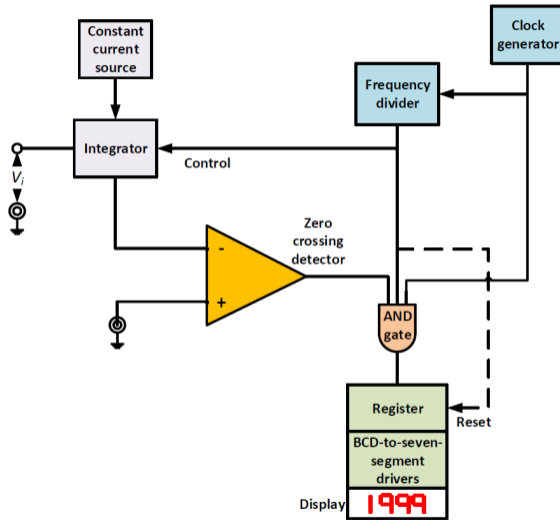


Dual Slope DVM block

## Limitations of Ramp type DVM


- The ramp type DVM **requires precise ramp voltage and precise time periods.** (Not accurate)
- The Dual-slope-integrator DVM eliminates this requirement.

# Dual Slope Digital Voltmeters:

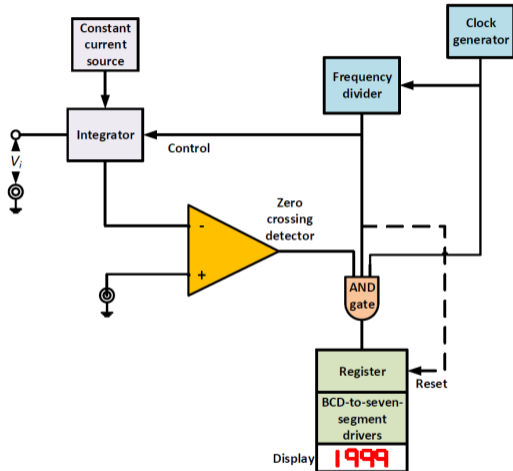


Dual Slope DVM block

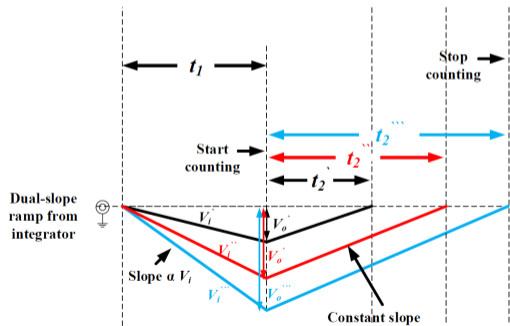- An integrator (e.g. capacitor) is either charged negatively from  $V_i$  or discharged at a constant rate according to the control signal.




# Dual Slope Digital Voltmeters:

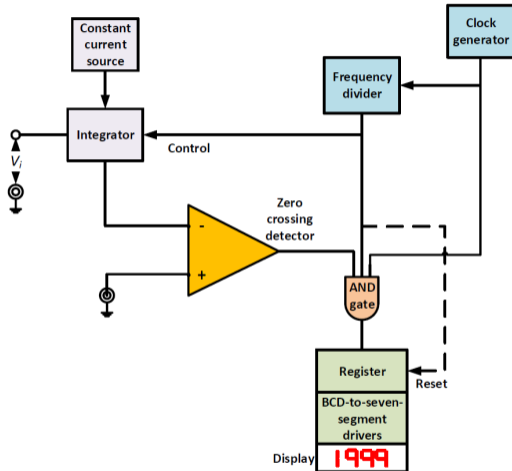


Dual Slope DVM block

- The control signal is derived from the **clock generator and a frequency divider**.
- During the charging time  $t_1$ , the integrator is charged to  $V_o$  that depends on  $V_i$ .
- During the discharging, the integrator is discharged in constant rate in duration  $t_2$  that **depends on  $V_o$  and hence on  $V_i$** .
- A voltage comparator is used as zero-crossing-detector to output high if integrator voltage is lower than zero.

# Dual Slope Digital Voltmeters:

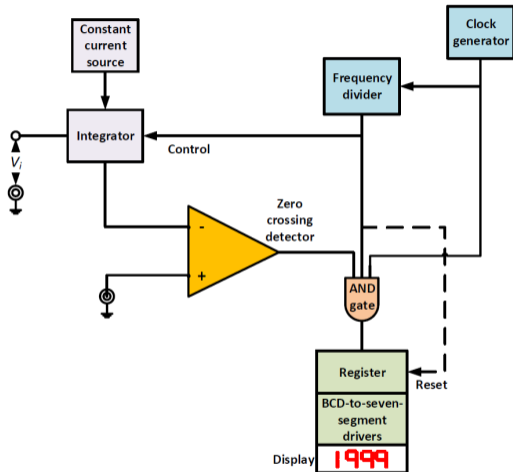

Dual Slope DVM block

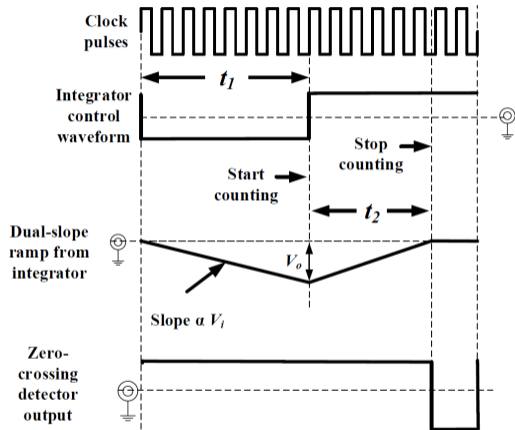

DVM waveform

# Dual Slope Digital Voltmeters:

How the Dual slope integrator DVM eliminates the need for accurate timing ?

(1) During charging:

$$V_o = -V_i t_1$$


(2) During discharging:

$$V_o = K t_2 \quad K \text{ is constant}$$

So,

$$V_i = -K \frac{t_2}{t_1}$$

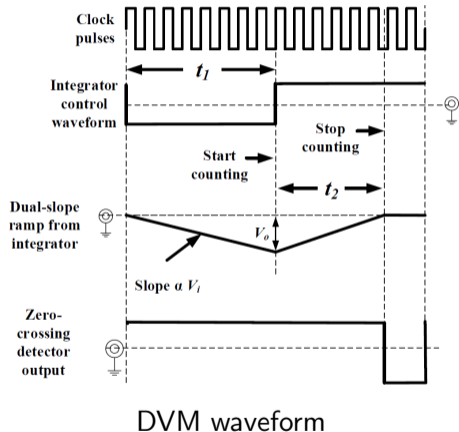Thus the input voltage measurement is not dependent on the clock frequency, but depends on the ratio  $\frac{t_1}{t_2}$ .




# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.**
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.
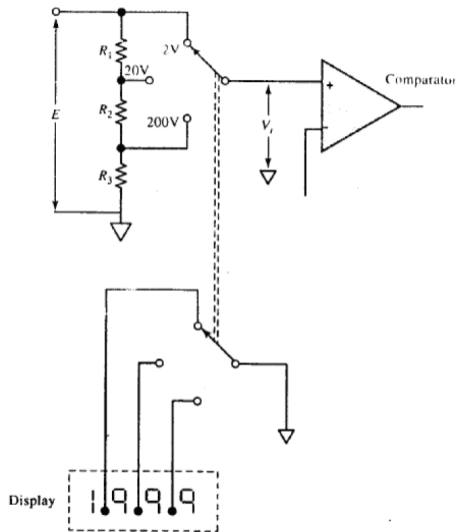
## DVM Range Changing:

The attenuation circuit is used to select the range of input voltage:

- if  $V_{in} \leq 1.999 V$ , the input is applied directly on the comparator.
- if  $1.999 V < V_{in} \leq 19.99 V$ , the input is attenuated and the decimal point is changed.
- and so on for  $19.99 V < V_{in} \leq 199.9 V$



## DVM Range Changing



# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.**
- 6 Types of Digital Multi-meters.

# Digital Voltmeter Accuracy:

## Accuracy in DVMs:

Digital voltmeter accuracy is usually stated as:

$$\pm(0.5\% \text{ rdg} + 1 \text{ digit})$$

where 1 digit refers to the extreme right (least significant digit) that depends on the range.

### Example

If the accuracy is  $\pm(0.5\% \text{ rdg} + 1 \text{ digit})$

What is the maximum error of reading

1.800 V on:

- (1) the 2 V scale.
- (2) the 20 V scale.

### Solution:

(1) error =

$$\pm[0.5\% \times 1.8V + 0.001] = \pm 0.01V$$

(2) error =

$$\pm[0.5\% \times 1.8V + 0.01] = \pm 0.019V$$

# Table of Contents

- 1 Introduction.
- 2 Ramp Type Digital Voltmeters.
- 3 Dual Slope Digital Voltmeters.
- 4 DVM Range Changing.
- 5 Digital Voltmeter Accuracy.
- 6 Types of Digital Multi-meters.**

# Types of Digital Multi-meters:



**Hand-held Multimeter**



**Bench-type Multimeter**

# Types of Digital Multi-meters:

## Clamp Meters:




### Advantage:

It is an electrical device having two jaws which open to allow **clamping around an electrical conductor**. This allows to measure electric current through conductor, without having to make physical contact with it, or **to disconnect it for insertion** through the probe.

# Types of Digital Multi-meters:
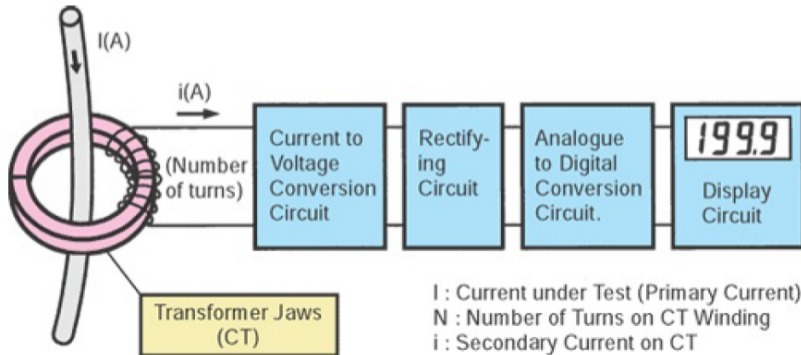
## How Do Clamp Meters Operate ?:

- A current transformer(CT) used to pick up magnetic flux generated as a result of current passing through a conductor.
- A secondary winding generates a current by electromagnetic induction that is proportional to the primary current.



# End of Lecture

Best Wishes

[haitham.elhussieny@feng.bu.edu.eg](mailto:haitham.elhussieny@feng.bu.edu.eg)