

ECE 344

Microwave Fundamentals

Lecture 05 – Part2: Impedance Matching

Prepared By
Dr. Sherif Hekal

Single-stub tuning

We consider a matching technique that uses a single open-circuited or short-circuited length of transmission line (a “stub”), connected either in parallel or in series with the transmission feed line at a certain distance from the load. Such a tuning circuit is convenient from a microwave fabrication aspect, since lumped elements are not required. The shunt tuning stub is especially easy to fabricate in microstrip or stripline form.


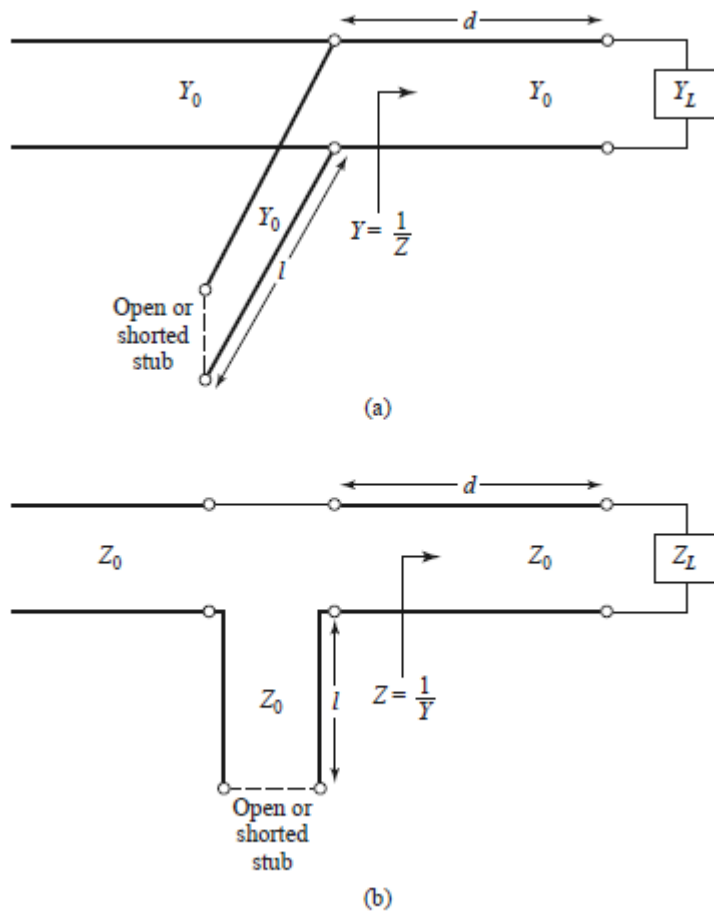


Figure: Single-stub tuning circuits. (a) Shunt stub. (b) Series stub.

In single-stub tuning, the two adjustable parameters are the distance, d , from the load to stub position, and the value of susceptance or reactance provided by the shunt or series stub.

For the shunt-stub case, the basic idea is to select d so that the admittance, Y , seen looking into the line at distance d from the load is of the form $Y_0 + jB$. Then the stub susceptance is chosen as $-jB$, resulting in a matched condition.

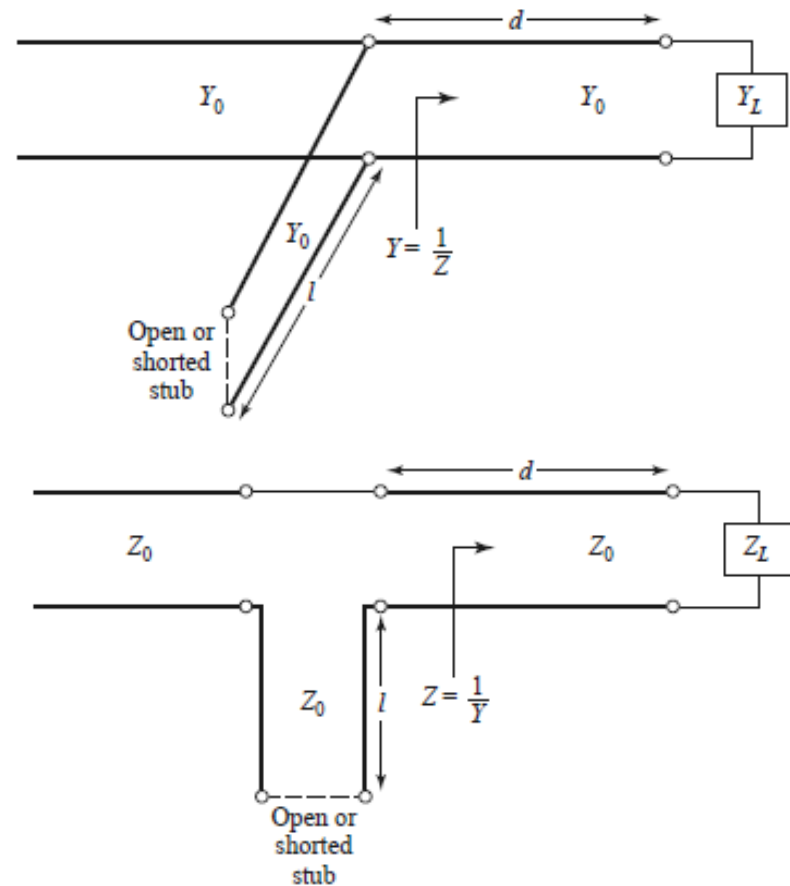
For the series stub case, the distance d is selected so that the impedance, Z , seen looking into the line at a distance d from the load is of the form $Z_0 + jX$. Then the stub reactance is chosen as $-jX$, resulting in a matched condition.




We can determine the two adjustable parameters using Smith chart and analytic solutions. The Smith chart solutions are fast, intuitive, and usually accurate enough in practice. The analytic expressions are more accurate, and useful for computer analysis.

Transmission-Line Matching

Single-Stub Tuning

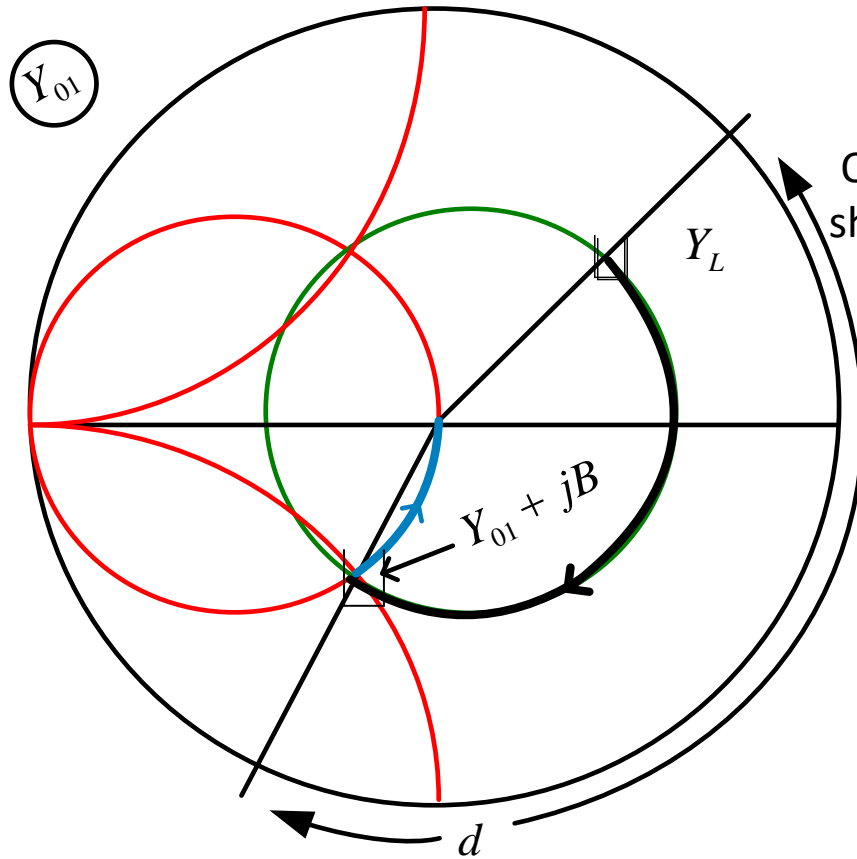


Γ plane

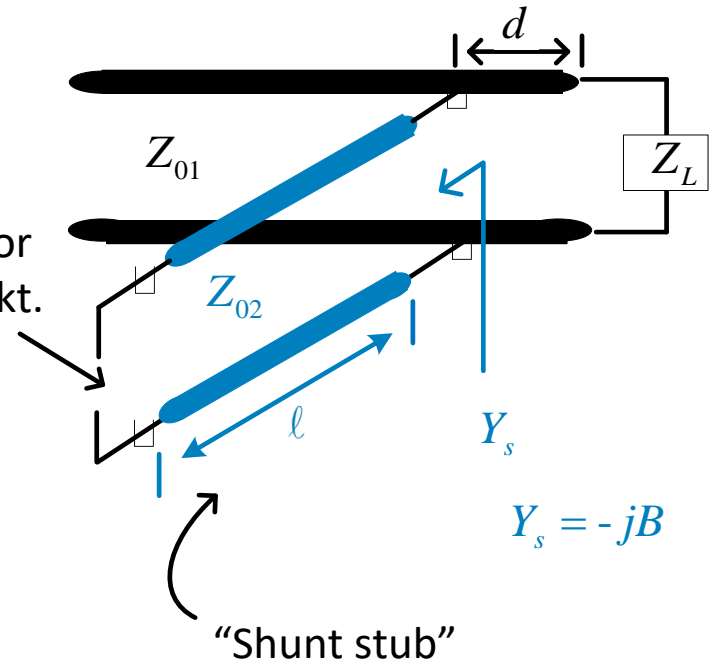

Note: Only one of two possible solutions is shown.


Transmission-Line Matching (cont.)

Short ckt. Load on stub

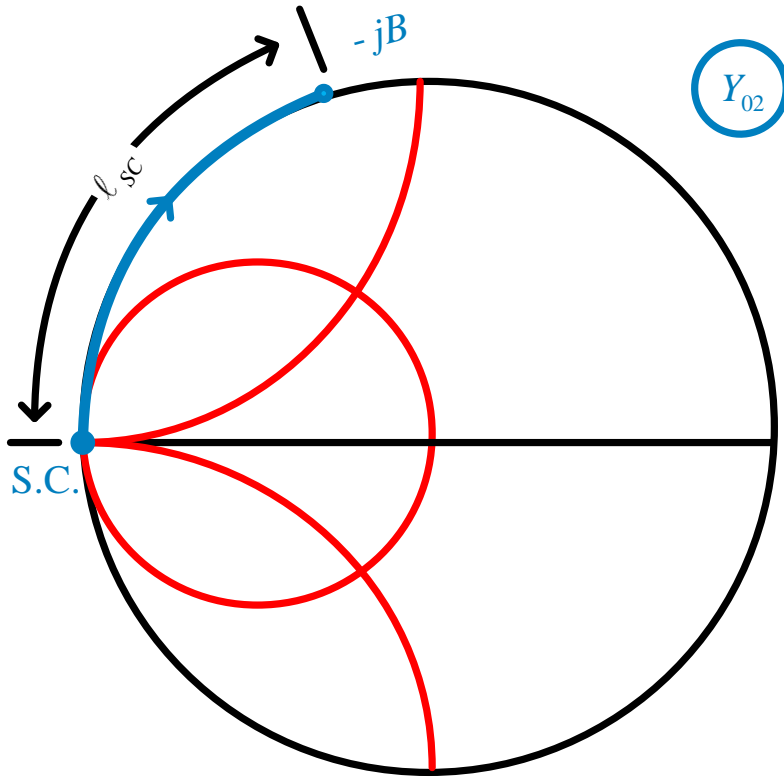

Γ plane


Open ckt. Load on stub

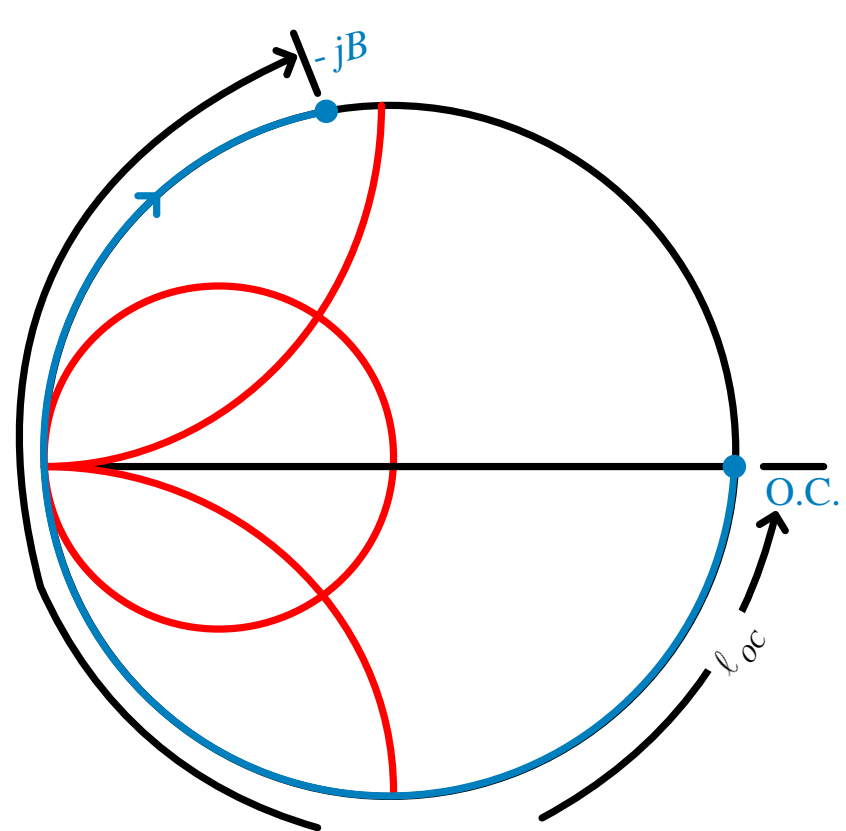


Γ plane

Transmission-Line Matching (cont.)


Series stub

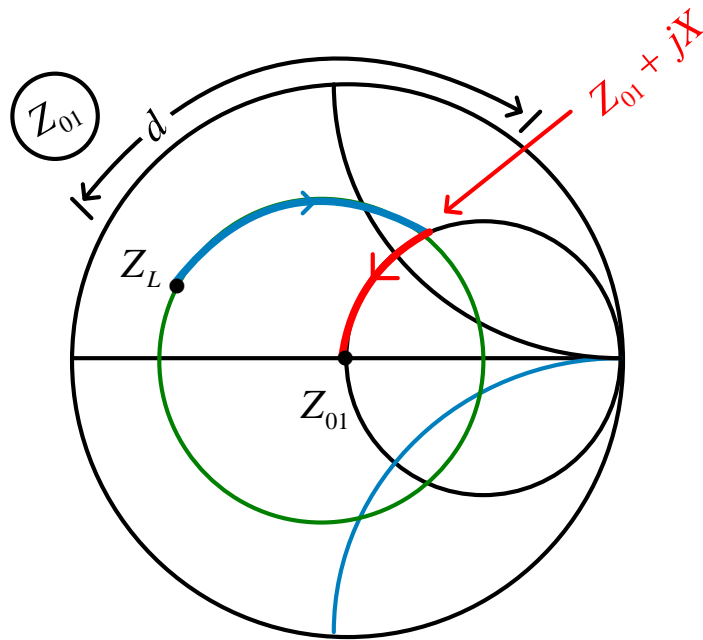

Γ plane

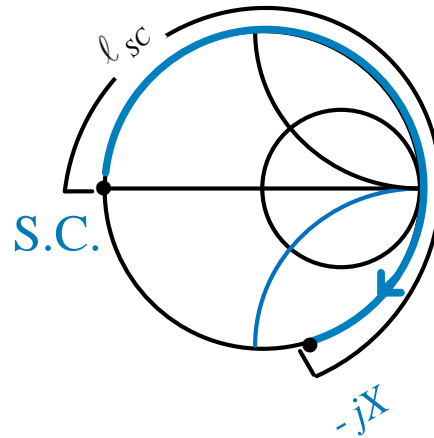

S.C.

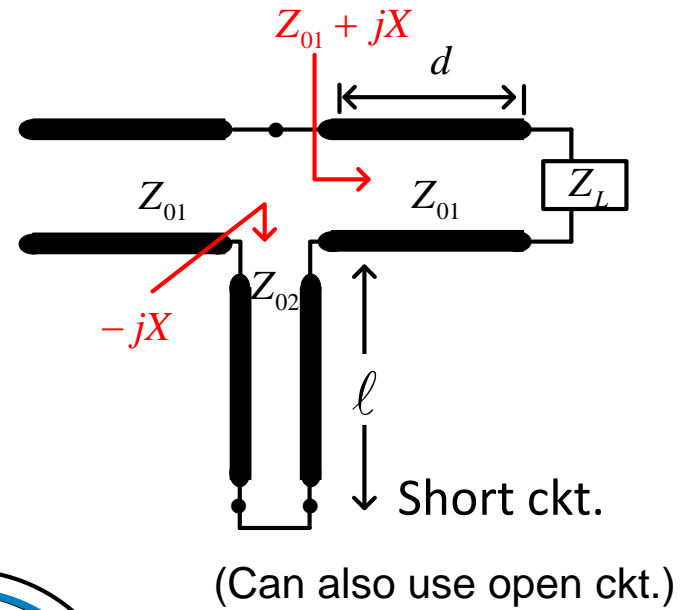

Note: Only one of two possible solutions is shown.

Example:

Single-stub shunt tuning

For a load impedance $Z_L=15+j10 \Omega$, design two single-stub shunt tuning networks to match this load to a 50Ω line. Assuming that load is matched at 2 GHz, and the load consists of a resistor and inductor in series, plot the reflection coefficient magnitude from 1 GHz to 3 GHz for each solution.


Solution:

Here, we use ADS tool to get the two networks.

DesignGuide



Filter

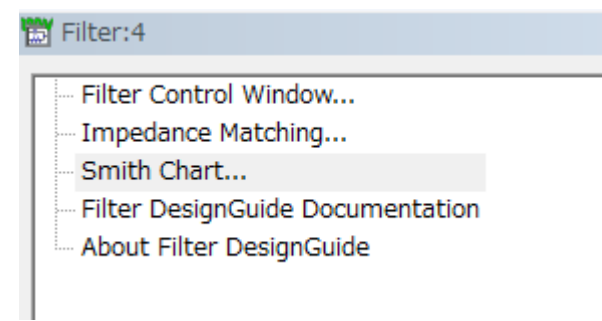

Smith Chart Utility

File Edit View Circ Help

Palette

Freq (GHz) 2 Z0 (Ohms) 50 Normalize

Current Schematic [test_sprj] 4 SmartCom

Define Source/Load Network Terminations...

Network Response

Start Freq: 0 Stop Fr

Network Schematic

ZS* ZL
P1 P2

Lock Source Impedance Lock Load Impedance

Gamma: 0.00000 < 0.00000 Z: 1.00000 +j 0.00000

VSWR: 1.00000 Y: 1.00000 +j 0.00000

Legend: Load (diamond), Source (circle)


Switch for admittance and impedance Smith Charts


Impedance matching technique

Freq (GHz) Z0 (Ohms) Normalize

Current Schematic [smith_chart_prj]: 1 SmartCor DA_Smit

 Define Source/Load Network Terminations...




First input frequency=2 GHz
 Select Z_L and input $Z_L=15+j10$
 Select transmission component 
 Rotate clockwise to make $Y=1-j1.33$
 You can get the rotation angle is 15.809 Deg

$$d_1 = 15.809 / 360 * \lambda = 0.044\lambda$$

Lock Source Impedance Lock Load Impedance

Gamma: 0.55350 < 123.690 Z: 0.36119 +j 0.47962

VSWR: 3.47925 Y: 1.00192 +j -1.33044

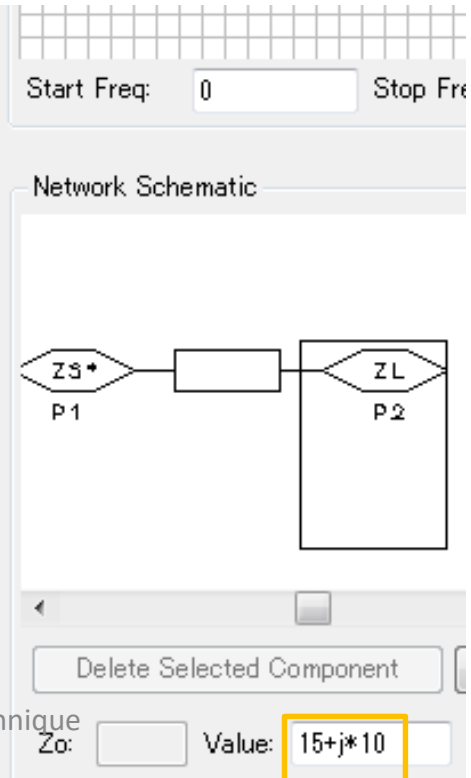

Palette

Freq (GHz) Z0 (Ohms) Normalize


Define Source/Load Network Terminations...


Current Schematic SmartComp

Open stub
 $Z_L = \infty$

Maximum value: 9950

53.072 Deg

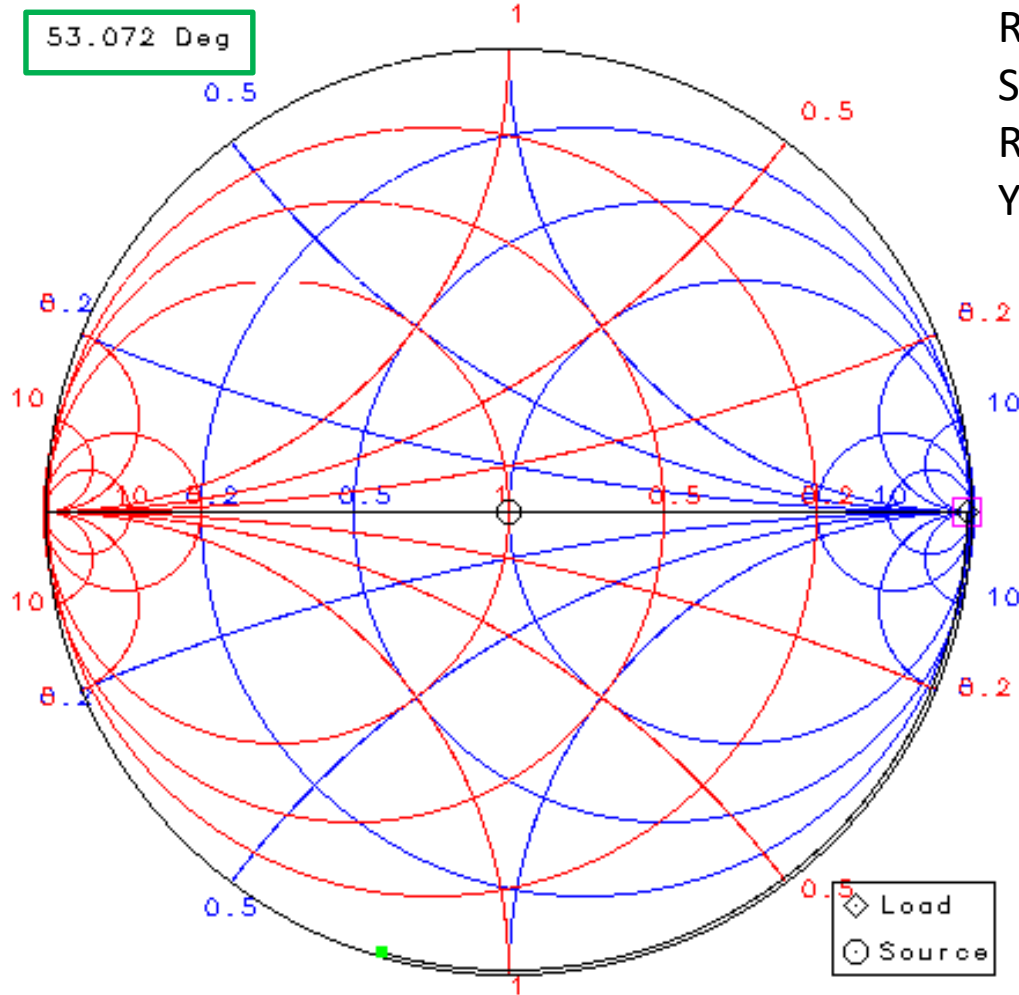


Reset
 Select transmission component 
 Rotate clockwise to make $Y=j1.33$
 You can get the rotation angle is 53.072 Deg

$$l_1 = 53.091 / 360 * \lambda = 0.147 \lambda$$

Start Freq: Stop Freq:

Network Schematic

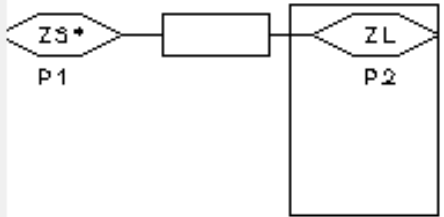

Delete Selected Component

Zo: Value:

Palette




Lock Source Impedance Lock Load Impedance

Gamma: < Z: +j

VSWR: Y: +j

Freq (GHz) Z0 (Ohms) Normalize SmartCo

 Define Source/Load Network Terminations...



Reset


Select Z_L and input $Z_L=15+j10$

Select transmission component 

Rotate clockwise to make $Y=1+j1.33$

You can get the rotation angle is 139.572 Deg
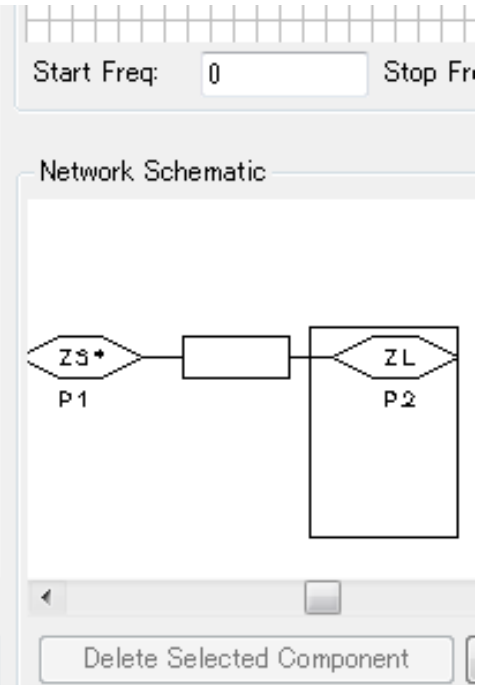
$$d_1 = 139.572 / 360 * \lambda = 0.388\lambda$$



Palette

Lock Source Impedance Lock Load Impedance

Gamma: Z: +j

VSWR: Y: Impedance matching technique

Value:

Freq (GHz) Z0 (Ohms) Normalize


Current Schematic [test_a_prj]: 1


Define Source/Load Network Terminations...

Open stub

$$Z_L = \infty$$


126.949 Deg

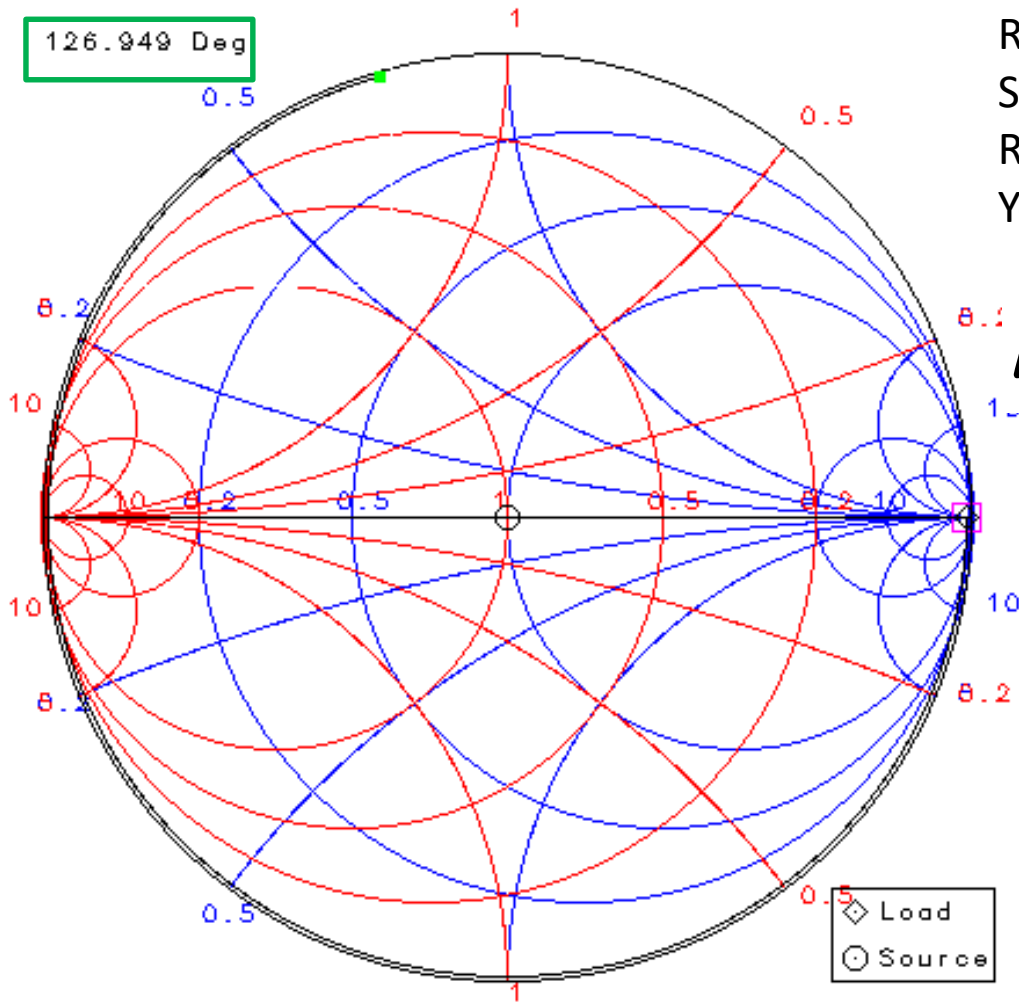

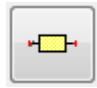Reset
 Select transmission component 
 Rotate clockwise to make $Y = -j1.33$
 You can get the rotation angle is 126.949 Deg

$$l_2 = 126.949 / 360 * \lambda = 0.353\lambda$$

Start Freq: Stop Freq:

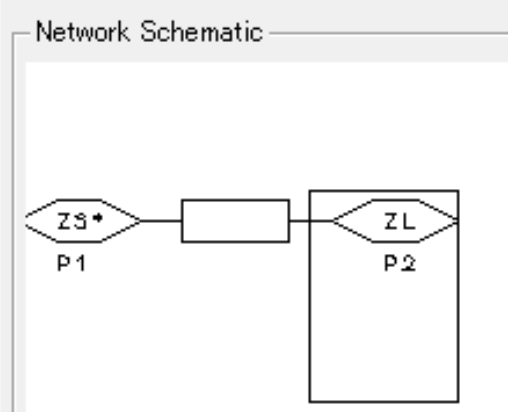

Palette



Lock Source Impedance Lock Load Impedance

Gamma: < Z: +j

VSWR: Y: +j

Impedance matching technique

Value:

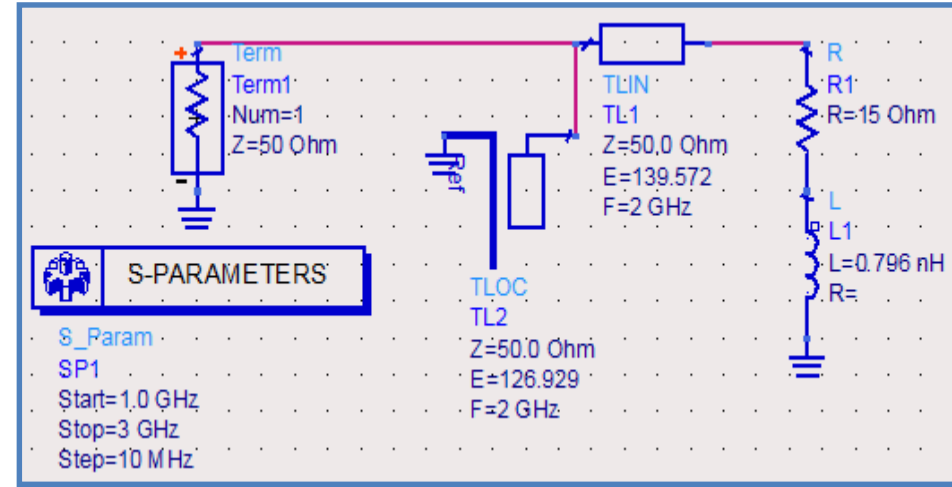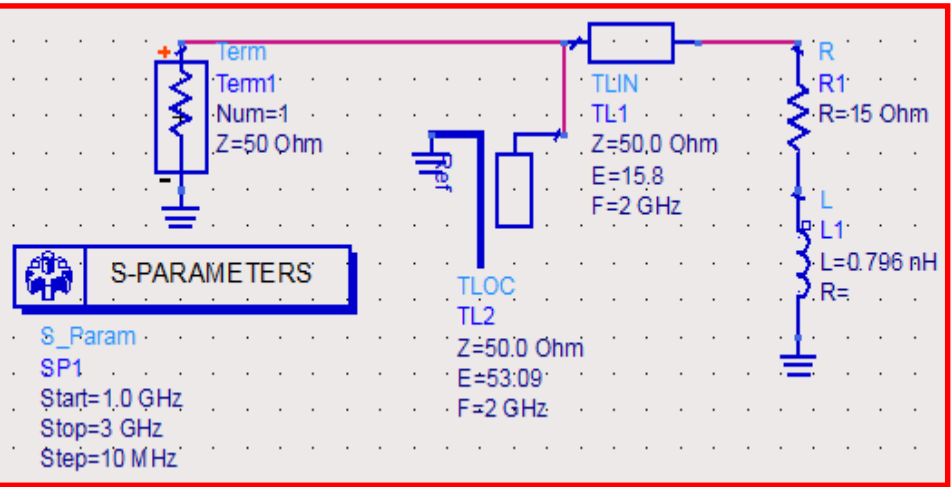

Solution 1

Solution 2


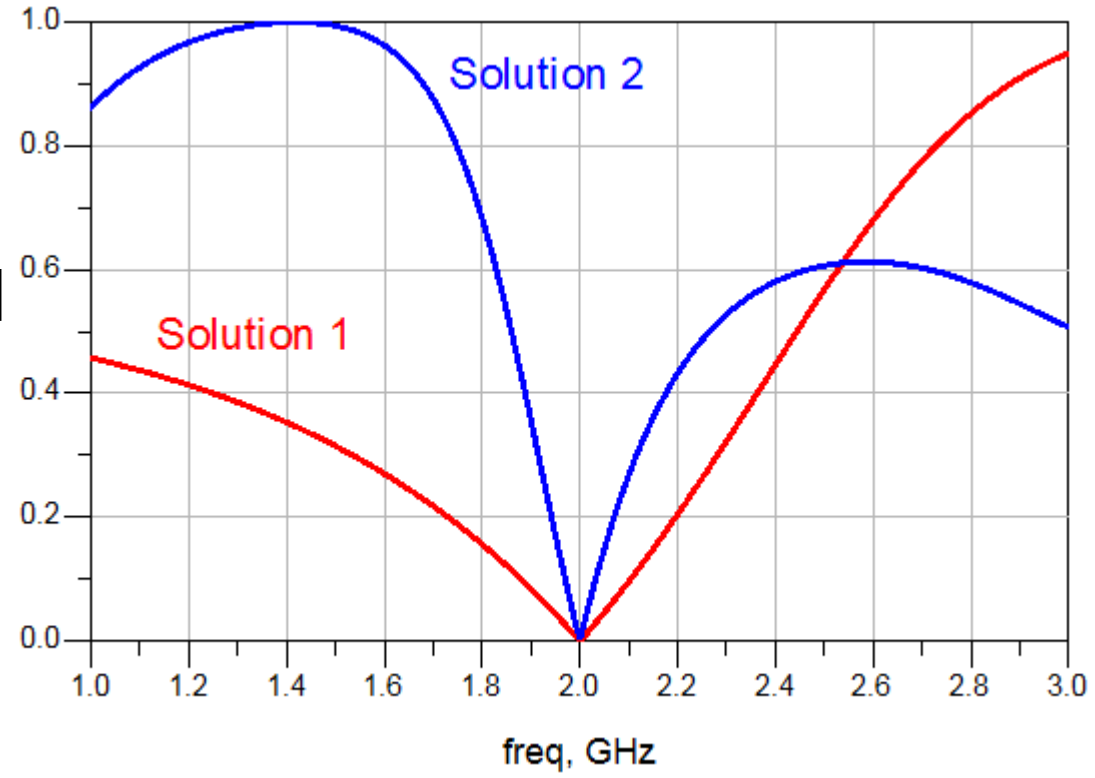
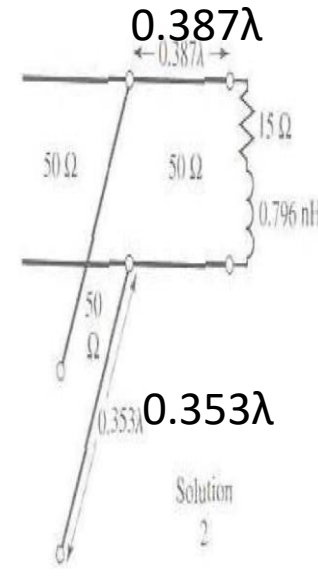
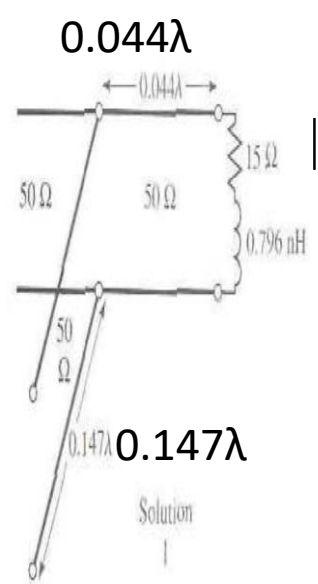


Figure: Reflection coefficient magnitude versus frequency for the tuning circuits.

Analytic Solution

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$
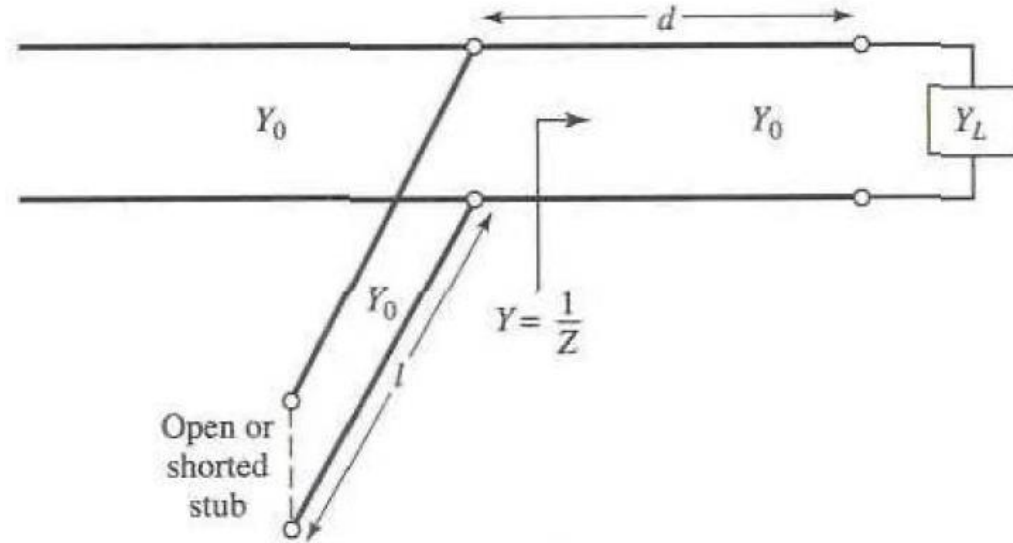
$$G_{in} = Y_0 \frac{Y_L + jY_0 \tan \beta l}{Y_0 + jY_L \tan \beta l}$$



$$\begin{aligned} Y &= G_0 \frac{G_L + jB_L + jG_0 t}{G_0 + j(G_L + jB_L)t} = G_0 \frac{G_L + j(B_L + G_0 t)}{G_0 - B_L t + jG_L t} = G_0 \frac{[G_L + j(B_L + G_0 t)][G_0 - B_L t - jG_L t]}{(G_0 - B_L t)^2 + (G_L t)^2} \\ &= G_0 \frac{G_L(G_0 - B_L t) - jtG_L^2 + j(B_L + G_0 t)(G_0 - B_L t) + (B_L + G_0 t)G_L t}{(G_0 - B_L t)^2 + (G_L t)^2} \\ &= G_0 \frac{G_L G_0 (1 + t^2) + j(B_L G_0 - B_L^2 t + G_0^2 t - B_L G_0 t^2 - tG_L^2)}{(G_0 - B_L t)^2 + (G_L t)^2} \end{aligned}$$

where $t = \tan \beta d$

In order to get a matched condition, we will choose d (which implies t) to make the real part of the admittance Y to be equal to Y_0 , then we have

$$G_L G_0 (1 + t^2) = (G_0 - B_L t)^2 + (G_L t)^2$$

solving for t gives

$$t = \frac{G_0 B_L \pm \sqrt{G_0^2 B_L^2 - (G_L^2 + B_L^2 - G_L G_0)(G_0^2 - G_L G_0)}}{(G_L^2 + B_L^2 - G_L G_0)}$$

$$= \frac{G_0 B_L \pm \sqrt{G_L G_0 [(G_L - G_0)^2 + B_L^2]}}{(G_L^2 + B_L^2 - G_L G_0)}$$

Thus, the two principal solutions for d are

$$t = \tan \beta d$$

$$\frac{d}{\lambda} = \frac{1}{2\pi} \begin{cases} \tan^{-1} t & \text{for } t \geq 0 \\ \pi + \tan^{-1} t & \text{for } t < 0 \end{cases}$$

To find the required stub lengths, first use t in the above equation to find the stub susceptance, $B_s = -B$, where B is defined as follows:

$$B = G_0 \frac{(B_L G_0 - B_L^2 t + G_0^2 t - B_L G_0 t^2 - t G_L^2)}{(G_0 - B_L t)^2 + (G_L t)^2} = G_0 \frac{B_L G_0 (1 - t^2) + t(G_0^2 - G_L^2 - B_L^2)}{(G_0 - B_L t)^2 + (G_L t)^2}$$

The open-circuited stub length is found as

$$\frac{l_o}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{B_s}{Y_0} \right) = \frac{-1}{2\pi} \tan^{-1} \left(\frac{B}{Y_0} \right)$$

$$Z_{ino} = -jZ_0 \cot \beta l$$

$$jB_s = \frac{1}{Z_{ino}} = \frac{1}{-jZ_0 \cot \beta l} = jY_0 \tan \beta l$$

While the short-circuited stub length is found as

$$\frac{l_s}{\lambda} = \frac{-1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B_s} \right) = \frac{1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B} \right)$$

$$Z_{ins} = jZ_0 \tan \beta l$$

$$jB_s = \frac{1}{Z_{ins}} = \frac{1}{jZ_0 \tan \beta l}$$

$$= -jY_0 \frac{1}{\tan \beta l} \Rightarrow \tan \beta l = -\frac{Y_0}{B_s}$$

If the length given by above formulas is negative, $\lambda/2$ can be added to give a positive result.

Using the above equations, we can calculate the above example.


$$t_1 = 0.28472 \quad \Rightarrow \quad \frac{d_1}{\lambda} = 0.044 \quad \Rightarrow \quad B_1 = -1.33G_0 \quad \Rightarrow \quad \frac{l_1}{\lambda} = 0.147$$

$$t_2 = -0.85694 \quad \Rightarrow \quad \frac{d_2}{\lambda} = 0.387 \quad \Rightarrow \quad B_2 = 1.33G_0 \quad \Rightarrow \quad \frac{l_2}{\lambda} = 0.353$$

We can see that the same results are obtained.


Homework-1

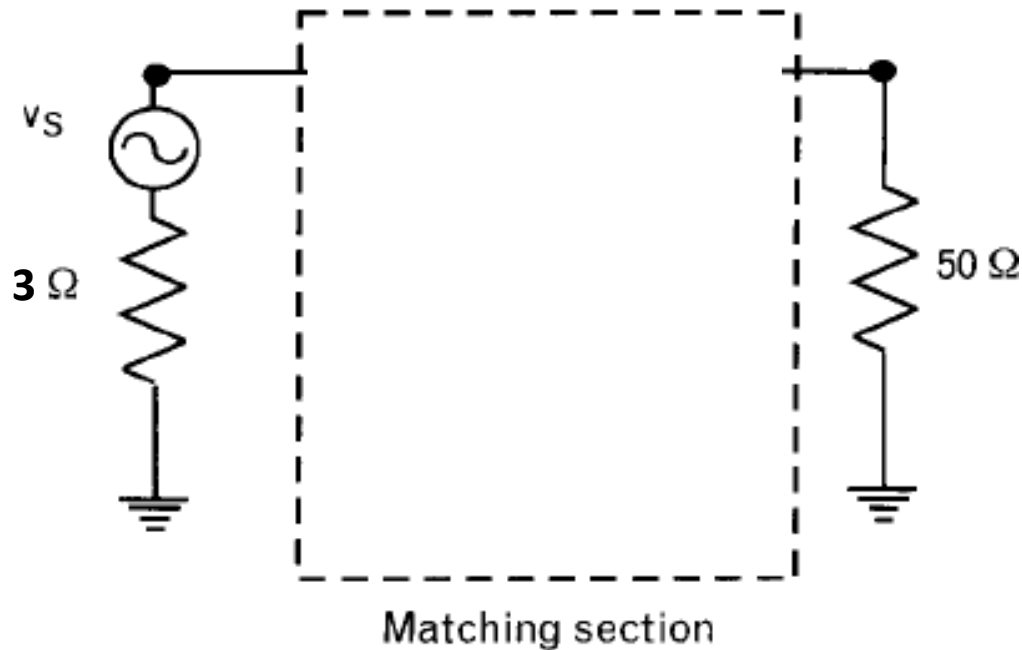Design three different matching networks (single L-C matching circuits, single series stub, and single shunt stub) from 3- Ω to 50- Ω , where the center frequency is 2.4 GHz. Plot the frequency responses using ADS tool and compare their bandwidths.



Impedance matching technique

Quarter-Wave Transformer

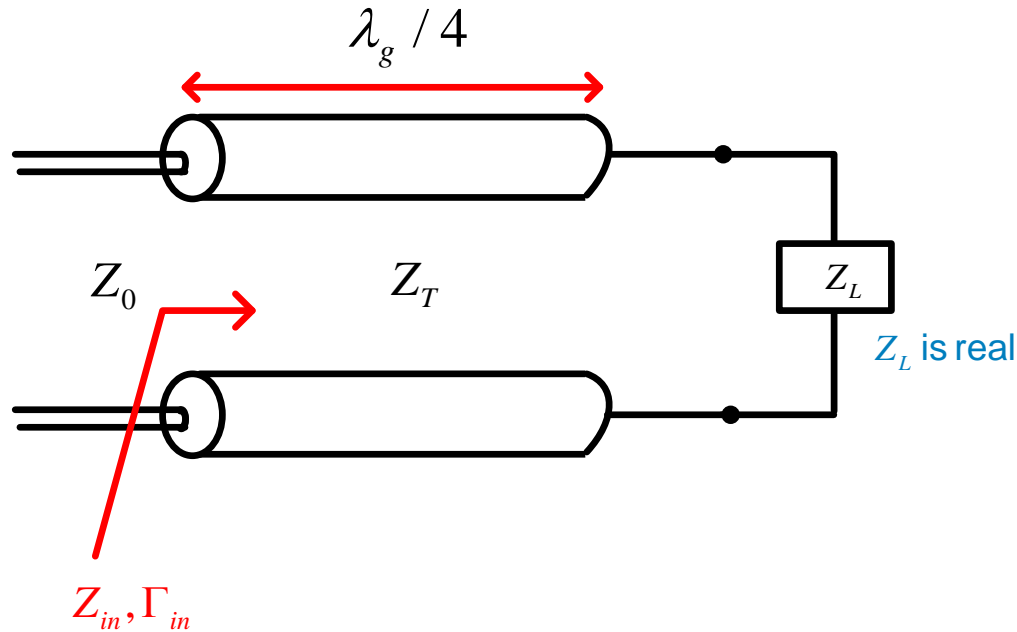

$$@ f = f_0$$

$$\beta l = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{4} = \frac{\pi}{2}$$

$$\Gamma_{in} = 0 \quad \text{when} \quad Z_T = \sqrt{Z_0 Z_L}$$


$$Z_{in} = \frac{Z_T^2}{Z_L}$$

Only true at f_0 where $l = \lambda_g / 4$

Note: If Z_L is not real, we can always add a reactive load in series or parallel to make it real (or add a length of transmission line between the load and the transformer to get a real impedance).

Quarter-Wave Transformer

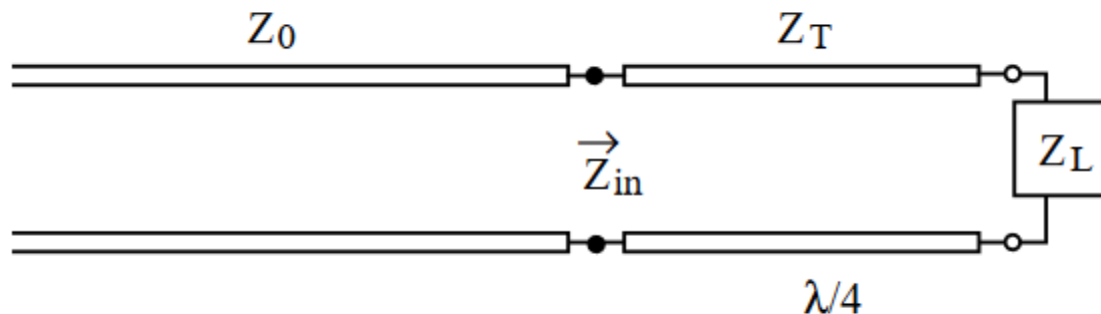A quarter wave transformer, like low-frequency transformers, changes the impedance of the load to another value so that matching is possible.



A quarter-wave transformer uses a section of line of characteristic impedance Z_T of $\frac{\lambda}{4}$ long. To have a matching condition, we want $Z_{in} = Z_0$.


$$Z_{in} = Z_T \frac{Z_L + jZ_T \tan \frac{\pi}{2}}{Z_T + jZ_L \tan \frac{\pi}{2}} = \frac{Z_T^2}{Z_L}, \quad (1)$$

since $\tan \beta l = \tan \frac{2\pi}{\lambda} \frac{\lambda}{4} = \tan \frac{\pi}{2} = \infty$. In order for $Z_{in} = Z_0$, we need that

$$Z_T^2 = Z_0 Z_L \Rightarrow Z_T = \sqrt{Z_0 Z_L}. \quad (2)$$

Quarter-Wave Transformer

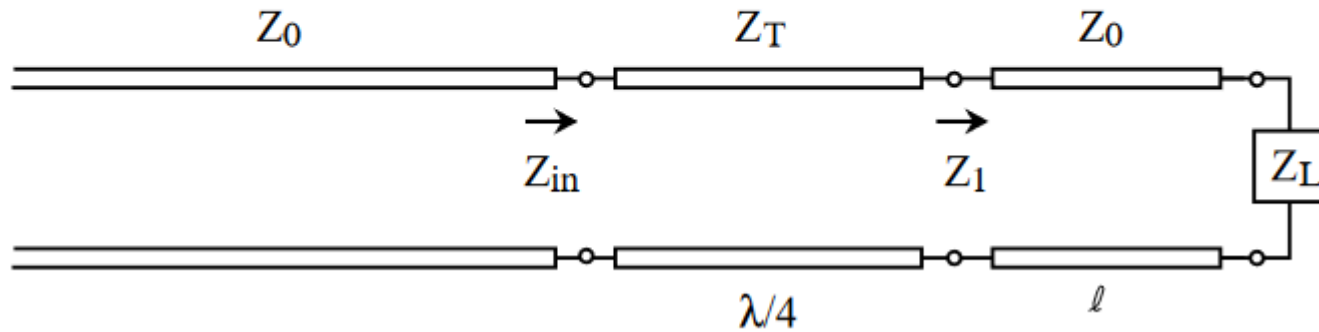If Z_0 and Z_L are both real, then Z_T is real, and we can use a lossless line to perform the matching. If Z_L is complex, it can be made real by adding a section of line to it.



Quarter-Wave Transformer

Example

Given that $Z_L = (30 + j40)\Omega$, $Z_0 = 50\Omega$, find the shortest l and Z_T so that the above circuit is matched. Assume that Z_T is real and lossless.

We want Z_1 to be real and Z_{in} to be $Z_0 = 50\Omega$ in order for Z_T to be real and the matching condition satisfied. We find that $Z_{nL} = 0.6 + j0.8$. In order to make Z_{n1} real, the shortest l from the Smith Chart is $\frac{\lambda}{8}$. Then $Z_{n1} = 3.0$, and $Z_1 = 150\Omega$. Since $Z_{in} = 50\Omega$, we need

$$Z_T = \sqrt{Z_{in}Z_1} = \sqrt{50 \times 150} = 86.6\Omega$$

in order for matching condition to be satisfied.

Quarter-Wave Transformer

