

# ECE 344

## Microwave Fundamentals

### Lecture 07:

### Microwave Network Analysis

### Multiport Networks

Prepared By  
Dr. Sherif Hekal


# Multiport Networks

A general circuit can be represented by a multi-port network, where the “ports” are defined as access terminals at which we can define voltages and currents.


## Examples:

Note: Equal and opposite currents are assumed on the two wires of a port.

### 1) One-port network

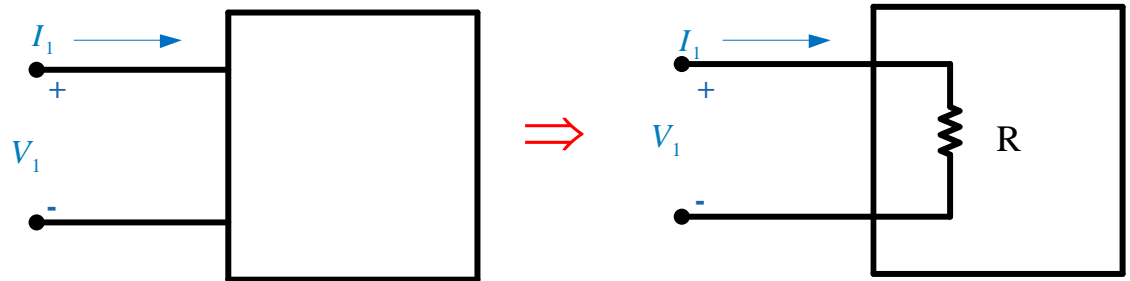

### 2) Two-port network

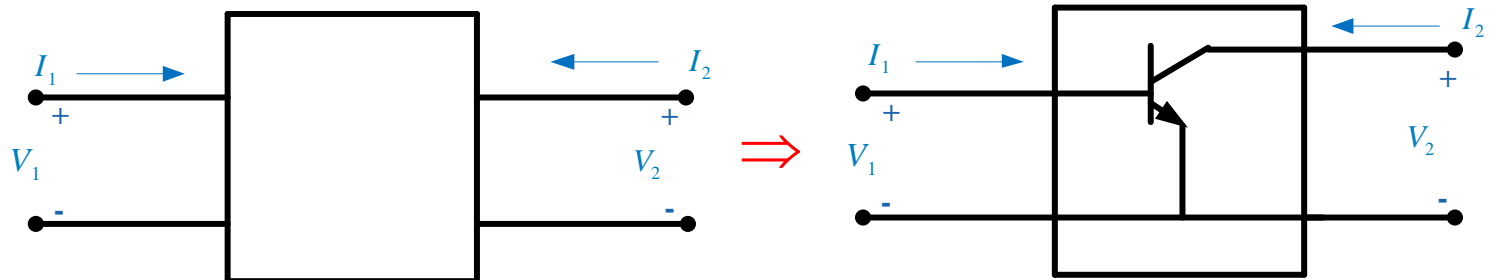

# Multiport Networks (cont.)

## 3) $N$ -port network


To represent multi-port networks we use:

- $Z$  (impedance) parameters
- $Y$  (admittance) parameters
- $ABCD$  parameters

Not easily measurable at high frequency


- $S$  (scattering) parameters

Measurable at high frequency

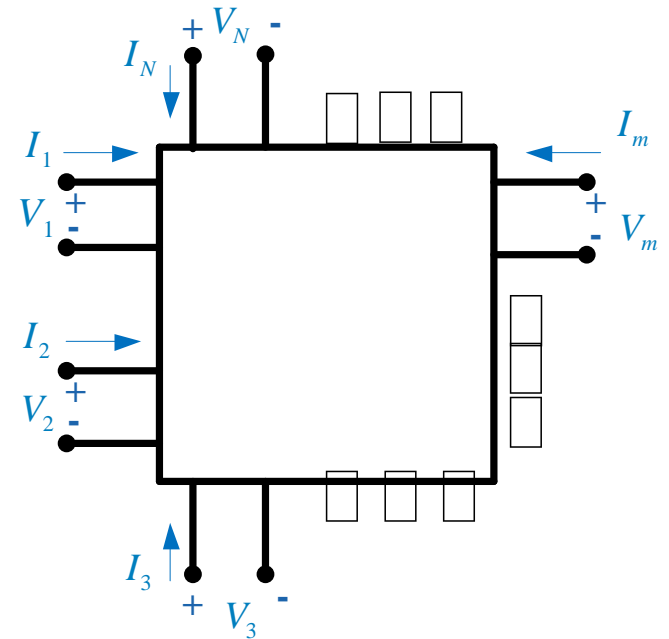
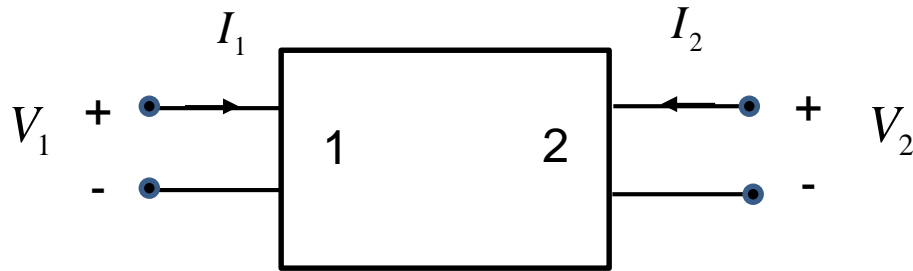
# Two-Port Networks

Consider a general **2-port** linear network:



In terms of Z-parameters, we have (from superposition):

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Impedance ( $Z$ ) matrix

Therefore

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow [V] = [Z][I]$$

# Elements of Z-Matrix: Z-Parameters

(open-circuit parameters)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Port 2 open circuited

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

Port 1 open circuited

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

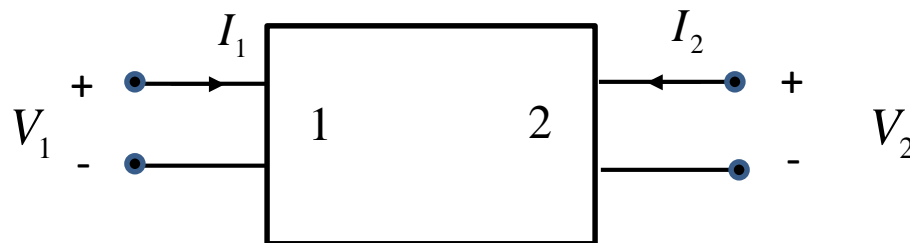

# Z-Parameters (cont.)


*N*-port network

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

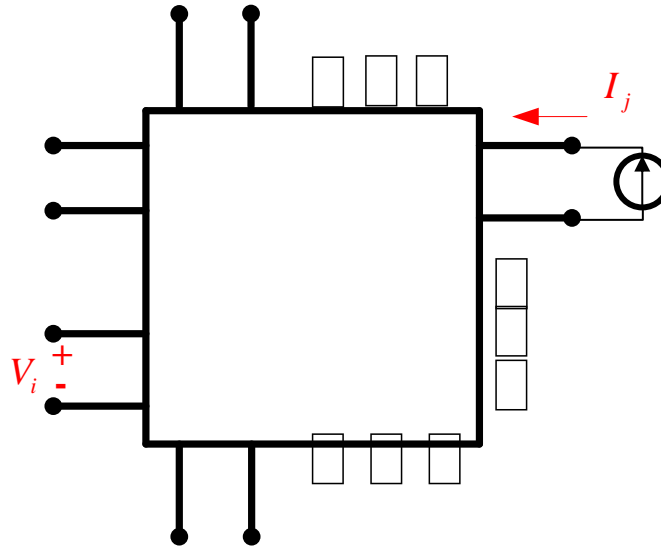

We inject a current into port  $j$  and measure the voltage (with an ideal voltmeter) at port  $i$ . All ports are open-circuited except  $j$ .

# Z-Parameters (cont.)

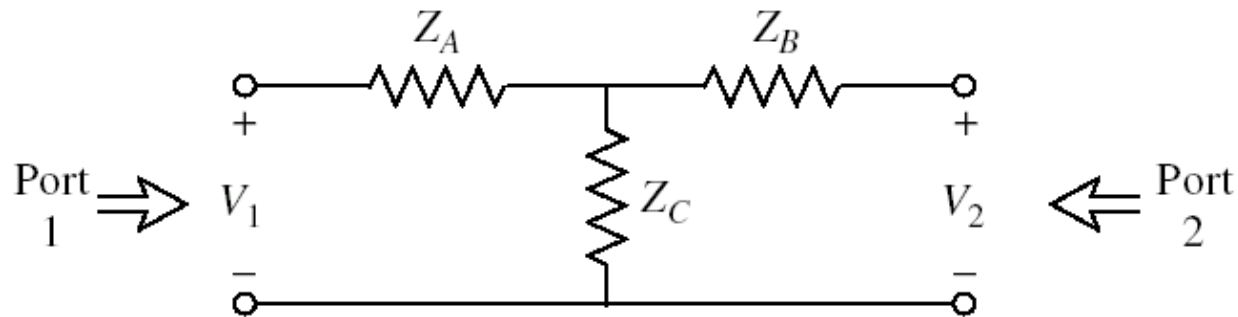

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = ? \quad Z_A + Z_C$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = ? \quad Z_B + Z_C$$


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = ? \quad Z_C$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = ? = Z_{12}$$
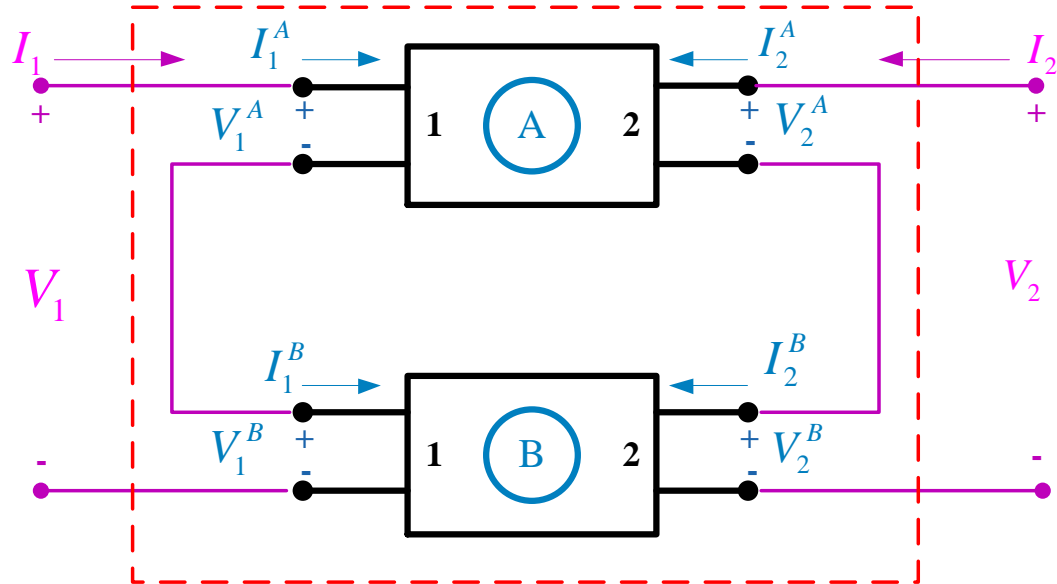
# Z-Parameters (cont.)

Z-parameters are convenient for series connected networks.

$$\begin{aligned}
 \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} V_1^A \\ V_2^A \end{bmatrix} + \begin{bmatrix} V_1^B \\ V_2^B \end{bmatrix} \\
 &= \begin{bmatrix} Z^A \\ Z^B \end{bmatrix} \begin{bmatrix} I^A \\ I^B \end{bmatrix} \\
 &= (\begin{bmatrix} Z^A \\ Z^B \end{bmatrix}) \begin{bmatrix} I \\ I \end{bmatrix} \\
 &= (\begin{bmatrix} Z^A \\ Z^B \end{bmatrix}) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \\
 &= \begin{bmatrix} Z^A + Z^B \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}
 \end{aligned}$$



Series:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11}^A + Z_{11}^B & Z_{12}^A + Z_{12}^B \\ Z_{21}^A + Z_{21}^B & Z_{22}^A + Z_{22}^B \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$I_1 = I_1^A = I_1^B$$

$$I_2 = I_2^A = I_2^B$$



# Admittance ( $Y$ ) Parameters

Consider a linear 2-port network:

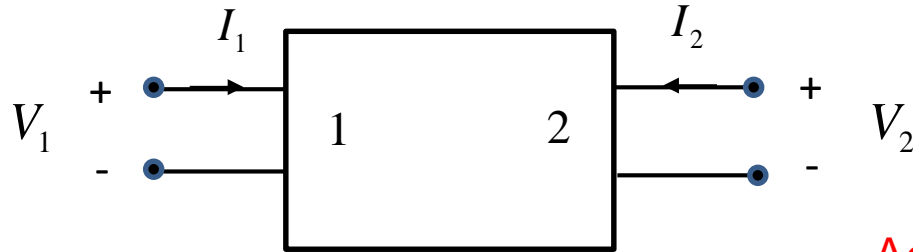

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Admittance matrix

or


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow [I] = [Y][V]$$

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \quad k \neq j}$$

Short-circuit parameters

# Y-Parameters (cont.)


$$Y_{ij} = \frac{I_i}{V_j} \bigg|_{V_k=0 \quad k \neq j}$$

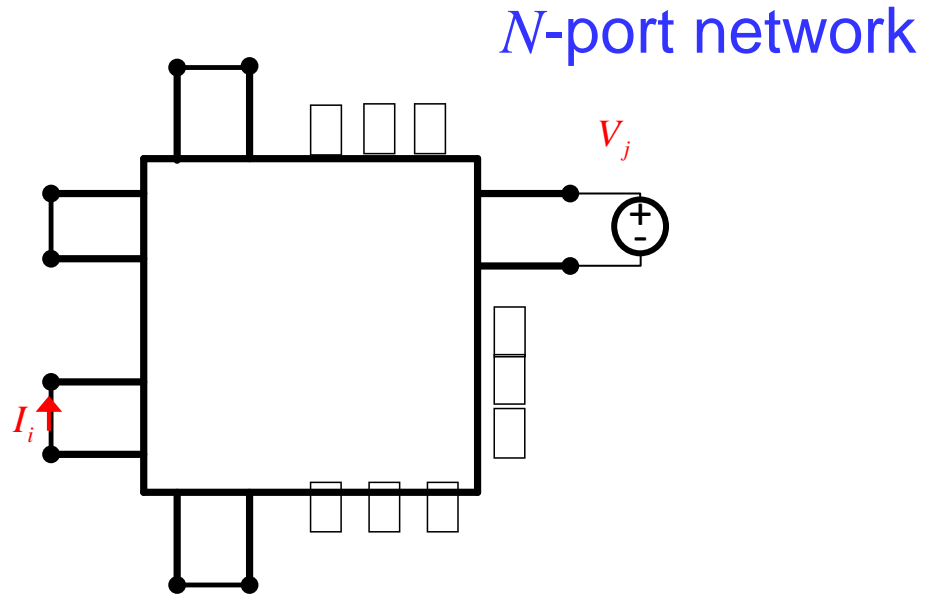

We apply a voltage across port  $j$  and measure the current (with an ideal current meter) at port  $i$ . All ports are short-circuited except  $j$ .
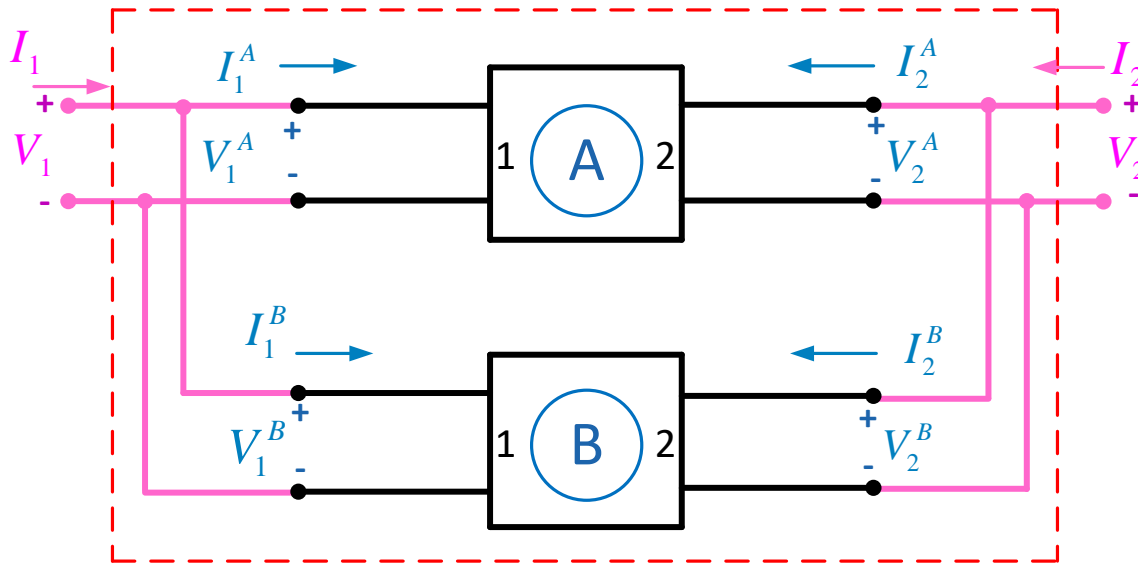
# Y-Parameters (cont.)

Y-parameters are convenient for parallel connected networks.



Parallel:

$$V_1 = V_1^A = V_1^B$$

$$V_2 = V_2^A = V_2^B$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1^A \\ I_2^A \end{bmatrix} + \begin{bmatrix} I_1^B \\ I_2^B \end{bmatrix} = \begin{bmatrix} Y_{11}^A & Y_{12}^A \\ Y_{21}^A & Y_{22}^A \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} Y_{11}^B & Y_{12}^B \\ Y_{21}^B & Y_{22}^B \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11}^A + Y_{11}^B & Y_{12}^A + Y_{12}^B \\ Y_{21}^A + Y_{21}^B & Y_{22}^A + Y_{22}^B \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

# Relation Between $Z$ and $Y$ Parameters

Relation between  $[Z]$  and  $[Y]$  matrices:

$$[V] = [Z][I]$$

$$[I] = [Y][V]$$

Hence:

$$\begin{aligned}[V] &= [Z]([Y][V]) \\ &= ([Z][Y])[V]\end{aligned}$$

It follows that

$$[Z][Y] = [U] = \text{Identity Matrix}$$

Therefore  $[Y] = [Z]^{-1}$

# Reciprocal Networks

If a network does not contain non-reciprocal devices or materials\* (i.e. ferrites, or active devices), then the network is “reciprocal.”

$$\Rightarrow Z_{ij} = Z_{ji} \quad (Y_{ij} = Y_{ji})$$

Note: The inverse of a symmetric matrix is symmetric.

$[Z]$  and  $[Y]$  are symmetric matrices


\* A reciprocal material is one that has symmetric permittivity and permeability tensors. A reciprocal device is one that is made from reciprocal materials.

**Example of a nonreciprocal material: a biased ferrite**

(This is very useful for making isolators and circulators.)
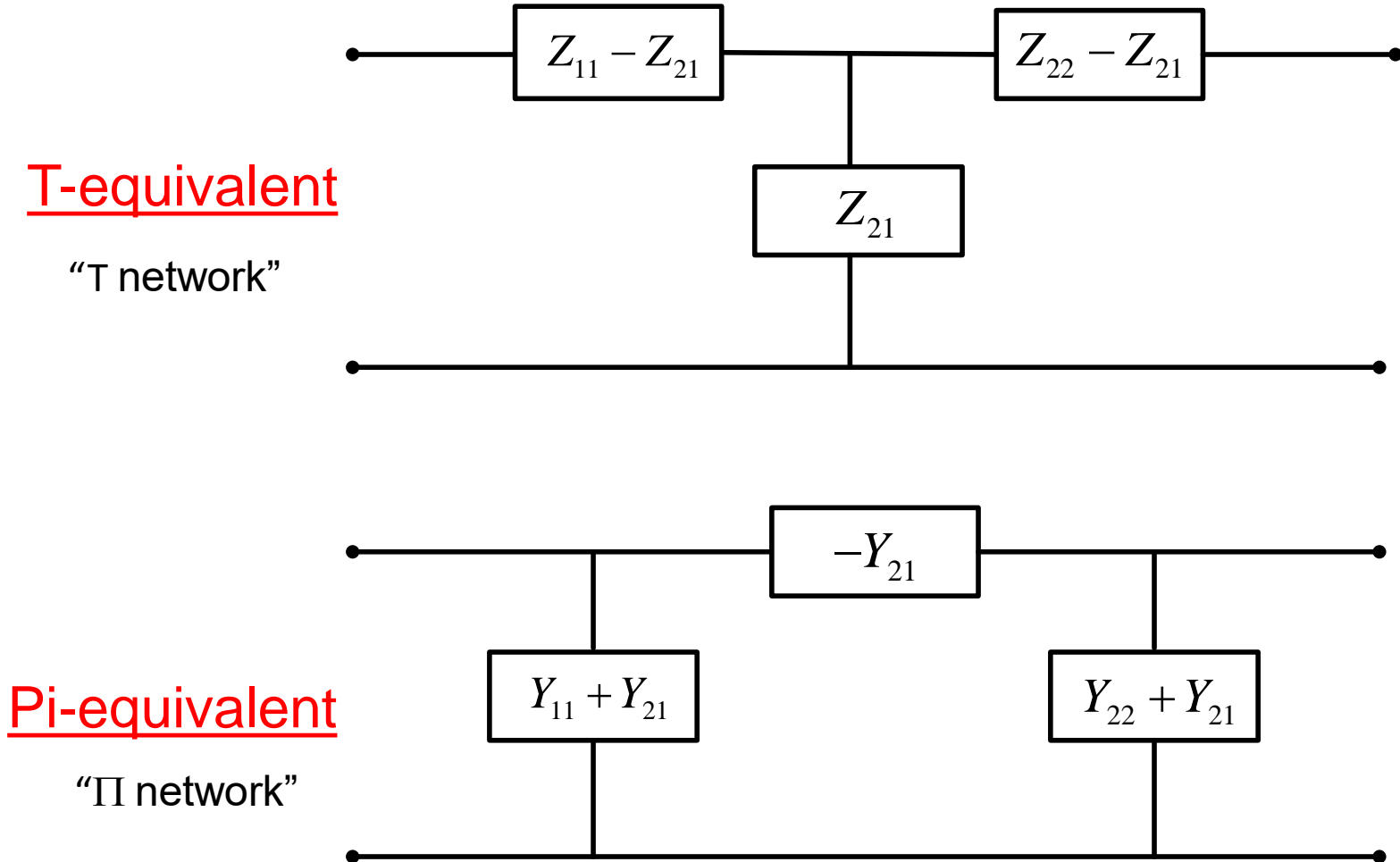
# Reciprocal Networks (cont.)

We can show that the equivalent circuits for reciprocal 2-port networks are:



# ABCD-Parameters

They are defined only for 2-port networks.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I'_2 \end{bmatrix}$$



$$I'_2 = -I_2$$


$$A = \left. \frac{V_1}{V_2} \right|_{I'_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I'_2=0}$$

$$B = \left. \frac{V_1}{I'_2} \right|_{V_2=0}$$

$$D = \left. \frac{I_1}{I'_2} \right|_{V_2=0}$$

# Cascaded Networks

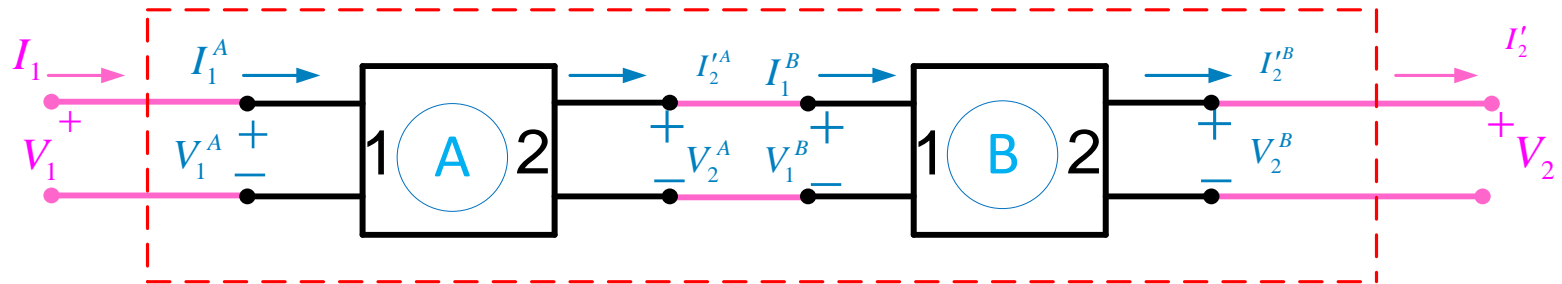

$$\begin{aligned} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} V_1^A \\ I_1^A \end{bmatrix} = [ABCD^A] \begin{bmatrix} V_2^A \\ I_2'^A \end{bmatrix} \\ &= [ABCD^A] \begin{bmatrix} V_1^B \\ I_1^B \end{bmatrix} \\ &= [ABCD^A] [ABCD^B] \begin{bmatrix} V_2^B \\ I_2'^B \end{bmatrix} \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [ABCD^{AB}] \begin{bmatrix} V_2 \\ I_2' \end{bmatrix}$$

A nice property of the ABCD matrix is that it is easy to use with cascaded networks: you simply multiply the ABCD matrices together.



# Scattering Parameters

Problems to use Z- or Y-matrix in microwave circuits

- ❑ difficult in defining voltage and current for non-TEM lines
- ❑ no equipment available to measure voltage and current in complex value  
(eg. sampling scope in microwave range, impedance meter <3GHz)
- ❑ difficult to make open and short circuits over broadband
- ❑ active devices not stable as terminated with open or short circuit


# Scattering Parameters

- At high frequencies,  $Z$ ,  $Y$ , &  $ABCD$  parameters are difficult (if not impossible) to measure.
  - $V$  and  $I$  are not always uniquely defined (e.g., microstrip, waveguides).
  - Even if defined,  $V$  and  $I$  are extremely difficult to measure (particularly  $I$ ).
  - Required open and short-circuit conditions are often difficult to achieve.
- Scattering ( $S$ ) parameters are often the best representation for multi-port networks at high frequency.

Note: We can always convert from  $S$  parameters to  $Z$ ,  $Y$ , or  $ABCD$  parameters.
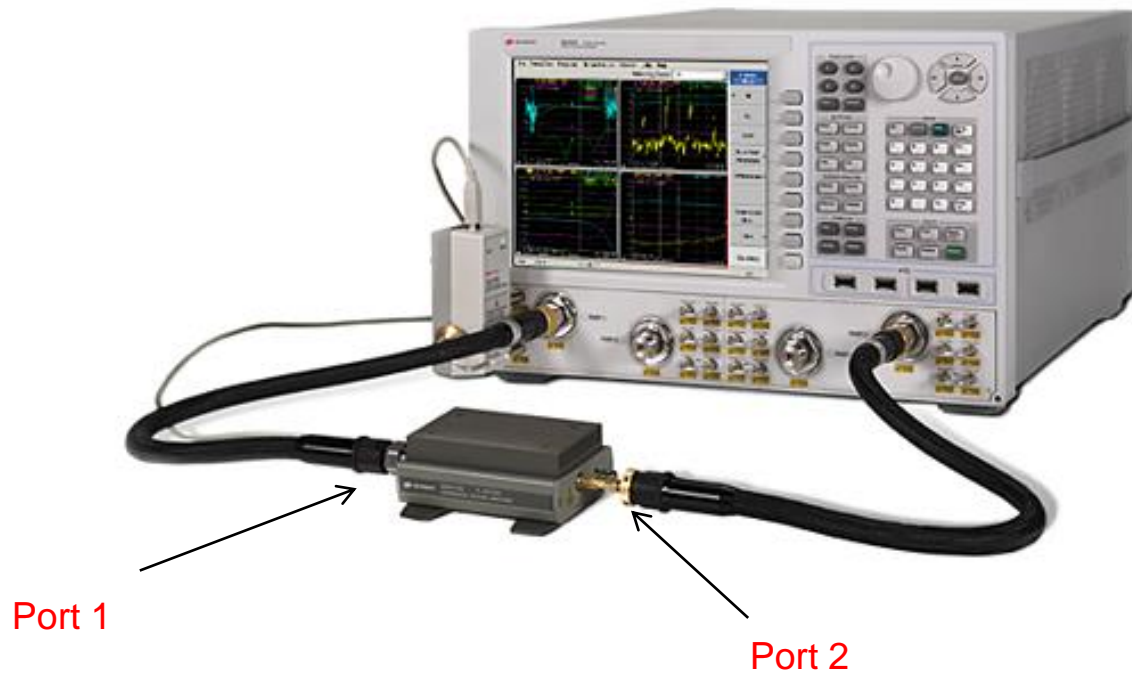
# Scattering Parameters (cont.)


A Vector Network Analyzer (VNA) is usually used to measure  $S$  parameters.



Keysight (formerly Agilent) VNA shown performing a measurement.
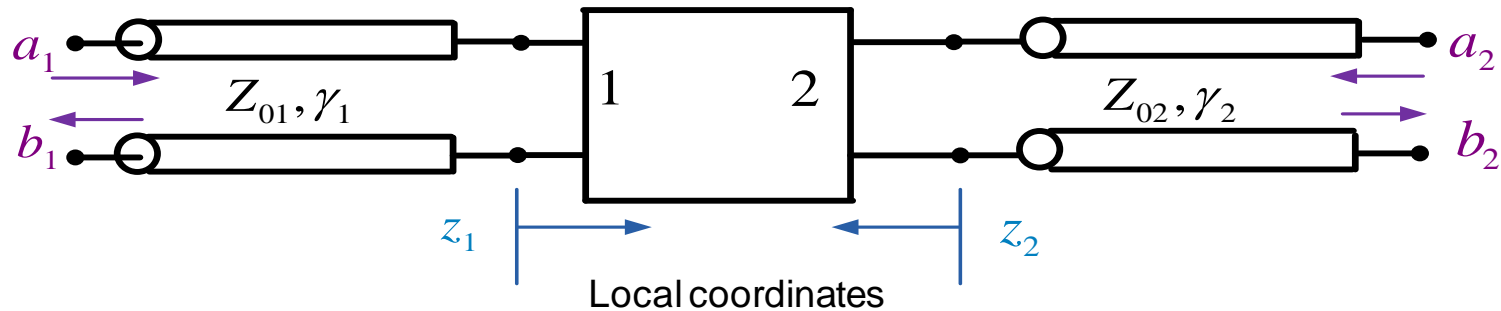
# Scattering Parameters (cont.)

S-parameters are defined  
assuming transmission lines are connected to each port.



On each transmission line:

$$V_i(z_i) = V_{i0}^+ e^{-\gamma_i z_i} + V_{i0}^- e^{+\gamma_i z_i} = V_i^+(z_i) + V_i^-(z_i)$$

$$I_i(z_i) = \frac{V_i^+(z_i)}{Z_{0i}} - \frac{V_i^-(z_i)}{Z_{0i}} \quad i = 1, 2$$


We define:

$$\text{Incoming wave function} \equiv a_i(z_i) \equiv V_i^+(z_i) / \sqrt{Z_{0i}}$$

$$\text{Outgoing wave function} \equiv b_i(z_i) \equiv V_i^-(z_i) / \sqrt{Z_{0i}}$$
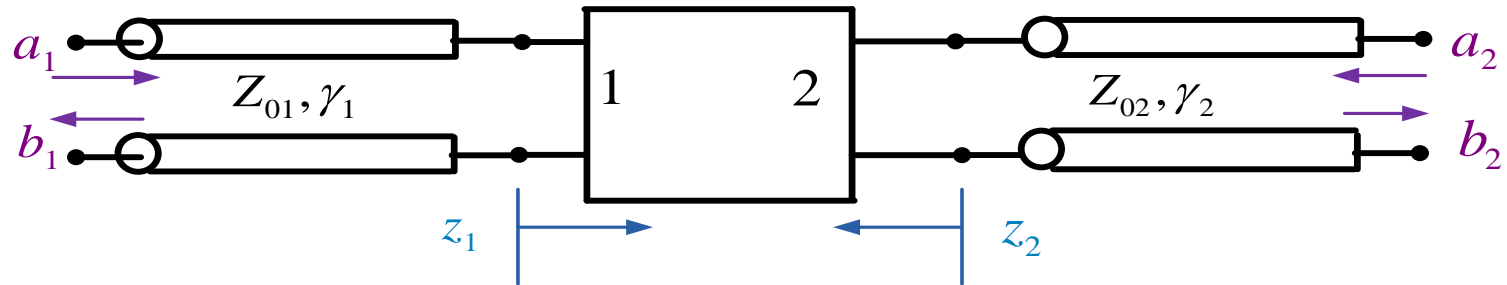
# Scattering Parameters (cont.)

Why are the wave functions ( $a$  and  $b$ ) defined as they are?



$$P_i^+(0) = \frac{1}{2} \operatorname{Re} \left[ V_i^+(0) I_i^{+*}(0) \right] = \frac{1}{2} \frac{|V_i^+(0)|^2}{Z_{0i}} \quad (\text{assuming lossless lines})$$

Recall:  $a_i(0) \equiv V_i^+(0) / \sqrt{Z_{0i}}$


$$\Rightarrow P_i^+(0) = \frac{1}{2} |a_i(0)|^2$$

Similarly,

$$P_i^-(0) = \frac{1}{2} \frac{|V_i^-(0)|^2}{Z_{0i}} = \frac{1}{2} |b_i(0)|^2$$
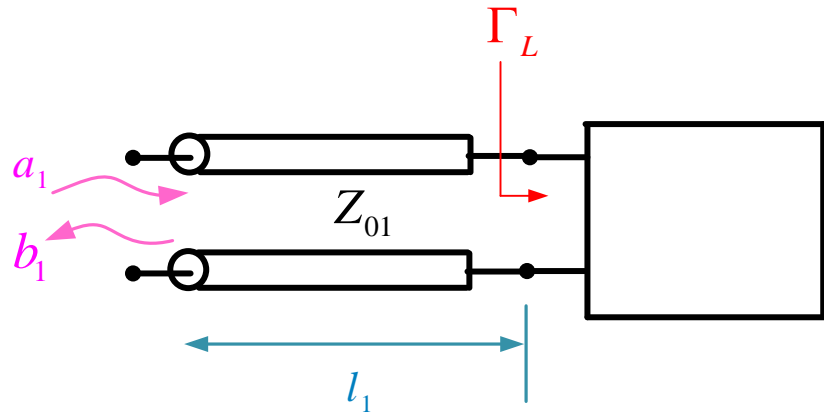
# For a One-Port Network

$$\begin{aligned}\Gamma_L &= \frac{V_1^-(0)}{V_1^+(0)} \\ &= \frac{V_1^-(0)/\sqrt{Z_{01}}}{V_1^+(0)/\sqrt{Z_{01}}} \\ &= \frac{b_1(0)}{a_1(0)}\end{aligned}$$



$$\Gamma_L = S_{11}$$


For a one-port network,  $S_{11}$  is the same as  $\Gamma_L$ .

$$S_{11} \equiv \frac{b_1(0)}{a_1(0)}$$

Incoming wave function  $\equiv a_i(z_i) \equiv V_i^+(z_i)/\sqrt{Z_{0i}}$

Outgoing wave function  $\equiv b_i(z_i) \equiv V_i^-(z_i)/\sqrt{Z_{0i}}$

# For a Two-Port Network

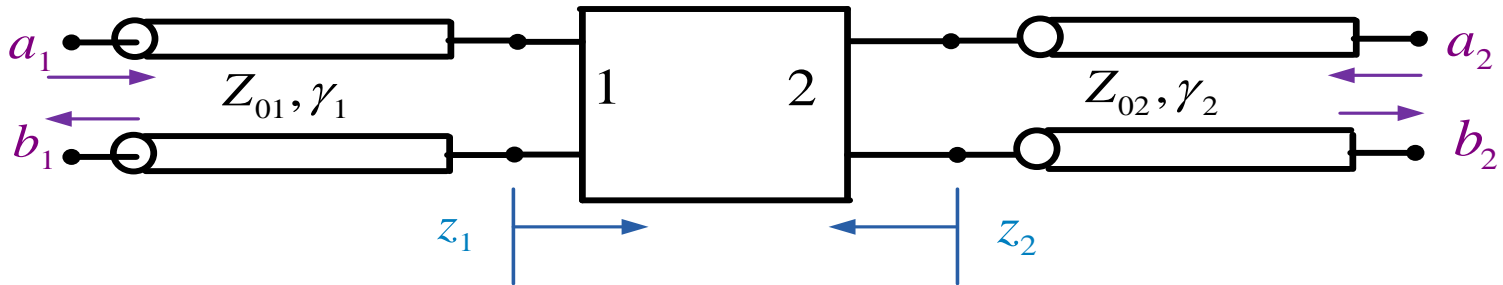

From linearity:

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$

Scattering matrix

$$\Rightarrow \begin{bmatrix} b_1(0) \\ b_2(0) \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1(0) \\ a_2(0) \end{bmatrix} \Rightarrow [b] = [S][a]$$

# Scattering Parameters

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$

$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right _{a_2=0}$	← Output is matched	← input reflection coef. w/ output matched
$S_{12} = \left. \frac{b_1(0)}{a_2(0)} \right _{a_1=0}$	← Input is matched	← reverse transmission coef. w/ input matched
$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right _{a_2=0}$	← Output is matched	← forward transmission coef. w/ output matched
$S_{22} = \left. \frac{b_2(0)}{a_2(0)} \right _{a_1=0}$	← Input is matched	← output reflection coef. w/ input matched




# Scattering Parameters (cont.)

For a general multiport network:

$$S_{ij} = \left. \frac{b_i(0)}{a_j(0)} \right|_{a_k=0, k \neq j}$$


All ports except  $j$  are semi-infinite with no incident wave (or with matched load at ports).

$N$ -port network

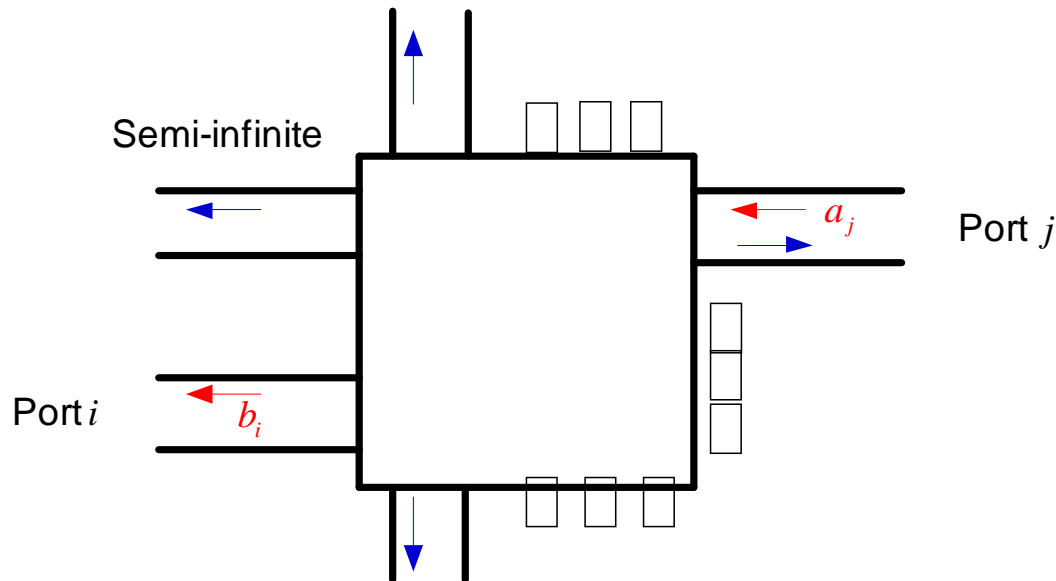

# Scattering Parameters (cont.)

Illustration of a three-port network

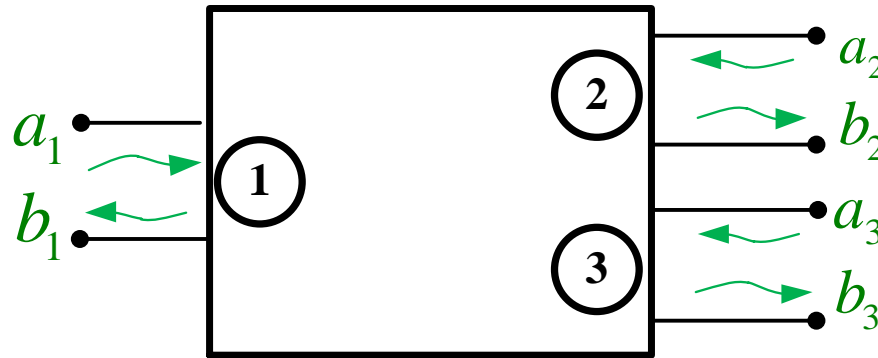


$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0) + S_{13}a_3(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0) + S_{23}a_3(0)$$

$$b_3(0) = S_{31}a_1(0) + S_{23}a_2(0) + S_{33}a_3(0)$$
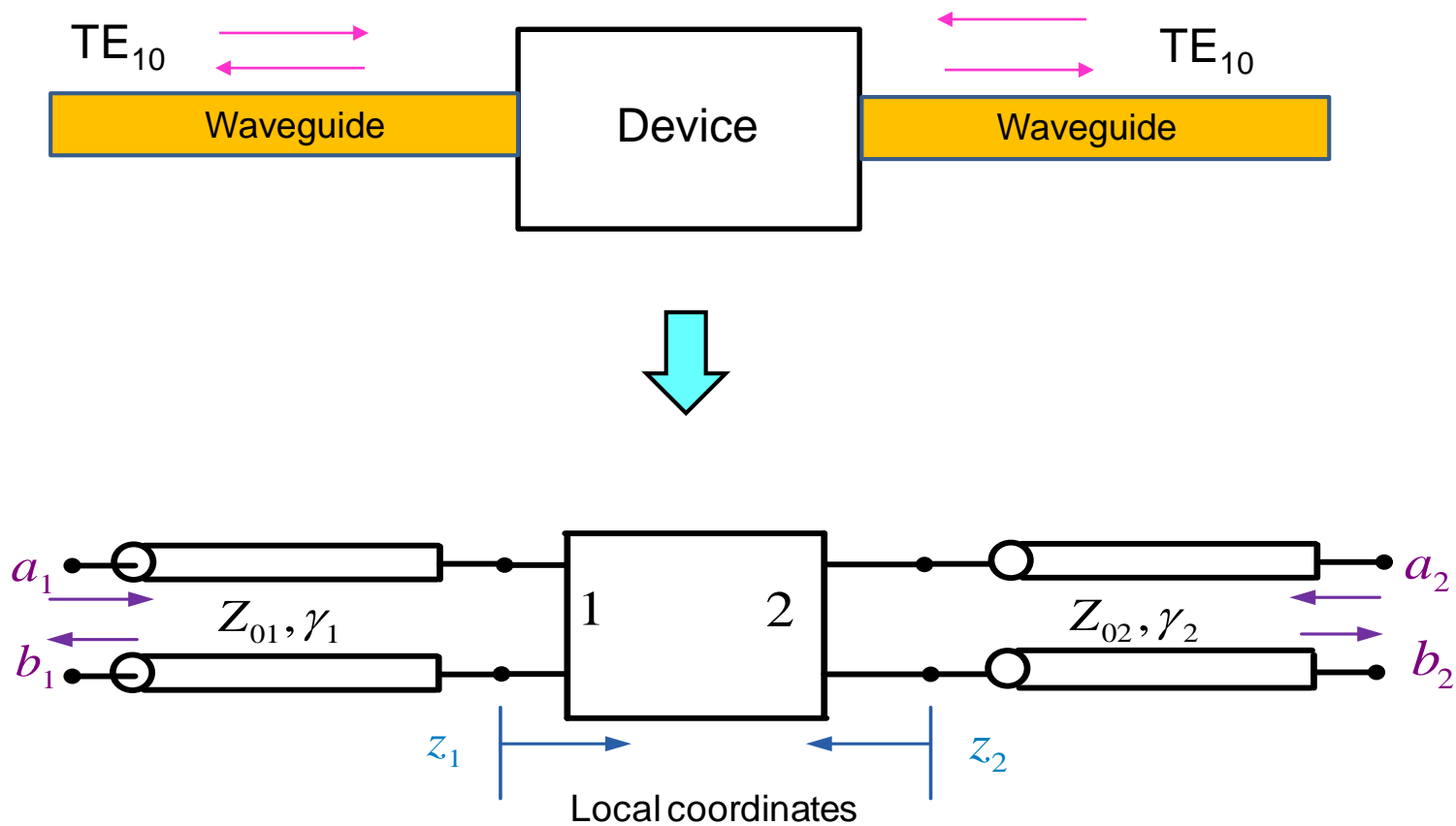
# Scattering Parameters (cont.)

A microwave system may have waveguides entering a device. In this case, the transmission lines are TEN models for the waveguides.



# Properties of the $S$ Matrix

For **reciprocal** networks, the  $S$ -matrix is symmetric.

$$S_{ij} = S_{ji} \quad i \neq j$$

$$\Rightarrow [S] = [S]^T$$

**Example of a nonreciprocal material: a biased ferrite**

# Properties of the $S$ Matrix (cont.)

❖ For lossless networks, the  $S$ -matrix is unitary.

$$\Rightarrow [S]^T [S]^* = [S]^* [S]^T = [U]$$

Identity matrix

Equivalently,

$$[S]^{T*} = [S]^{-1}$$

Notation:

$$[S]^\dagger = [S]^H = [S]^{T*}$$

(“Hermetian conjugate” or  
“Hermetian transpose”)

$$\text{so } [S]^\dagger = [S]^{-1}$$

Note :

$$\text{If } [A][B] = [U]$$

then

$$[B][A] = [U]$$

$N$ -port network

$$\text{Take } (i, j) \text{ element } \Rightarrow \sum_{k=1}^N S_{ik}^T S_{kj}^* = \sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij} \quad \delta_{ij} = \begin{cases} 1; & i = j \\ 0; & i \neq j \end{cases}$$

# Properties of the $S$ Matrix (cont.)

$$\sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij}$$

Interpretation: The inner product of columns  $i$  and  $j$  is zero unless  $i = j$ .

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{23} & S_{33} \end{bmatrix}$$

$\underline{S}_1$  vector

$\underline{S}_3$  vector

The rows also form orthogonal sets (see the note on the previous slide).

$$\underline{S}_i \cdot \underline{S}_j^* = \delta_{ij}$$

# Scattering Parameters (cont.)

Note: If all lines entering the network have the same characteristic impedance, then

$$S_{ij} = \frac{b_i(0)}{a_j(0)} = \frac{V_i^-(0)}{V_j^+(0)} \Big|_{V_k^+=0 \ k \neq j}$$

In general:


$$S_{ij} \equiv \frac{V_i^-(0)}{V_j^+(0)} \Big|_{V_k^+=0 \ k \neq j} \quad \text{“unnormalized” scattering parameters}$$

$$S_{ij} \equiv \frac{b_i(0)}{a_j(0)} \Big|_{a_k=0 \ k \neq j} \quad \text{“normalized” scattering parameters}$$

Note: The unitary property of the scattering matrix requires normalized parameters.  
We use normalized parameters in these notes.
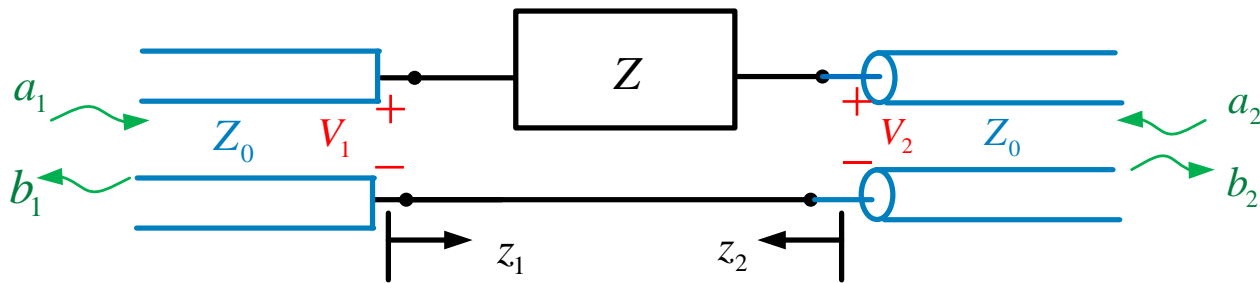
# Example


Find the  $S$  parameters for a series impedance  $Z$ .



Note that **two** different coordinate systems are being used here!



# Example (cont.)

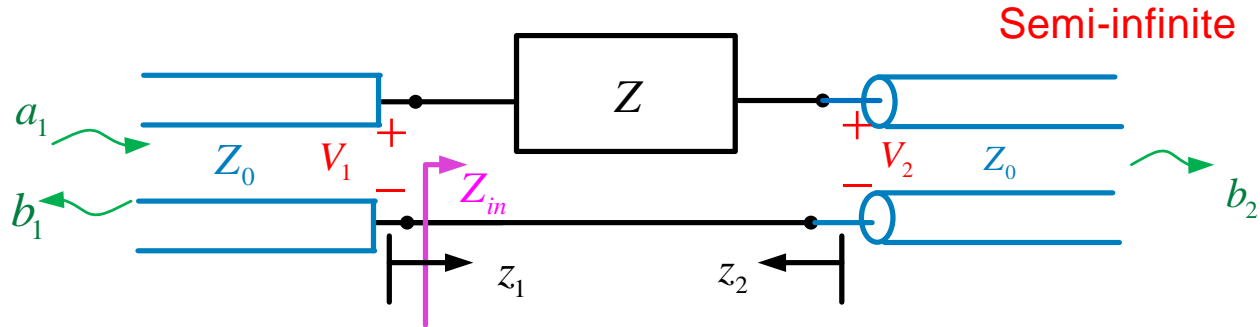

$S_{11}$  Calculation:

$$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right|_{a_2=0} = \frac{V_1^-(0)}{V_1^+(0)} = \left. \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|_{a_2=0} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0}$$


$$\Rightarrow S_{11} = \frac{Z}{Z + 2Z_0}$$

By symmetry:

$$S_{22} = S_{11}$$

# Example (cont.)

$S_{21}$  Calculation:

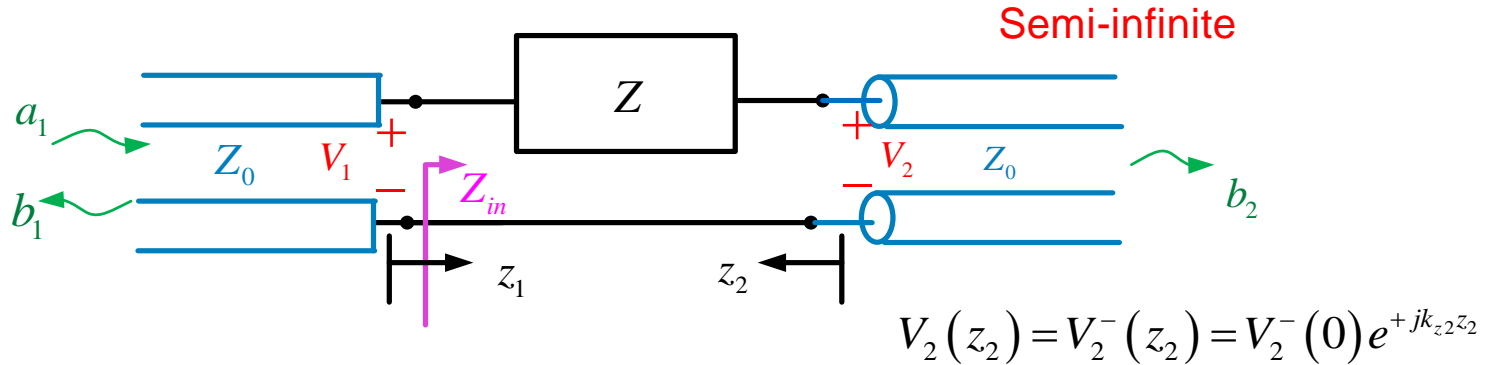

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0}$$

$$= \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0}$$

Voltage divider:  $V_2^-(0) = V_2(0) = V_1(0) \left( \frac{Z_0}{Z + Z_0} \right)$

We also have

$$V_1(0) = V_1^+(0)(1 + S_{11}) = a_1(0)\sqrt{Z_0}(1 + S_{11})$$

so


$$V_2^-(0) = a_1(0)\sqrt{Z_0}(1 + S_{11}) \left( \frac{Z_0}{Z + Z_0} \right)$$

Note:

$$V_2^-(0) = b_2(0)\sqrt{Z_0}$$

$$V_1^+(0) = a_1(0)\sqrt{Z_0}$$

# Example (cont.)

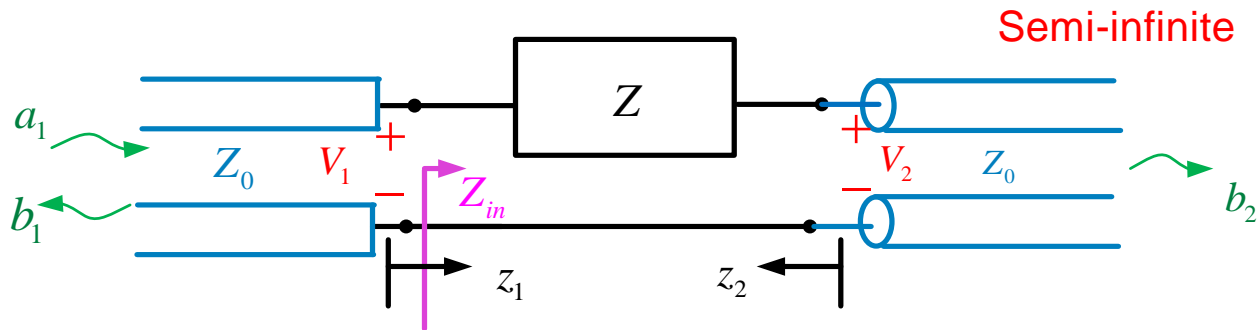

Hence

$$S_{21} = \frac{a_1(0) \sqrt{Z_0} (1 + S_{11}) \left( \frac{Z_0}{Z + Z_0} \right)}{a_1(0) \sqrt{Z_0}}$$

$$= (1 + S_{11}) \left( \frac{Z_0}{Z + Z_0} \right) = \left( 1 + \frac{Z}{Z + 2Z_0} \right) \left( \frac{Z_0}{Z + Z_0} \right) = \left( \frac{2Z + 2Z_0}{Z + 2Z_0} \right) \left( \frac{Z_0}{Z + Z_0} \right)$$


We then have

$$S_{21} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{12} = S_{21}$$
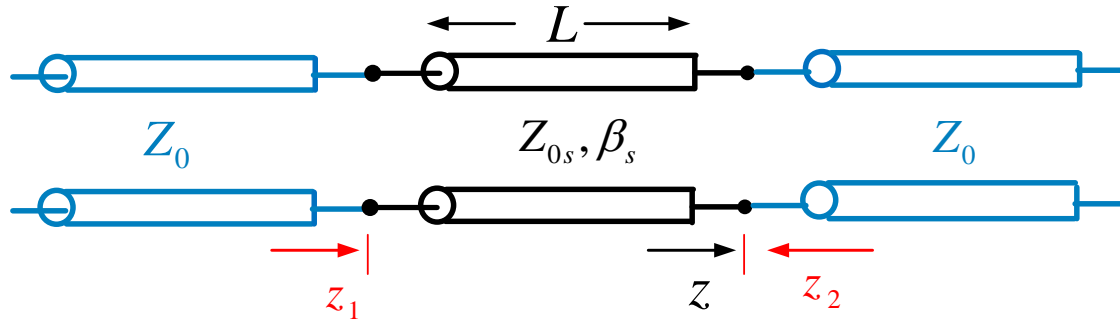
# Example


Find the  $S$  parameters for a length  $L$  of transmission line.



Note that **three** different coordinate systems are being used here!

# Example (cont.)


$S_{11}$  Calculation:

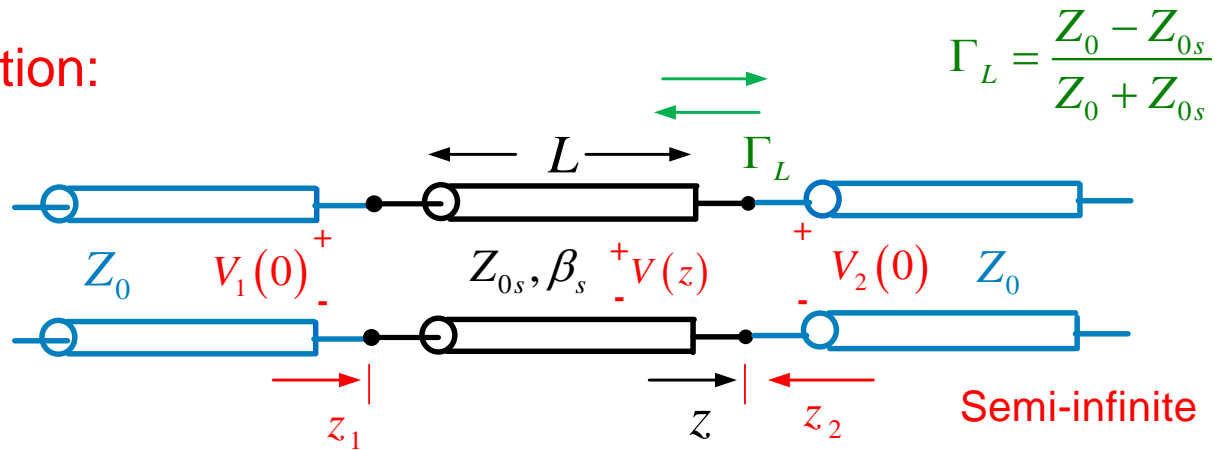

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{in}|_{a_2=0} - Z_0}{Z_{in}|_{a_2=0} + Z_0} = S_{22} \text{ (by symmetry)}$$

$$Z_{in}|_{a_2=0} = Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} = Z_{0s} \frac{(1 + \Gamma_L e^{-j2\beta_s L})}{(1 - \Gamma_L e^{-j2\beta_s L})}$$

# Example (cont.)

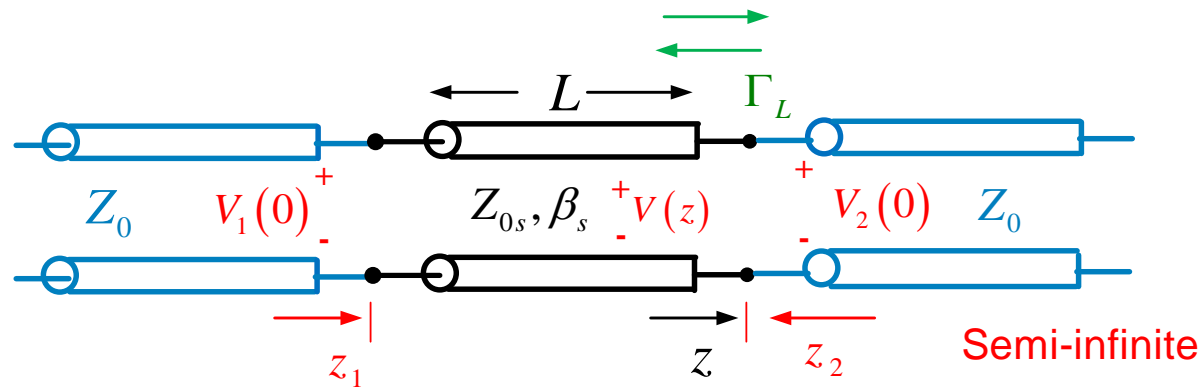


Hence

$$S_{11} = S_{22} = \frac{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} - Z_0}{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} + Z_0}$$

Note: If  $Z_{0s} = Z_0 \Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$

# Example (cont.)

$S_{21}$  Calculation:

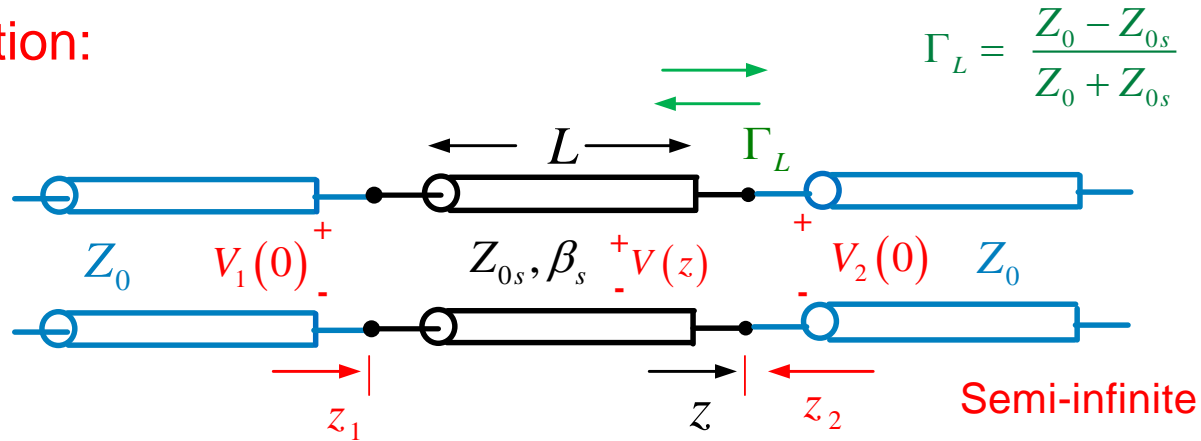

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \frac{V_2^-(0)/\sqrt{Z_0}}{V_1^+(0)/\sqrt{Z_0}} \Big|_{a_2=0}$$


Total voltage at port 1:  $V_1(0) = V_1^+(0)(1 + S_{11})$

Hence, for the denominator of the  $S_{21}$  equation we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

We now try to put the numerator of the  $S_{21}$  equation in terms of  $V_1(0)$ .

# Example (cont.)

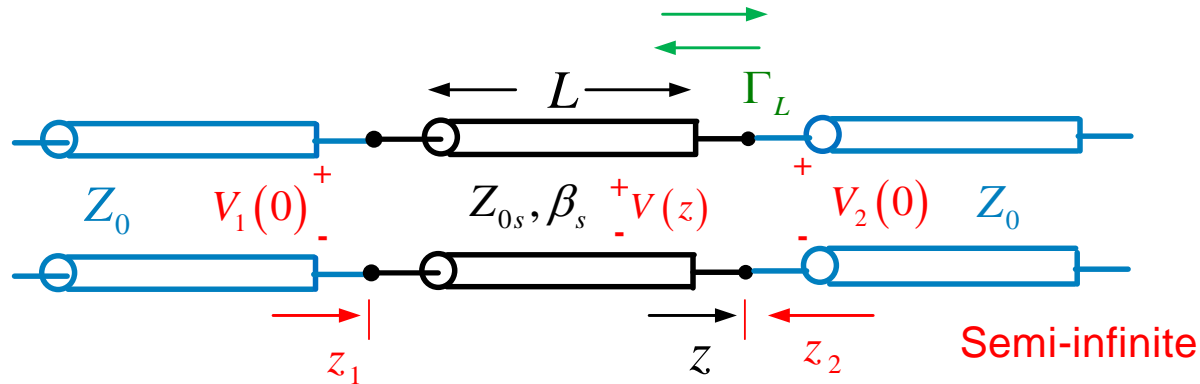

$$V_2^-(0) = V_2(0) = V(0) = V^+(0)(1 + \Gamma_L)$$

Next, we need to get  $V^+(0)$  in terms of  $V_1(0)$ :

$$V(z) = V^+(0)e^{-j\beta_s z} (1 + \Gamma_L e^{+j2\beta_s z})$$

$$\Rightarrow V_1(0) = V(-L) = V^+(0)e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})$$


$$\Rightarrow V^+(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})}$$

Hence, we have

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$



# Example (cont.)

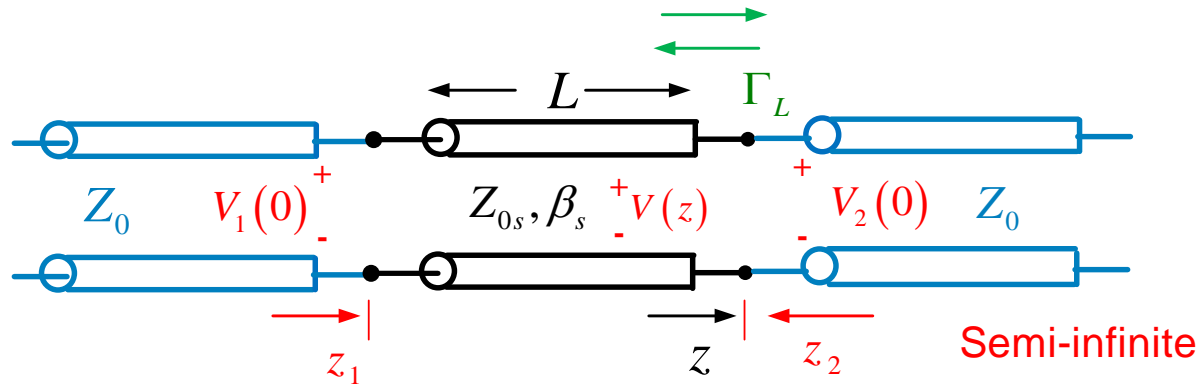

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Therefore, we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

$$S_{21} = \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}}$$

so

$$S_{21} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}} = S_{12} \text{ by symmetry}$$

# Example (cont.)

Special cases:

a)  $Z_{0s} = Z_0$

$$Z_{0s} = Z_0 \Rightarrow S_{11} = S_{22} = 0, \quad \Gamma_L = 0$$


$$S_{21} = S_{12} = e^{-j\beta_s L}$$

b)  $L = \frac{\lambda_g}{2}$

$$L = \frac{\lambda_g}{2} \Rightarrow \beta_s L = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{2} = \pi$$

$$\Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$$
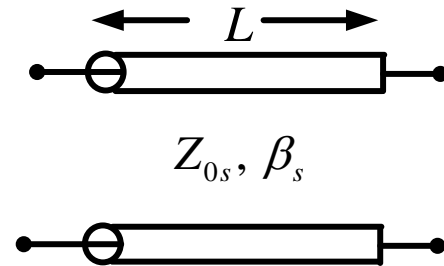
$$e^{-j\beta_s L} = -1, \quad e^{-j2\beta_s L} = +1 \Rightarrow S_{21} = -1$$



a)  $[S] = \begin{bmatrix} 0 & e^{-j\beta_s L} \\ e^{-j\beta_s L} & 0 \end{bmatrix}$


b)  $[S] = \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix}$

# Example

Find the  $S$  parameters for a step-impedance discontinuity.

$S_{11}$  Calculation:
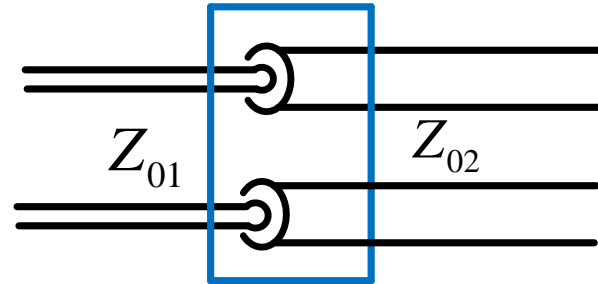
$$S_{11} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$
$$S_{22} = \frac{Z_{01} - Z_{02}}{Z_{02} + Z_{01}} = -S_{11}$$




$S_{21}$  Calculation:

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0} = \left. \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}} \right|_{a_2=0}$$
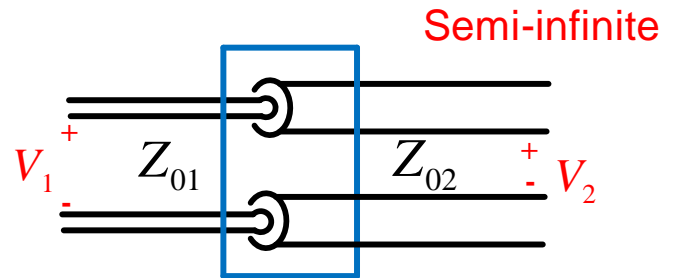
# Example (cont.)

Because of continuity of the voltage across the junction, we have:



$$V_2^-(0) \Big|_{a_2=0} = V_2(0) \Big|_{a_2=0} = V_1(0) \Big|_{a_2=0} = V_1^+(0)(1 + S_{11})$$

$$S_{21} = \frac{V_2^-(0)}{\sqrt{Z_{02}}} \Big|_{a_2=0} = \frac{V_1^+(0)(1 + S_{11})}{\sqrt{Z_{02}}} \Big|_{a_2=0} = \frac{V_1^+(0)}{\sqrt{Z_{01}}} \Big|_{a_2=0} \left( 1 + \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \right) = \frac{2Z_{02}}{Z_{02} + Z_{01}}$$

so


$$S_{21} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{02}}}$$

Hence

$$S_{21} = S_{12} = 2 \frac{\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}}$$
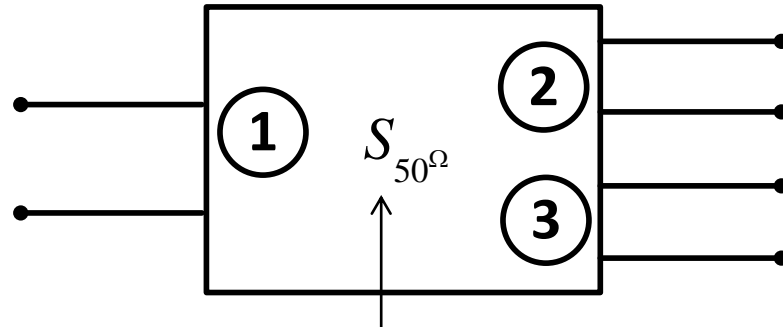
# Example

$$[S_{50\Omega}] = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$



These are the  $S$  parameters assuming  $50\ \Omega$  lines entering the device.

Not unitary  $\rightarrow$  **Not lossless**

(For example, column 2 dotted with the conjugate of column 3 is not zero.)


- 1) Find the input impedance looking into port 1 when ports 2 and 3 are terminated in  $50\ [\Omega]$  loads.
- 2) Find the input impedance looking into port 1 when port 2 is terminated in a  $75\ [\Omega]$  load and port 3 is terminated in a  $50\ [\Omega]$  load.

# Example (cont.)

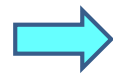
1) If ports 2 and 3 are terminated in  $50 [\Omega]$ : ( $a_2 = a_3 = 0$ )

$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3$$

$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = S_{11} = 0 \quad \Rightarrow \quad Z_{in1} = Z_{01}$$



$$Z_{in1} = 50[\Omega]$$

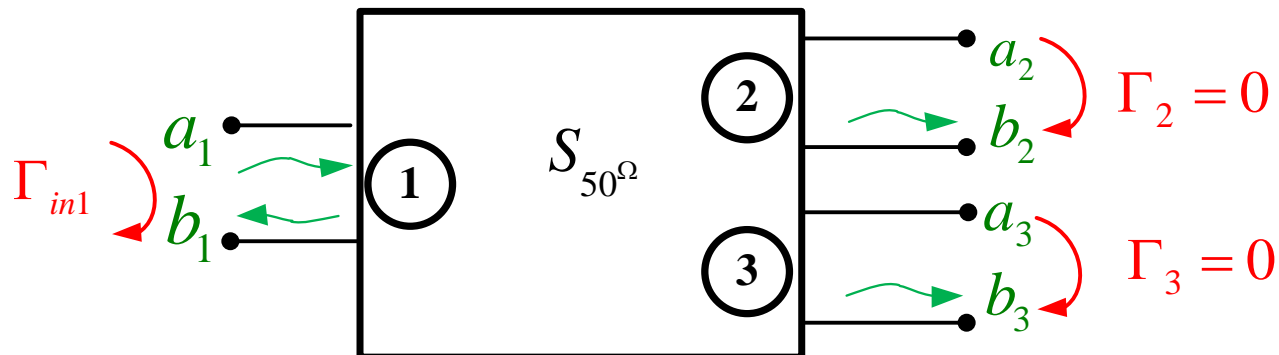


# Example (cont.)

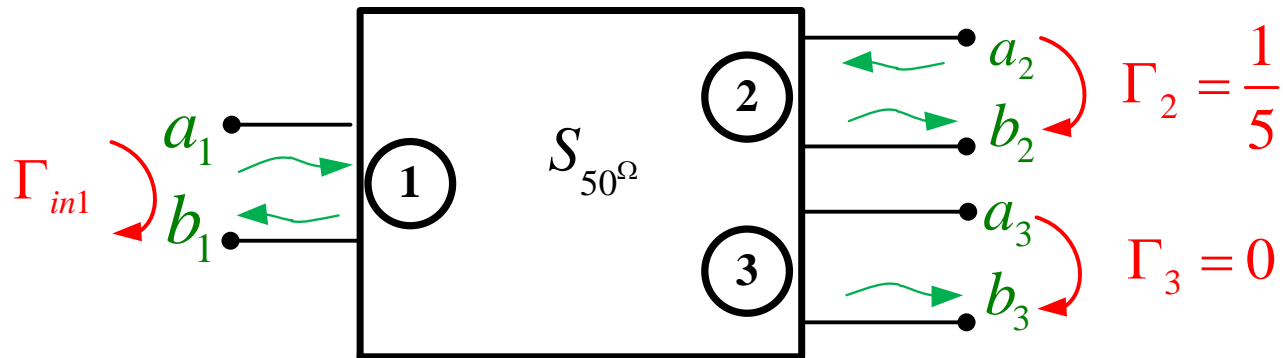2) If port 2 is terminated in 75 [ $\Omega$ ] and port 3 in 50 [ $\Omega$ ]:


$$\Gamma_2 = \frac{a_2}{b_2} = \frac{75 - 50}{75 + 50} = \frac{1}{5}$$

$$\Gamma_3 = \frac{a_3}{b_3} = \frac{50 - 50}{50 + 50} = 0$$


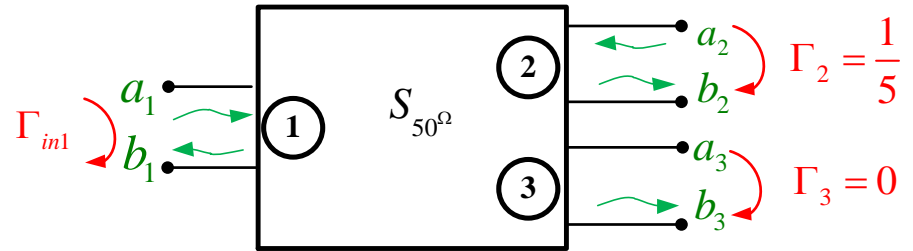
# Example (cont.)

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$



$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = \cancel{S_{11}} + S_{12} \frac{a_2}{a_1} + S_{13} \frac{a_3}{a_1}$$

$$= S_{12} \left( \frac{\Gamma_2 b_2}{a_1} \right) = S_{12} (\Gamma_2 S_{21}) = \left( \frac{-j}{\sqrt{2}} \right) \left( \frac{1}{5} \right) \left( \frac{-j}{\sqrt{2}} \right) = -\frac{1}{10}$$

$b_2 / a_1 = S_{21} + \cancel{S_{22}} \left( \frac{a_2}{a_1} \right) + \cancel{S_{23}} \left( \frac{a_3}{a_1} \right)$


$$a_2 = \Gamma_2 b_2$$

$$Z_{in1} = 50 \left( \frac{1 + \Gamma_{in1}}{1 - \Gamma_{in1}} \right) = 44.55 [\Omega]$$


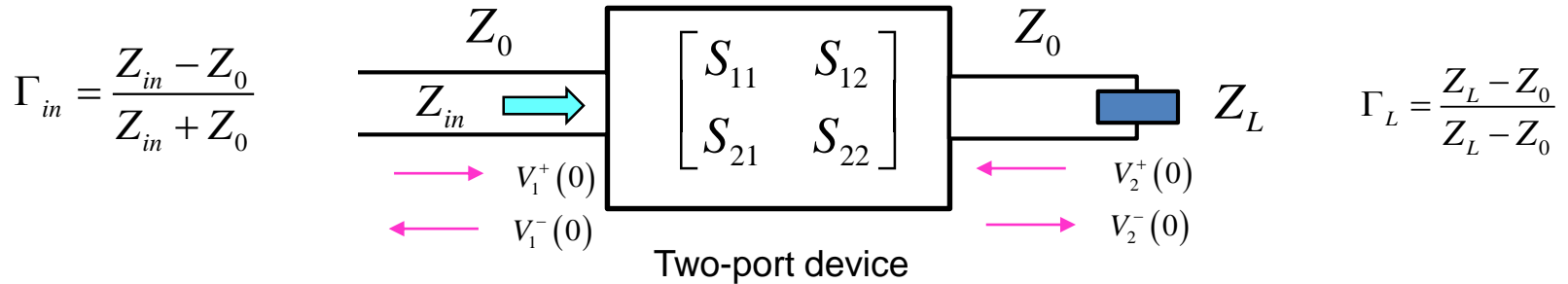
# Example

Find  $\Gamma_{in}$  for the system shown below.




Assume :  $V_1^+(0) = 1V$

so  $\Gamma_{in} = V_1^-(0) = S_{11}(1) + S_{12}V_2^+(0)$

We also have:

$$\left. \begin{aligned} V_2^+(0) &= \Gamma_L V_2^-(0) \\ V_2^-(0) &= S_{21}(1) + S_{22}V_2^+(0) \end{aligned} \right\} \begin{aligned} V_2^+(0) &= \Gamma_L (S_{21}(1) + S_{22}V_2^+(0)) \\ &\downarrow \\ V_2^+(0) &= \frac{\Gamma_L S_{21}}{1 - S_{22}\Gamma_L} \end{aligned}$$

# Example (cont.)

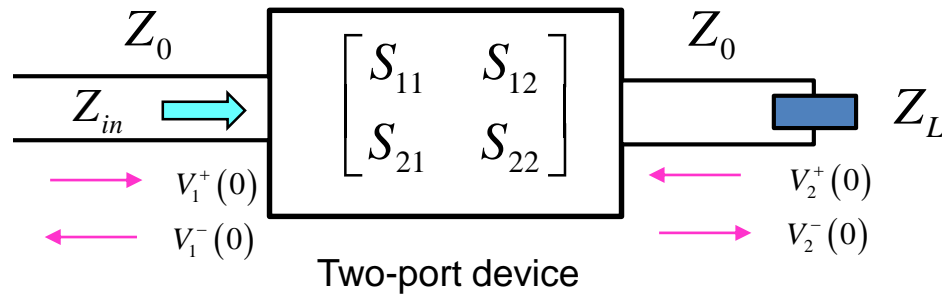

Hence

$$\begin{aligned}\Gamma_{in} &= S_{11} + S_{12} V_2^+(0) \\ &= S_{11} + S_{12} \left( \frac{\Gamma_L S_{21}}{1 - S_{22} \Gamma_L} \right)\end{aligned}$$

so

$$\Gamma_{in} = S_{11} + \left( \frac{\Gamma_L S_{12} S_{21}}{1 - S_{22} \Gamma_L} \right) \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

# Conversion Between Parameters (Two-Ports)

**TABLE 4.2** Conversions Between Two-Port Network Parameters

	<i>S</i>	<i>Z</i>	<i>Y</i>	<i>ABCD</i>
<i>S</i> <sub>11</sub>	<i>S</i> <sub>11</sub>	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> <sub>12</sub>	<i>S</i> <sub>12</sub>	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> <sub>21</sub>	<i>S</i> <sub>21</sub>	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> <sub>22</sub>	<i>S</i> <sub>22</sub>	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
<i>Z</i> <sub>11</sub>	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>11</sub>	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
<i>Z</i> <sub>12</sub>	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>12</sub>	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
<i>Z</i> <sub>21</sub>	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>21</sub>	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
<i>Z</i> <sub>22</sub>	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>22</sub>	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
<i>Y</i> <sub>11</sub>	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	<i>Y</i> <sub>11</sub>	$\frac{D}{B}$
<i>Y</i> <sub>12</sub>	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	<i>Y</i> <sub>12</sub>	$\frac{BC - AD}{B}$
<i>Y</i> <sub>21</sub>	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	<i>Y</i> <sub>21</sub>	$\frac{-1}{B}$
<i>Y</i> <sub>22</sub>	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	<i>Y</i> <sub>22</sub>	$\frac{A}{B}$
<i>A</i>	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	<i>A</i>
<i>B</i>	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	<i>B</i>
<i>C</i>	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	<i>C</i>
<i>D</i>	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	<i>D</i>


$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \quad \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; \quad Y_0 = 1/Z_0.$

# Example

Derive  $S_{ij}$  from the  $Z$  parameters.


(The result is given inside row 1, column 2, of the previous table.)

$S_{11}$  Calculation:

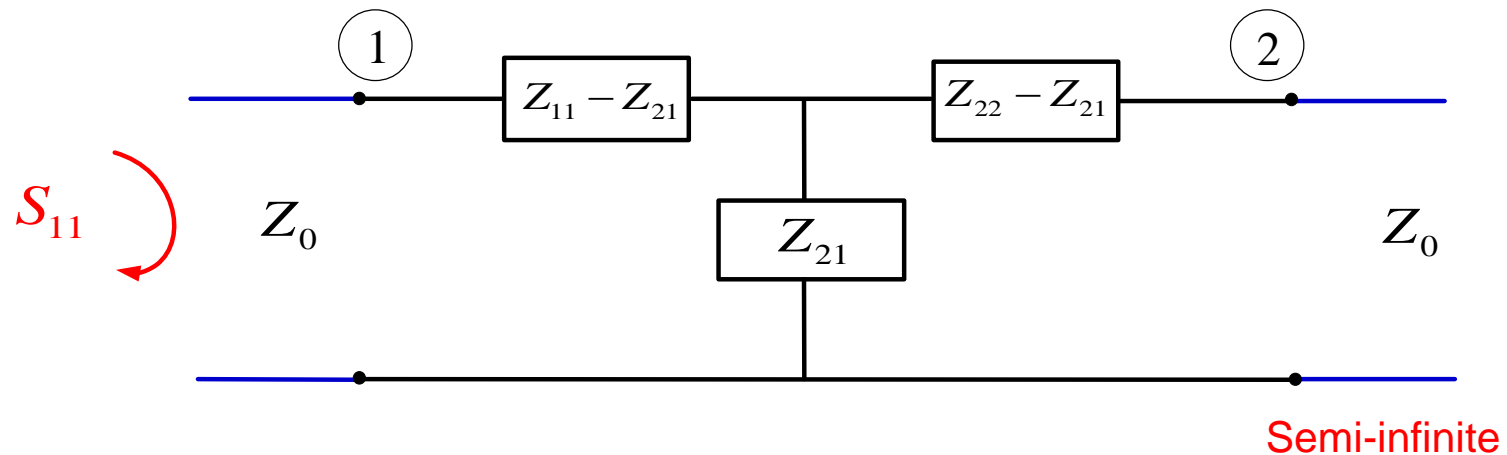

$$S_{11} = \Gamma_{in1} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \quad Z_{in} = (Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]$$

# Example (cont.)

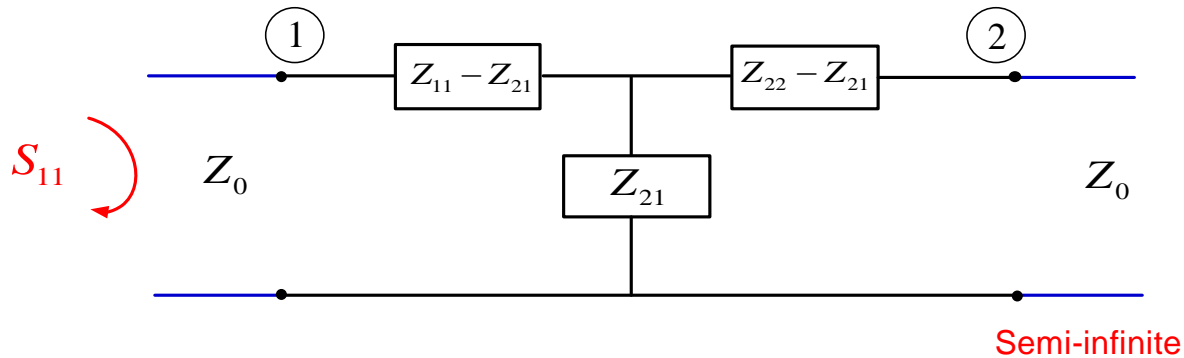

$$Z_{in} = (Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]$$


$$= (Z_{11} - Z_{21}) + \frac{Z_{21} (Z_{22} + Z_0 - Z_{21})}{Z_{22} + Z_0}$$

$$= \frac{(Z_{11} - Z_{21})(Z_{22} + Z_0) + Z_{21} (Z_{22} + Z_0 - Z_{21})}{Z_{22} + Z_0}$$

$$= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - \cancel{Z_{21}Z_{22}} - \cancel{Z_{21}Z_0} + \cancel{Z_{21}Z_{22}} + \cancel{Z_{21}Z_0} - Z_{21}^2}{Z_{22} + Z_0}$$

$$= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - Z_{21}^2}{Z_{22} + Z_0}$$

# Example (cont.)

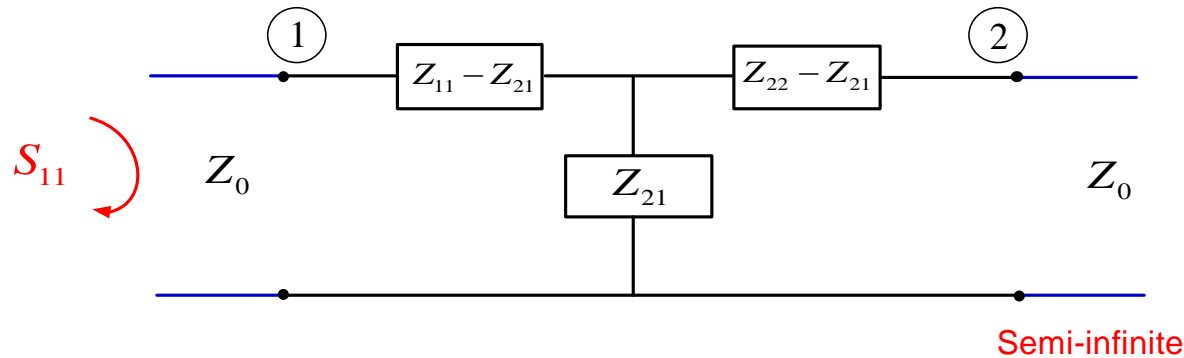

We have:


$$Z_{in} = \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2}{Z_{22} + Z_0}$$

SO

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \frac{(Z_0 + Z_{22})}{(Z_0 + Z_{22})} = \frac{(Z_{11}(Z_0 + Z_{22}) - Z_{21}^2) - Z_0(Z_0 + Z_{22})}{(Z_{11}(Z_0 + Z_{22}) - Z_{21}^2) + Z_0(Z_0 + Z_{22})}$$


We next simplify this.

# Example (cont.)

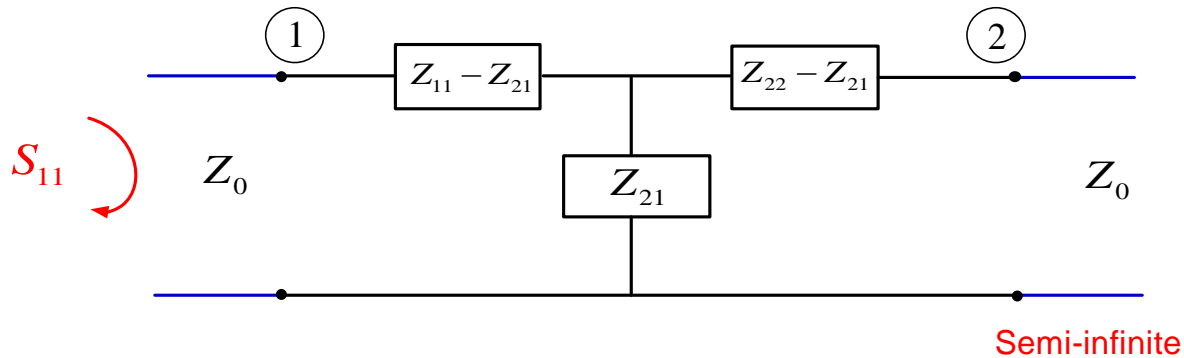

$$\begin{aligned}
 S_{11} &= \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 - Z_0(Z_0 + Z_{22})}{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 + Z_0(Z_0 + Z_{22})} \\
 &= \frac{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 - Z_0^2 - Z_0Z_{22}}{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 + Z_0^2 + Z_0Z_{22}} \\
 &= \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}
 \end{aligned}$$

# Example (cont.)

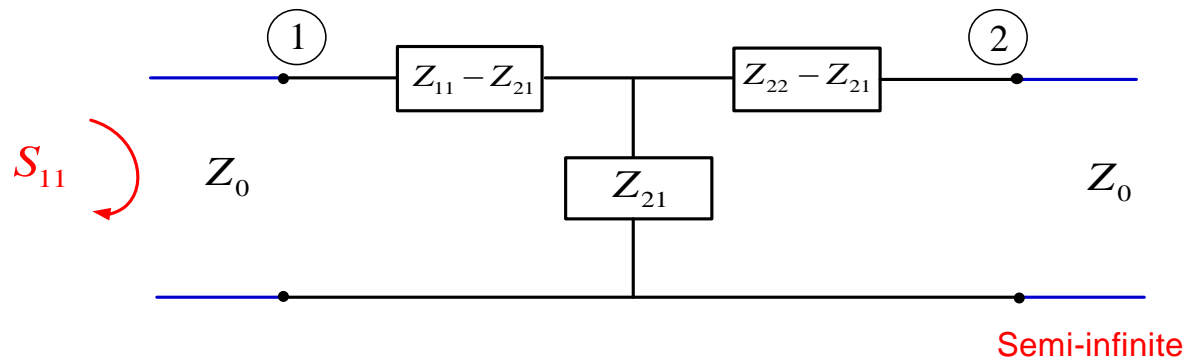

Hence

$$S_{11} = \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

This agrees with the table.

Note: To get  $S_{22}$ , simply let  $Z_{11} \rightarrow Z_{22}$  in the previous result.

Hence, we have:


$$S_{22} = \frac{(Z_0 + Z_{11})(Z_{22} - Z_0) - Z_{21}^2}{(Z_0 + Z_{11})(Z_{22} + Z_0) - Z_{21}^2}$$

This agrees with the table.



# Example (cont.)

$S_{21}$  Calculation:

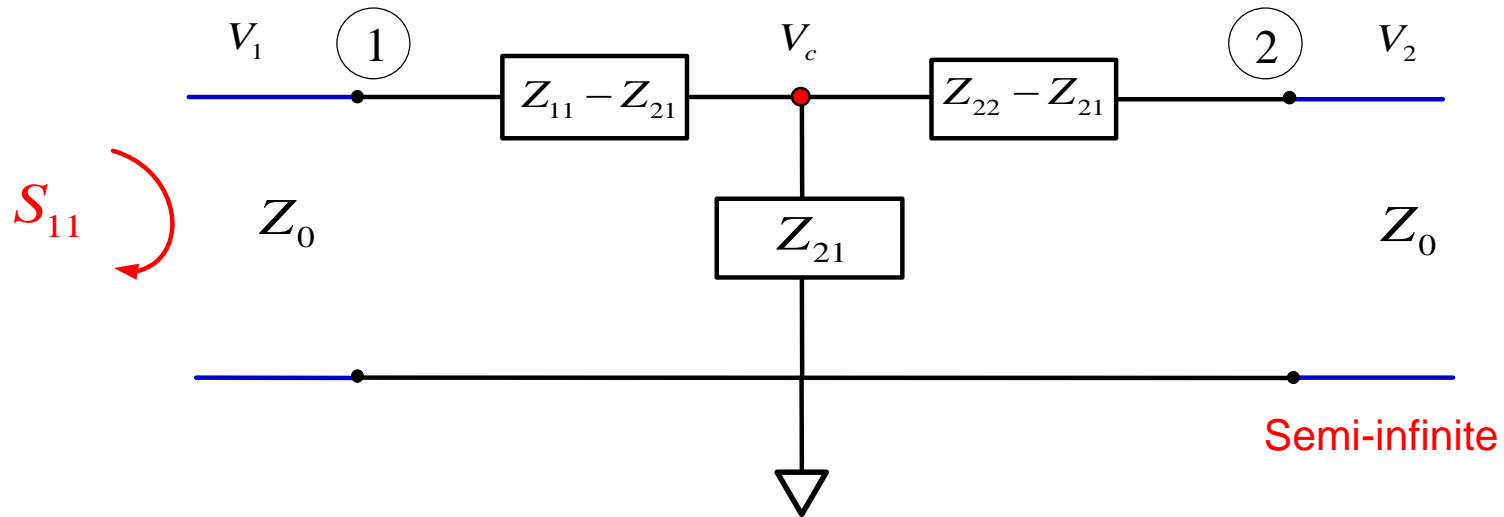

Assume  $V_1^+(0) = 1$  [V]


$$\Rightarrow S_{21} = V_2^-(0) = V_2(0)$$

Also,  $V_1(0) = V_1^+(0)(1 + S_{11}) = 1 + S_{11}$

Use voltage divider equation twice to get  $V_2(0)$ :  $V_1(0) \rightarrow V_c \rightarrow V_2(0)$

# Example (cont.)

$$V_1(0) = 1 + S_{11}$$

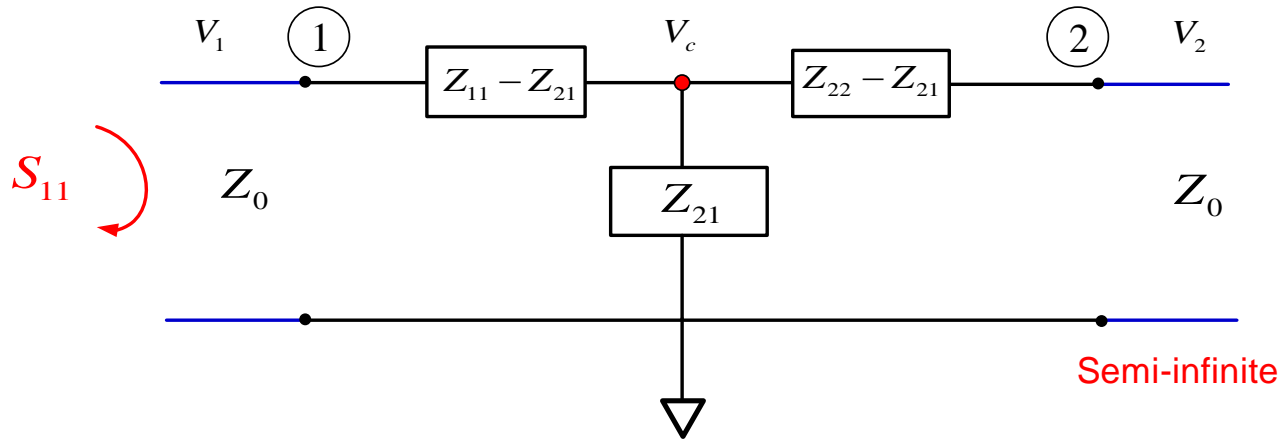


Use voltage divider equation twice:

$$V_c = V_1(0) \left( \frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right)$$

$$V_2(0) = V_c \left( \frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

# Example (cont.)

$$V_1(0) = 1 + S_{11}$$

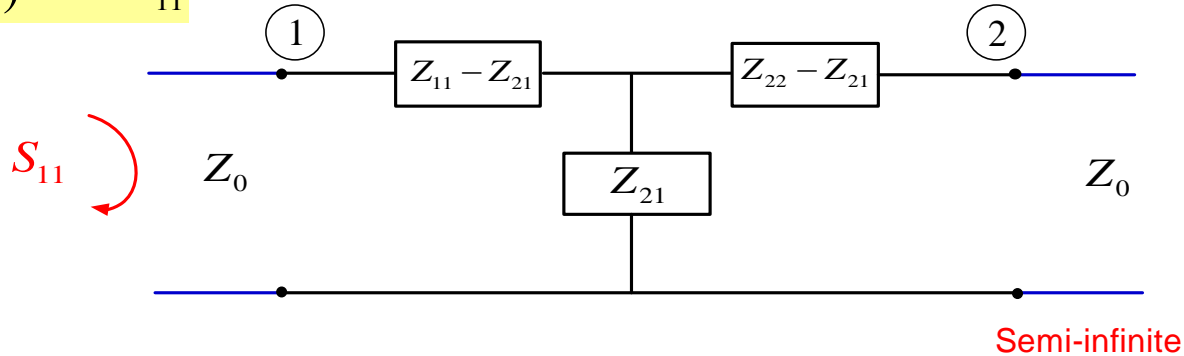

Hence

$$S_{21} = V_2(0) = (1 + S_{11}) \left( \frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right) \left( \frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

where

$$1 + S_{11} = 1 + \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

# Example (cont.)

Our result:

$$S_{21} = (1 + S_{11}) \left( \frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right) \left( \frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

where

$$1 + S_{11} = 1 + \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

After simplifying, we should get the result in the table:

(You are welcome to check it!)


$$S_{21} = S_{21} = \frac{2Z_{12}Z_0}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

This is the result in the table.
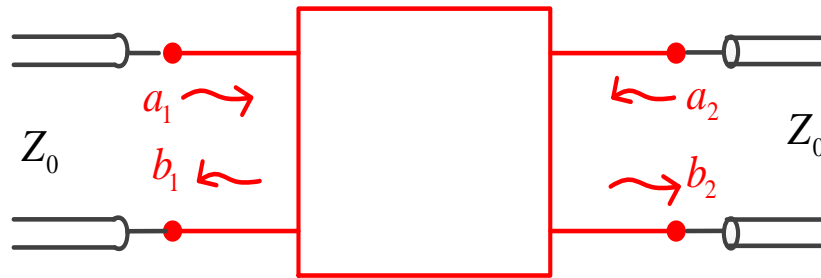
# Signal-Flow Graph

This is way to graphically represent  $S$  parameters.

Please see the Pozar book for more details.




The wave amplitudes are represented as nodes in the single-flow graph.

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

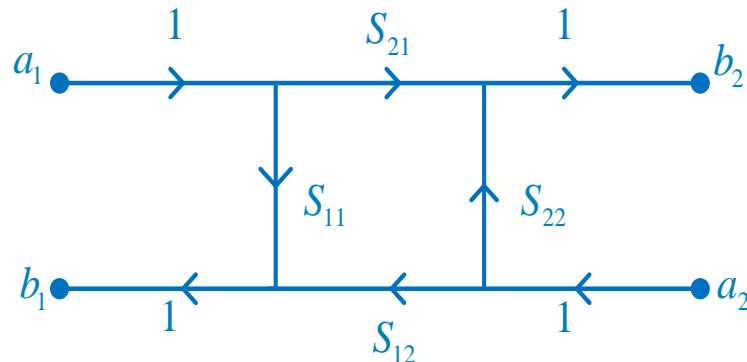(wave amplitudes evaluated at  $z_i = 0$ )



Rule: The value at each node is the sum of the values coming into the node from the various other nodes.