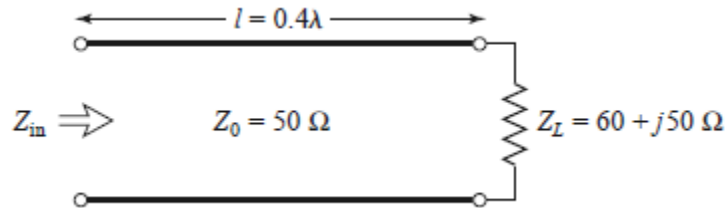


1 Use the Smith chart to find the following quantities for the transmission line circuit shown in the accompanying figure:

- The SWR on the line.
- The reflection coefficient at the load.
- The load admittance.
- The input impedance of the line.
- The distance from the load to the first voltage minimum.
- The distance from the load to the first voltage maximum.




2 Use the Smith chart to find the shortest lengths of a short-circuited  $75 \Omega$  line to give the following input impedance:

- $Z_{in} = 0$ .
- $Z_{in} = \infty$ .
- $Z_{in} = j75 \Omega$ .
- $Z_{in} = -j50 \Omega$
- $Z_{in} = j10 \Omega$

3 Repeat Problem 2 for an open-circuited length of  $75 \Omega$  line.

4 A slotted-line experiment is performed with the following results: distance between successive minima = 2.1 cm; distance of first voltage minimum from load = 0.9 cm; SWR of load = 2.5. If  $Z_0 = 50 \Omega$ , find the load impedance.

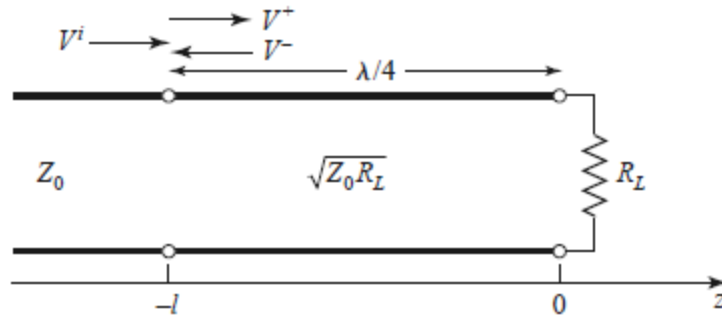5 Consider the quarter-wave matching transformer circuit shown in the accompanying figure. Derive expressions for  $V^+$  and  $V^-$ , the respective amplitudes of the forward and reverse traveling waves on the quarter-wave line section, in terms of  $V^i$ , the incident voltage amplitude.



6 A  $50 \Omega$  transmission line is matched to a 10 V source and feeds a load  $z_l = 100 \Omega$ . If the line is  $2.3 \lambda$  long and has an attenuation constant  $\alpha = 0.5 \text{ dB}/\lambda$ , find the powers that are delivered by the source, lost in the line, and delivered to the load.

**Good Luck**

*Dr. Sherif Hekal*