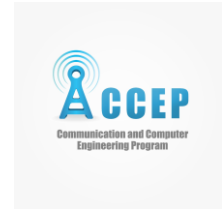




Benha University
Faculty of Engineering- Shoubra
Communications and Computer Engineering Program



Final Exam – Term 191
Academic Year 2018-2019
Course: Solid State Electronic Devices

Date: 23/01/2019
Duration: 2 hours
Code: CCE201

- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- No. of questions: 4
- Total Mark: 40 Marks

- [1] A red, a yellow and a green LED in series as shown in Fig. 1.
- (a) Specify the supply voltage (V_S) at least you should connect so that they are light on if each one needs voltage drops of 2 V, 2.5 V, and 2.5 V respectively.
 - (b) Specify the value of resistor R to have current $I = 15$ mA.
 - (c) Assume $V_S = 10$ V. Reconstruct the circuit again so that we can add another two LEDs (yellow & green), series in one branch, and passing current $I_2 = 10$ mA while the current passing through the first three LEDs $I_1 = 20$ mA.

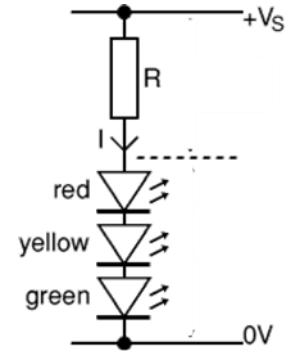


Figure 1

(10 Marks)

- [2] The voltage-regulator circuit, shown in Fig. 2 is designed to provide a constant voltage of 5V to a load from a variable supply voltage. The load current varies from 0 to 100mA and the source voltage varies from 8 to 10V. If the Zener diode is ideal, specify the value of the resistance R.

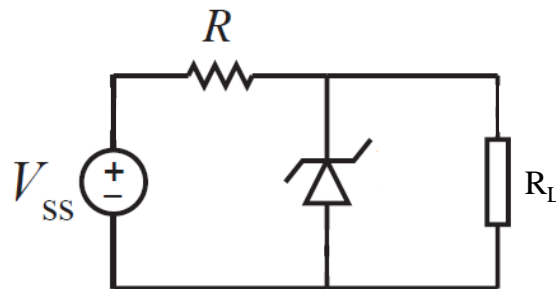


Figure 2

(10 Marks)

- [3] Design two different clipper circuits to clip the portions of input voltage that are above (5V) or below (-3V). Assume that ideal diodes are available. Ideal Zener diodes of any breakdown voltage required are also available.

(5 Marks)

[4] Consider the common-emitter BJT amplifier circuit shown in Fig. 3.

Assume $V_{CC} = 15\text{ V}$, $\beta = 150$, $V_{BE} = 0.7\text{ V}$, $R_E = 1\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_1 = 47\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_L = 47\text{ k}\Omega$, $R_S = 100\ \Omega$.

- Determine I_{CQ} and V_{CEQ} .
- What is the maximum (peak to peak) output voltage swing available in this amplifier?
- Draw the AC equivalent circuit and determine the AC model parameters.
- Find R_{in} , R_{out} , and A_v .

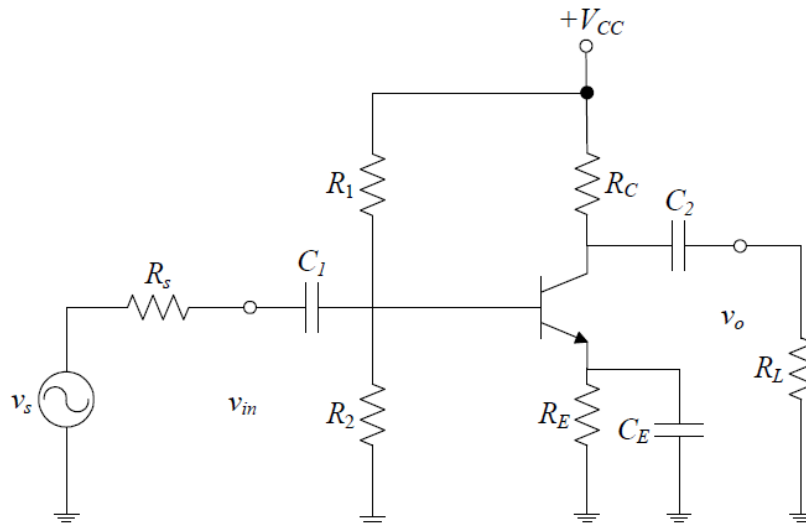


Figure 3

(15 Marks)

Good Luck

Dr. Sherif Hekal