



- [1] In the circuit of Fig. 1, let v_S have a peak value of 10 V and $R = 2 \text{ k}\Omega$. Find the peak value of i_D and the dc component of v_o . Use the CVD model where $V_D = 0.7 \text{ V}$.

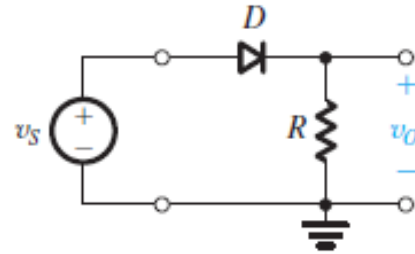


Fig. 1

- [2] Find the values of I and V in the circuits shown in Fig. 2. Use the Ideal diode model.

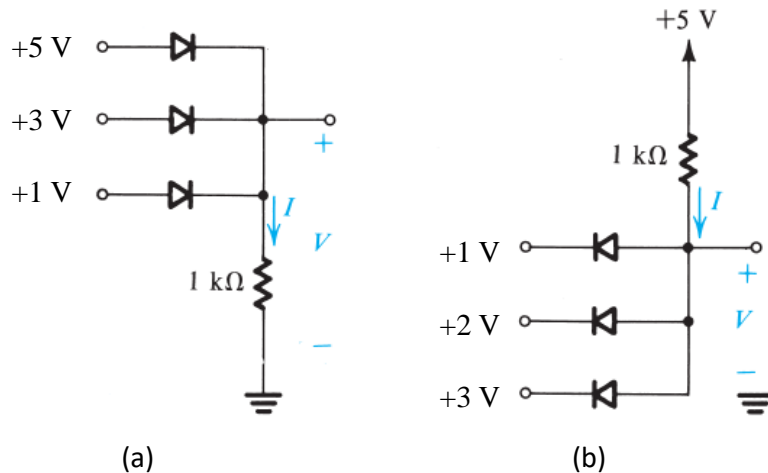


Fig. 2

- [3] A red, a yellow and a green LED in series as shown in Fig. 3. Specify the following:

- The supply voltage at least you should connect so that they are light on if each one needs a voltage drop of 2 V, 2.5 V, and 2.5 V respectively.
- The value of resistor R to have current $I = 20 \text{ mA}$.

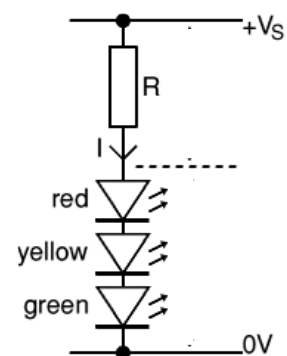


Fig. 3