



- [1] In the circuit of Fig. 1, let  $v_S$  have a peak value of 10 V and  $R = 2.5 \text{ k}\Omega$ . Find the peak value of  $i_D$  and the dc component of  $v_o$ . Use the ideal diode model where  $V_D = 0 \text{ V}$ .

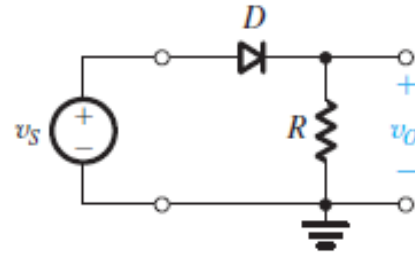


Fig. 1

- [2] Find the values of  $I$  and  $V$  in the circuits shown in Fig. 2. Use the CVDM where  $V_D = 0.7 \text{ V}$ .

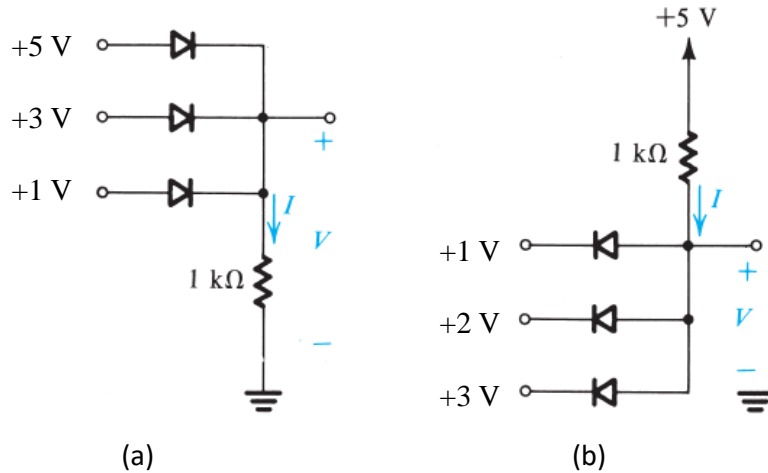


Fig. 2

- [3] A red, a yellow and a green LED in series as shown in Fig. 3. Specify the following:

- The supply voltage at least you should connect so that they are light on if each one needs a voltage drop of 2 V, 2.5 V, and 2.5 V respectively.
- The value of resistor  $R$  to have current  $I = 20 \text{ mA}$ .

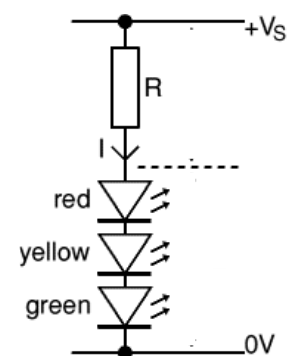


Fig. 3